

• Announcements:

- ↳ Lab#3 handed out and online
- ↳ Lab#2 due the Friday, 4/3, after we get back from Spring Break, at 5 p.m.
- ↳ Need evening lecture next week, Tuesday, 7 p.m., room TBA

• Today:

- ↳ Go through Lab#3
- ↳ Go through Midterm Exam & Hand Back <sup>so</sup> <sub>No  $V_i$  (sort of)</sub>
- ↳ Output Stages

Last Time -

Output Stages

- Class A (Emitter or Source Follower)
- Class B
- Class AB (we'll do this one later)

Purpose: Drive loads


- ① Deliver power w/ small distortion.
- ② Minimize output impedance  $\rightarrow$  so that the amplifier gain is insensitive to the load.

Desirable Attributes:

- ① High  $R_{in}$ ; Low  $R_{out}$ .
- ② Low quiescent power.
- ③ Minimal effect on the amplifier freq. response.
- ④ Should be able to handle large input/output swings.  
(i.e.,  $V_i$  may be  $> V_T$ , invalidating small-signal approximations)



Emitter Follower (Class A)

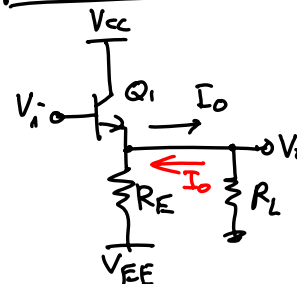


Two main cases:

- ①  $I_o > 0$ :  $I_o$  comes from  $Q_1$   
 $\Rightarrow$  adequate  $I_o$  can be supplied so long as  $Q_1$  stays in forward-active
- ②  $I_o < 0$ : (i.e.,  $V_o < 0$ )  $I_o$  must be sunk to  $V_{EE}$  through  $R_E$   
 $I_o = \frac{V_o - V_{EE}}{R_E}$   $\rightarrow$  gets smaller as  $V_o$  decreases  
 $|I_o|$

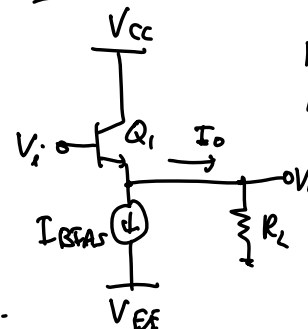
Problem!

Solution: Replace  $R_E$  w/ a current source!



Now, can source  $I_o$  thru  $Q_1$ .  
And can sink  $I_o$ :  $I_{EAS}$  (or less)  
 $\uparrow$   
 $\nrightarrow I_o$  doesn't get small  
as  $V_o$  decreases  
Can maintain driving point! ✓

Actual Implementation:

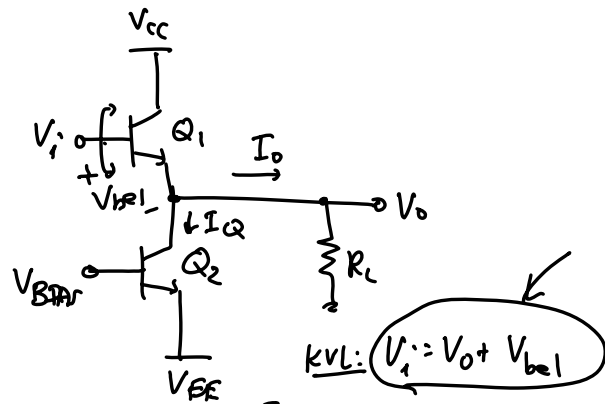

In general:  $V_{BE1} \neq \text{const.} \Rightarrow V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$   
( $Q_1$  in F.A.R.)

$$I_{C1} = I_O + I_Q = I_Q + \frac{V_O}{R_L}$$

$$\therefore V_i = V_O + V_T \ln\left(\frac{I_Q + \frac{V_O}{R_L}}{I_{S1}}\right)$$

