

• Announcements:


- As has been mentioned numerous times in lecture, your Lab#2 reports are individual reports; not group reports
- Evening lecture next week, Tuesday, 7 p.m., in TBD

• Today:

- Finish Output Stages
- Start Stability & Compensation

Last Time -

= Class A:

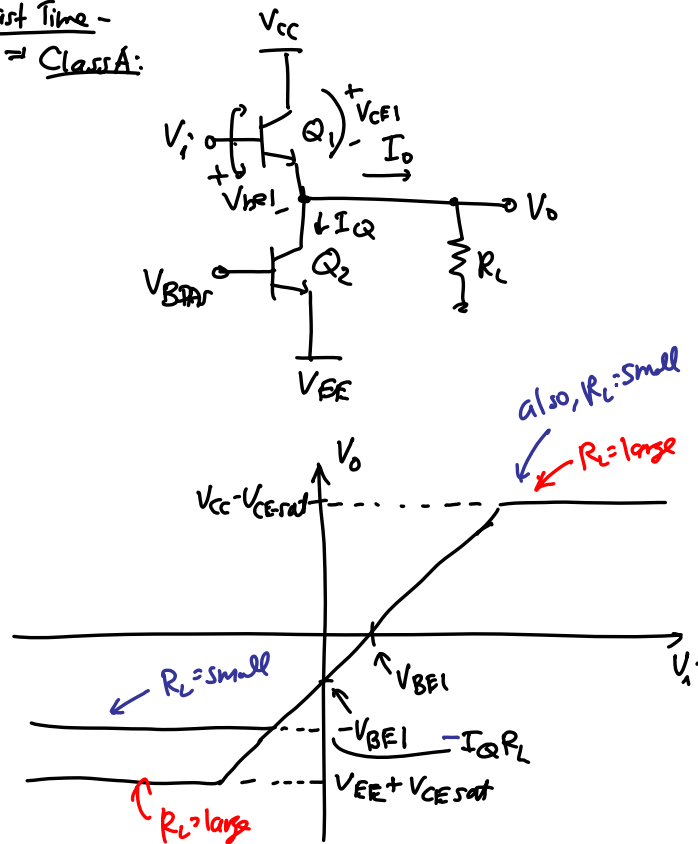

Two Cases:

Case ①: $R_L = \text{large} \rightarrow I_o < I_Q$

$\Rightarrow I_o$ not doing much $\rightarrow I_{C1}$ not doing much

For $V_i = \text{large and (+)}$: Q_1 must source $I_o + I_Q$

$V_o = V_i - V_{BE1}$ at some point Q_1 will saturate as $V_o \uparrow$
 \hookrightarrow get V_{omax}

$V_{omax} = V_{CC} - V_{CE(sat)}$
 \hookrightarrow and $V_i = V_{CC} - V_{CE(sat)} + V_{BE1}$

For $V_i = \text{large and (-)}$: V_o follows V_i until Q_2 saturates

$V_{omim} = V_{EE} + V_{CE(sat)}$
 $\hookrightarrow V_i = V_o + V_{BE1} = V_{EE} + V_{CE(sat)} + V_{BE1}$

Case ②: $R_L = \text{small} \rightarrow$ thw, I_o can be large!

For $V_i = (+)$ and large: Q_1 can source as much current as needed until it saturates (or until it fries)

For $V_i = (-)$ and large: $V_o = +I_o R_L \rightarrow \text{min } V_o = -I_Q R_L$

$\Rightarrow Q_1$ cuts off ($I_{C1} = 0$)

$\Rightarrow V_o$ clamps @ $-I_Q R_L$

\Rightarrow further decrease in $V_i \rightarrow$ no Δ in V_o !


Need $I_Q = \text{large}$ to avoid this problem!

Problem: too much power consumption

$P_Q = (V_{CC} - V_{EE}) I_Q \Rightarrow$ DC power consumption!
 \hookrightarrow if want large output swing, must consume power!

Solution: Class B Output Stage

DC can attain zero quiescent power

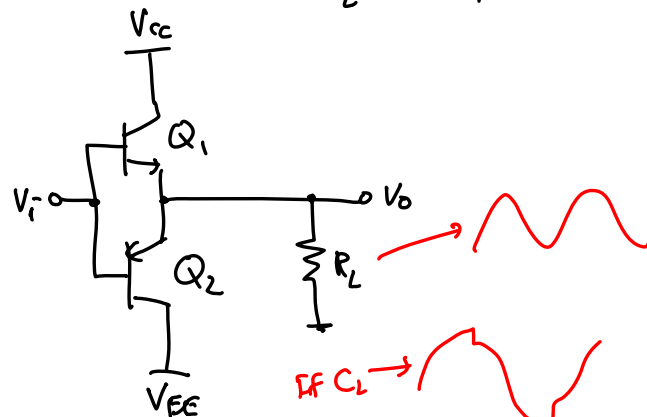


Operation:


$$|V_i| < V_{BE(on)} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_o = 0V$$

$$V_{CC} > |V_i| > V_{BE(on)} \rightarrow V_o \approx V_i - V_{BE(on)}$$

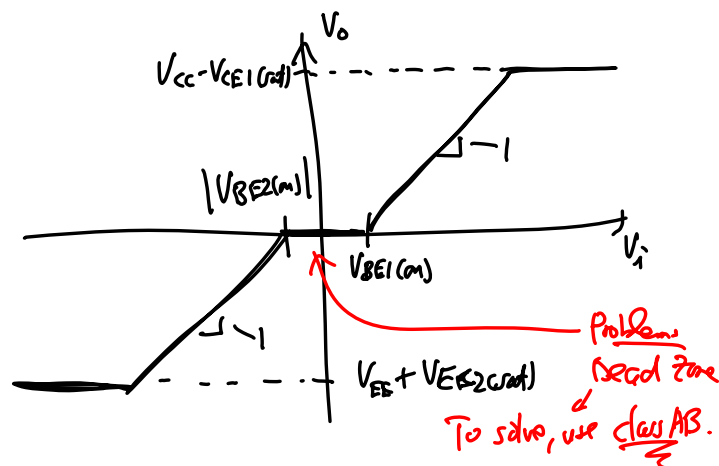
$$V_{omax} = V_{CC} - V_{CE1(sat)}, V_{omin} = V_{EE} + V_{CE2(sat)}$$



Stability & Compensation

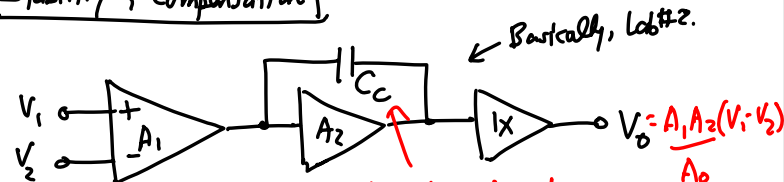

Used C_c to set BW:

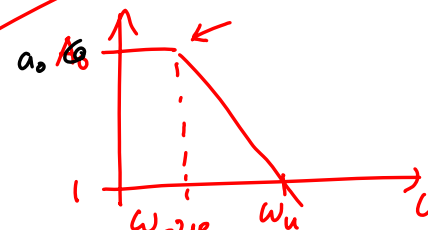

Why is C_c needed?

Stability & Compensation in Op Amps

In general, op amps are used in neg FB loops.


Those cause instability.

Reasons:

- ① Feedback sets the biasing \rightarrow no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity or input range.
(e.g., emitter degeneration is a type of FB)
- ④ Gain determined by external FB components \rightarrow more accurate than op amp gain.
- ⑤ FB sets R_i and R_o .
- ⑥ FB can improve temperature stability.

⇒ Problem: any FB loop can become unstable under certain conditions → ∴ must compensate to suppress instability!

Ex. Non-inverting Amplifier

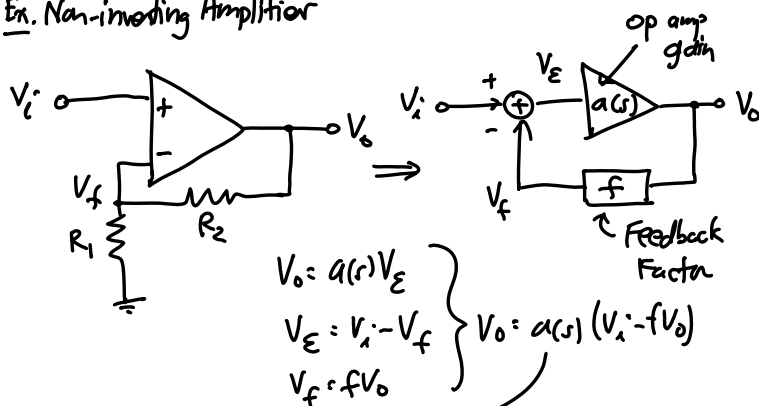

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$

closed loop voltage gain

Loop Transmission $T(s) = a(s)f$

Instability occurs when $A(s) \rightarrow \infty$.

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} \leftarrow \text{will also go unstable if denominator} = (-)$$

$a(s)f = -1$

In General:

If $|a(s)f| \geq 1$ when $\angle a(s)f = -180^\circ \Rightarrow$ Instability

This is a simplified form of the Nyquist Criterion.

Stability of FB Ckt. Using a Single Pole Op Amp

For a single pole op amp: $a(s) = \frac{a_0}{1 - \frac{s}{P_1}} \equiv$ op amp transfer function

Thur: closed loop Xfa Fcn

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0f} \frac{1}{1 - \frac{s}{P_1(1 + a_0f)}}$$

much high 3dB freq.

$A_0 =$ closed loop dc gain $\rightarrow (1 + a_0f) \approx a_0f \times \text{smaller than } a_0$


$= \frac{1}{f}$

$T_0 = a_0f =$ loop gain (defined at dc)

$T(s) = a(s)f =$ loop transmission (defined for general frequencies)

Bode Plot: → use to determine

$(1 + a_0f) \approx a_0f$ & $a(s)f$ when $|a(s)f| = 1 \leftarrow$ then can determine stability

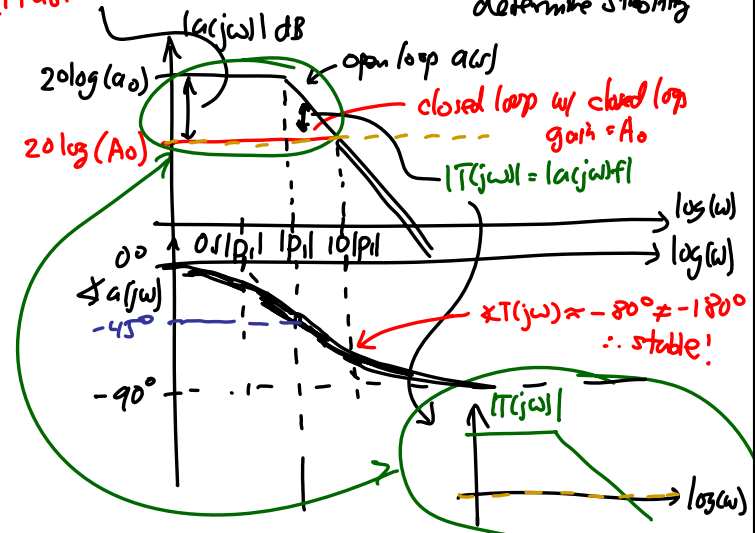

Remarks:

① For the case of a single pole op amp, FB can never reach $\angle T(j\omega) = -180^\circ$!

② Thus, an op amp FB ckt. w/ $f = \text{const.}$ and using a single-pole op amp is always stable!

↓

But add a few non-dominant poles \rightarrow then instability is possible!

Since now, $\angle T(j\omega)$ can reach -180° !