

• Announcements:

- ↪ Your project cannot use ideal current sources; all you have is Vdd and Vss
- ↪ You need to design your own current sources if you need them
- ↪ You should also try to minimize area, as usual (e.g., a design using an enormous resistor will not be as good as one using a much smaller one, or no resistor at all)



• Today:

↪ CMOS Op Amp Compensation

Last Time -

Choosing  $C_c$  (assume no RHP zeros &  $|p_3| \gg |p_2|$ )  
 ⇒ assume  $\frac{1}{sC_c} \ll$  (surrounding resistance) @ high freq.

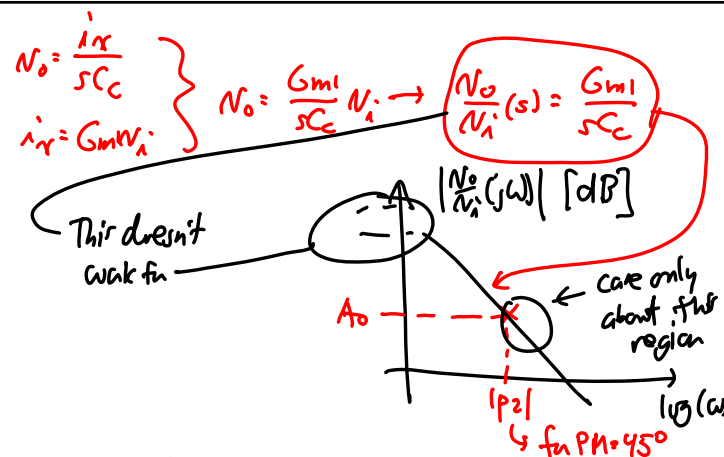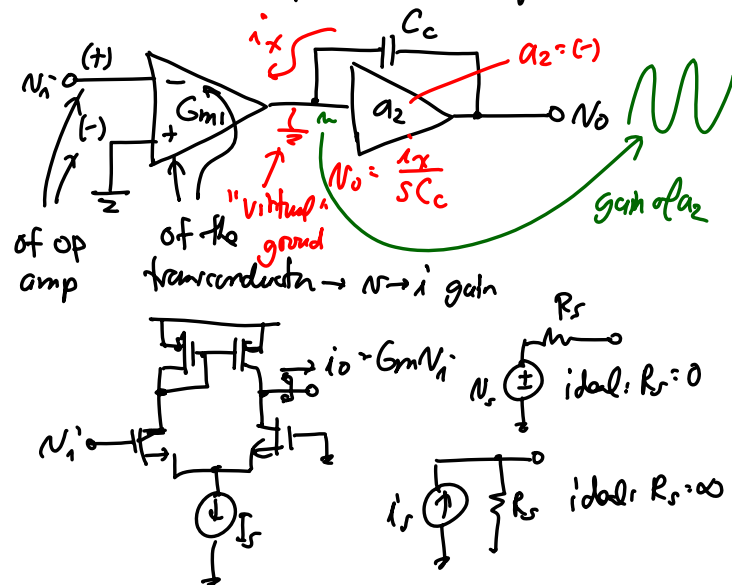① Case: Two-stage Amplifier, Miller compensation



$$\left| \frac{N_o}{N_i}(j\omega) \right| = \frac{Gm_1}{\omega C_c} \Rightarrow \text{this should equal } A_o \text{ @ the freq. } \omega \text{ corresponding to the target phase margin}$$

For PM = 45°:

$$\omega_{ulg} = \omega @ |T(j\omega)| = 1$$

“ulg” = “unity loop gain”

For PM = 45° →  $\omega_{ulg} = \omega_2$  ← freq. of the 2nd pole in the  $a(j\omega)$  transfer function

$$\left| \frac{N_o}{N_i}(j\omega_2) \right| = A_o = \frac{Gm_1}{\omega_2 C_c}$$


$$C_c = \frac{Gm_1}{\omega_2 A_o} \leftarrow \text{For PM} = 45^\circ \text{ (provided high-order poles are far away, i.e., } |p_3| \gg |p_2|)$$

For PM = 60°:

$$\omega_{ulg} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{N_o}{N_i}(j\frac{\omega_2}{1.73}) \right| = A_o = \frac{Gm_1}{(\frac{\omega_2}{1.73}) C_c}$$

$$C_c = \frac{1.73 Gm_1}{\omega_2 A_o} \leftarrow \text{For PM} = 60^\circ$$

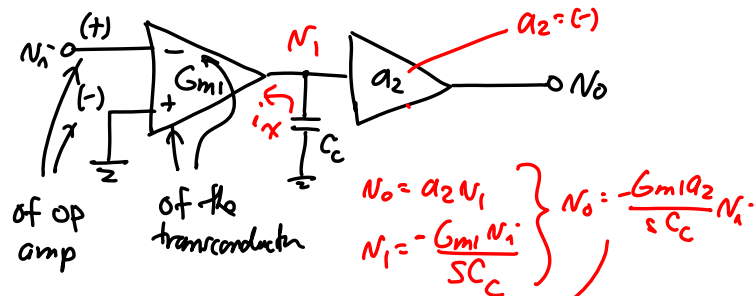② Case: Two-Stage Amplifier, Shunt  $C_c$  Compensation



$\therefore \frac{N_o}{N_i}(s) = -\frac{G_{m1} a_2}{s C_c}$  } Closed loop gain  $A_{cl}$  must again intersect this curve @ the right  $\omega_{lg}$  for a given PM

For PM = 45°:

$$\left| \frac{N_o}{N_i}(j\omega_{lg}) \right| = A_o \cdot \frac{G_{m1} a_2}{\omega_{lg} C_c}$$


For PM = 45°:  $\omega_{lg} = \omega_2 \Rightarrow$

$$C_c = \frac{G_{m1} a_2}{\omega_2 A_o} \leftarrow \text{For PM} = 45^\circ$$



For PM = 60°:

$$C_c = \frac{1.73 G_{m1} a_2}{\omega_2 A_o}$$

Case ③: Single-Stage Amplifier, Shunt  $C_c$  Compensation  
e.g., telescopic op amp

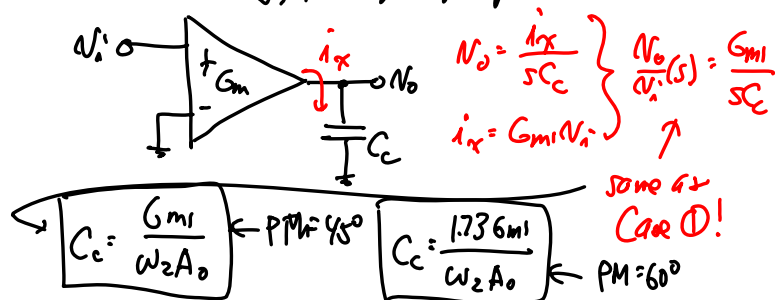

CMOS 2-Stage Op Amp Compensation

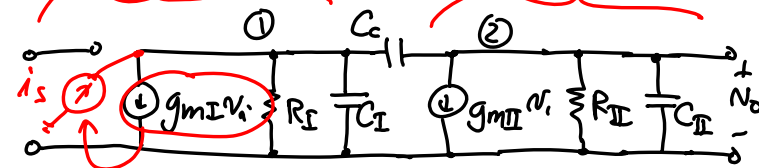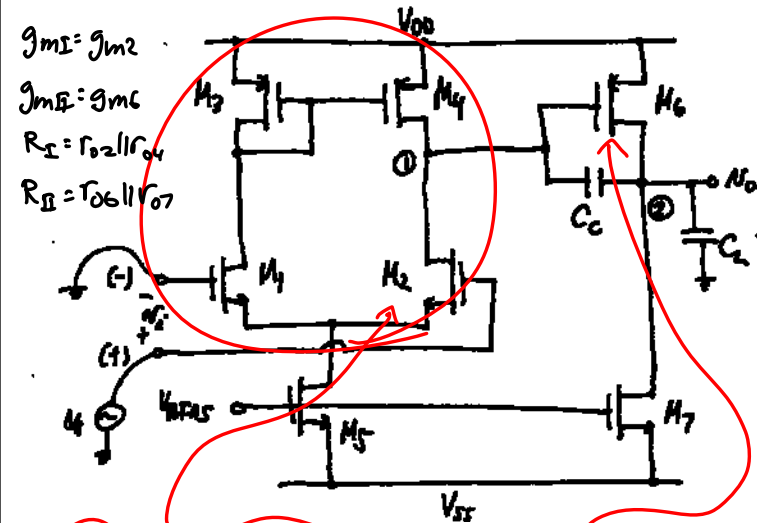

$$\text{KCL ①: } i_s = \frac{N_i}{R_I} + s C_I N_i + (N_i - N_o) s C_c$$

$$\text{KCL ②: } g_{mII} N_i + \frac{N_o}{R_{II}} + s C_{II} N_o + (N_o - N_i) s C_c = 0$$

$$\frac{N_o}{i_s} = \frac{(g_{mII} - s C_c) R_I R_{II}}{1 + s[(C_{II} + C_c) R_{II} + (C_I + C_c) R_I + g_{mII} R_I R_{II} C_c] + s^2 R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$$= \frac{N(s)}{D(s)}$$

This Xfer fun has 2 poles & a zero!

The zero:  $N(s) = 0 \rightarrow \boxed{z = \frac{g_{mII}}{C_c}} \leftarrow (+) \text{ and real}$   
 $z = s$

The poles:

$$D(s) = \left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) = 1 - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

$$[p_2 \gg p_1] \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

$\uparrow$  i.e.,  $p_1$  is a dominant pole

Thus:

$$p_1 = - \frac{1}{(C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_I R_{II} C_c}$$

As  $C_c \uparrow \rightarrow p_1 \downarrow \rightarrow \approx - \frac{1}{g_{mII} R_I R_{II} C_c}$


For the 2nd pole:

$$p_1 p_2 = \frac{1}{R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$$\boxed{p_2 \approx - \frac{g_{mII} C_c}{C_I C_{II} + C_c C_I + C_c C_{II}}}$$

As  $C_c \uparrow \rightarrow p_2 \approx - \frac{g_{mII}}{C_I + C_{II}} \leftarrow \text{This is higher than before!}$

$C_c \uparrow \rightarrow p_2 \uparrow$

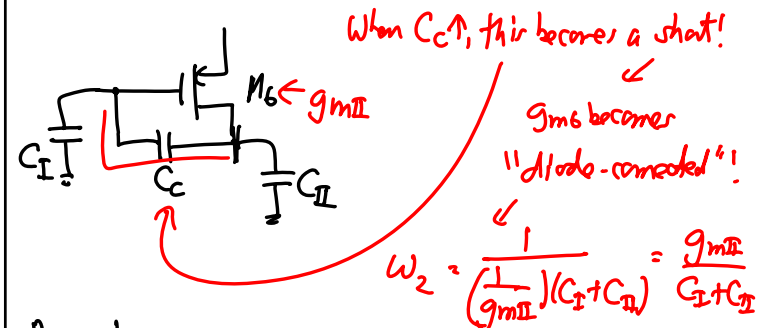


Remarks:

- ① Note that as  $C_c \uparrow \rightarrow p_1 \downarrow \rightarrow 0$
- ② As  $C_c \uparrow \rightarrow p_2 \uparrow \rightarrow p_2 = \frac{g_{mII}}{C_I + C_{II}}$
- ③ With  $C_c = 0$  (i.e., before compensation)

$$p_1 = - \frac{1}{R_I C_I}, \quad p_2 = - \frac{1}{R_{II} C_{II}}$$

- ④ On a pole zero diagram:

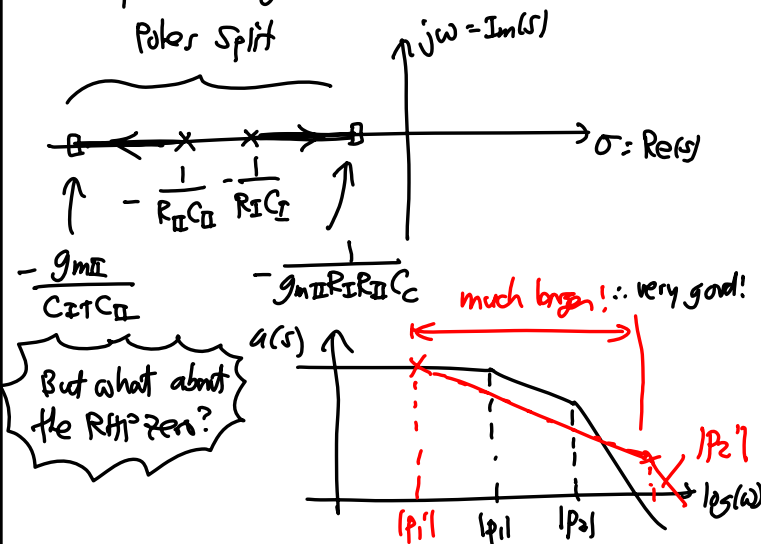


Again, we're mainly concerned here w/ phase margin; i.e., stability.

How does a RHP zero affect the PM?

→ compare a LHP zero w/ a RHP zero:

① LHP zero: (and 2 poles)

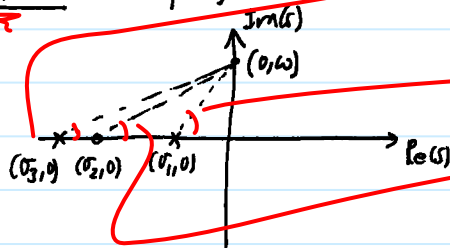


$$|H(j\omega)| = \frac{\sqrt{\omega^2 + \sigma_2^2}}{\sqrt{\omega^2 + \sigma_1^2} \sqrt{\omega^2 + \sigma_3^2}} \quad \omega \rightarrow 0 \quad 0 - \sigma_2$$

$$\angle H(j\omega) = +\tan^{-1}\left(\frac{\omega}{-\sigma_2}\right) - \tan^{-1}\left(\frac{\omega}{-\sigma_1}\right) - \tan^{-1}\left(\frac{\omega}{-\sigma_3}\right)$$


$$= \tan^{-1}\left(\frac{\omega}{|\sigma_2|}\right) - \tan^{-1}\left(\frac{\omega}{|\sigma_1|}\right) - \tan^{-1}\left(\frac{\omega}{|\sigma_3|}\right)$$

Thus:

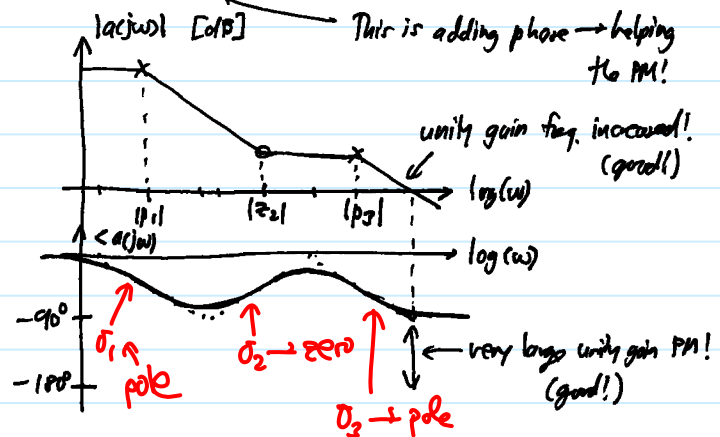

A LHP zero can really improve the performance + stability of an op amp PS ckt.

② RHP zero: (and 2 poles)

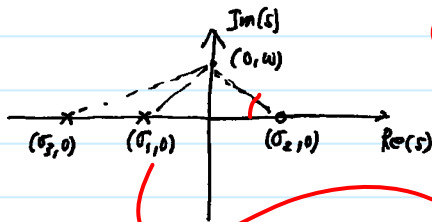


$$|H(j\omega)| = \frac{\sqrt{\omega^2 + \sigma_2^2}}{\sqrt{\omega^2 + \sigma_1^2} \sqrt{\omega^2 + \sigma_3^2}} \quad \text{same as above!}$$

$$\angle H(j\omega) = +\tan^{-1}\left(\frac{\omega}{-\sigma_2}\right) - \tan^{-1}\left(\frac{\omega}{-\sigma_1}\right) - \tan^{-1}\left(\frac{\omega}{-\sigma_3}\right)$$

$$= +\tan^{-1}\left(-\frac{\omega}{|\sigma_2|}\right) - \tan^{-1}\left(\frac{\omega}{|\sigma_1|}\right) - \tan^{-1}\left(\frac{\omega}{|\sigma_3|}\right)$$

Thus:

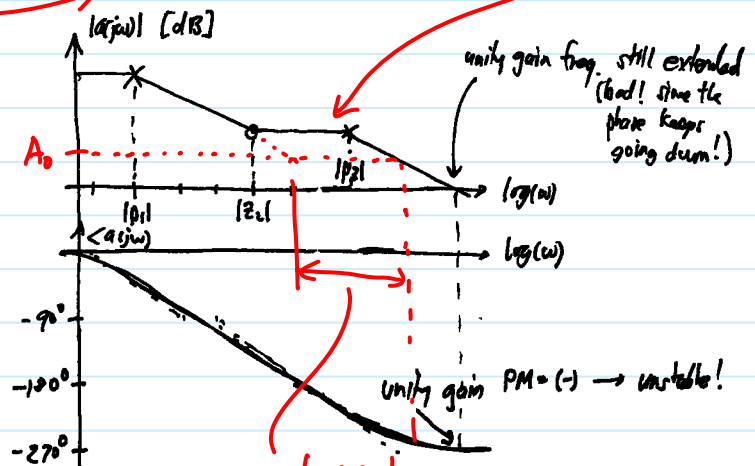

A RHP zero is detrimental because:

- ① extends the  $\omega_{u1}$
- ② while continuing to drop the phase

↓  
instability!

Problem!

→ to solve, must first understand where the zero comes from!

more unstable! X