

• **Announcements:**

↳ Make-up lecture tonight, 7 p.m., in 247 Cory


• **Today:**

↳ RHP Zero Issues for Compensation

↳ Slew Rate Design

Last Time -

**CMOS 2-Stage OpAmp Compensation**

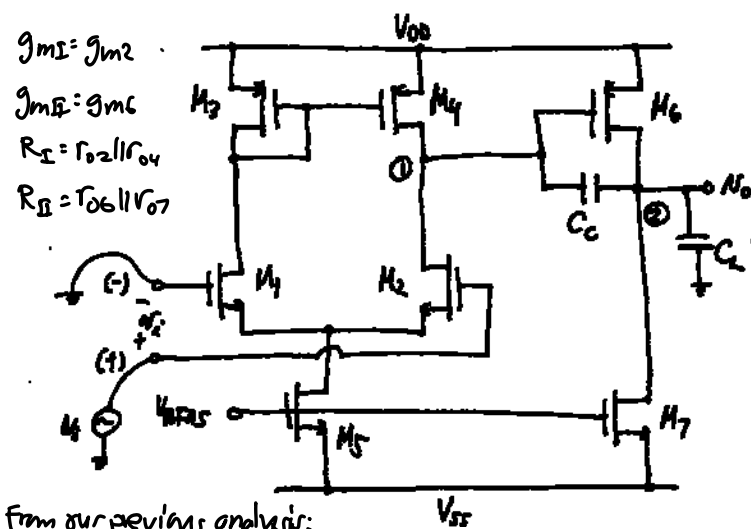


From our previous analysis:

$$p_1 = -\frac{1}{g_{mII} R_I R_{II} C_c} \quad [C_c \gg C_{I1} \text{ or } C_{I2}] \quad [C_c \gg C_I]$$


$$p_2 = -\frac{g_{mII} C_c}{C_I C_{II} + C_c (C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{m6}}{C_1}$$

$$z = +\frac{g_{mII}}{C_c} \leftarrow \text{RHP zero (this will cause problems)}$$

Where does the RHP zero come from?

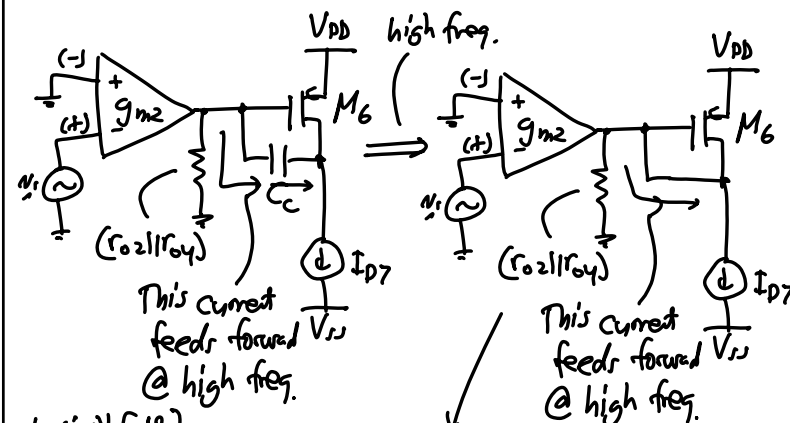


$|a(j\omega)|$  [dB]

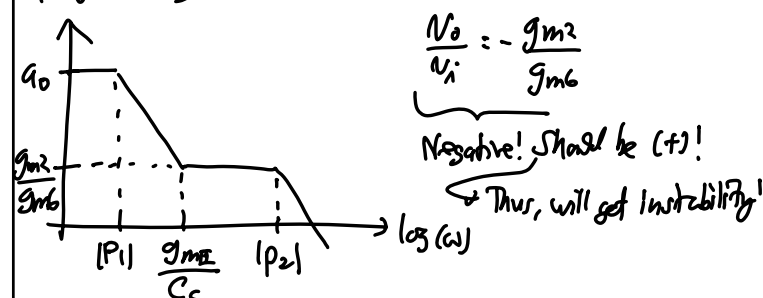

Observation:

The Miller effect (for compensation) requires the FB path  
↳ BUT: the feedforward path (that causes the zero) isn't needed!

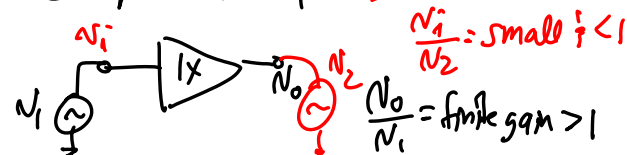Solution: ① kill the feedforward path } Stick in a unity gain buffer in series w/ the  $C_c$   
② keep the feedback path



The Ckt:

Apply KCL:

$$p_1 \approx -\frac{1}{g_{mII} R_I R_{II} C_c} \quad (\text{Same as before})$$

$$p_2 \approx -\frac{g_{mII} C_c}{C_{II}(C_I + C_c)} \approx -\frac{g_{mII}}{C_{II}} \quad [C_c \gg C_I]$$

$$p_3 \approx \frac{-1}{R_o(C_I C_c / (C_I + C_c))} \approx \frac{-1}{R_o C_c} \leftarrow \text{Series combination of } C_I \text{ \& } C_c.$$

Cover from this node

$$z_2 \approx -\frac{1}{R_o C_c} \leftarrow \text{LHP zero! (Good!)}$$

Remarks:

- ① An additional pole  $p_3 = -\frac{1}{R_o C_I}$  has been created! But since  $R_o$  is small (for a buffer) and  $C_I$  is small,  $p_3$  is at a very high freq.  $\rightarrow$  contributes very little phase @  $\omega_{ulg}$ , where  $|TC(j\omega)| = 1$ .
- ② A LHP zero now emerges,  $z_2 = -\frac{1}{R_o C_c}$ .  
This helps stability as discussed before.  
(by contributing  $C_I$  phase shift  $\rightarrow$  PMF)

Actual Implementation of Beta-Band Zero Cancellation

$$R_{o8} \approx \frac{1}{g_{m8}} = \frac{1}{\sqrt{2\mu_n C_{ox} (W/L) I_{D8}}} \rightarrow \text{want this sufficiently small to drive } |p_3| \uparrow$$

must use large enough  $I_{D8}$   
 $\hookrightarrow$  Problem: power dissipation!

Solution: a better technique!

Nulling Resistor in Series w/  $C_c$

Doing KCL:

$$p_1 \approx -\frac{1}{g_{mII} R_I R_{II} C_c}$$

$$p_2 \approx \frac{-g_{mII} C_c}{C_I C_{II} + C_c(C_I + C_{II})} \approx -\frac{g_{mII}}{C_{II}} \quad \left. \begin{array}{l} \text{Same as} \\ \text{before} \end{array} \right\}$$

$$p_3 = -\frac{1}{R_2 C_I} \leftarrow \text{pole due to } R_2$$

$$z_1 = \frac{1}{C_c \left( \frac{1}{g_{mII}} - R_2 \right)} \leftarrow \text{relocated zero (function of } R_2 \text{)}$$

Note: The position of the zero depends upon the value of the "nulling resistor"  $R_2$ .


If  $R_2 < \frac{1}{g_{mII}}$  then  $z_1$  is in the RHP  
If  $R_2 > \frac{1}{g_{mII}}$  then  $z_1$  " " " LHP!

This is great!  $\rightarrow$  can convert the zero to a LHP one!

can even stick it right on top of a pole!  
 $H(s) = \dots \frac{(s-z_1)}{(s-p_1)}$   
If  $z_1 = p_1$

The Root Locus:

Where everything starts w/o the  $R_2$

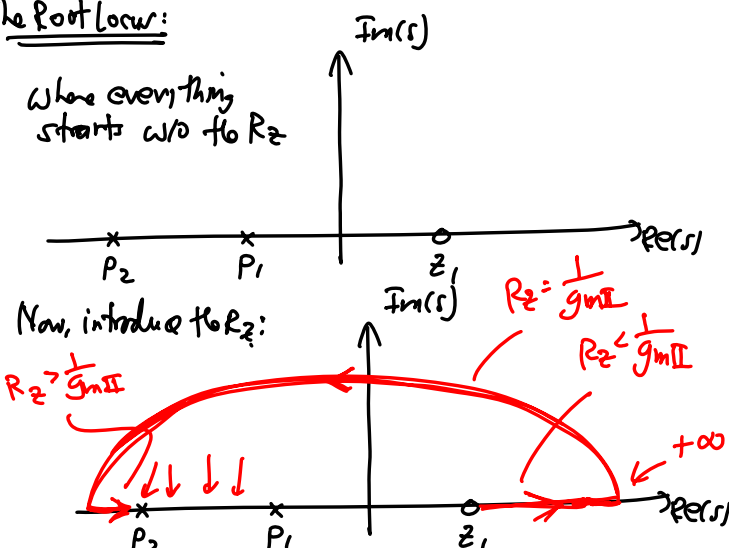

Now, introduce the  $R_2$ :

### Zero Placement Strategies

① Eliminate  $z_1$ ,  $\rightarrow$  move it to  $\infty$ :

$$z_1 = \frac{1}{C_c \left( \frac{1}{g_{mII}} - R_2 \right)} \rightarrow \infty \text{ when } R_2 = \frac{1}{g_{mII}} \text{ (lead cap.)}$$

After doing this:  $p_3 \approx -\frac{g_{mII}}{C_I}$   
This is good... but we can do better...  
 $p_2 \approx -\frac{g_{mII}}{C_{II}}$   
Usually,  $C_{II} \gg C_I$ , so these poles are far apart... but be careful...

② Eliminate  $p_3$  by placing  $z_1$  on top of it:

$$z_1 = p_3 \Rightarrow \frac{1}{C_c \left( \frac{1}{g_{mII}} - R_2 \right)} = -\frac{1}{R_2 C_I}$$

$$R_2 = \frac{1}{g_{mII} \left( 1 - \frac{C_I}{C_c} \right)}$$

After this:

①  $p_3$  gone,  $p_1$  &  $p_2$  left


② Now, can place w/  $\omega_p$  @  $p_2$  and really get PM=45°  
(w/o worrying about the influence of  $p_3$ )

But can still do better than this...  $\rightarrow$  over

③ Eliminate  $p_2$  by placing  $z_1$  on top of it:

$$z_1 = p_2 \rightarrow \frac{1}{C_c \left( \frac{1}{g_{mII}} - R_2 \right)} = - \frac{g_{mII}}{C_{II}}$$
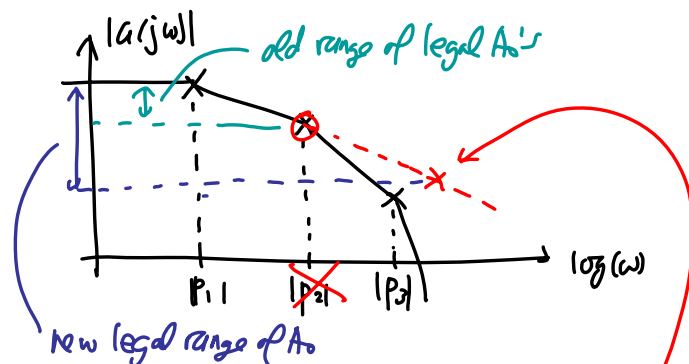
$$R_2 = \left( \frac{C_c + C_{II}}{C_c} \right) \left( \frac{1}{g_{mII}} \right) = \frac{1}{g_{mII}} \left( 1 + \frac{C_{II}}{C_c} \right)$$



With this choice of  $R_2$ :

$$p_3 = - \frac{1}{R_2 C_I} = - \frac{1}{\left( \frac{C_c + C_{II}}{C_c} \right) \left( \frac{1}{g_{mII}} \right) C_I}$$

$$p_3 = - \frac{g_{mII} C_c}{C_I (C_c + C_{II})} \leftarrow \text{This becomes the new } p_2!$$

For  $PM = 45^\circ$ :

$$C_c = \frac{g_{mI}}{|p_3| A_0} = \frac{g_{mI}}{g_{mII}} \frac{C_I (C_c + C_{II})}{C_c A_0}$$

the "new"  $|p_2|$  solve for  $C_c$

$$C_c \cong \sqrt{\frac{g_{mI}}{g_{mII}} \frac{C_I C_{II}}{A_0}}$$

For  $PM = 45^\circ$ .

For  $PM = 60^\circ$ :

$$C_c = \frac{1.73 g_{mI}}{|p_3| A_0} \rightarrow C_c \cong \sqrt{\frac{1.73 g_{mI}}{g_{mII}} \frac{C_I C_{II}}{A_0}}$$

$[C_I \ll C_{II}]$   $\uparrow$  For  $PM = 60^\circ$ .


Remark. If settling time is important, then approach ③ may not be the best approach. The reason is that if the zero is not exactly equal to the pole, then a "doublet" ensues, which actually can hurt the settling time.

Discussed in a handout to be posted on the course website.  $\rightarrow$  also, discussed in Razavi, problem 10.11.

Actual Implementation

$\Rightarrow$  resistors are too big!  $\rightarrow \therefore$  implement using a much smaller MOS resistor!

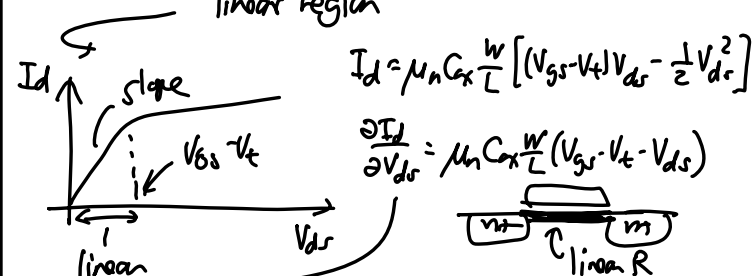MOS Resistor: just an MOS transistor operated in the linear region



$$R_{s,s} = \left[ \frac{dI_d}{dV_{DS}} \right]^{-1} \bigg|_{V_{GS}=V_{GS}, V_{DS}=V_{DS}} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t - V_{DS})} \approx \frac{1}{g_{ds}}$$

a variable resistor controlled by  $V_{GS}$ !