

• **Announcements:**

- ↗ As has been announced previously, there will be no lecture next week (this is why we've been having evening lectures)
- ↗ There will still be discussion and labs
- ↗ Mehmet will take Yang's discussion and lab sections, since Yang will also be gone
- ↗ HW#10 is due the week after next
- ↗ Use the smaller HW load to finish your project

• **Today:**

- ↗ Settling Time
- ↗ Power Supply Rejection Ratio (PSRR)

Last Time -

Settling Time


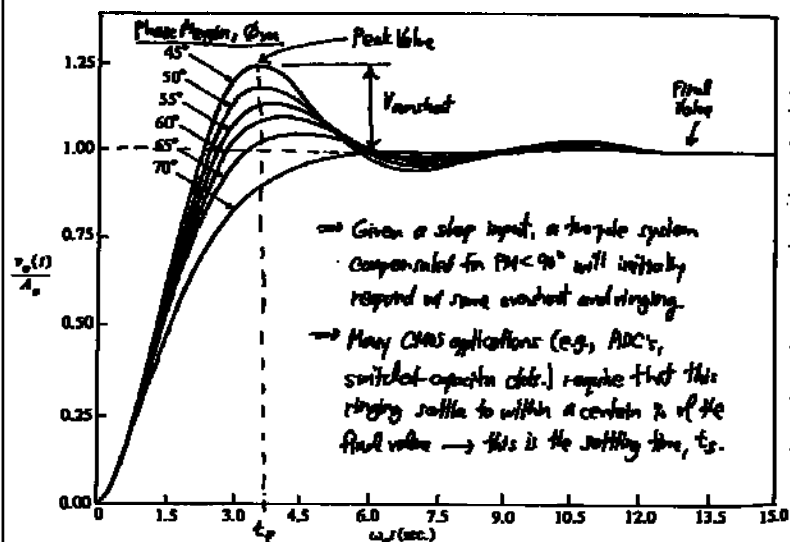


Figure 8.2-3 Response of second-order system with various phase margins.

Obtain Expressions for:

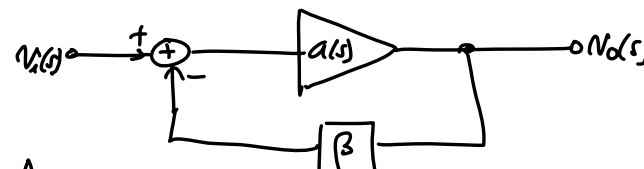- ① $V_{\text{overshoot}}$
 - ② Settling Time, T_s
- as functions of phase margin, Φ_m



Assume: $\beta = \text{const w freq.}$

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)\beta}$$

$$a(s) = \frac{a_0}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})} = \frac{a_0 \omega_1 \omega_2}{(s + \omega_1)(s + \omega_2)}$$

$$A(s) = \frac{a_0 \omega_1 \omega_2}{s^2 + (\omega_1 + \omega_2)s + \omega_1 \omega_2 (1 + a_0 \beta)}$$

$$= \frac{A_0 \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2} = \frac{A_0 \omega_0^2}{s^2 + (\frac{\omega_0}{Q})s + \omega_0^2}$$

$[\omega_0 = \omega_n]$

General Lowpass Biquad
Transfer Functions

where by direct comparison:

$$\omega_n = \sqrt{\omega_1 \omega_2 (1 + a_0 \beta)}$$

$$2\zeta \omega_n = \omega_1 + \omega_2 \rightarrow \zeta = \frac{\omega_1 + \omega_2}{2\omega_n} = \frac{1}{2} \frac{\omega_1 + \omega_2}{\sqrt{\omega_1 \omega_2 (1 + a_0 \beta)}}$$

$$A_0 \omega_n^2 = a_0 \omega_1 \omega_2 \rightarrow A_0 = \frac{a_0}{1 + a_0 \beta} \quad \checkmark$$


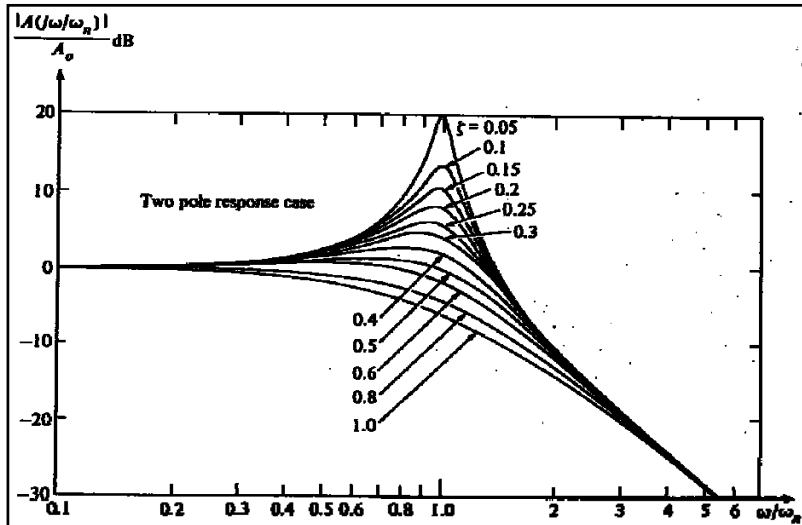



Figure C-2 Gain magnitude response for various values of ζ for a second-order, low-pass system.

Properties of the General Laplace Biquad Xfer Function

Pole-zero Diagram -

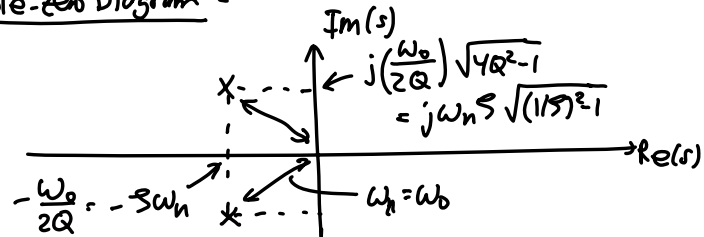

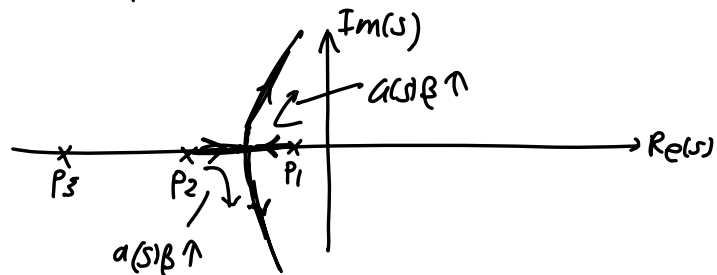Root locus: poles move as the loop gain increases



Time Domain Behavior -


$$V_o(t) = A_o V_i \left[1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta \omega_n t} \sin(\sqrt{1-\zeta^2} \omega_n t + \phi) \right]$$

$$\text{where } \phi = \tan^{-1} \left[\frac{\sqrt{1-\zeta^2}}{\zeta} \right]$$

For $\zeta < 1$:

$$\% \text{Overshoot} = \frac{\text{Peak Value} - \text{Final Value}}{\text{Final Value}} = \exp \left[\frac{-\pi \zeta}{\sqrt{1-\zeta^2}} \right]$$
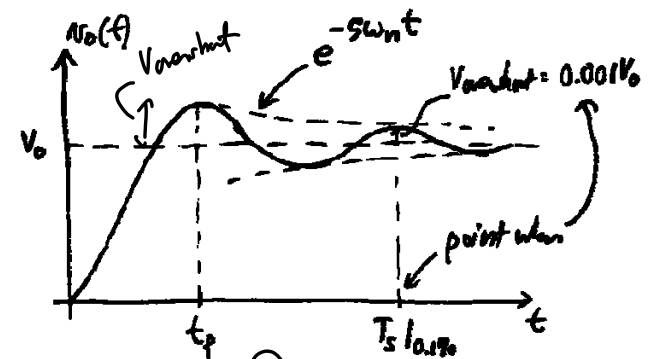
$$V_{\text{overshoot}} = V_o \exp \left[\frac{-\pi \zeta}{\sqrt{1-\zeta^2}} \right]$$



Find t_p : where $\sin(\cdot) = \frac{3\pi}{2}$

$$\sqrt{1-\zeta^2} \omega_n t_p + \phi = \frac{3\pi}{2}$$

$$[\zeta = \text{small} \rightarrow \phi \approx \frac{\pi}{2}] \Rightarrow t_p = \frac{\pi}{\omega_n \sqrt{1-\zeta^2}}$$

Approx. Determination of 0.1% Settling Time -

$$V_{\text{overshoot}} e^{-\zeta \omega_n (T_s - t_p)} = 0.001 V_o$$

$$T_s = t_p - \frac{1}{\omega_n} \ln \left[\frac{0.001 V_o}{V_{overshoot}} \right]$$

$$s = -\frac{1}{\omega_n(T_s - t_p)} \ln \left[\frac{0.001 V_o}{V_{overshoot}} \right]$$

Determine $\phi_m = f(s)$ -

⇒ first, get an expression for loop X-mirror:

$$A(s) = \frac{G(s)}{1 + a(s)\beta}$$

↙ rearrange

$$a(s)\beta = \frac{\beta A(s)}{1 - \beta A(s)} = \frac{\beta A_0 \omega_n^2}{s^2 + 2s\omega_n + \omega_n^2 - \beta A_0 \omega_n^2}$$

$$\left[\beta \propto \frac{1}{A_0} \right] \Rightarrow = \frac{\omega_n^2}{s^2 + 2s\omega_n s} = \frac{\omega_n^2}{s(s + 2s\omega_n)}$$

↑
pole
@ origin

↑
LHP pole

⇒ Get freq. @ which

$$|a(s)\beta| = 1 \rightarrow \omega_{ulg}$$


$$|a(j\omega)\beta| = \frac{\omega_n^2}{\sqrt{\omega^4 + \omega^2 4s^2 \omega_n^2}} \Rightarrow = 1$$

Solve quadratic

$$\omega_{ulg} = \omega_n \left[\sqrt{4s^2 1 - 2s^2} \right]^{1/2}$$

↑
Freq. for phase margin determination.

Find expression for phase:

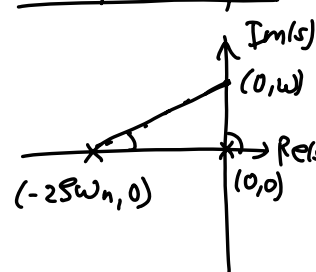

$$\phi = -\tan^{-1}\left(\frac{\omega}{0}\right) - \tan^{-1}\left(\frac{\omega}{2s\omega_n}\right)$$

$$= -90^\circ - \tan^{-1}\left(\frac{\omega}{2s\omega_n}\right)$$

Phase Margin:

$$\phi_m = 180^\circ + \phi|_{\omega = \omega_{ulg}}$$

$$= 90^\circ - \tan^{-1}\left(\frac{\omega_{ulg}}{2s\omega_n}\right)$$

$$\phi_m = \tan^{-1}\left(\frac{2s\omega_n}{\omega_{ulg}}\right)$$

$$s = \frac{1}{2} \frac{\omega_{ulg}}{\omega_n} \tan \phi_m$$

$$T_s = t_p - \frac{2}{\omega_{ulg} \tan \phi_m} \ln \left[\frac{0.001 V_o}{V_{overshoot}} \right]$$

⇒ But don't rely on it then this. See the following papers:

- ① B.J. Razavi, R.G. Meyer, and P.R. Gray. "Relationship between frequency response and settling time of operational amplifiers," IEEE J. of Solid-State Circuits, vol. 22, no. 6, pp. 877-882, Dec. 1987.
- ② R.J. Apfel and P.R. Gray. "A fast-settling monolithic operational amplifier using doublet compression techniques," IEEE J. of Solid-State Circuits, vol. 22, no. 6, pp. 522-528, Dec. 1987.

Power Supply Rejection (PSRR)

In today's mixed-signal ckt:

No problem for
Big problem for

Ex. CMOS Diff. Input Stage w/ Current Mirror Load

Thus:

$$\frac{N_o}{N_{dd}} \approx 1 \Rightarrow \text{supply noise directly seen @ output!}$$

Definition: Power Supply Rejection Ratio (PSRR)

$$\text{PSRR} \triangleq \frac{\text{Gain From Input to Output}}{\text{Gain From Supply to Output}} = \frac{A_v|_{N_{dd}=0}}{A_{dd}|_{V_i=0}}$$

Thus, for the above example: $\text{PSRR} \approx \frac{g_{m2}(r_{o2}||r_{o4})}{1}$

$\Rightarrow \text{PSRR} \approx g_{m2}(r_{o2}||r_{o4})$

For more complicated circuits, much more work is involved.
 ↳ to make it easier, use a unity gain configuration
 ↳ can also get $\text{PSRR} = f(\omega)$

Ex. PSRR+

$$N_o = A_v(N_1 - N_2) + A_{dd}N_{dd}$$

$$N_o(1 + A_v) = A_{dd}N_{dd}$$

$$\frac{N_o}{N_{dd}} = \frac{A_{dd}}{1 + A_v} = \frac{1}{\frac{1}{A_{dd}} + \frac{A_v}{A_{dd}}} \approx \frac{1}{\text{PSRR}^+} = \frac{N_o}{N_{dd}}$$

Thus, just find this Xfer Function to get PSRR+ when the op-amp is hooked into unity gain FB!

Two-Stage OpAmp PSRR⁺ Want $PSRR^+ = f(\omega)$ \uparrow freq.

Debrute force network analysis:

KCL[Ⓐ]: $G_I N_{dd} = (G_I + sC_c + sC_f) V_{N1} - (g_{mI} + sC_c) V_{No}$
 KCL[Ⓑ]: $(g_{mII} + g_{ds6}) V_{No} = (g_{mII} - sC_c) V_{N1} + (G_{II} + sC_c + sC_{II}) V_{No}$

$G_I = g_{ds1} + g_{ds4} = g_{ds2} + g_{ds5}$
 $G_{II} = g_{ds6} + g_{ds7}$
 $g_{mI} = g_{m1} = g_{m2}$
 $g_{mII} = g_{m6}$

$[g_{ds} = \frac{1}{r_o}]$
 For saturated device.

math & rearranging

Get:

$$\left(\frac{V_{No}}{V_{dd}} \right)_{\text{closed-loop}} = \frac{N(s)}{D(s)} = \left(\frac{\text{numerator}}{\text{denominator}} \right) \text{ polynomial}$$

Then use: $N(s) = 1 + \left(\frac{s}{z_1} + \frac{s}{z_2} \right) + \frac{s^2}{2\tau_2^2} \approx 1 + \frac{s}{z_1} + \frac{s^2}{2\tau_2^2}$

$$PSRR^+ = A_{No}^+ \left[\frac{(1 + \frac{s}{GB})(1 + \frac{s}{\omega_{p1}})}{(1 + \frac{s}{GB/A_{No}^+})} \right]$$

Where $GB = \text{Gain BW Product} = \frac{g_{mI}}{C_c}$
 $A_{No}^+ = \text{DC PSRR}^+ = \frac{g_{mI} g_{mII}}{G_I g_{ds6}}$
 $\omega_{p1} = \frac{g_{mII}}{C_{II}} \quad \omega_p^+ = \frac{GB}{A_{No}^+}$

To maximize PSRR⁺: (@dc) decrease g_{ds6} , raise g_{mII}

$$PSRR^- = A_{No}^- \left[\frac{(1 + \frac{s}{GB})(1 + \frac{s}{\omega_{p2}})}{(1 + \frac{s}{\omega_{p-}})} \right]$$

where $A_{No}^- = \frac{g_{mI} g_{mII}}{G_I g_{ds7}}$
 $GB = \frac{g_{mI}}{C_c} \quad \omega_{p-} = \frac{G_I}{C_c + C_{II}} \approx \frac{G_I}{C_c}$
 $\omega_{p2} = \frac{g_{mII}}{C_{II}}$

To maximize PSRR⁻: ① decrease g_{ds7}
 ② increase $g_{mII} = g_{m6}$

Remarks.

① Since often $g_{m7} < g_{m6} \rightarrow \text{often } \text{PSRR}^- > \text{PSRR}^+ (\text{@dc})$

$$\frac{\omega_p^-}{\omega_p^+} = \frac{\cancel{C_1/C_2}}{\cancel{C_1 g_{m6}} / \cancel{g_{m2} C_2}} = \frac{g_{m2}}{g_{m6}} \rightarrow \text{that's quite large}$$

$\therefore \omega_p^- \gg \omega_p^+$

Thus, for an NMOS input op amp, PSRR^- is often better than PSRR^+ . \rightarrow in design, need to worry more about PSRR^+ !

③ Some methods for reducing PSRR:

- (i) Use buffer-based zero-cancellation in the compensation loop.
- (ii) Use cascode circuitry, or balanced circuit topologies.
- (iii) Supply-independent biasing.
- (iv) Design strategies to minimize parasitic capacitive feedthrough.