

• Announcements:

⇒ Project is due this Friday, 5/1, at 8 p.m.

• Today:

⇒ Feedback: Pros & Cons

⇒ Inspection Analysis of FB Ckts

⇒ Effect of Feedback on Z_i and Z_o


Last Time -

⇒ finished CMOS op amp design

↓ New Topic (well, not entirely new... but there's a lot more important stuff to know)

Feedback

⇒ we know this:

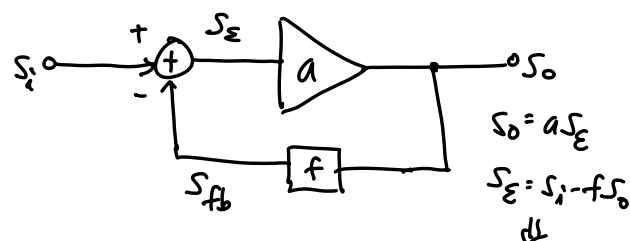

$$\frac{S_o}{S_i} = \frac{a}{1+af} = A$$

Benefits of Negative FB

- ① Stabilizes the gain of the amp against parameter changes & active device variations
- ② Modifies R_i and R_o → basically improves their values according to the type of amplifier implemented
e.g., voltage amp: R_i : large, R_o : small

@ input: If R_i : large, $V_i \approx V_s$.
($R_i \gg R_s$)

@ output: If R_o : small, $V_o \approx V_o'$.
($R_o \ll R_L$)

current-to-voltage amp: R_i : small, R_o : small

voltage-to-current amp: R_i : large, R_o : large

current-to-current amp: R_i : small, R_o : large

③ Reduces distortion; improves linearity.

④ Increases bandwidth (w-3dB).

Disadvantages of Neg. FB

① Gain is reduced → reduction factor ~ equal to the amount of gain stabilization, distortion reduction, etc...

Solution: Add more stages of gain → but this adds cost & power...

② Feedback causes stability problems (if not compensated properly)

Gain Sensitivity Reduction Via FB

$$A = \frac{a}{1+af} \rightarrow \frac{dA}{da} = \frac{(1+af) - af}{(1+af)^2} = \frac{1}{(1+af)^2}$$

For a Δ in op amp gain: Δa


$$\frac{\Delta A}{A} = \frac{1}{(1+af)^2} \rightarrow SA = \frac{\Delta a}{a} \cdot \frac{1}{(1+af)^2}$$

↑ much smaller than Δg

... and the fractional change:

$$\frac{\Delta A}{A} = \frac{1+af}{a} \frac{\Delta g}{(1+af)^2} \Rightarrow \frac{\Delta A}{A} = \frac{\frac{\Delta g}{g}}{1+af}$$

Distortion Reduction via FB

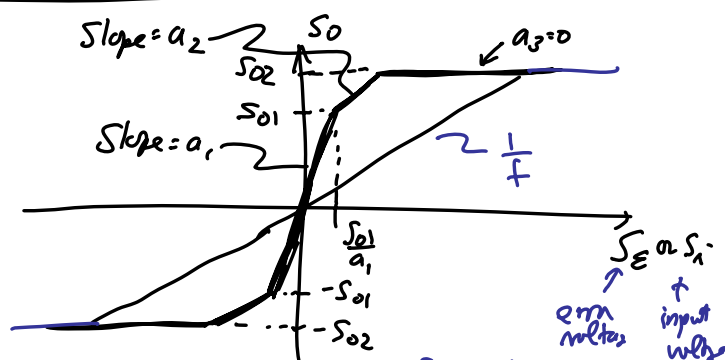

Now, close the loop:

$$0 < S_0 < S_{01}: A_1 = \frac{a_1}{1+af} \approx \frac{1}{f}$$

$$S_{01} < S_0 < S_{02}: A_2 = \frac{a_2}{1+af} \approx \frac{1}{f}$$




"Inspection" Analysis of FB Cktr.

↓ start with...

Identification of FB Connection Types


Series Connection - FB network part in series w/ amplifier part

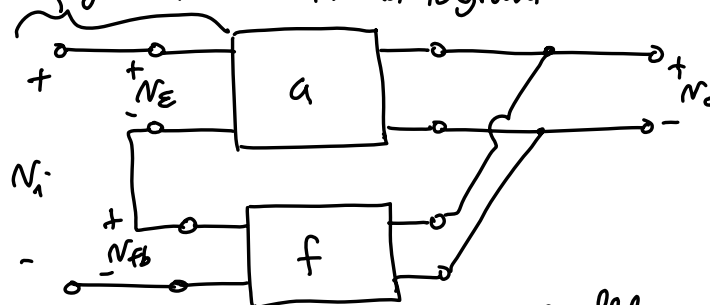must go thru both the FB part & the amplifier part to get from the node of interest to ground









Shunt Connection - FB network part in shunt w/ amplifier part

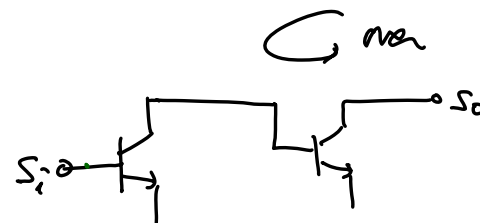can get from the node of interest to ground via either FB network part or the amplifier part



Examples:

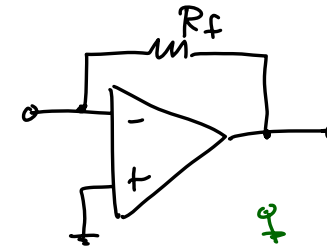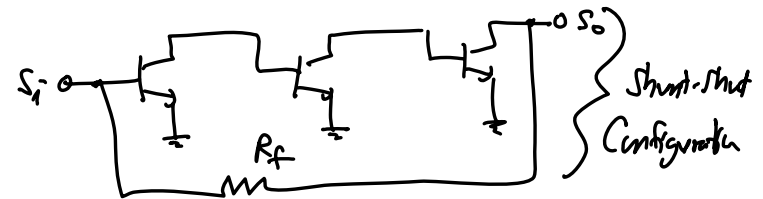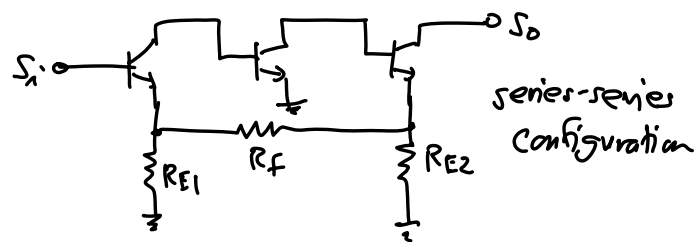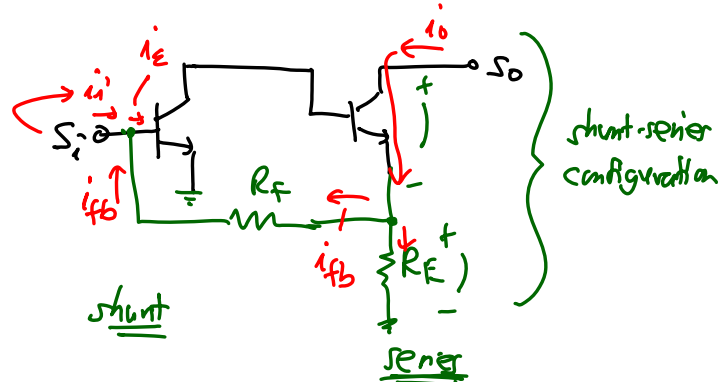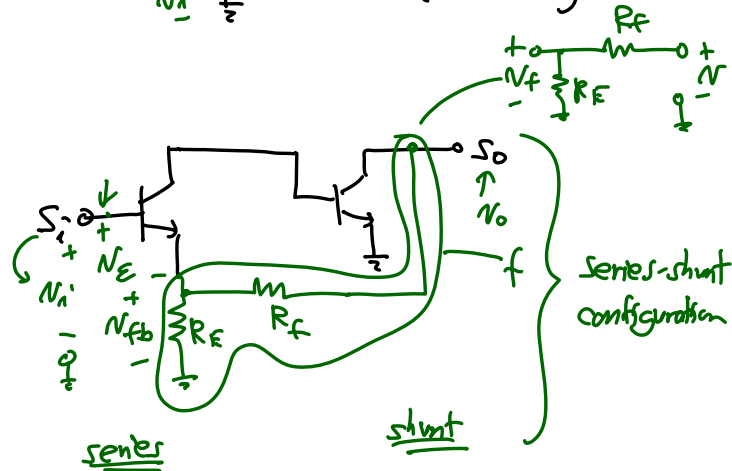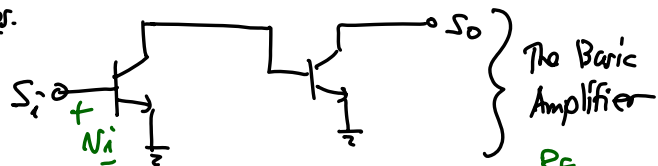

⇒ From the above, we can summarize from different combinations:

Feedback Configurations

Input		Output	
Variable	Connection	Connection	Variable
(voltage)	series	series	(current)
(current)	shunt	shunt	(voltage)
	$i \rightarrow i$	$N \rightarrow N$	

Effect of FB on z_i & z_o

Ex. Series-Shunt FB

Assumption: FB network has ideal impedances
i.e., it does not load the basic amplifier

