

• Announcements:

↳ Project is due this Friday, 5/1, at 8 p.m.

• Today:

↳ Effect of Feedback on  $Z_i$  and  $Z_o$ .

↳ Feedback loading


↳ Procedure for inspection analysis of FB

Last Time -

Identification of FB Connection Types

Series Connection - FB network part in series w/ amplifier part

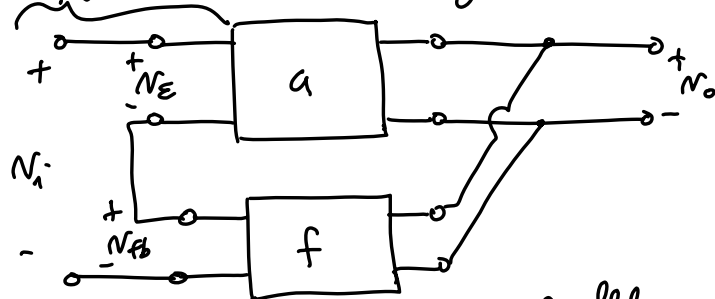↳ must go thru both the FB part & the amplifier part to get from the node of interest to ground



Shunt Connection - FB network part in shunt w/ amplifier part


↳ can get from the node of interest to ground via either FB network part or the amplifier part

Effect of FB on  $Z_i$  &  $Z_o$

Ex. Series-Shunt FB

Assumption. FB network has ideal impedances

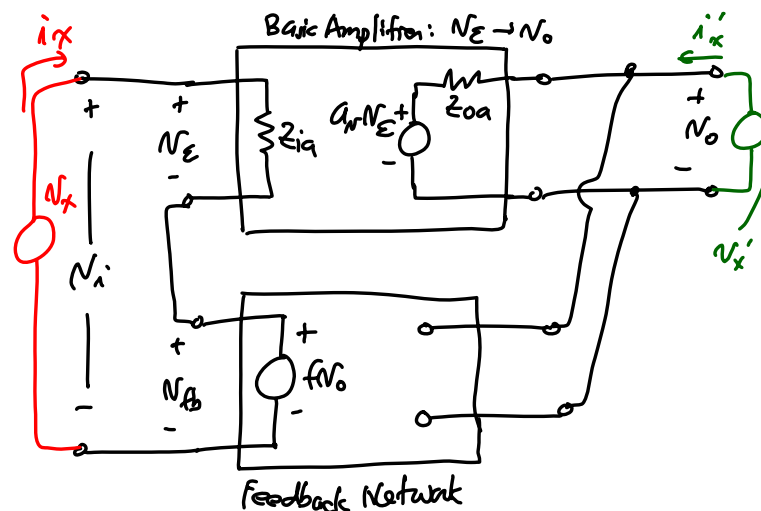↳ i.e., it does not load the basic amplifier



Find the T.F. -

$$\left. \begin{aligned} N_E &= N_i - N_{fb} \\ N_o &= a_r N_E \\ N_{fb} &= f N_o \end{aligned} \right\} \Rightarrow \frac{N_o}{N_i} = \frac{a_r}{1 + a_r f} \quad (\text{as expected})$$

Find  $Z_i = \frac{N_x}{i_x}$ :

$$N_x = N_\varepsilon + N_{fb}$$

$$= N_\varepsilon + f N_o = N_\varepsilon + a_v f N_\varepsilon = N_\varepsilon (1 + a_v f)$$

$$i_x = \frac{N_\varepsilon}{Z_{ia}}$$

$$Z_i = \frac{N_x}{i_x} = \frac{N_\varepsilon (1 + a_v f)}{\frac{N_\varepsilon}{Z_{ia}}} = \boxed{Z_{ia} (1 + a_v f) = Z_i}$$

↑  
loop gain!

When we  
series connect  
@ input

Input impedance raised! by  $(1 + a_v f)$ !  
↳ makes for a better voltage  
amplifier!

Find  $Z_o = \frac{N_x'}{i_x'}$  (w/ input shorted)

$$N_\varepsilon + N_{fb} = N_\varepsilon + f N_x' = 0 \rightarrow N_\varepsilon = -f N_x'$$

$$i_x' = \frac{N_x' - a_v N_\varepsilon}{Z_{oa}} = \frac{N_x' + a_v f N_x'}{Z_{oa}}$$

$$\frac{N_x'}{i_x'} = \boxed{\frac{Z_{oa}}{1 + a_v f} = Z_o}$$


Output impedance  
reduced by a factor  
of  $(1 + a_v f)$

⇒ Again, makes for a  
better voltage amplifier!

Overall, series-shunt FB  
improves the impedance characteristics of  
a  $v \rightarrow v$  amplifier:  $Z_i \uparrow$ ,  $Z_o \downarrow$  due to FB

Ex. Shunt-Series FB

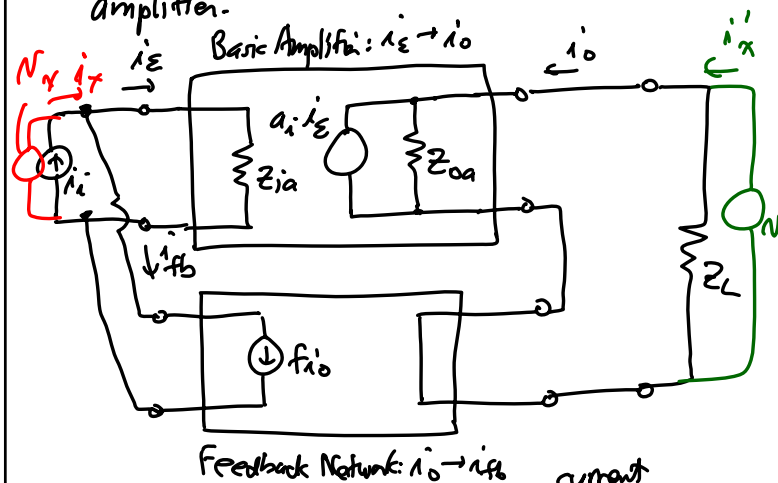⇒ Again, assume FB network does not load the  
amplifier.



Find the T.F.:

$$i_o = a_i i_\varepsilon$$

$$i_\varepsilon = i_x - i_{fb} = i_x - f i_o$$

$$\frac{i_o}{i_x} = \frac{a_i}{1 + a_i f}$$

current gain

current gain

Same as with  $v \rightarrow v$ .

It's a unusual form!

Find  $Z_i = \frac{N_x}{i_x}$ :

$$\frac{N_x}{i_x} = \frac{Z_{ia}}{1 + a_i f} = \boxed{Z_i}$$

↑  
loop gain

⇒ Again, a shunt  
connection reduces the  
impedance by  $(1 + a_i f)$ !

Find  $z_o = \frac{N_x}{i_x}$ :  $\frac{v_{x'}}{i_x} = \boxed{z_{oa}(1+a_i f) = z_o}$

series connection raises the impedance by  $(1+a_i f)$

everything together makes for a better  $i \rightarrow i$  amplifier when using shunt-series FB!

Summary.


① series connection:  $z \rightarrow z(1+T)$   $\swarrow T = \text{loop gain}$

② shunt connection:  $z \rightarrow \frac{z}{1+T}$


$\Rightarrow$  looked @ the handout & the prepared notes on "FB Loading".

Determine the FB Loading of an Amplifier

Ex. Non-Inverting Amplifier

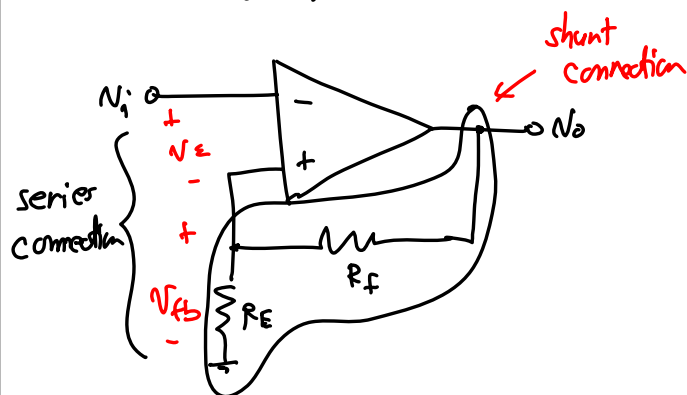

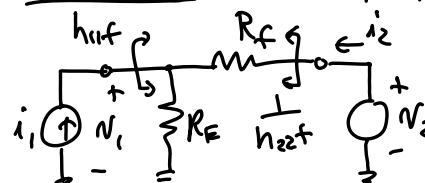The FB Network (in terms of h-parameters)




$$h_{22f} = \frac{i_2}{v_2} \Big|_{i_1=0} = \frac{1}{R_E + R_f} \quad (\text{this is loading})$$

This is a  
conductance.

$$h_{12f} = \frac{v_1}{v_2} \Big|_{i_1=0} = \frac{R_E}{R_E + R_f} = f \quad (\text{feedback gain factor})$$

$$h_{11f} = \frac{v_1}{i_1} \Big|_{v_2=0} = R_E \parallel R_f \quad (\text{this is loading})$$

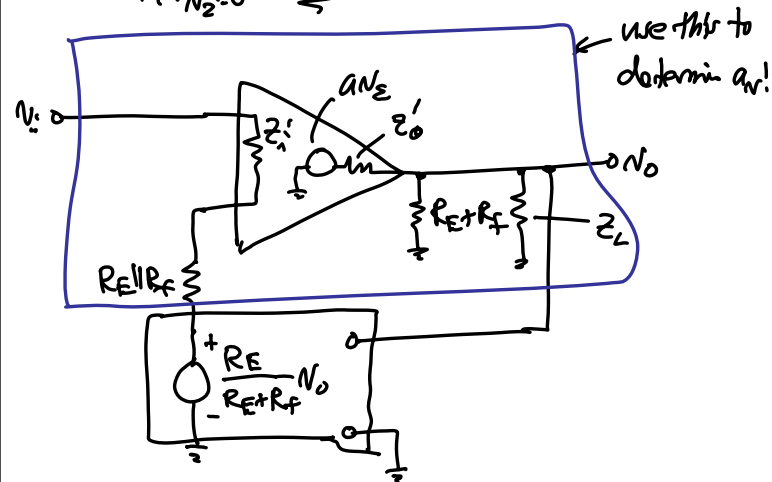


## Loading From the FB Network

Ex. Series-Shunt FB (now including loading from the FB network)

Series Connection: resistors & voltage sources add when in series  $\rightarrow$  so represent amplifier & FB networks by  $R$ 's &  $V$ 's to make the math simpler

Shunt Connection: conductances & current sources add when in parallel  $\rightarrow$  so represent amplifier & FB networks by  $G$ 's &  $I$ 's to make the math simpler

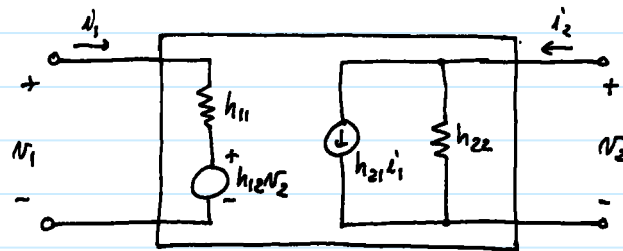For these representations, use h-parameter networks for a & f.



Port Equations:

$$V_1 = h_{11}i_1 + h_{12}V_2$$


$$i_2 = h_{21}i_1 + h_{22}V_2$$

Elements:

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

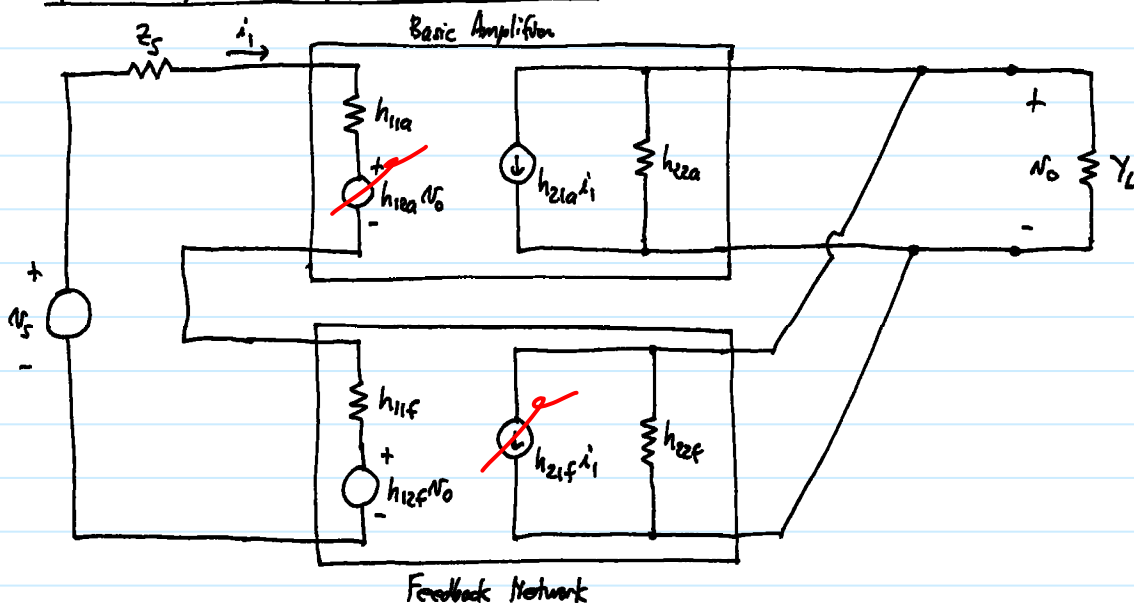h-parameter representation of the series-shunt FB ckt:




In general, transistor amplifiers & FB networks are uni-directional  $\rightarrow$  they have large gains in the forward direction, but very small gains in the reverse:

$$|h_{12a}| \ll |h_{12f}| \rightarrow \text{neglect } h_{12a} \text{ (set to 0)}$$

$$|h_{21a}| \gg |h_{21f}| \rightarrow \text{neglect } h_{21f} \text{ (set to 0)}$$

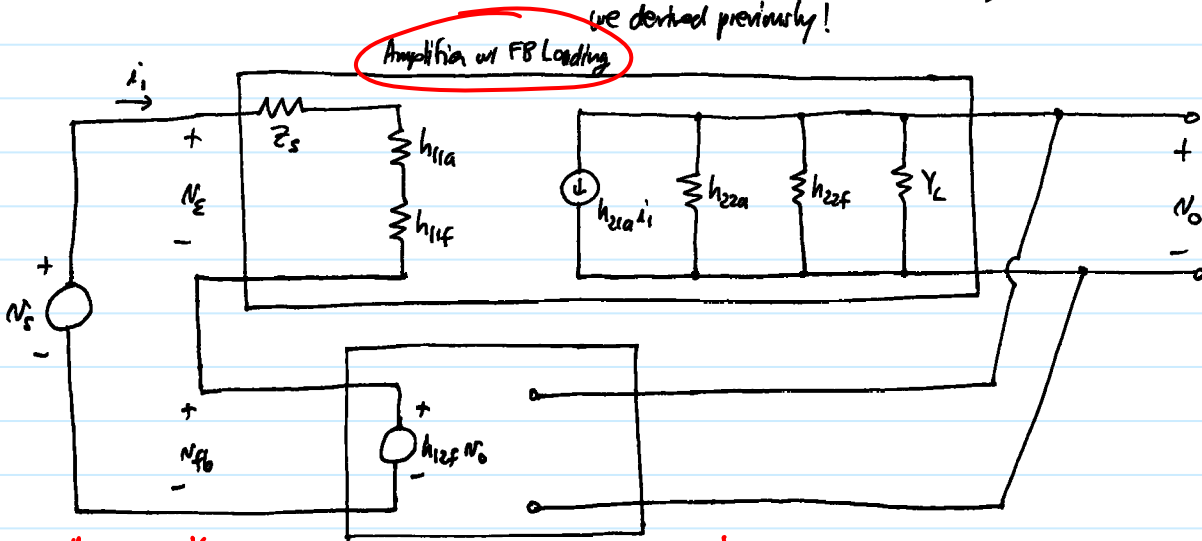⇒ move impedances to idealize the FB network → once ideal, we can use the general equations we derived previously!



Associated w/ the  
"Amplifier w/ FB Loading"

$$Z_i = Z_s + h_{11a} + h_{11f}$$

$$Y_o = Y_L + h_{22a} + h_{22f}$$

Idealized FB Network

closed loop gain

$$\frac{N_o}{N_s} = A = \frac{a}{1+af}, \text{ where } \begin{cases} a = -\frac{h_{21a}}{Z_i Y_o} \\ f = h_{12f} \left( = \frac{N_{fb}}{N_o} \right) \end{cases}$$

$$N_s = i_i Z_i \rightarrow i_i = \frac{N_s}{Z_i}$$

$$N_o = h_{21a} i_i / Y_o$$

$$\therefore \frac{N_o}{N_s} = a = \frac{-h_{21a}}{Y_o Z_i}$$

Thus, the key to inspection analysis of FB ckt: Xfer FB impedances to load the basic amplifier, then use our "inspection" formulas.