

• **Announcements:**

- ↪ HW#11 will be due Monday, 5/11, at 5 p.m., in the EE 140 box
- ↪ Error in specification of problem 2 of HW#11. See email.


• **Today:**

- ↪ Feedback loading (continued)
- ↪ Example FB Analysis Procedure

Last Time -

Determine the FB Loading of an Amplifier

Example: Non-Inverting Amplifier

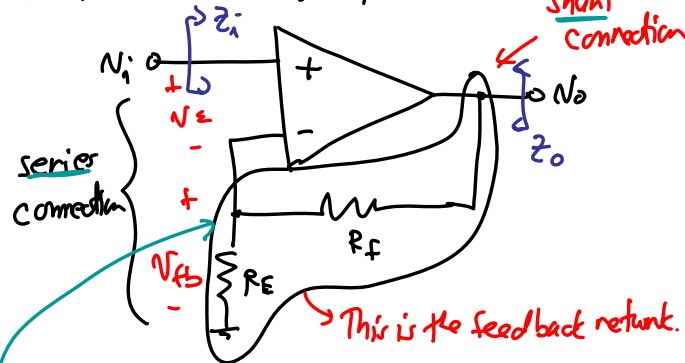


Objective: Use $A_o = \frac{a_v}{1 + a_v f}$ to get A_o .


For FB loading @ output node, open this node.

In order to use this equation, we must know
(i) $a_v \triangleq$ gain of the amplifier
(ii) $f \triangleq$ gain of the feedback (also, called the feedback factor)

In general:

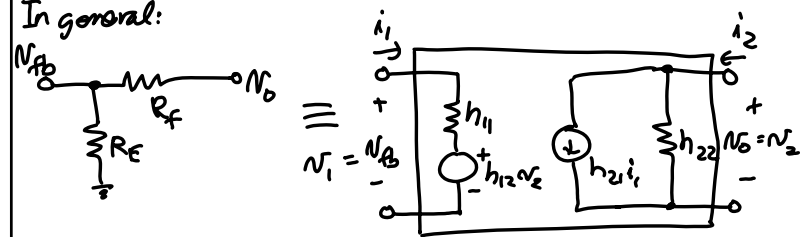


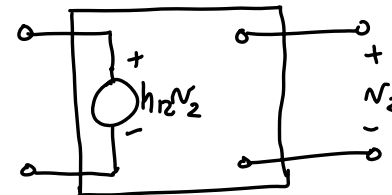But to simplify things, we would like to be able to represent the feedback network by just:



Where: ① The small h_{21} is neglected.
② All impedances have been moved out of the f-network and moved to the a_v -network.

Pictorially:

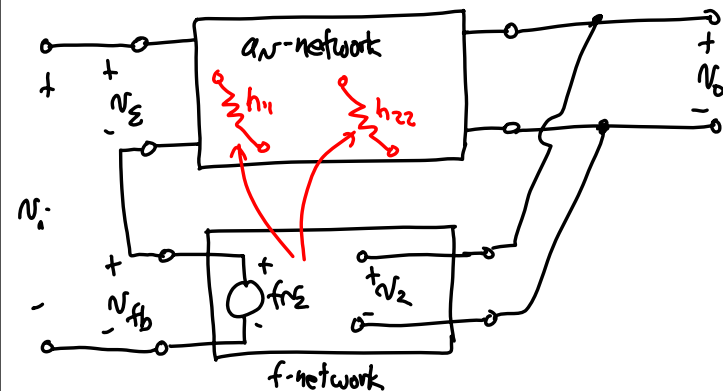

The FB Network: (find the h-parameter representation)

we'll first get this, then we'll move its impedance to the a_v -network

h-parameter Network (just a reminder)

Port Equations:

$$N_1 = h_{11}i_1 + h_{12}N_2$$

$$i_2 = h_{21}i_1 + h_{22}N_2$$

Elements:

$$h_{11} = \left. \frac{N_1}{i_1} \right|_{N_2=0} \quad h_{12} = \left. \frac{N_1}{N_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{N_2=0} \quad h_{22} = \left. \frac{i_2}{N_2} \right|_{i_1=0}$$

$h_{22f} = \left. \frac{i_2}{N_2} \right|_{i_1=0} = \frac{1}{R_E + R_F}$ (this is loading at port 2, i.e., the amplifier output port)

This is a conductance.

$h_{12f} = \left. \frac{N_1}{N_2} \right|_{i_1=0} = \frac{R_E}{R_E + R_F} = f$ (feedback gain factor)

$h_{11f} = \left. \frac{N_1}{i_1} \right|_{N_2=0} = R_E || R_F$ (this is loading at port 1, i.e., at the amplifier input port)

So we have:

put all the impedance complexity into the " a_v -network"

Next Stage Impedance


Move the R_F 's f/ the f-network

use this to determine a_v !

The new simplified f-network $\rightarrow f = \frac{R_E}{R_E + R_F}$

The new a_v -network \rightarrow use this to determine a_v in $A_0 = \frac{a_v}{1 + a_v f}$

Determine the a_v gain:

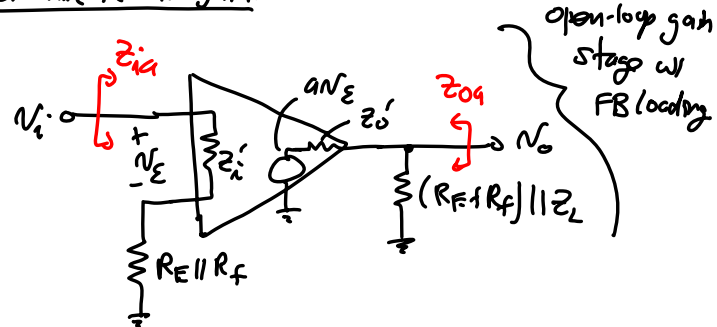

$$V_o = a_v \epsilon \left\{ \frac{(R_E + R_f) \parallel Z_L}{(R_E + R_f) \parallel Z_L + Z_o'} \right\}; \quad \epsilon = V_i \left(\frac{Z_i'}{Z_i' + R_E \parallel R_f} \right)$$

$$\therefore \left. \frac{V_o}{V_i} \right|_{\text{FB loading}} = \left(\frac{Z_i'}{Z_i' + R_E \parallel R_f} \right) a \left(\frac{(R_E + R_f) \parallel Z_L}{(R_E + R_f) \parallel Z_L + Z_o'} \right) = a_v$$

We know f : $f = \frac{R_E}{R_E + R_f}$

Get closed loop gain, A_o for $a_v = \text{large}$

$$A_o = \frac{V_o}{V_i} = \frac{a_v}{1 + a_v f} \approx \frac{1}{f} = 1 + \frac{R_f}{R_E}$$

Must use this if a_v is not large.

What about R_i & R_o ?

for the amplifier w/ FB loading, open-loop

$$Z_{i_a} = Z_i' + R_E \parallel R_f$$

$$Z_{o_a} = Z_o' \parallel (R_E + R_f) \parallel Z_L$$


$$Z_i = (Z_i' + R_E \parallel R_f)(1 + a_v f)$$

$$Z_o = \frac{Z_o' \parallel (R_E + R_f) \parallel Z_L}{1 + a_v f}$$


$$\omega_{-3dB} |_{\text{closed loop}} = \left[\omega_{-3dB} |_{\text{open-loop}} \right] \times (1 + a_v f)$$

To determine loading by FB:

Input Loading

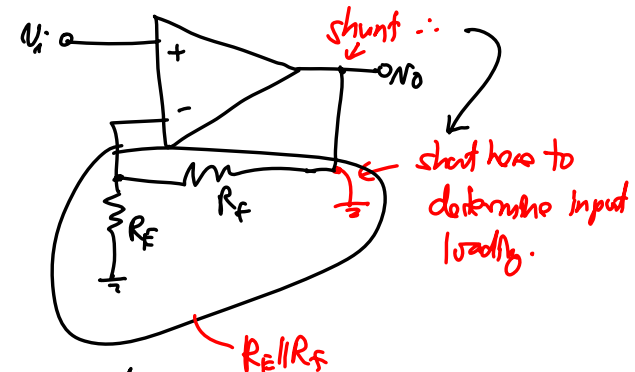

Output Loading:

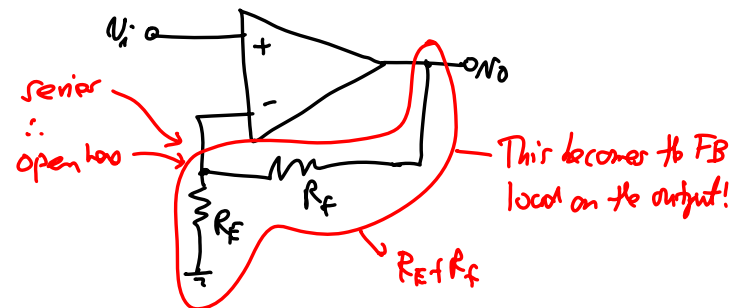

Example: Transresistance Amplifier

Wants a current input

① Determine type of FB: \rightarrow shunt \rightarrow \rightarrow FB Natural \rightarrow shunt

② Biasing:

$I_{FB} = I_{B1} \leftarrow i_{iB} \approx 0 \leftarrow$ Note: Shouldn't do this if R_f is very large.

$I_{C2} \approx I_{E2} = \frac{V_{BE(on)}}{R_{E2}} \quad I_{C1} = \frac{V_{CC} - 2V_{BE(on)}}{R_{C1}}$

③ What kind of gain?

shunt-shunt FB $\rightarrow i_i \rightarrow v$ gain

\therefore we're looking for $R_m = \frac{V_o}{i_i} = \frac{r_m}{1 + r_m f}$

④ Determine r_m :

$r_{m2} + (\beta + 1)(R_{E2} \parallel R_f \parallel R_L)$

Get Gain: $\frac{V_o}{i_i} = \frac{V_{o1}}{i_{i1}} \cdot \frac{V_{o2}}{V_{o1}} \cdot \frac{V_o}{V_{o2}} = \frac{V_o}{i_i} \Big|_{OL w/ FB load} = r_m$

$V_{o1} = i_i (r_{\pi1} \parallel R_f) \rightarrow \frac{V_{o1}}{i_{i1}} = r_{\pi1} \parallel R_f$

$\frac{V_{o2}}{V_{o1}} = -g_{m1} (R_{C1} \parallel [r_{\pi2} + (\beta + 1)(R_{E2} \parallel R_f \parallel R_L)])$

$\frac{V_o}{V_{o2}} \approx 1$

$r_m = \frac{V_o}{i_i} \Big|_{OL w/ FB load} = -g_{m1} (r_{\pi1} \parallel R_f) [R_{C1} \parallel (\quad)] = r_m$

Find f :

$f = \frac{i_{iB}}{V_o} = -\frac{1}{R_f}$

Thus: $T = r_m f = (-g_{m1} (r_{\pi1} \parallel R_f) [R_{C1} \parallel (\quad)]) (-\frac{1}{R_f})$

$T \approx g_{m1} R_{C1} \left(\frac{r_{\pi1} \parallel R_f}{R_f} \right)$

⑤ Finally, get all parameters:

$R_m = \frac{r_m}{1 + r_m f} \approx \frac{1}{f} = -R_f \Rightarrow R_m = -R_f$

if $r_m f = \text{large}$


$$R_i = \frac{R_{i0}|_{\omega \text{ FB loading}}}{1 + r_{mf}} = \frac{r_{\pi 1} \parallel R_f}{1 + g_{m1} R_{C1} \frac{(r_{\pi 1} \parallel R_f)}{R_f}} = R_i$$

large \therefore this = $r_{\pi 1}$

$$R_o = \frac{R_{o0}|_{\omega \text{ FB loading}}}{1 + r_{mf}} = \frac{\frac{r_{\pi 2} + R_{C1}}{\beta + 1} \parallel R_{E2} \parallel R_f \parallel R_L}{1 + g_{m1} R_{C1} \frac{(r_{\pi 1} \parallel R_f)}{R_f}} = R_o$$

Find ω_{-3dB} :

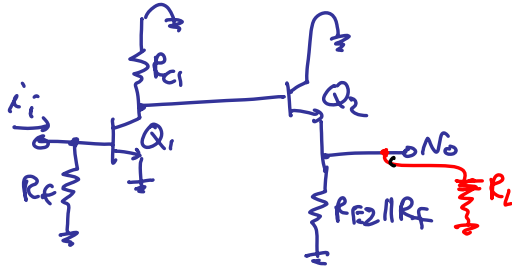- ① Find the ω_{-3dB} of the open-loop amplifier w/ FB loadings, i.e., of this: \rightarrow use OCTC analysis



- ② Multiply by $(1+T)$:

$$\omega_{-3dB}|_{\text{closed-loop}} = (1+T) \times \omega_{-3dB}|_{\text{OL w FB loading}}$$