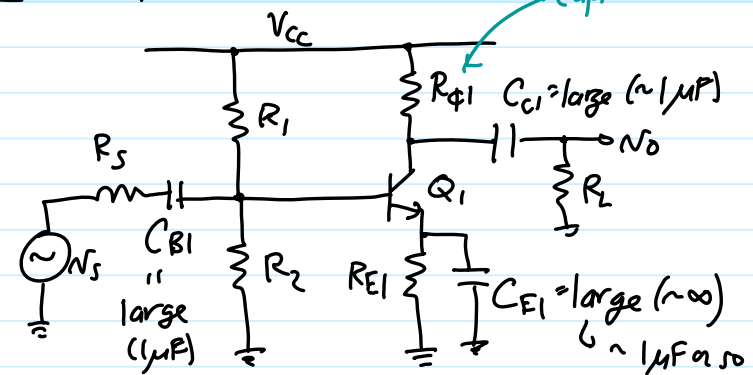


• Today:


- ↳ Inspection analysis for input resistance, output resistance, and gain
- But first: Logistics
- Passed out sign up sheet for discussion sections
- Problem with the Wednesday section: 2:30-3:30 p.m. might not work
 - ↳ Possible to switch to Thursday, 2-3?
- Some people cannot make the Monday 5-7 lab
 - ↳ Solution: whenever the lab is such that instruments in the lab need to be used, the lab will be 4-6 on Monday; otherwise, it will be 5-7

Procedure for Small-Signal Analysis (a quick run down)


Ex. Discrete Common Emitter Ckt.



Convert to S.S. Ckt.

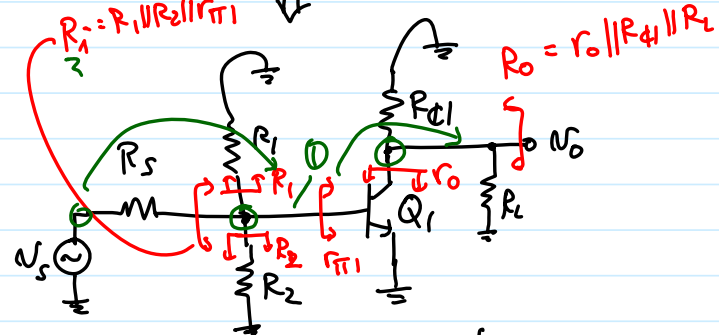


replace X with small-signal ckt

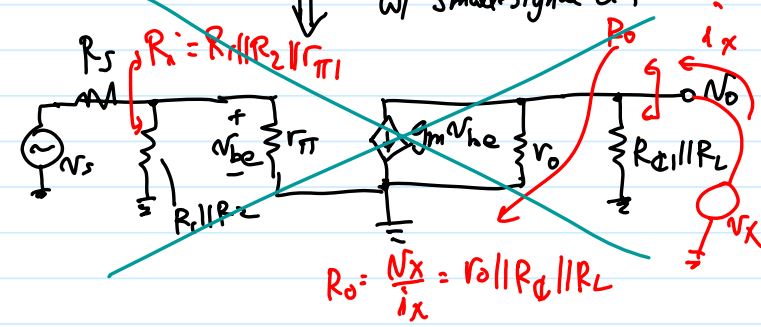

Procedure:

- ① Find the DC operating pt. → get voltages & currents at all nodes & branches, respectively
- ② Determine S.S. parameters for devices in the signal path (e.g., g_m , r_{π} , r_o , ...)
- ③ Convert the full ckt. to the S.S. ckt.
⇒ zero out DC sources
⇒ short out large capacitors
- ④a) If needed, replace Xristor w/ its small-signal ckt.
⇒ this should NOT be needed often
⇒ when is it needed? → generally it comes where there is feedback!
- ④b) Analyze by inspection based on prior S.S. analysis experience! → this should be the case 99% of the time
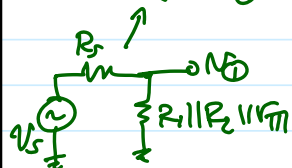
$$A_v = \frac{v_O}{v_i} = - \left(\frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi} + R_s} \right) g_m (R_E \parallel R_L)$$




$$\frac{v_O}{v_i} = \frac{R_1 \parallel R_2 \parallel r_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi} + R_s}$$

$$\frac{v_O}{v_i} = -G_m R_{\odot} = -g_m (R_E \parallel R_L \parallel r_o) \approx -g_m (R_E \parallel R_L)$$

\uparrow \uparrow \uparrow
 g_m $R_{\odot} = R_E \parallel R_L \parallel r_o$ $r_o \gg R_E \parallel R_L$


Ex. Common-Emitter:

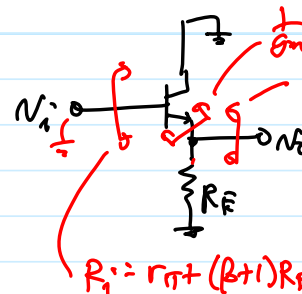

$$\frac{v_O}{v_i} = \frac{R_E}{r_{\pi} + R_E} = \frac{(B+1)R_E}{r_{\pi} + (B+1)R_E}$$


$$\frac{1}{g_m} \sim \frac{R_E}{B} = r_{\pi}$$

Ex. Common-Base:

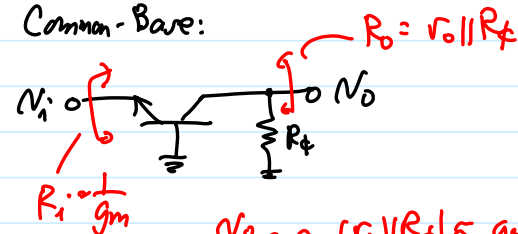

$$\frac{v_O}{v_i} = g_m (r_o \parallel R_E) \approx g_m R_E$$

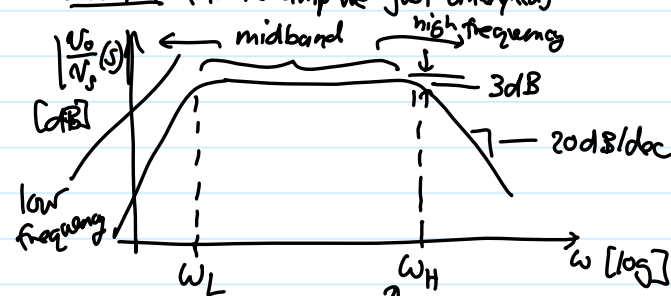
⇒ so far, we've been talking about "midband" analysis
⇒ Bode Plot: (for the amp we just analyzed)



we want this!
⇒ use OCTC (open circuit time constant) analysis

Useful Inspection Formulas

The General Case (Midband)

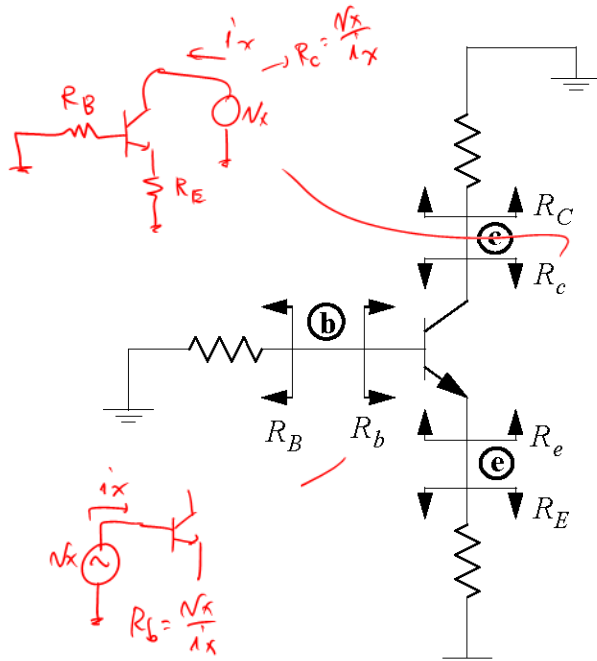

Node Resistances:

$$R_{\odot} = R_C \parallel R_c$$

$$R_{\ominus} = R_E \parallel R_e$$

$$R_{\oplus} = R_B \parallel R_b$$

$$R_b = (r_e + R_E)(\beta + 1) = r_{\pi} + (\beta + 1)R_E$$

$$R_e = \frac{r_{\pi} + R_B}{\beta + 1} \cong \frac{1}{g_m} + \frac{R_B}{\beta + 1}$$

$$R_c = r_o \left[1 + \frac{g_m R_E}{1 + (R_B/r_{\pi})} \right]$$

Base-to-Collector Gain:

$$\frac{v_c}{v_b} = -G_m R_{\odot} \quad G_m = \frac{g_m}{1 + g_m R_E}$$


Emitter-to-Collector Gain:

$$\frac{v_c}{v_e} = -G_m R_{\odot} \quad G_m = -\left(\frac{r_{\pi}}{r_{\pi} + R_B} \right) g_m$$

Base-to-Emitter Gain:

$$\frac{v_e}{v_b} = \frac{R_E \parallel r_o}{R_E \parallel r_o + r_e}$$

High Frequency Analysis

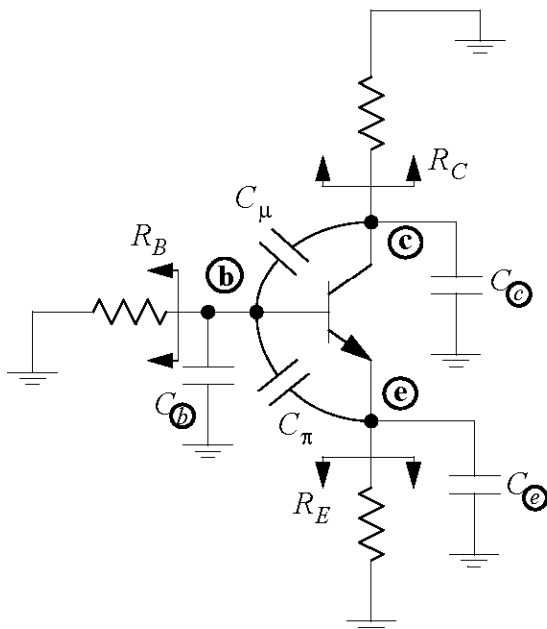

$$\omega_H = \frac{1}{\tau_{\oplus} + \tau_{\odot} + \tau_{\ominus} + \tau_{\mu o} + \tau_{\pi o}}$$

$$\tau_b = C_{\oplus} R_{\oplus}$$

$$\tau_c = C_{\odot} R_{\odot}$$

$$\tau_e = C_{\ominus} R_{\ominus}$$

$$\tau_{\pi o} = C_{\pi} R_{\pi o}$$


$$\tau_{\mu o} = C_{\mu} R_{\mu o}$$

$$R_{\pi o} = r_{\pi} \parallel \frac{R_B + R_E}{1 + g_m R_E}$$

$$R_{\mu o} = R_{\oplus} + R_{\odot} + G_m R_{\odot} R_{\oplus}$$

Frequent Cases (Midband)

Common Emitter

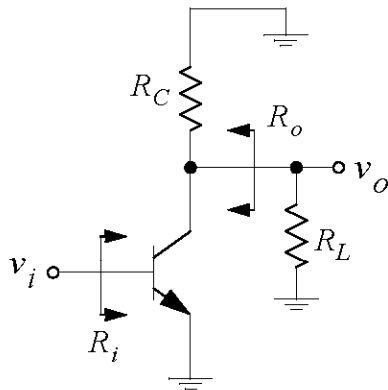


$$R_i = r_\pi$$

$$R_o = r_o \parallel R_C \approx R_C$$

$$\frac{v_o}{v_i} = -g_m(r_o \parallel R_C \parallel R_L) \approx -g_m(R_C \parallel R_L)$$

Common Collector (Emitter Follower)

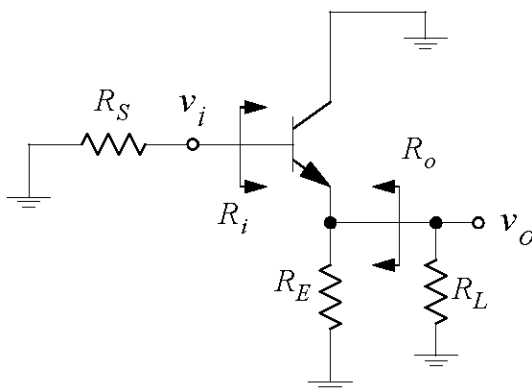


$$R_i = r_\pi + (\beta + 1)(r_o \parallel R_E \parallel R_L)$$

$$\approx r_\pi + (\beta + 1)(R_E \parallel R_L)$$

$$R_o \cong \left(\frac{1}{g_m} + \frac{R_S}{\beta + 1} \right) \parallel R_E$$

$$\frac{v_o}{v_i} = \frac{(r_o \parallel R_E \parallel R_L)}{(r_o \parallel R_E \parallel R_L) + r_e} = \frac{(\beta + 1)(r_o \parallel R_E \parallel R_L)}{(\beta + 1)(r_o \parallel R_E \parallel R_L) + r_\pi} \approx \frac{(\beta + 1)(R_E \parallel R_L)}{(\beta + 1)(R_E \parallel R_L) + r_\pi}$$

Common Base

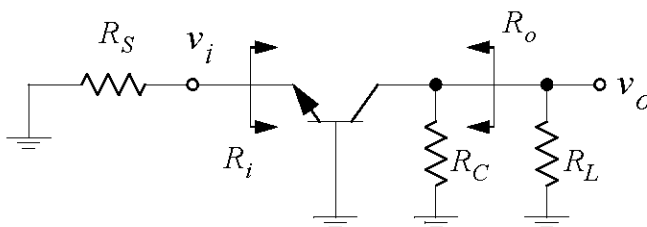

$$R_i = r_e \cong \frac{1}{g_m}$$

$$R_o = r_o(1 + g_m R_S) \parallel R_C \approx R_C$$

$$\frac{v_o}{v_i} \cong g_m(R_C \parallel R_L)$$