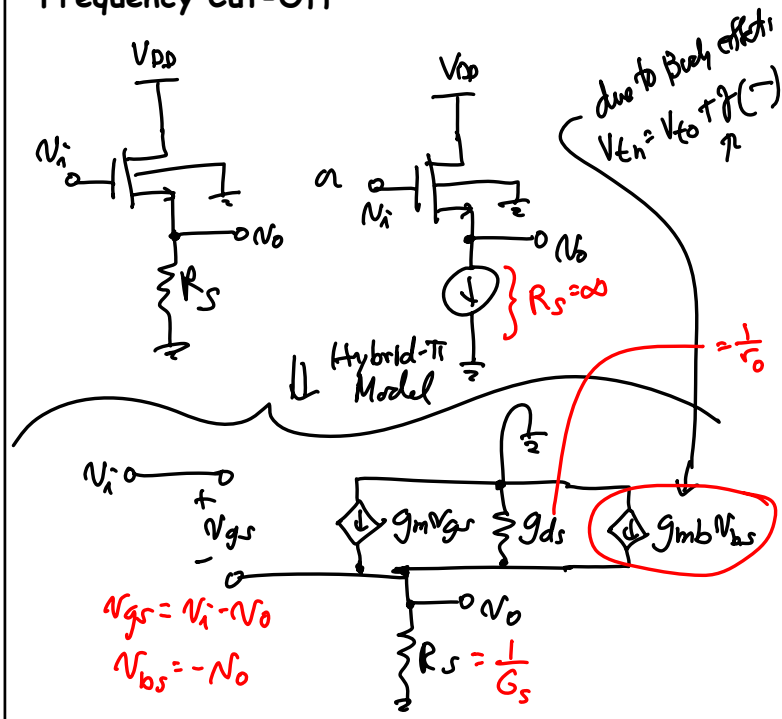


Logistics:

- I will miss Thursday, Feb. 12
  - Make up lecture time:
    - Monday, 10-11:30 a.m.? ~~X~~
    - Wednesday, 5-6:30 p.m.? ~~X~~
    - Thursday, 3-4:30 p.m.? ~~X~~
    - Thursday, 5-6:30 p.m.? ~~X~~
- Th 7 p.m. ??? possible.  
→ Tu 7 p.m. ← weekend?

Today:

- Open-Circuit Time Constant Analysis for High Frequency Cut-Off
- Short-Circuit Time Constant Analysis for Low Frequency Cut-Off



$$g_m(V_i - V_o) = N_o(g_{mb} + g_{ds} + G_S)$$

$$\Rightarrow A_v = \frac{N_o}{V_i} \approx \frac{g_m}{g_m + g_{mb} + g_{ds} + G_S}$$


$$\left[ R_S = \infty \rightarrow G_S = 0 \right]$$

$$g_{ds} \ll g_m + g_{mb}$$


$$A_v \approx \frac{g_m}{g_m + g_{mb}} \approx \frac{1}{1 + \eta}, \quad \eta = \frac{\gamma}{2\sqrt{V_{SG} + 2\phi_f}}$$


Body factor

To make it '1', do this:

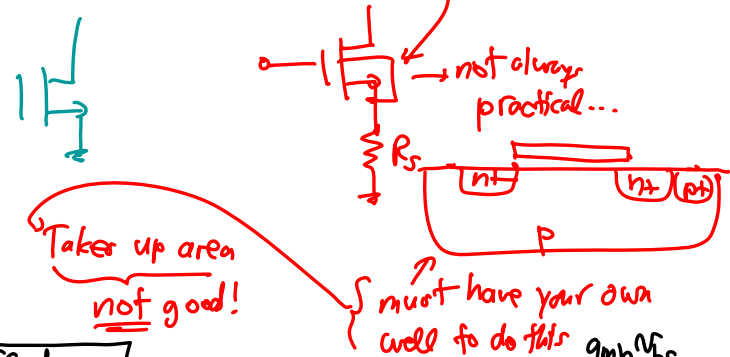


Effect  $g_{mb}$

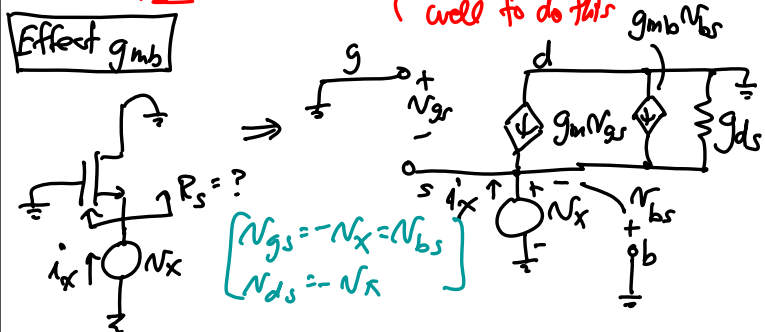

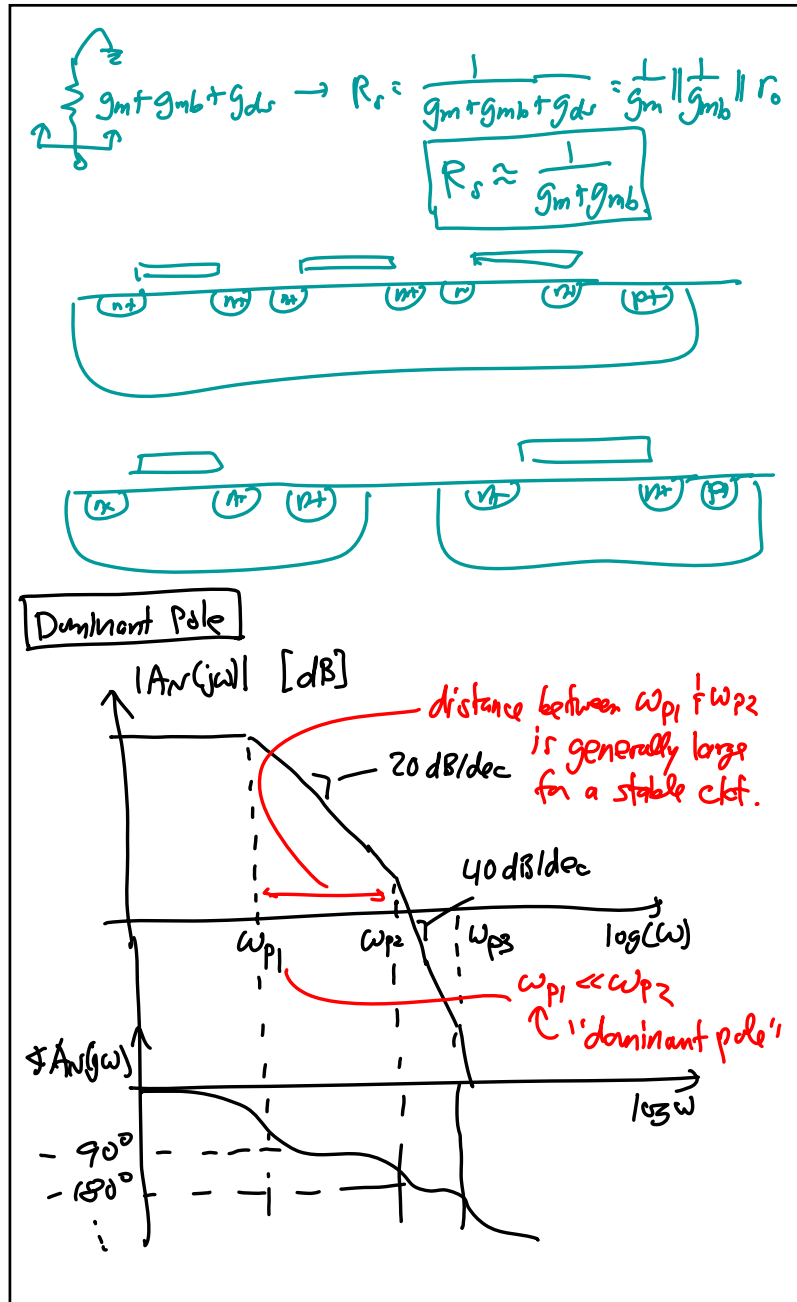

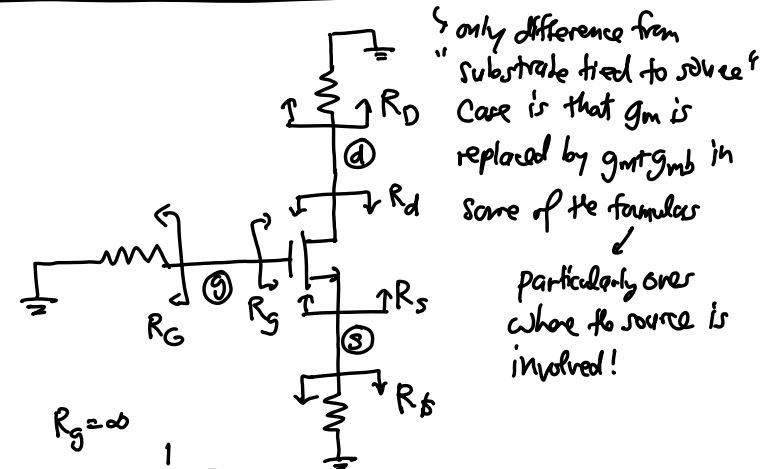Mos Inspection Formulas w/ Substrate Grounded



$$R_g = \infty$$

$$R_s = \frac{1}{g_m + g_{mb}}$$

$$R_d = r_o [1 + (g_m + g_{mb}) R_B]$$

$$\frac{N_d}{N_g} = -G_m R_d, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_B}$$


$$\frac{N_d}{N_s} = -G_m R_d, \quad G_m = -(g_m + g_{mb})$$

$$\frac{N_s}{N_B} = \frac{g_m R_B}{1 + (g_m + g_{mb}) R_B}$$

Remark When the substrate is tied to the source,  $g_{mb} = 0$ .
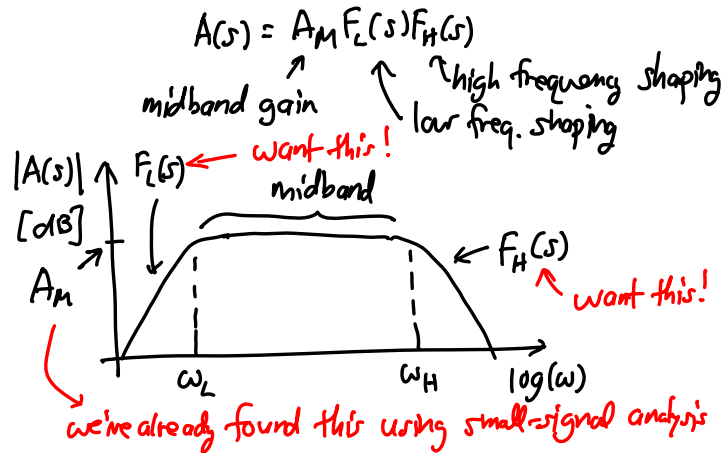
### Freq. Response

Recall that the transfer function of a general amplifier can be expressed as a function of frequency via:



### High Freq. Response Determination Using Open Ckt. Time Constant (OCTC) Analysis

In general:

$$F_H(s) = \frac{1 + a_1 s + a_2 s^2 + \dots + a_{n_z} s^{n_z}}{1 + b_1 s + b_2 s^2 + \dots + b_{n_p} s^{n_p}}, \quad n_p > n_z$$

$$= \frac{\prod_{j=1}^{n_z} \left(1 - \frac{s}{z_j}\right)}{\prod_{i=1}^{n_p} \left(1 - \frac{s}{p_i}\right)} = \frac{\prod_{j=1}^{n_z} \left(1 + \frac{s}{\omega_{zj}}\right)}{\prod_{i=1}^{n_p} \left(1 + \frac{s}{\omega_{pi}}\right)}$$

from which:

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn_p}} = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{k=1}^{n_p} \tau_{pk}$$

$\uparrow$  coeff. of the 1<sup>st</sup> order term

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{n_p} \tau_{pi} = \sum_j C_j R_{jo} = \sum_j \tau_{jo}$$

where  $C_j$  are capacitors in the H.F. ckt., i.e., small ones  
 $R_{jo} \triangleq$  driving pt. resistance seen between the terminals of  $C_j$  determined with

- ① all small ( $< 1nF$ ) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e.,  $> 1\mu F$  or  $> 1nF$ )

In calculating the H.F. response, we use the dominant pole approximation:

(i)  $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pn_p}$

(ii)  $F_H(s) \approx \frac{1}{1 + \frac{s}{\omega_H}}$


$\rightarrow$  (ii)  $b_1 \approx \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \approx \frac{1}{b_1} = \frac{1}{\sum_j \tau_{jo}} = \frac{1}{\sum_j C_j R_{jo}}$

When there is no dominant pole, an approximate expression for  $\omega_H$  is:

$$\omega_H \approx \sqrt{\frac{1}{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots - \frac{1}{\omega_{z1}^2} - \frac{1}{\omega_{z2}^2} - \dots}}$$

(just FYI)

Example A.F. Analysis C.F. Ckt.

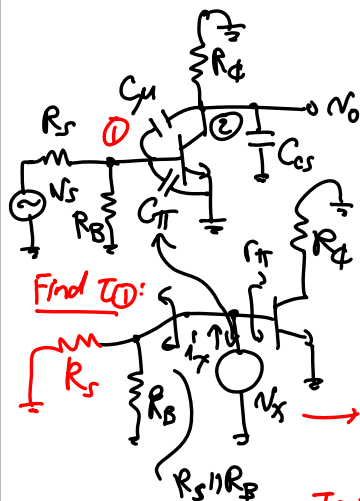

Find  $\tau_{D1}$ :

$$R = \frac{V_x}{I_x} = r_{\pi} \parallel R_s \parallel R_B$$

$$\tau_{D1} = C_{\pi} (r_{\pi} \parallel R_s \parallel R_B)$$

Find  $\tau_{\mu 0}$ : replace  $C_{\mu}$  w/  $N_x$  use inspection formula

$$R_{\mu 0} = \frac{V_x}{I_x} = R_1 + R_2 + g_m R_1 R_2$$

$$R_{\mu 0} = R_s \parallel R_B \parallel r_{\pi} + r_o \parallel R_d + g_m (R_s \parallel R_B \parallel r_{\pi}) (r_o \parallel R_d)$$

$$\tau_{\mu 0} = R_{\mu 0} C_{\mu}$$

Find  $\tau_{D2}$ :

$$\tau_{D2} = C_{cs} (r_o \parallel R_d) \approx C_{cs} R_d$$

$$\omega_H = \frac{1}{\tau_{D1} + \tau_{\mu 0} + \tau_{D2}}$$