


Logistics:

- I will miss Thursday, Feb. 12
- Make up lecture time:
↳ Tonight, Tuesday, 7 p.m., 247 Cory

Today:

- High Frequency Cut-Off Examples
- Short-Circuit Time Constant Analysis for Low Frequency Cut-Off

Problem 1(c)

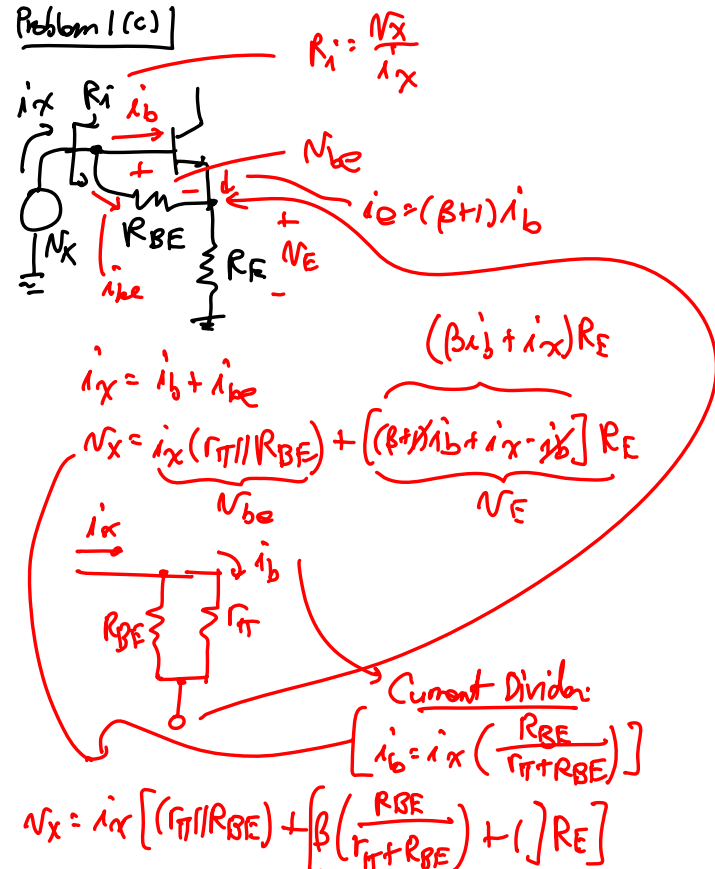

Handwritten derivation of R_i :

$$R_i = \frac{V_x}{I_x} = (r_{\pi} \parallel R_{BE}) + (\beta' + 1)R_E$$

$$\beta' = \beta \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right)$$

Input Resistance Formula:

Handwritten formula:


$$R_i = r_{\pi} \parallel R_{BE} + (\beta + 1)R_E \approx r_{\pi}(1 + g_m R_E)$$

Handwritten derivation of the input resistance formula:

$$R_i = (r_{\pi} \parallel R_{BE})(1 + g_m R_E)$$



$$= (r_{\pi} \parallel R_{BE}) + g_m \left(\frac{r_{\pi} R_{BE}}{r_{\pi} + R_{BE}} \right) R_E$$

$$= (r_{\pi} \parallel R_{BE}) + \beta \left(\frac{R_{BE}}{r_{\pi} + R_{BE}} \right) R_E$$

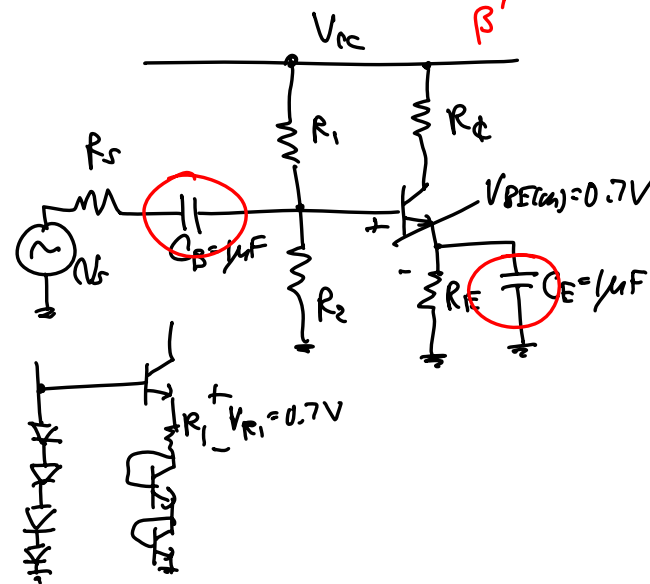

Lecture 7: High Frequency Inspection Analysis


Last Time - OCTC

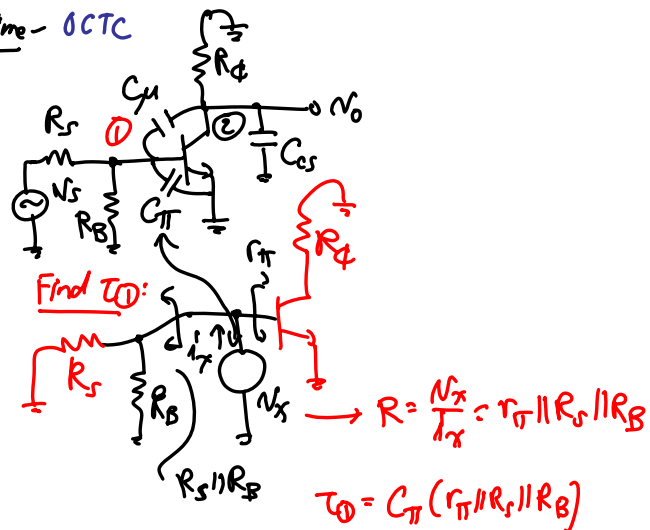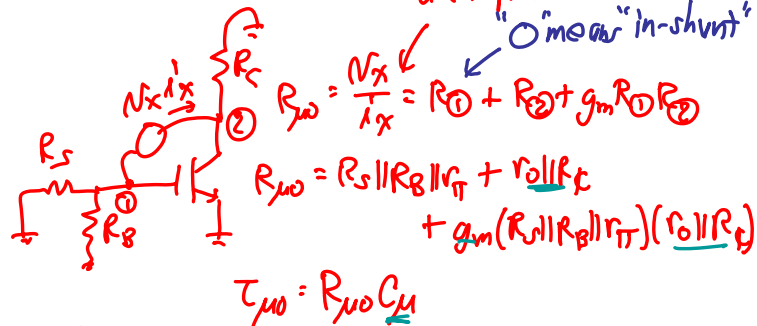Find $T_{\mu 0}$: replace C_{μ} w/ N_x use inspection formula
 "O'meter in-shunt"Find T_2 :


$$T_2 = C_{cs} (r_{o1} \parallel R_C) \approx C_{cs} R_C$$

$$\omega_H = \frac{1}{T_1 + T_{\mu 0} + T_2}$$

Now, use Miller's Theorem

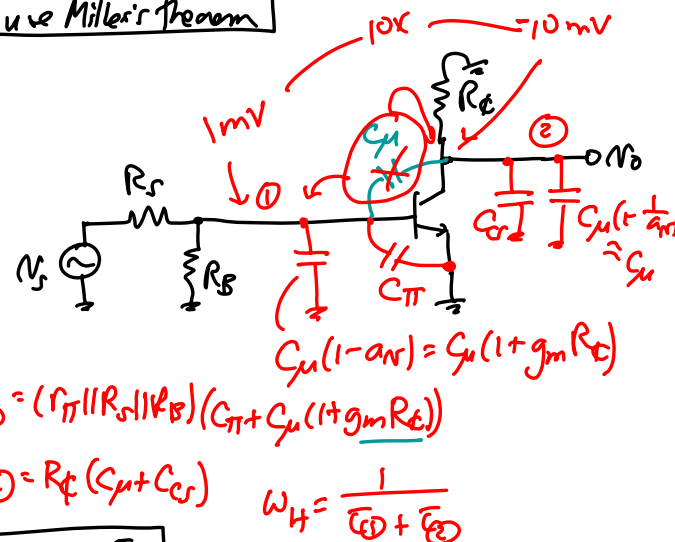

Multi-Stage Ex.

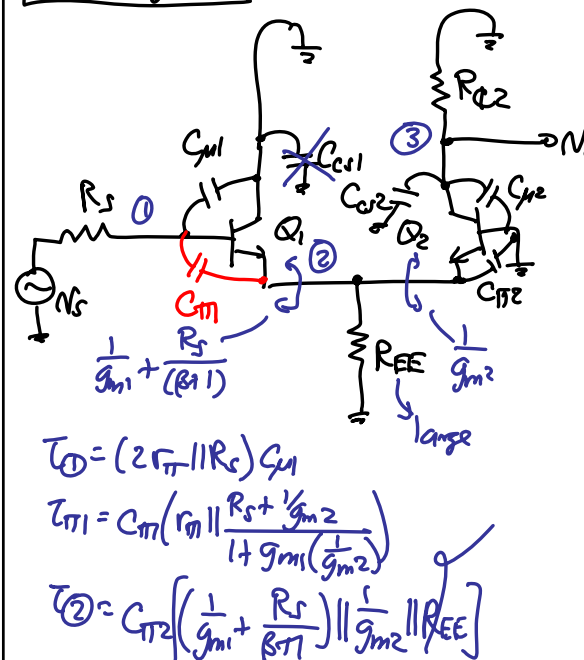

$\tau_3 = (C_{m2} + C_{cs2}) R_{t2}$

$$\omega_H = \frac{1}{\tau_0 + \tau_1 + \tau_2 + \tau_3}$$

MOS Two-Stage Amplifier

Step 1: Eliminate cgs.

Step 2: Determine time constants.

$$\tau_0 = [C_{gs1} + C_{gd1}(1 + g_{m1}R_{D1})] R_S$$


$$\tau_2 = [C_{gd1} + C_{db1} + C_{gd2}] (R_{D1} \parallel R_{D2}) \sim R_{D1}$$

$$\tau_3 = C_{cs2} \left(\frac{1}{g_{m2} + g_{mb2}} \parallel R_{t2} \right)$$

$$\tau_{gs2} = C_{gs2} \left(\frac{R_{D1} + R_{S2}}{1 + (g_{m2} + g_{mb2}) R_{S2}} \right)$$

$$\omega_H = \frac{1}{\tau_0 + \tau_2 + \tau_3 + \tau_{gs2}}$$

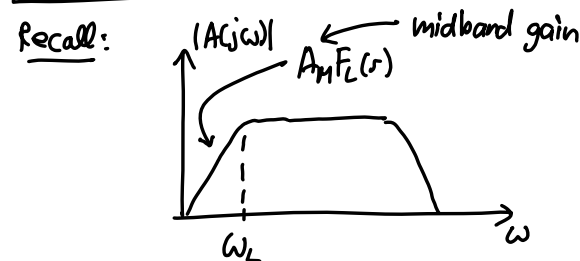Low Freq. Amplifier Response Using Short Circuit Time Constant Analysis (SCTC)



In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}, \quad n_z = \# \text{ poles} = \# \text{ zeros}$$

We can express the coefficient e_1 by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn_p}$$

For the case of a dominant pole:

↳ i.e., the highest freq. pole

$$F_L(s) \approx \frac{s}{s + \omega_L} = \frac{s}{s + e_1} \rightarrow e_1 \approx \omega_{p1} = \omega_L$$

$$\therefore \omega_L \approx e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{js}} = \sum_j \frac{1}{\tau_{js}}$$

where $C_j \triangleq$ various large ($> 10 \text{ nF}$) capacitors in the ckt. (e.g., the bypass caps.)

$R_{js} \triangleq$ driving point resistance seen between the terminals of C_j determined with:

For readability, can go to Sedra & Smith

① all large capacitors short-circuited, except C_j , which is replaced by the test voltage source for R determination

Lecture 7: High Frequency Inspection Analysis

- ② all independent sources eliminated
(i.e., short voltage sources, open current sources)
- ③ open all H.F. capacitors (i.e., small caps
in the pF range, or $< 1\text{ nF}$)

Again, for the case where there are no dominant poles,
a reasonable approximation is:

$$\omega_L \cong \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$