

**PROBLEM SET #2**

Issued: Tuesday, Jan.31, 2012

Due: Tuesday, Feb.7, 2012, 6:00 p.m. in the EE 140 homework box in 240 Cory

- Use inspection analysis to write expressions for the input resistance  $R_i$ , output resistance  $R_o$ , and gain  $v_o/v_I$  for each of the amplifiers in Fig PS2.1. For part (d), you need to consider two cases assuming: (1)  $r_o$  is very large; (2)  $r_o$  is on the same order as  $(R_D//R_3)$ . The expressions should be in terms of the given elements and parameters of the small-signal equivalent circuits (i.e.,  $g_m$ ,  $g_{mb}$ ,  $r_\pi$ ,  $r_o$ ,  $\beta$ , etc.) for the transistors used. For each circuit, assume that all capacitors shown have infinite values.

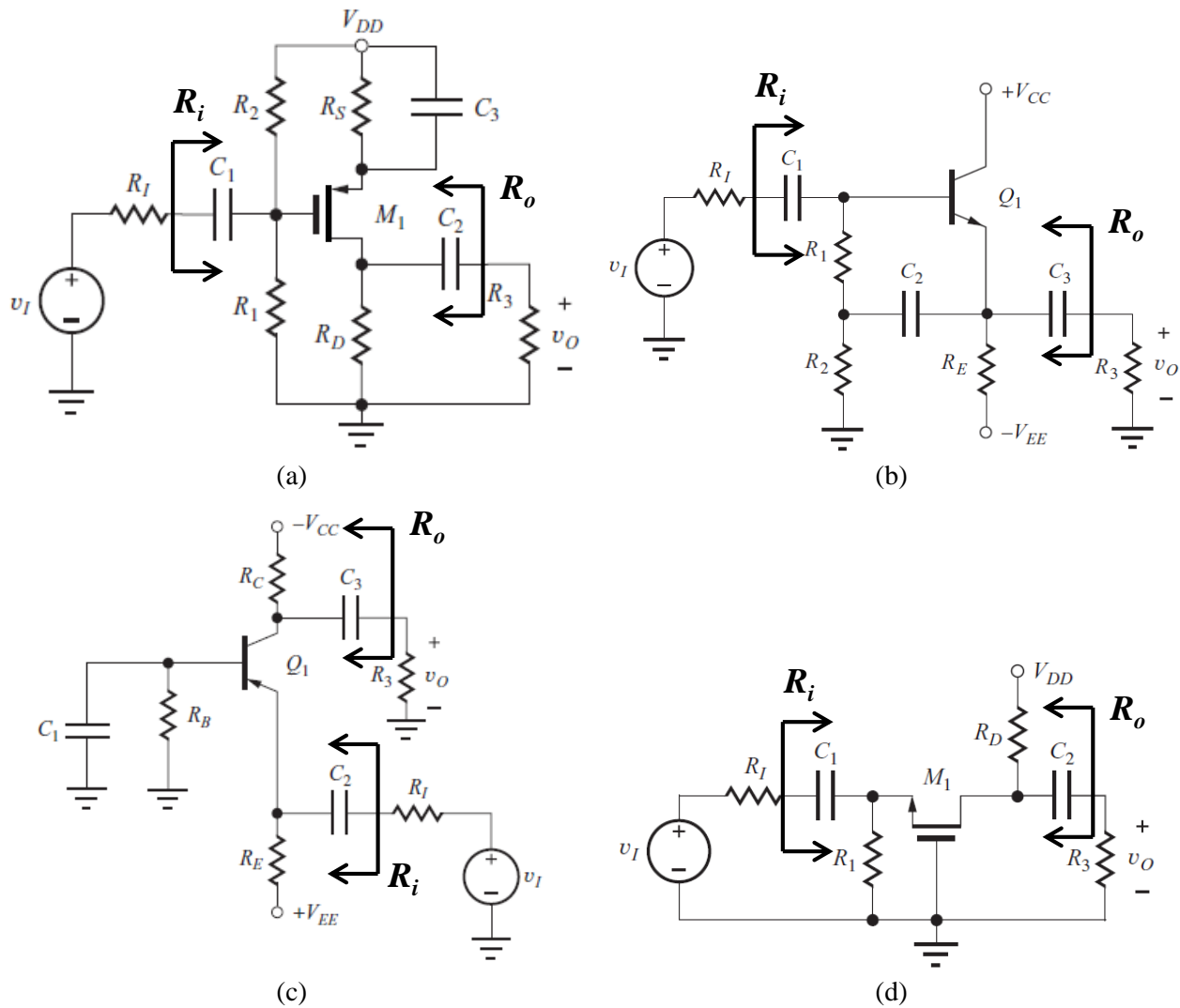


Fig. PS2.1

2. If the emitter resistor  $R_E$  in Fig. PS2.2 can be absorbed into the transistor by redefining the small-signal parameters,
  - a. What is the redefined  $g'_m$ ,  $r'_\pi$  and  $r'_o$ ?
  - b. What is the common-emitter small-signal current gain  $\beta'_o$ ?

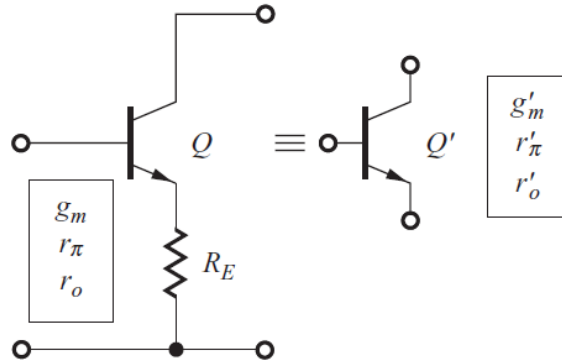


Fig. PS2.2

3. For the circuit in Fig. PS2.3, transistor  $Q_1$  have  $\beta = 20$  and transistor  $Q_2$  have  $\beta = 100$ . Neglect the effect of  $r_o$ . Use  $V_{BE} = 0.7$  V.
  - a. Find the DC emitter current of  $Q_1$  and  $Q_2$ . Also find the DC voltages  $V_{B1}$  and  $V_{B2}$ .
  - b. If a load resistance  $R_L = 500 \Omega$  is connected to the output terminal, find the voltage gain from the base to the emitter of  $Q_2$ ,  $v_o/v_{b2}$ , and find the input resistance ( $R_{ib2}$ ) looking into the base of  $Q_2$ .
  - c. Analyze the circuit of emitter follower  $Q_1$  to determine its input resistance  $R_i$ , and the gain from its base to its emitter,  $v_{e1}/v_{b1}$ .
  - d. If the circuit is fed with a source having a  $100 \text{ k}\Omega$  resistance, find the overall voltage gain  $v_o/v_s$  including the resistances added in parts b.

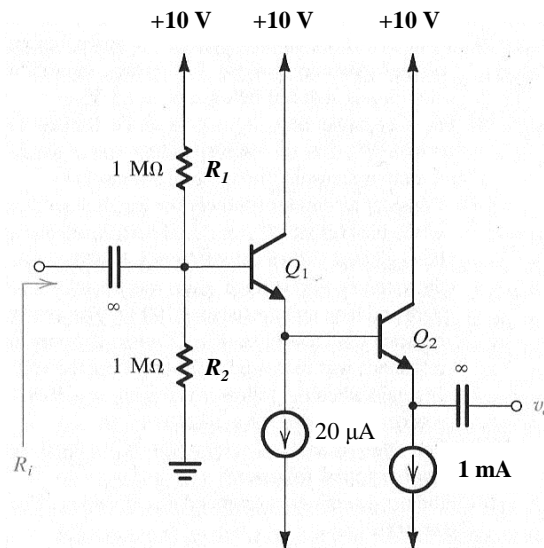


Fig. PS2.3

4. For the common-emitter stage shown schematically in Fig. PS2.4, assume  $R_I$  (source resistance) =  $330\Omega$ ,  $R_G=100\text{k}\Omega$ ,  $R_S=150\Omega$ ,  $R_A=16\text{k}\Omega$ ,  $R_D=10\text{k}\Omega$ ,  $R_3=220\text{k}\Omega$ ,  $+V_{DD}=5\text{V}$ ,  $-V_{SS}=-5\text{V}$ , and  $C_1, C_2, C_3$  are all infinite. For the transistor, assume  $\beta_F=65$ ,  $V_A=50\text{V}$ .
- Calculate the DC operating point ( $I_C, V_{CE}$ ) of the transistor.
  - Calculate the input resistance and output resistance.
  - What is the overall voltage gain for this common-emitter amplifier?

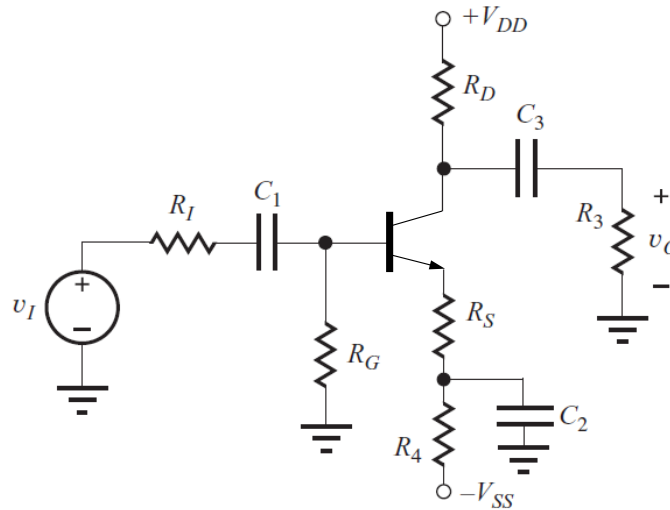


Fig. PS2.4

5. Find the DC operating point, voltage gain, input resistance, and output resistance of the amplifier shown in Fig. PS2.5 if  $R_F = 1\text{M}\Omega$ ,  $R_3 = 100\text{k}\Omega$ ,  $k' = 100\mu\text{A}/\text{V}^2$ ,  $V_{TN} = 1\text{V}$ ,  $\lambda = 0.02$ ,  $(W/L)_1 = 10/1$ ,  $(W/L)_2 = 2/1$  and  $V_{DD} = 5\text{V}$ . Assume  $C_1$  and  $C_2$  infinite.

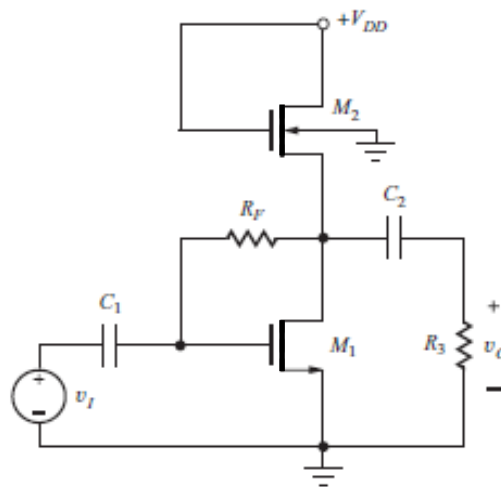


Fig. PS2.5