

**PROBLEM SET #3**

Issued: Tuesday, Feb. 7, 2012

Due: Tuesday, Feb. 14, 2012, 6:00 p.m. in the EE 140 homework box in 240 Cory

1. Estimate the  $f_L$  and  $f_H$  of a multistage amplifier shown in Fig. PS3.3.

The transistor parameters are listed in the following table:

	$g_m$	$r_o$	$\beta_o$	$C_{GS}, C_\pi$	$C_{GD}, C_\mu$	$r_g, r_b$
$M_1$	10 mS	12 k $\Omega$	$\infty$	5 pF	1 pF	0 $\Omega$
$Q_2$	68 mS	55 k $\Omega$	150	50 pF	1 pF	100 $\Omega$
$Q_3$	80 mS	35 k $\Omega$	80	50 pF	1 pF	100 $\Omega$

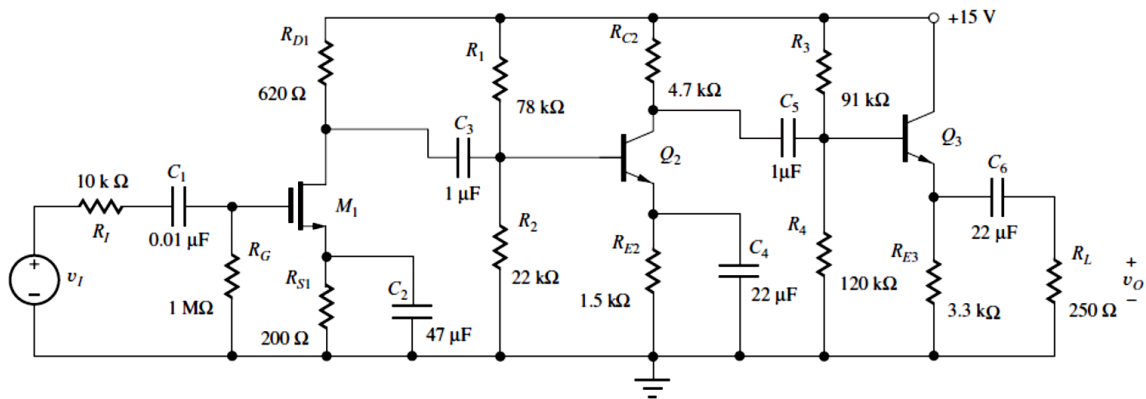


Fig. PS3.1

2. For the small-signal circuits shown schematically in Fig. PS3.2, assume  $R_S = 5\text{k}\Omega$ ,  $R_L = 3\text{k}\Omega$ ,  $C_L = 4\text{pF}$ . For the transistors, assume  $I_C = 1\text{mA}$ ,  $\beta_F = 100$ ,  $f_T = 500\text{MHz}$  (at  $I_C = 1\text{mA}$ ),  $C_\mu = 0.4\text{pF}$ ,  $C_{cs} = 1\text{pF}$ ,  $r_b = 0\Omega$ , and  $r_o = \infty$ .
  - a. Calculate the low-frequency, small signal voltage gain  $v_o/v_i$  for each circuit.
  - b. Calculate and compare the 3-dB frequencies of the two circuits.

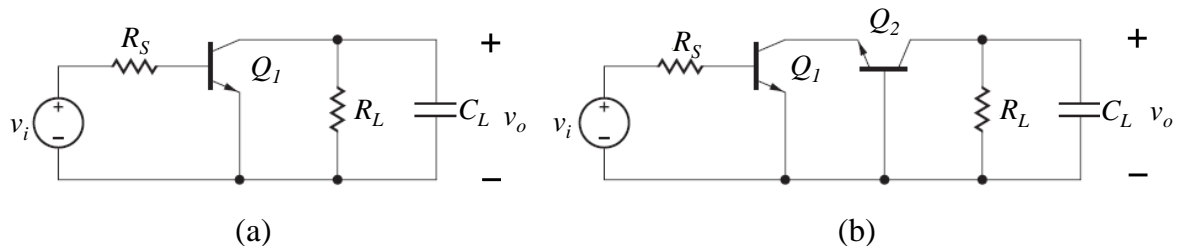


Fig. PS3.2

3. The ac schematic of a wideband MOS current amplifier is shown in Fig. PS3.3. The transistors have parameters  $L_{drawn} = 3\mu\text{m}$ ,  $L_d = 0.1\mu\text{m}$ ,  $X_d = 0\mu\text{m}$ , the length of the drain and source diffusion is  $2L_{drawn}$  ( $L_{DE}$  and  $L_{SE}$  in the lecture module),  $C_{j0} = 0.08\text{fF}/\mu\text{m}^2$ ,  $C_{jsw0} = 0.5\text{fF}/\mu\text{m}$ ,  $n = 0.5$ ,  $\psi_0 = 0.65\text{V}$ ,  $\mu_n = 700\text{cm}^2/\text{V}\cdot\text{s}$ ,  $t_{ox} = 400\text{\AA}$ ,  $\lambda = 0$ , and  $V_t = 0.7\text{V}$ . Size of transistors:  $W_1 = 9\mu\text{m}$ ,  $W_2 = 36\mu\text{m}$ . Both transistors use the minimum channel length. Assume the bias point at the gate of  $M_1$  is  $V_{G1} = 1\text{V}$ .
- Calculate the low-frequency small-signal current gain  $i_o/i_i$ .
  - Estimate the -3-dB frequency.

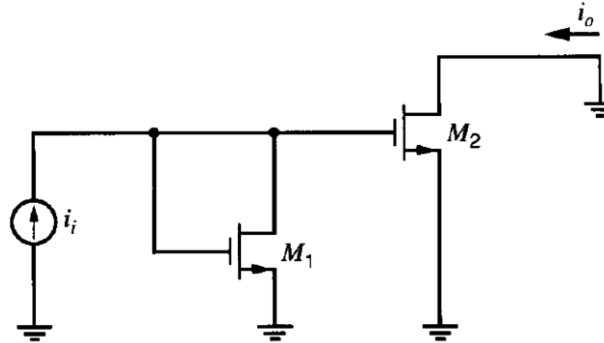


Fig. PS3.3

4. A BJT differential amplifier shown in Fig. PS3.4 operating with a 1-mA current source  $I_{EE}$  uses transistor for which  $\beta_F = 100$ ,  $f_T = 600\text{MHz}$ ,  $C_\mu = 0.5\text{pF}$ ,  $r_b = 100\Omega$  and  $r_o = \infty$ . Both the input resistance  $R_S$  and load resistances  $R_L$  are  $10\text{k}\Omega$ .
- Determine the low-frequency value of the overall differential gain. Estimate the -3-dB frequency  $f_H$  and the gain-bandwidth product.
  - Suppose the circuit is modified by including  $100\text{-}\Omega$  resistor  $R_E$  in each of the emitters. Determine the low-frequency value of the overall differential gain. And estimate the  $f_H$  and gain-bandwidth product.
  - From part (b), suppose you are requested to increase the 3-dB frequency of the differential amplifier to  $1\text{MHz}$  by changing the value of the emitter resistance  $R_E$  (as the  $100\text{-}\Omega$  resistors in part (b)). Find the value of  $R_E$  to achieve this goal. What does the dc gain become? Also determine the resulting gain-bandwidth product.
  - Now, suppose the circuit in part (a) (with no  $R_E$ ) is modified by eliminating the load resistor  $R_L$  of the left-hand-side transistor and the input signal (still series with the  $R_S$ ) is fed to the base of the left-hand-side transistor while the base of the other transistor in the pair is grounded. Find the dc gain and  $f_H$ .

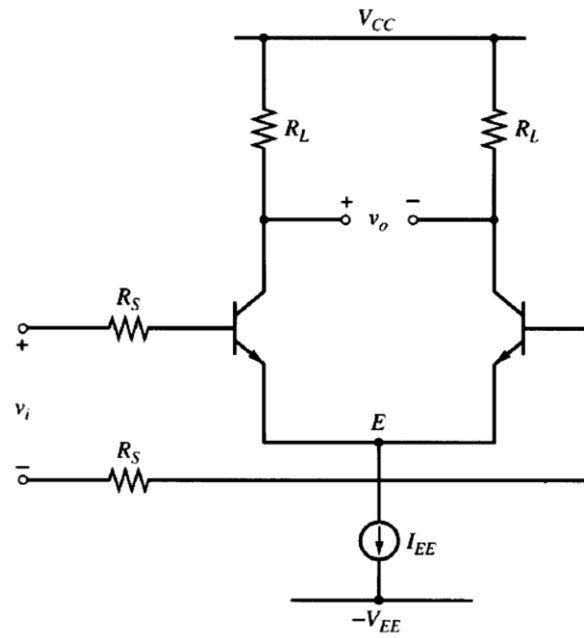


Fig. PS3.4