

PROBLEM SET #7

Issued: Tuesday, Mar. 6, 2012

Due: Tuesday, Mar. 13, 2012, 6:00 p.m. in the EE 140 homework box in 240 Cory

- Use inspection analysis to write an expression for the gain v_{out}/v_{in} for each of the amplifiers in Fig. PS7.1. The expression should be in terms of the small signal equivalent circuits (i.e., g_m , g_{mb} , r_π , r_o , β , etc.) for the transistors used. Assume the transistors are matched and neglect the parasitic capacitances of transistors.

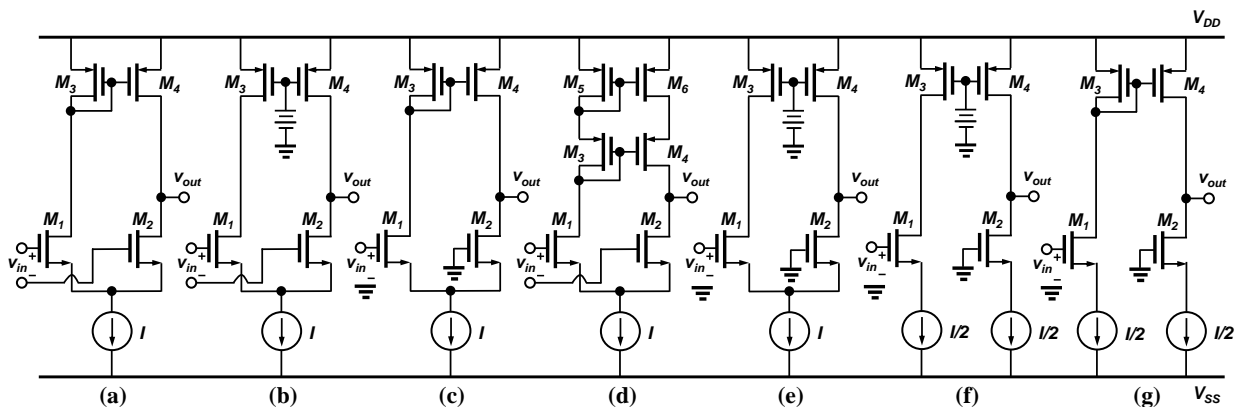


Fig. PS7.1

- For the BJT differential amplifier shown in Fig. PS7.2, assume $V_T = 25\text{mV}$ and $V_A \rightarrow \infty$:
 - Write an expression in terms of $(I_{TAIL}R_C)$ for the differential gain.
 - Write an expression for the maximum permitted value for the input common mode voltage V_{CM} while the transistors remain comfortably in the active region with their collector voltages not lower than their base voltages (i.e., $V_{CB} \geq 0$). Express this maximum in terms of V_{CC} and the differential gain obtained in (a) and hence show that for a given value of V_{CC} , the higher the gain achieved, the lower the input common-mode range.
 - Assume $R_C = 5\text{k}\Omega$, $R_{TAIL} = 1\text{M}\Omega$, and $I_{TAIL} = 1\text{mA}$. Suppose two small signals are fed to the bases of the two input transistors with $v_{i1} = 2v_{i2} = 5\text{mV}$. Calculate the output common mode voltage v_{oc} , and differential output voltage v_{od} .
 - Assuming $I_{TAIL} = 0$ (i.e., only R_{TAIL} exists) and $\beta = 200$, select values of R_C and R_{TAIL} to give a differential input resistance of $2\text{M}\Omega$, a differential voltage gain of 500, and a CMRR of 500.
 - Assume the β s of two transistors are β_1 and β_2 and everything else is matched. Show that the input offset voltage is approximately $V_T \times [(1/\beta_1) - (1/\beta_2)]$.
 - Assume the collector load resistors R_C and the scale currents I_S of the transistors are mismatched by 10%. Calculate the input offset voltage.

- (g) Suppose a design error has resulted in a gross mismatch in the circuit where Q_1 has an emitter-base junction area twice that of Q_2 . Assuming the input signal is a small differential signal, express I_{C1} and I_{C2} in terms of I_{TAIL} .
- (h) Continuing from (g), if $R_C = 5\text{k}\Omega$, $R_{TAIL} = 1\text{M}\Omega$ and $I_{TAIL} = 1\text{mA}$, calculate A_{cm} , A_{cm-dm} , and A_{dm} . Assume β is very large.

 


Fig. PS7.2

3. The op amp in the circuit of Fig. PS7.3 has an open-loop gain of 10,000, an offset voltage of 1mV, and an input-bias current of 100nA.
- What is the output voltage if the op amp is ideal?
 - What is the actual output voltage for the worst-case polarity of offset voltage?
 - What is the worst-case percentage error in the output voltage compared to the ideal output voltage?
 - Assuming the op amp has a finite 3dB frequency of 100 kHz, estimate the closed loop 3dB frequency.

 


Fig. PS7.3

4. For the differential amplifier with current mirror load shown in Fig. PS7.4(a), assume all transistors have the same $k'W/L = 3.2 \text{ mA/V}^2$, and $\lambda = 0.05$. Neglect body effect.
- (a) Find the required bias current I for a gain $v_o/v_{id} = 80 \text{ V/V}$ for the circuit in Fig. PS7.4(a).
- (b) Suppose the ideal current source is implemented in two cases: (1) a simple current mirror as shown in Fig. PS7.4(b); (2) a cascade current mirror as shown in Fig. PS7.4(c). Assume I_{REF} is adjusted to the bias current obtained in part (a). Find the CMRR for both cases.

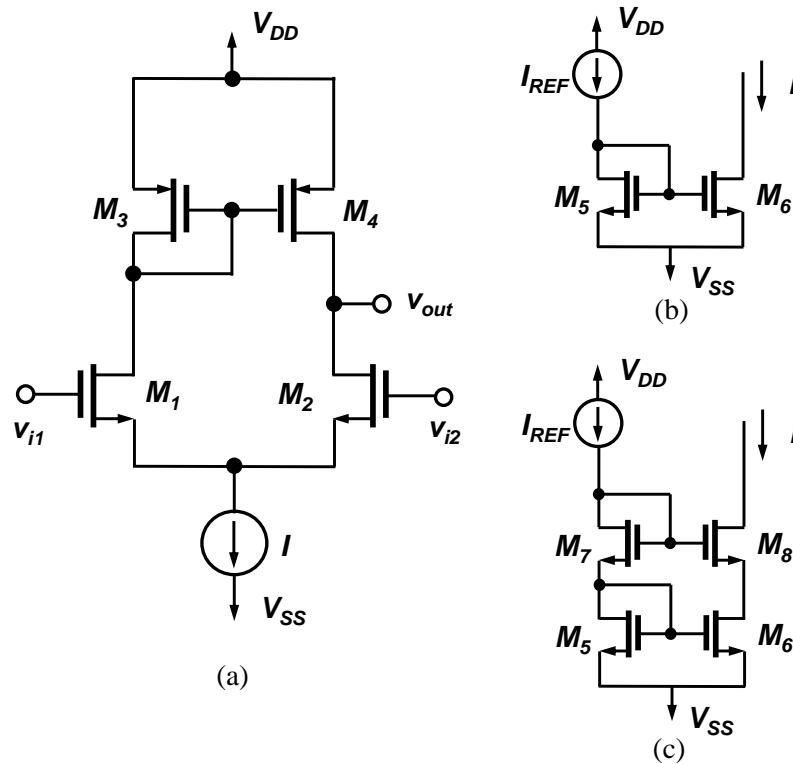


Fig. PS7.4