

PROBLEM SET #9

Issued: Tuesday, Apr. 3, 2012

Due: Tuesday, Apr. 10, 2012, 6:00 p.m. in the EE 140 homework box in 240 Cory

- Consider a class B output stage depicted in Fig. PS9.1(a). Assume $V_{CC} = 10\text{V}$, and both transistors have the same $|V_{th}| = 1\text{V}$ and $\mu C_{OX}W/L = 200\mu\text{A}/\text{V}^2$.
 - Assuming the input is fed with a sine-wave signal with a 5-V amplitude (i.e., $V_{in} = 5\sin(\omega t)$) and $R_L \rightarrow \infty$, sketch the output voltage waveform.
 - (Continuing from part (a)) For what value of load resistor R_L is the peak output voltage reduced to half of the input signal amplitude (i.e., $|V_{out,peak}| = 2.5\text{V}$)?
 - The class B output stage is connected with an op amp into a feedback configuration as shown in Fig. PS9.1(b). The op amp has an open loop voltage gain $A_0 = 100\text{ V/V}$. Sketch the transfer characteristic v_{out} vs. v_{in} . Assume $R_L \rightarrow \infty$.
 - (Continuing from part (c)) The 5-V-amplitude input signal is now connected to the input of the circuit in Fig. PS9.1(b). Assuming the op amp has a slew rate of $10\text{V}/\mu\text{S}$, calculate the maximum allowable frequency of the input signal for the output waveform NOT having distortion due to slew rate limitation.

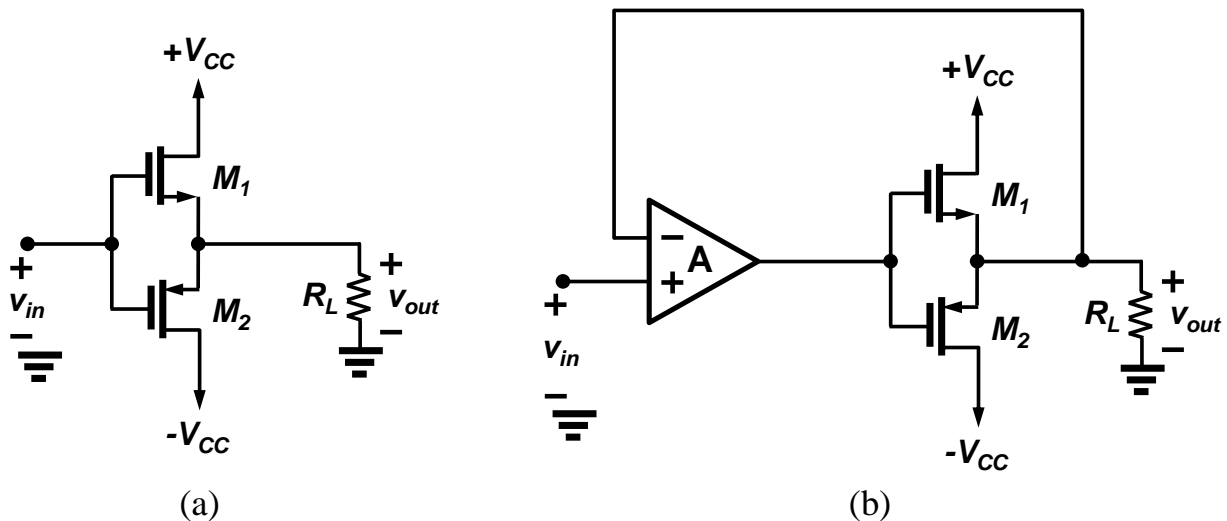


Fig. PS9.1

- In the circuit of Fig. PS9.2, $V_{CC} = 20\text{V}$, $I_Q = 0.1\text{mA}$, $R_L = 1\text{k}\Omega$, and for all devices $\beta_F = 150$, $I_S = 10^{-15}\text{A}$, $V_T = 26\text{mV}$, and $|V_{CEsat}| = 0.2\text{V}$.
 - Calculate the value of V_{in} and the current in each device for $V_{out} = 0, \pm 5\text{V}$, and $\pm 10\text{V}$. Then sketch the transfer characteristic of V_{out} vs. V_{in} from $V_{out} = 10\text{V}$ to -10V .
 - Calculate the largest possible positive and negative output signal levels.

- (c) Suppose that you want to achieve a positive peak level equal to the negative peak output level for this circuit by adjusting the I_Q value. What value of I_Q is required to achieve this?

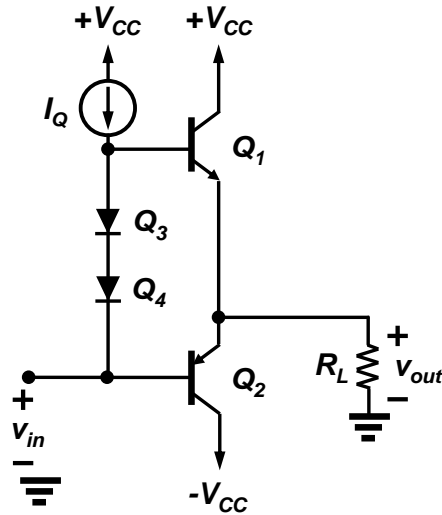


Fig. PS9.2

3. In the amplifier of Fig. PS9.3, assume $\mu_n C_{OX} = 2\mu_p C_{OX} = 200\mu\text{A}/\text{V}^2$, $\lambda_p = 2\lambda_n = 0.2$, $(W/L)_{1-4} = 50/0.5$ and $I_{SS} = I_1 = 1\text{mA}$.
- Assuming $C_X = C_Y = 0.5\text{pF}$, estimate the poles at nodes X and Y , and the phase margin for unity-gain feedback.
 - If $C_X = 1\text{pF}$, estimate the maximum tolerable value of C_Y that yields a phase margin of 60° for unity-gain feedback.

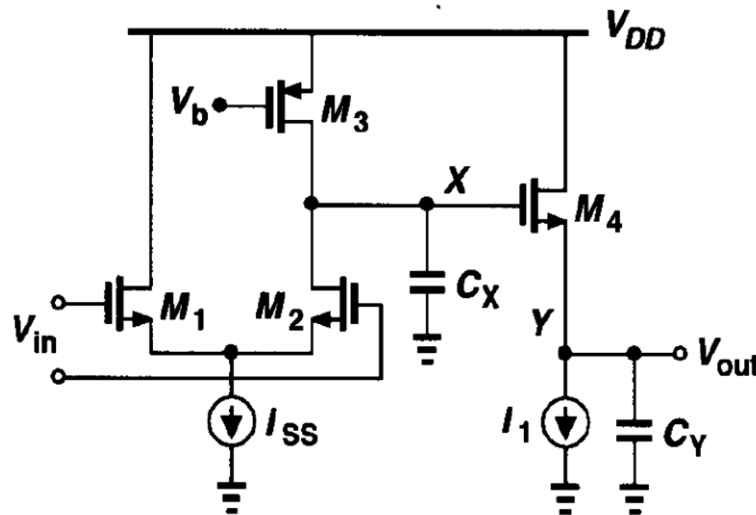


Fig. PS9.3

4. An amplifier has a low-frequency forward gain of 5000 and its transfer function has three negative real poles with magnitudes 300kHz, 2MHz, and 25MHz.
 - (a) Suppose the amplifier is to be compensated by reducing the magnitude of the most dominant pole and assume the remaining poles do not move. Calculate the dominant-pole magnitude required for unity-gain compensation with 60° phase margin, and the corresponding bandwidth of the circuit with the feedback applied.
 - (b) Repeat (a) for compensation in a feedback loop with a closed-loop gain of 20dB and 60° phase margin.

5. An op amp having a low-frequency gain of 1000 and a single pole roll-off at 10^4 rad/s is connected in a negative-feedback loop via a feedback network having a transmission k and a two-pole roll-off also at 10^4 rad/s. Find the critical value of k at which oscillation will occur.