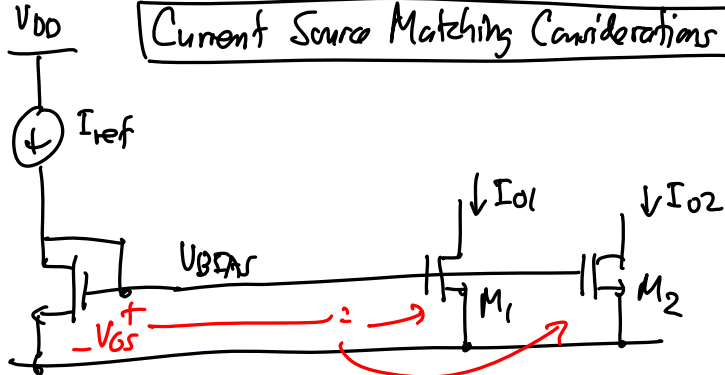


**Lecture 12: Op Amps & Emitter Coupled Pair**

- **Announcements:**
  - ↳ Pre-Lecture materials online
  - ↳ Change Th OH to 2-3 p.m. (right after class)
- **Lecture Topics:**
  - ↳ Op Amp Review
  - ↳ Emitter Coupled Pair (ECP)
  - ↳ Half Circuits
  - ↳ Source Coupled Pair w/ Current Mirror Load

• **Last Time:**




$$\therefore \frac{\Delta I_D}{I_D} = \frac{\Delta(W/L)}{(W/L)} - \frac{\Delta V_t}{(V_{ov}/2)}$$

*This could be (-), so this doesn't necessarily help!*

Fractional Current Mismatch  
 Geometry Based Component  
 ↑  
 Independent of Bias Pt.  
 ↑  
 Increases  $C_s$   $V_{ov}$   
 ↓  
 Today:  $V_{ov}$  ↑  $V_{ov}$   
 Fixed new  $X_{ov}$   
 generation, must make  $(\frac{W}{L}) \rightarrow$

- Now, start on Op Amps & ECP using the Pre-Lecture handout
- Half Circuits:

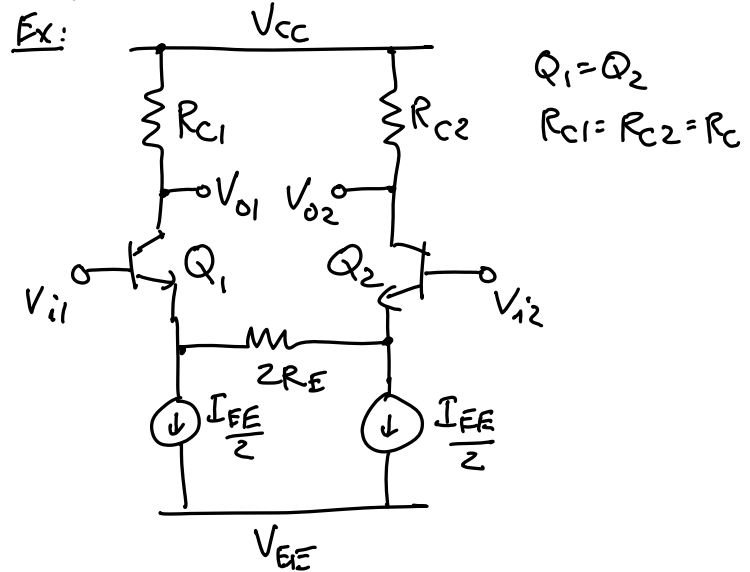


EE 140

Ideal Op Amps

CTN

1

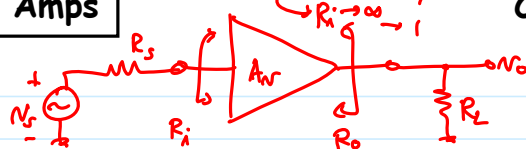Gain:  $\frac{V_o}{V_s} = \frac{R_i}{R_i + R_s} \cdot A_v \cdot \frac{R_o}{R_o + R_L} \rightarrow R_o \rightarrow 0 \rightarrow 1$



Ideal Voltage Amplifier

→ ideal when  $\frac{V_o}{V_s} = A_v$ ; i.e., when source and load  $R$ 's do not influence the gain of the amplifier.

For this to occur, the voltage division at the input & output must be eliminated.

This happens when:

$R_i = \infty$  } These resistance values define an  
 $R_o = 0$  } ideal voltage amplifier.


We'll look at other amplifier types later.

→ This, then, naturally leads us to:

Ideal Operational Amplifiers (Op Amps)


→ The work horse of analog electronics → combinations of op amps w/ feedback components allow the implementation of analog computers, sampled-data systems, analog filters, A/D converters, DAC's, instrumentation amplifiers

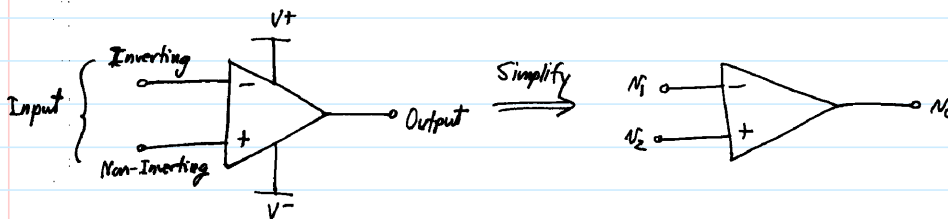In general, have a minimum of 5 terminals:



Perhaps the best way to define an op amp is thru its equivalent ckt:


Equivalent Ckt. of an Ideal Op Amp:

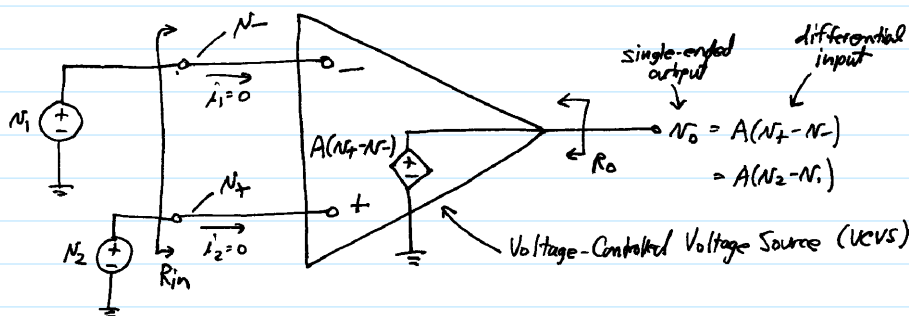

EE 140 Ideal Op Amps CTN 2

Properties of Ideal Op Amps:

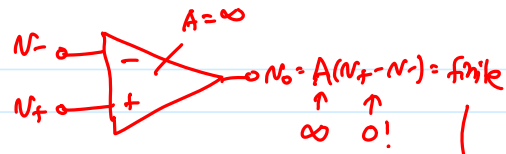- ①  $R_{in} = \infty$  leads to ④  $i_+ = i_- = 0$
- ②  $R_o = 0$
- ③  $A = \infty$  leads to ⑤  $V_+ = V_-$ , assuming  $N_o = \text{finite}$




Why? Because for  $\infty(N_+ - N_-) = N_o = \text{finite}$   
 $\therefore N_+ - N_- = 0 \rightarrow N_+ = N_-$   
 $\parallel \frac{N_o}{\infty} \Rightarrow \text{virtual short ckt. (virtual ground)}$

Big assumption! ( $N_o = \text{finite}$ )

How can we assume this?  $\Rightarrow$  only when there is an appropriate negative feedback path!

Negative Feedback

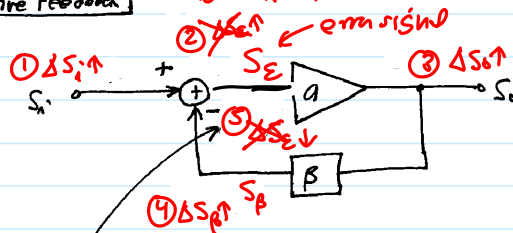$\rightarrow$  to determine whether a net flows  $\rightarrow$  FB, do perturbation analysis:



where  $S$  could be a current, voltage, displacement, etc.,...

Negative feedback acts to oppose or subtract from input.

$$\left. \begin{aligned} S_o &= a S_e \\ S_e &= S_i - \beta S_o \end{aligned} \right\} \Rightarrow S_o = a(S_i - \beta S_o) \Rightarrow S_o(1 + a\beta) = a S_i \Rightarrow \boxed{\frac{S_o}{S_i} = \frac{a}{1 + a\beta}}$$

overall transfer function

$$[a \rightarrow \infty] \Rightarrow \frac{S_o}{S_i} \approx \frac{a}{a\beta} = \frac{1}{\beta} = \text{finite!}$$

$\therefore S_o = \frac{1}{\beta} S_i = \text{finite}$  ✓  
 (when there is neg. FB around the amplifier)

In Summary:

- ① Neg. FB can insure  $S_o = \text{finite}$  even with  $a = \infty$ .
- ② <sup>Overall</sup> Gain dependent (or overall T.F.) dependent only on external components. (e.g.,  $\beta$ )
- ③ Overall (closed-loop) gain  $\frac{S_o}{S_i}$  is independent of amplifier gain  $a$ .

$\leftarrow$  very important!  $\Rightarrow$  as you'll see, when designing amplifiers using transistors, it's easy to get large gain, but it's hard to get an exact gain.  
 i.e., if you're shooting for  $a = 50,000$ , you might get 47,000 or 60,000 instead.



EE 140

Basic Op Amp Design


CTN

4

How do we make an op amp? (It turns out, you already know!)


⇒ Basic Needed Attributes:

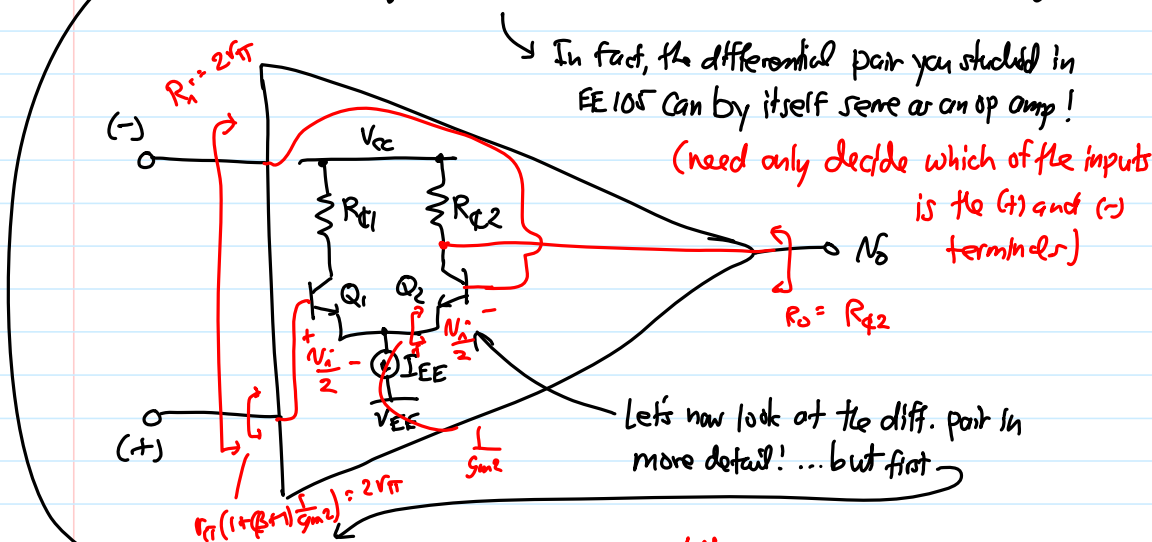- ① Gain (voltage gain).
- ② Two inputs, (+) and (-).
- ③ One output equal to the difference of the inputs multiplied by some gain.




Why have 2 inputs?

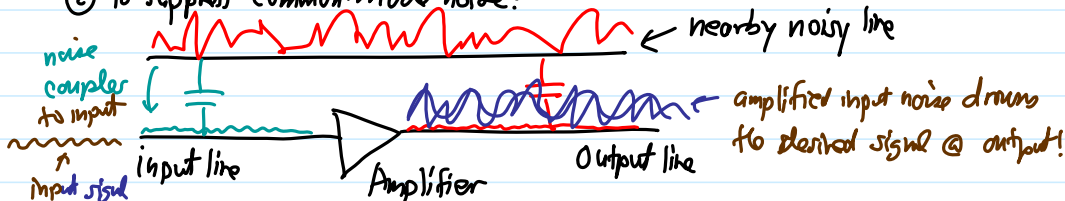- ① To get a virtual short for op amp dets.
- ② To suppress common-mode noise:



Can avoid this w/ a differential input:

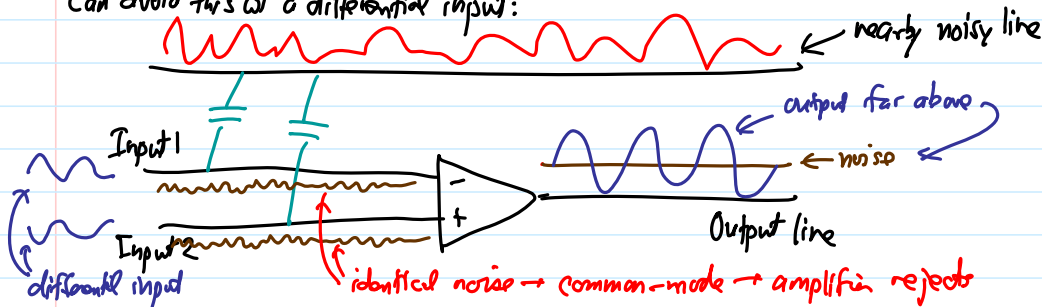


EE 140

Differential Pair (Bipolar)

CTN

5

Differential Pair (Emitter-Coupled Pair)

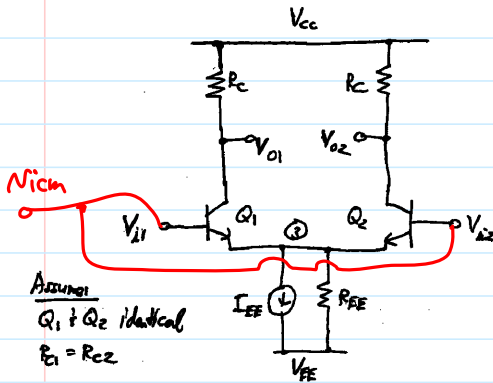

Purpose: Amplify the difference between two signals regardless of their common-mode DC values (or their common-mode values in general)

Definition:  $V_{id} = V_{i1} - V_{i2}$  (differential input)  
 $V_{icm} = \frac{V_{i1} + V_{i2}}{2}$  (common-mode input)

$$\Rightarrow \begin{cases} V_{i1} = V_{icm} + \frac{V_{id}}{2} \\ V_{i2} = V_{icm} - \frac{V_{id}}{2} \end{cases}$$



Differential Gain =  $A_d = \frac{V_{O1} - V_{O2}}{V_{id}} = \frac{V_{od}}{V_{id}}$  (want this to be large for this differential amplification)  
 Common-Mode Gain =  $A_{cm} = \frac{V_{O1}}{V_{cm}}$  or  $\frac{V_{O2}}{V_{cm}}$  (want this to be small so that the amp rejects common-mode signals)  
 Common-Mode Rejection Ratio = CMRR =  $\frac{A_{dm}}{A_{cm}}$  (should be very high to favor the differential-mode and reject the common-mode)

⇒ we also want a high Common-Mode Input Range to reject DC input offsets  
 ⇒ Note No need for bypass capacitors (large) to the inputs or outputs → can just use direct coupling!

Biases & Large Signal Common-Mode Behavior

Case:  $R_{EE} = \infty$  → ideal current source biasing →  $I_{E1} = I_{E2} = \frac{I_{EE}}{2}$  →  $V_{O1} = V_{O2} \Rightarrow V_{od} = 0$   
 If  $V_{cm} \uparrow \rightarrow V_{O1} \uparrow$ , but current draw from  $I_{EE}$  stays constant ∴  $I_{C1}$  &  $I_{C2}$  stay constant → bias pt. doesn't change  
 $g_m = \frac{1}{2} \frac{I_{EE}}{V_T}$

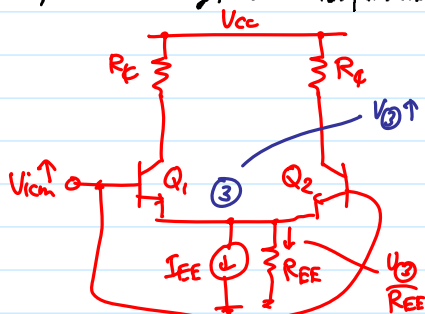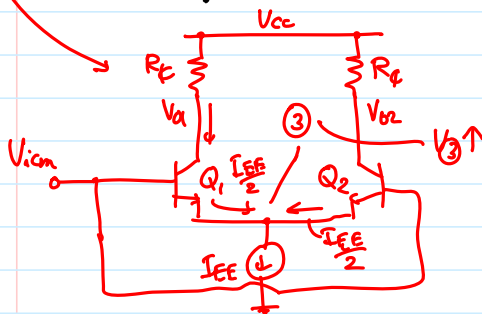Case:  $R_{EE} = \text{finite}$  →  $V_{O3} = V_{i1} - V_{BE}(cm)$   
 If  $V_{icm} \uparrow \rightarrow V_{O3} \uparrow \rightarrow I_{E1} = I_{EE} \uparrow$  (current draw =  $I_{EE} + \frac{V_{O2}}{R_{EE}}$ )  
 ⇒ in general,  $R_{EE}$  will be large, so this component won't be large, and the bias pt. won't Δ much



EE 140 Differential Mode Analysis CTN 6

Small-Signal Analysis of Diff. Pair

$N_{o1} = -\frac{1}{2} g_m N_{i1} R_c$   
 $N_{o2} = -\frac{1}{2} g_m N_{i2} R_c$   
 $N_{o1} = -\frac{1}{2} g_m R_c (N_{i1} - N_{i2})$   
 $N_{o2} = +\frac{1}{2} g_m R_c (N_{i1} - N_{i2})$   
 $N_{od} = N_{o1} - N_{o2} = -g_m R_c (N_{i1} - N_{i2})$   
 $\therefore \frac{N_{od}}{N_{id}} = A_{dm} = -g_m R_c$   
 $G_{m1} = \frac{g_m}{1 + g_m(\frac{R_c}{2})} = \frac{1}{2} g_m$

= Easiest to see this happening using the T-model! (for those who must see the model ckt)

$N_{o1} = -\frac{1}{2} g_m R_c N_{i1}$   
 $N_{o2} = +\frac{1}{2} g_m R_c N_{i1}$   
 $N_{o1} - N_{o2} = -g_m R_c N_{i1}$   
 $\therefore \frac{N_{od}}{N_{i1}} = -g_m R_c$   
 $\frac{N_{o1}}{N_{i1}} = -\frac{1}{2} g_m R_c$   
 $\frac{N_{o2}}{N_{i1}} = +\frac{1}{2} g_m R_c$   
 $\frac{N_{id}}{2} = \frac{1}{2} g_m N_{i1} = \frac{g_m}{2}$

Diff. Mode Analysis

Assume a ckt. w/ only diff. input:

$Q_1 = Q_2$   
 $R_{c1} = R_{c2} = R_c$   
 diff. mode ground!


~~not symmetric!~~

Total current thru  $I_{EE} = \text{const.}$   
 $\rightarrow V_E = \text{const.}$  as input changes  
 $\rightarrow$  (3) acts as an incremental ground!  $\rightarrow V_{(3)} = 0V$  (always!)  
 ∴ we can ground (3), and then have a **Differential Half Ckt.**

Note: Can really only make this for a purely symmetrical ckt!

EE 140 Common-Mode Analysis CTN 7

Differential Half Ckt.

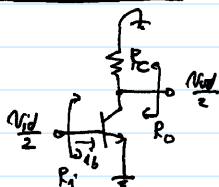

By inspection:  $\frac{V_{od}/2}{V_{id}/2} = \frac{V_{od}}{V_{id}} = A_{dm} = -g_m R_c$


$\frac{V_{id}/2}{i_b} = r_{\pi} \rightarrow R_{id} = \frac{V_{id}}{i_b} = 2r_{\pi} = R_{id}$

$\frac{V_{od}/2}{i_o} = r_o || R_c \rightarrow R_{od} = \frac{V_{od}}{i_o} = 2(r_o || R_c) \approx 2R_c = R_{od}$

S.S. params. determined w/  $I_c = \frac{I_{EE}}{2}$

Common-Mode Analysis

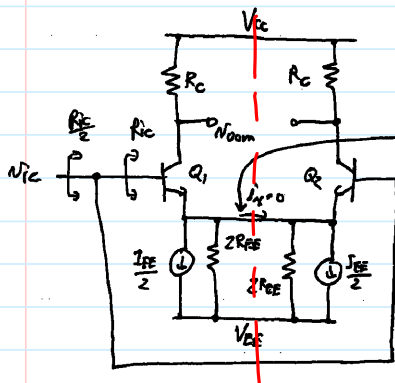
Assume a pure CM input  $\rightarrow$  tie inputs together



By symmetry,  $i_x = 0 \Rightarrow$  then, really have the equivalent of an open ckt. here

$\therefore \Rightarrow$  can split the ckt. into CM half-ckt.!

S.S. CM Half-Ckt.

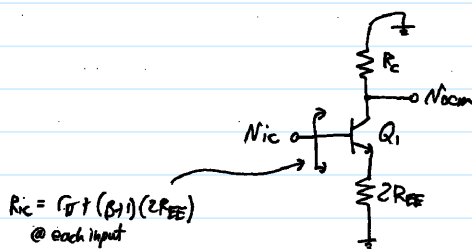

$R_{ic} = r_{\pi} + (\beta+1)(2R_{EE})$   
@ each input

$A_{cm} = \frac{N_{com}}{N_{ic}} = -\frac{g_m R_c}{1 + g_m(2R_{EE})} \approx -\frac{R_c}{2R_{EE}}$

Want small for large CMRR  $\therefore$  want  $R_{EE} = \text{large!}$

Common-Mode Rejection Ratio = CMRR =  $\frac{A_{dm}}{A_{cm}} = \frac{-g_m R_c}{-\frac{g_m R_c}{1 + g_m(2R_{EE})}} \Rightarrow \text{CMRR} = 1 + 2g_m R_{EE}$

Want as ideal a current source as possible!

Having looked at S.S. parameters, we now turn to large signal performance. Here, we'll be particularly interested in the linear range of the ECP.