

Lecture 13: SCP & Current Mirror Load

• Announcements:

- ↳ Pre-Lecture materials online
- ↳ Reminder: Changed Th OH to 2-3 p.m. (right after class)
- ↳ HW#4 had some misplaced problems that should have been on a later HW
- ↳ Problems 2 and 4 from HW#4 will be deferred to later HW's
- ↳ I will need to miss next Thursday's lecture; once again, there will be a make-up lecture in a room and time TBD


• Lecture Topics:

- ↳ Half Circuits Examples
- ↳ Source Coupled Pair w/ Current Mirror Load


• Last Time:

- Going through the handout on Op Amps and Differential Pairs
- Continue with this now ...
- Problem with LCD projector
 - ↳ Wasted some time trying to fix it
 - ↳ Used the board for the first portion of lecture, until the right people came to fix the projector
 - ↳ On the board, went through differential and common-mode half-circuit analysis, including emitter degenerated differential pairs
 - ↳ Some of the notes at the end of this

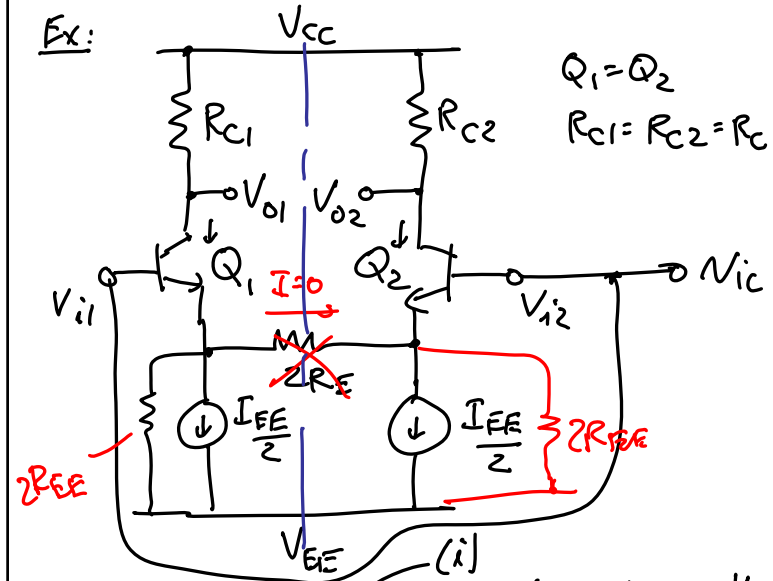- Projector fixed ... continue with half circuit example



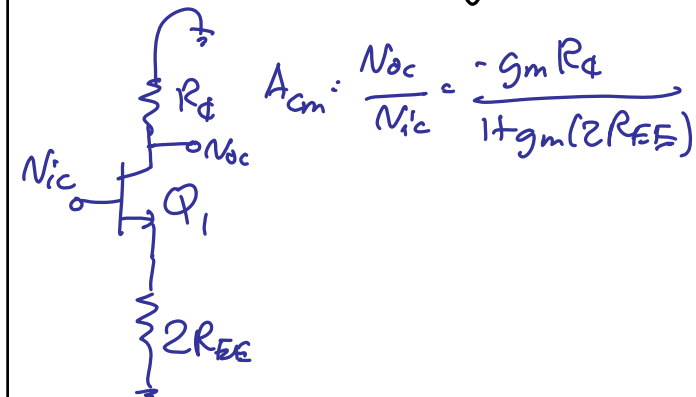→ did differential part on the board... see the end of these notes...
 (ii) find the common-mode gain.



If there is a mismatch in the load, e.g., $R_{C1} \neq R_{C2}$, then we can also define:

$$A_{cm-dm} \triangleq \text{Common-mode input to differential-mode output gain}$$

$$= \frac{N_{od}}{N_{ic}} = \frac{N_{o1} - N_{o2}}{N_{i1}} = \frac{N_{o1} - N_{o2}}{N_{i2}} \quad (\text{w/ } N_{i1} = N_{i2})$$


$$A_{dm-cm} \triangleq \text{differential-mode input to common-mode output gain}$$

$$= \frac{N_{oc}}{N_{id}} = \frac{N_{oc}}{N_{i1} - N_{i2}} \quad \left[\text{w/ } N_{oc} = \frac{1}{2}(N_{o1} + N_{o2}) \right]$$

You will be experiencing these in a future trv.

over for report of
 chalkboard
 material

Parts Done on the Chalkboard

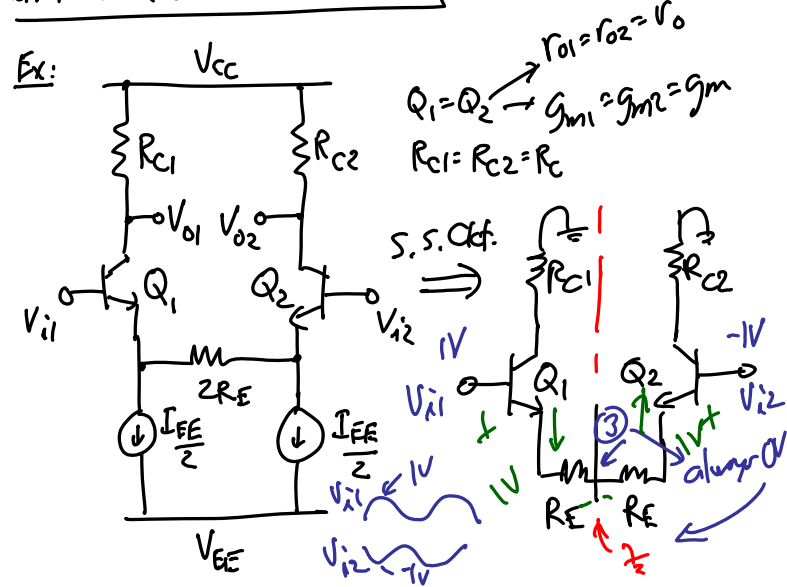

(i) Find the differential-mode gain: (A_{dm})


$$\frac{(N_{od}/2)}{(N_{id}/2)} = \frac{-g_m(R_C || R_E)}{1 + g_m R_E}$$

$$A_{dm} = \frac{N_{o1} - N_{o2}}{N_{i1} - N_{i2}} = \frac{N_{od}}{N_{id}} = \dots$$


Diff. Half Ckt.

EE 140 Differential Mode Analysis CTN 6

Small-Signal Analysis of Diff. Pair

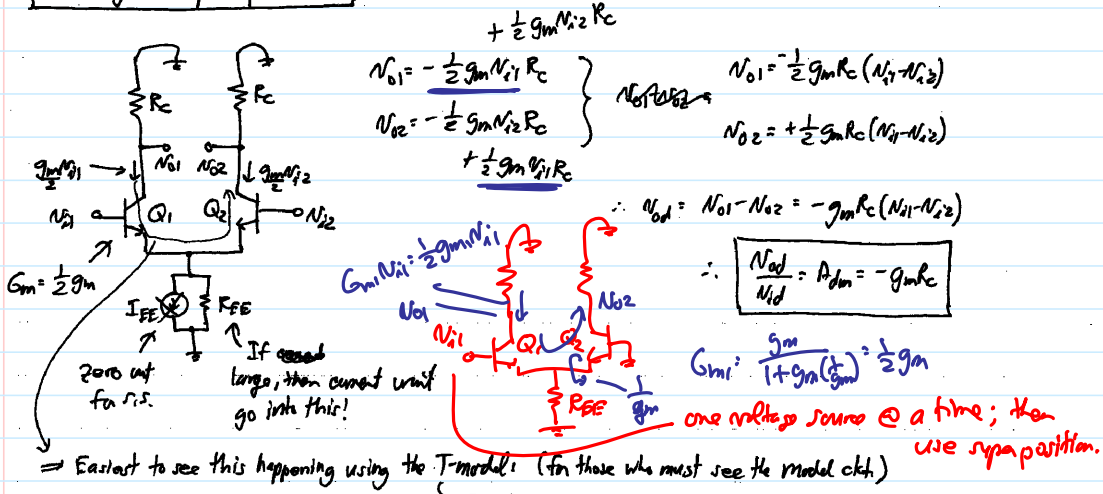


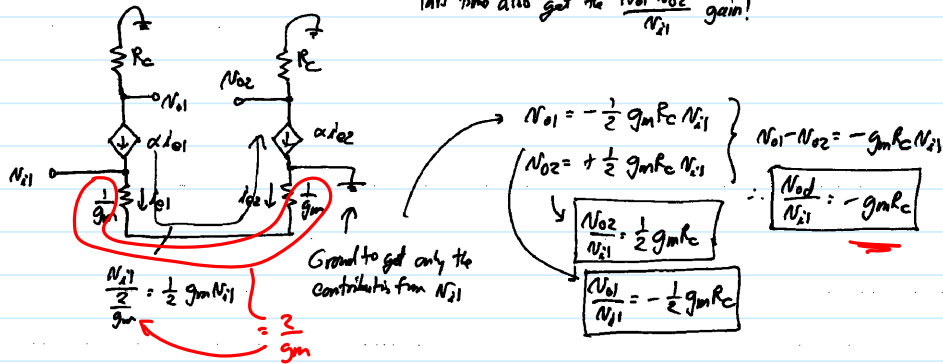= Easiest to see this happening using the T-model: (for those who must see the model ckt)




Diff. Mode Analysis

Assume a ckt. w/ only diff. input:

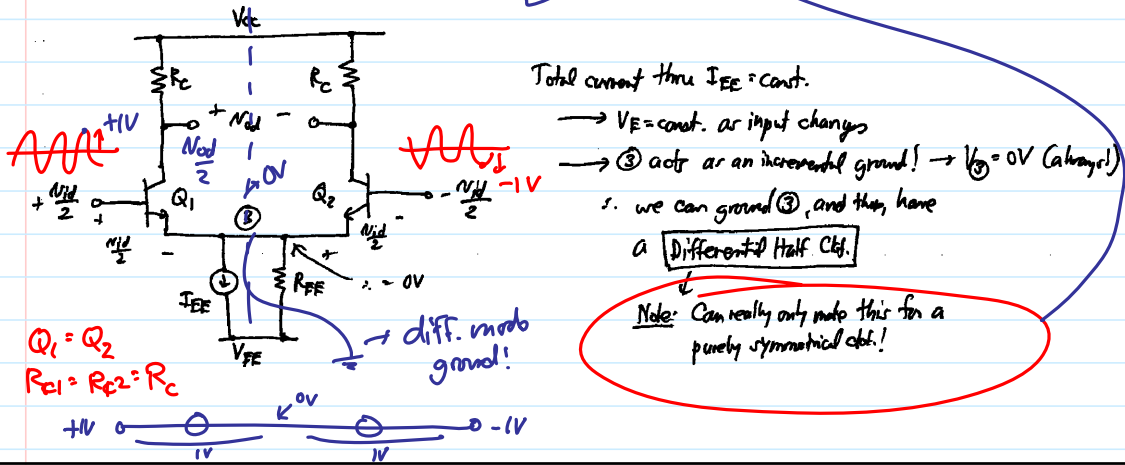

EE 140 Common-Mode Analysis CTN 7

Differential Half Ckt.

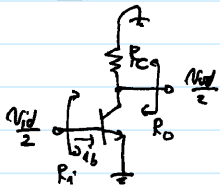


By inspection: $\frac{v_{Od/2}}{v_{id/2}} = \frac{v_{Od}}{v_{id}} = A_{dm} = -g_m R_c$

$\frac{v_{id/2}}{i_b} = r_{\pi} \rightarrow R_{id} = \frac{v_{id}}{i_b} = 2r_{\pi} = R_{id}$

S.S. params. determined w/ $I_c = \frac{I_{EE}}{2}$

Common-Mode Analysis

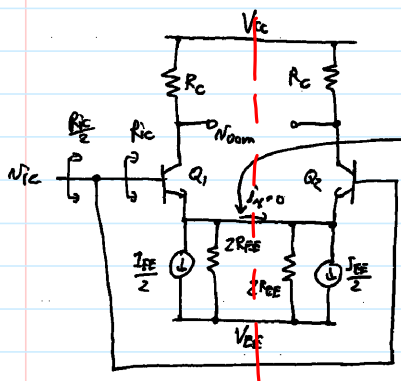
Assume a pure CM input \rightarrow tie inputs together



By symmetry, $i_x = 0 \Rightarrow$ then, really have the equivalent of an open ckt. here

$\therefore \Rightarrow$ can split the ckt. into CM half-ckt.!

S.S. CM Half-Ckt.

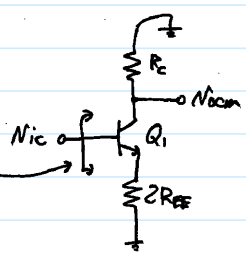

$R_{ic} = r_{\pi} + (\beta + 1)(2R_{EE})$
@ each input

$A_{cm} = \frac{v_{Ocm}}{v_{ic}} = -\frac{g_m R_c}{1 + g_m(2R_{EE})} \approx -\frac{R_c}{2R_{EE}}$

Want small for large CMRR \therefore want $R_{EE} = \text{large!}$


Common-Mode Rejection Ratio = $CMRR = \frac{A_{dm}}{A_{cm}} = \frac{-g_m R_c}{-\frac{g_m R_c}{1 + g_m(2R_{EE})}} \Rightarrow CMRR = 1 + 2g_m R_{EE}$

Want as ideal a current source as possible!

Having looked at S.S. parameters, we now turn to large signal performance. Here, we'll be particularly interested in the linear range of the ECP.

EE 140 Large Signal ECP Performance CTN 8

Large Signal ECP performance

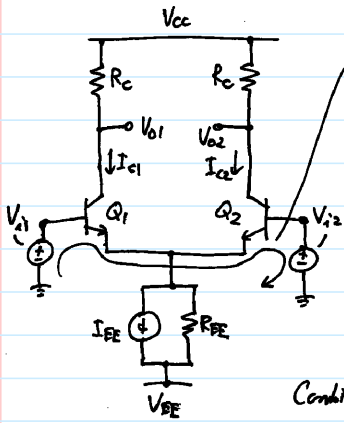

Find I_{c1} & I_{c2} :

KVL: $V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$

$I_{c1} = I_{s1} \exp\left(\frac{V_{be1}}{V_T}\right) \rightarrow V_{be1} = V_T \ln\left(\frac{I_{c1}}{I_{s1}}\right), V_{be2} = V_T \ln\left(\frac{I_{c2}}{I_{s2}}\right)$

$V_{i1} - V_T \ln\left(\frac{I_{c1}}{I_{s1}}\right) - V_T \ln\left(\frac{I_{c2}}{I_{s2}}\right) - V_{i2} = 0 \rightarrow \ln\left(\frac{I_{c1}}{I_{c2}}\right) = \frac{V_{i1} - V_{i2}}{V_T} = \frac{V_{id}}{V_T}$

$$\frac{I_{c1}}{I_{c2}} = \exp\left(\frac{V_{id}}{V_T}\right) \quad (1)$$

$$I_{EE} = I_{c1} + I_{c2} = \frac{1}{\alpha} (I_{c1} + I_{c2}) \quad (2)$$

Combine (1) & (2) to get:

$$I_{c1} = \frac{\alpha I_{EE}}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)}, \quad I_{c2} = \frac{\alpha I_{EE}}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} \quad (3)$$

Find V_{od} :

$$\left. \begin{aligned} V_{o1} &= V_{CC} - I_{c1} R_C \\ V_{o2} &= V_{CC} - I_{c2} R_C \end{aligned} \right\} V_{od} = V_{o1} - V_{o2} = (I_{c2} - I_{c1}) R_C$$

using (3)

$$= \alpha I_{EE} R_C \left\{ \frac{1}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} - \frac{1}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)} \right\}$$

$$\times \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right)} \quad \times \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right)}$$

$$= \alpha I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} - \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right) + \exp\left(-\frac{V_{id}}{2V_T}\right)} \right\}$$


$$= \alpha I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right) - \exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} \right\} = \alpha I_{EE} R_C \frac{\sinh\left(-\frac{V_{id}}{2V_T}\right)}{\cosh\left(-\frac{V_{id}}{2V_T}\right)}$$

$$\left. \begin{aligned} \sinh u &= \frac{1}{2} (e^u - e^{-u}) \\ \cosh u &= \frac{1}{2} (e^u + e^{-u}) \end{aligned} \right\} u = -\frac{V_{id}}{2V_T}$$

$$\therefore V_{od} = \alpha I_{EE} R_C \tanh\left(-\frac{V_{id}}{2V_T}\right)$$

From our knowledge of the Taylor series for $\tanh x \approx x - \frac{x^3}{3} + \frac{2}{15}x^5 - \dots$
This is fairly linear for small V_{id} , but gets nonlinear abruptly when V_{id} approaches a threshold value!


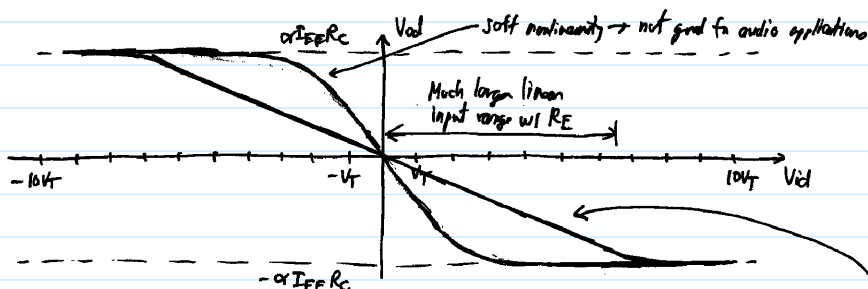
EE 140 Large Signal ECP Performance CTN 9



In the above curve, the $\frac{V_{od}}{V_{id}}$ Xfer function is really, only linear for $V_{id} < V_t \rightarrow$ beyond V_t , start to enter the non-linear realm of curve \rightarrow causes signal distortion: eg., phone breaking up, television static

To linearize: add emitter degeneration (same trick as used before for single Xsistor amplifiers)

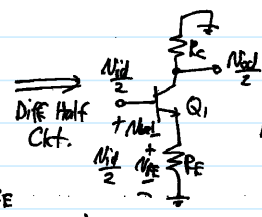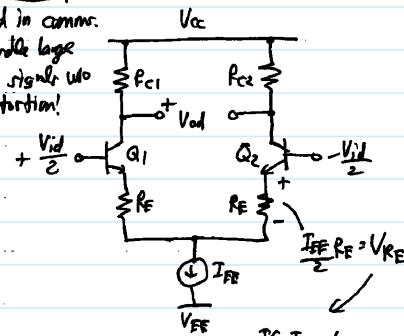Needed in comm. to handle large input signals w/o distortion!




$$A_{dm} = -\frac{g_m R_C}{1 + g_m R_E}$$

\Rightarrow s.f. gain reduced, but the linear range is increased

If I_{EE} is large, then this can force large supply voltages
 $\frac{N_{id}}{2} = N_{id1} + N_{RE}$
 This can still be $N_{id1} < V_t$ if this absorbs some of the input voltage!

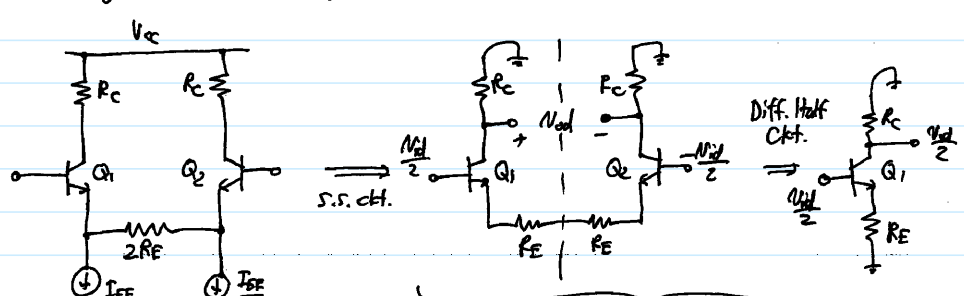
Alternative Biasing Technique If Need Larger DC Currents:-



Same S.S. performance w/o the need to drop a DC voltage across $R_E \rightarrow$ get both
 Can use Power $V_{CC} + V_{EE}$.

EE 140 MOS Source-Coupled Pair CTN 10

MOSFET Source-Coupled Pair

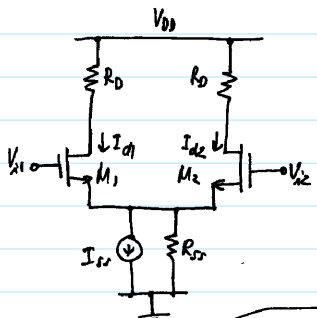

Assume: M_1 & M_2 are identical.

Find $\Delta I_d = I_{d1} - I_{d2} = f(V_{id})$.

\Rightarrow approach: get $V_{id} = f(\Delta I_d) \rightarrow$ then invert to get $\Delta I_d = f(V_{id})$

$$I_{d1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs1} - V_t)^2 \Rightarrow V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$$

$$\therefore V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}}$$

Define: $\Delta I_d = I_{d1} - I_{d2}$
 $I_d = \frac{I_{d1} + I_{d2}}{2}$

$$\left. \begin{aligned} I_{d1} &= I_d + \frac{\Delta I_d}{2} \\ I_{d2} &= I_d - \frac{\Delta I_d}{2} \end{aligned} \right\}$$

$$V_{id} = \sqrt{\frac{2(I_d + \frac{\Delta I_d}{2})}{k}} - \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_d + \frac{\Delta I_d}{2} - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2} + I_d - \frac{\Delta I_d}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_d - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2}$$

\Rightarrow now rearrange to get ΔI_d (algebra)

Solve for ΔI_d :
$$\Delta I_d = \frac{k}{2} V_{id} \left(\frac{2I_{ss}}{k/2} - V_{id}^2 \right)^{\frac{1}{2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left(\frac{2I_{ss}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_d$$

Large signal Equation for Differential Output Current

Valid so long as the devices stay saturated:


$$|V_{id}| \leq \sqrt{\frac{2I_{ss}}{k}} = \sqrt{\frac{2I_{ss}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

V_{GS} for $I_D = \frac{I_{ss}}{2}$

if true then input devices are both saturated

Thus, to extend the linear input range:

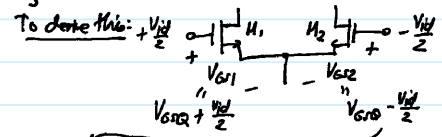- ① $I_{ss} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ② W/L
- ③ $L \uparrow$



When $V_{id} \geq V_{GSQ} - V_t = \Delta V$ then M_2 will cut-off

$\therefore V_{id} \leq 2(V_{GSQ} - V_t) \rightarrow$ to maintain saturation

$$V_{GSQ} - V_t = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$


Then plug in ΔI_d & solve for V_{id}

EE 140 Diff. Pair w/ Current Mirror Load


CTN

11

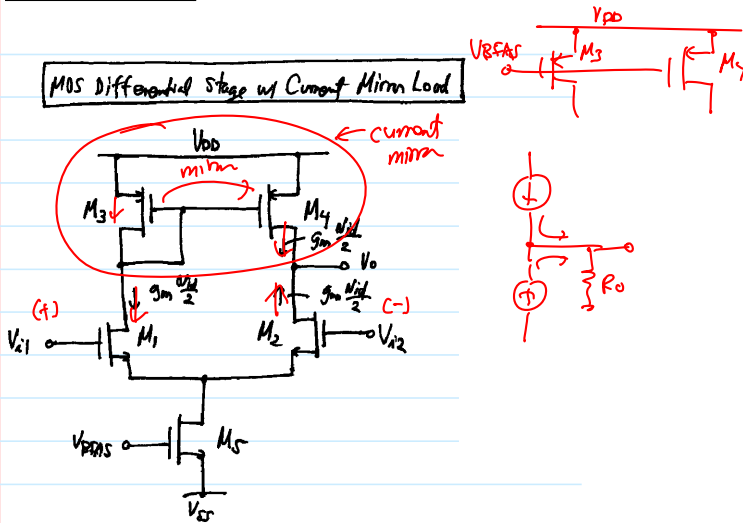MOS Differential Stage w/ Current Mirror Load



CMRR -

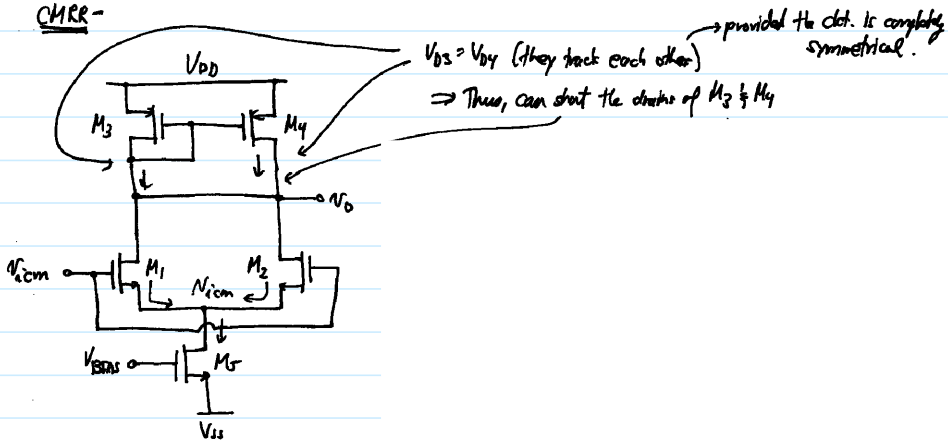

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep M_5 saturated