

Lecture 14: SCP & Vos

• Announcements:


- ↳ I will need to miss next Thursday's lecture
- ↳ Makeup lecture Friday, 3/9, 3-4:30 p.m., in 277 Cory

• Lecture Topics:


- ↳ Source Coupled Pair w/ Current Mirror Load
- ↳ Input Offset Voltage (Vos)
- ↳ Op Amp Non-Ideality
- ↳ Op Amp Finite Gain-BW

• Last Time:

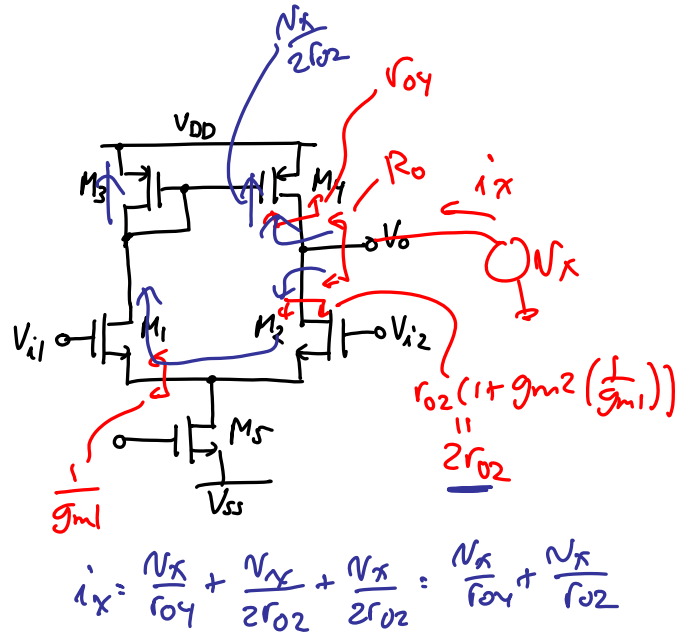- Going through the handout on Op Amps and Differential Pairs
- Continue with this now ...




$$R_{o2} \frac{N_x}{I_x} = r_{o2} || r_{o4}$$

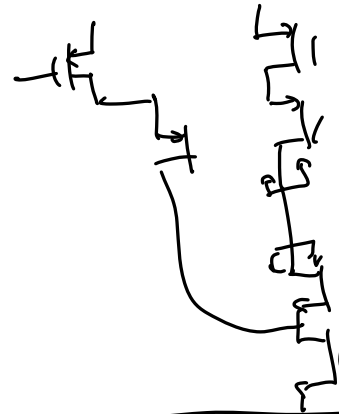

Vos of a mismatched SCP


Objective: Derive an expression for Vos.

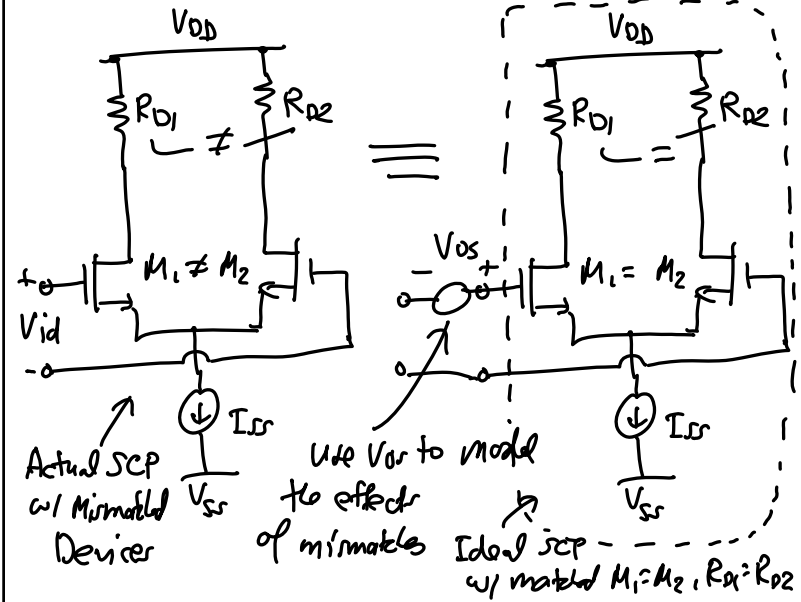

Vos arises due to variations in:

- ①  $X_{mirrors}, M_1 \neq M_2 \rightarrow \frac{W}{L} \neq V_t$  vary
- ②  $R_{D1} \neq R_{D2} \rightarrow$  cause variations in gain

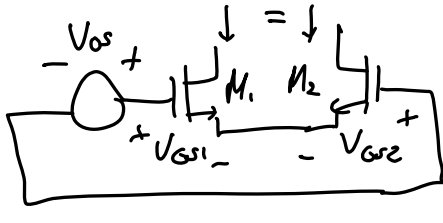Defn.  $V_{os} = V_{id}$  needed to get  $V_{od} = 0V$  in this ckt.



KVL:  $V_{os} - V_{GS1} + V_{GS2} = 0$   
 $\therefore V_{os} = V_{GS1} - V_{GS2}$

$$= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{os} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\Delta I_D = I_{D1} - I_{D2} \quad \left| \quad \Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$

$$I_D = \frac{I_{D1} + I_{D2}}{2} \quad \left| \quad \left(\frac{W}{L}\right) = \frac{1}{2} \left[ \left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$$

$$\Delta V_t = V_{t1} - V_{t2} \quad \left| \quad \Delta R_D = R_{D1} - R_{D2}$$

$$V_t = \frac{1}{2}(V_{t1} + V_{t2}) \quad \left| \quad R_D = \frac{1}{2}(R_{D1} + R_{D2})$$

Rearranging:

$$I_{D1} = I_D + \frac{\Delta I_D}{2} \quad \left| \quad \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} \quad \left| \quad V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2} \quad \left| \quad \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} \quad \left| \quad V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Substituting into (1):  $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{os} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[ \left(\frac{W}{L}\right) + \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[ \left(\frac{W}{L}\right) - \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}}$$

$$\left\{ V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox}(W/L)}} \right\} \quad \left\{ \frac{W}{L} \left[ 1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right] \right\}$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1 + nx)^m \rightarrow 1 + mnx$$

$n = \text{small}$

$$V_{os} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\left\{ 1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} - 1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} \right\}$$

$$= \Delta V_t + (V_{GS} - V_t) \left( \frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{os} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When  $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1}R_{D1} = I_{D2}R_{D2}$

↪ mismatch in  $I_D$  must be opposite that of  $R_D$

$\therefore \frac{\Delta I_D}{I_D} = -\frac{\Delta R_D}{R_D}$

$$V_{os} = \Delta V_{t} + \frac{1}{2}(V_{GS} - V_{t}) \left\{ -\frac{\Delta R_D}{R_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

↪ Threshold Voltage Mismatch  
 ↪ Bias dependent

↪ Geometric Variations (i.e., layout & litho)  
 ↪ scale w/ overdrive



EE 140

MOS Source-Coupled Pair

CTN

10

MOSFET Source-Coupled Pair

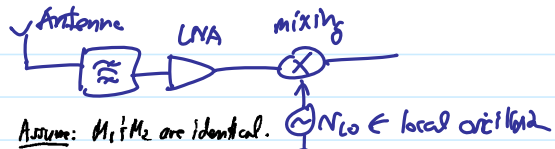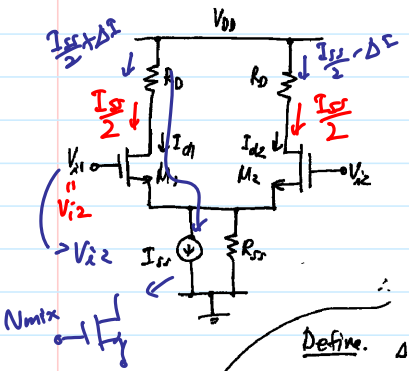

Assume:  $M_1, M_2$  are identical.  
Find  $\Delta I_d = I_{d1} - I_{d2} = f(V_{id})$ .  
 $\Rightarrow$  approach: get  $V_{id} = f(\Delta I_d) \rightarrow$  then invert to get  $\Delta I_d = f(V_{id})$   
 $I_{d1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs1} - V_t)^2 \Rightarrow V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$

$$\therefore V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}}$$

Define:  $\Delta I_d = I_{d1} - I_{d2}$   
 $I_d = \frac{I_{d1} + I_{d2}}{2}$

$$\left. \begin{aligned} I_{d1} &= I_d + \frac{\Delta I_d}{2} \\ I_{d2} &= I_d - \frac{\Delta I_d}{2} \end{aligned} \right\}$$

$$V_{id} = \sqrt{\frac{2(I_d + \frac{\Delta I_d}{2})}{k}} - \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_d + \frac{\Delta I_d}{2} - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2} + I_d - \frac{\Delta I_d}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_d - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2}$$

$\Rightarrow$  now rearrange to get  $\Delta I_d$  (algebra)

Solve for  $\Delta I_d$ :  $\Delta I_d = \frac{k}{2} V_{id} \left( \frac{2I_{ss}}{k} - V_{id}^2 \right)^{\frac{1}{2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left( \frac{2I_{ss}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_d$

Large signal Equation for Differential Output Current


Valid so long as the devices stay saturated:

$$|V_{id}| \leq \sqrt{\frac{2I_{ss}}{k}} = \sqrt{\frac{2I_{ss}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

if true then input devices are both saturated

Thus, to extend the linear input range:

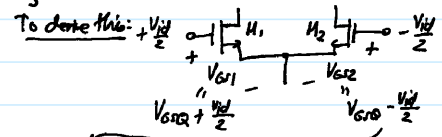
- ①  $I_{ss} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ②  $W/L$
- ③  $L \uparrow$



When  $V_{id} \geq V_{GSa} - V_t = \Delta V$  then  $M_2$  will cut-off  
 $\therefore V_{id} \leq 2(V_{GSa} - V_t) \rightarrow$  to maintain saturation  
 $V_{GSa} - V_t = \sqrt{\frac{2I_{d2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$   
Then plug in  $\Delta I_d$  & solve for  $V_{id}$


EE 140 Diff. Pair w/ Current Mirror Load CTN 11

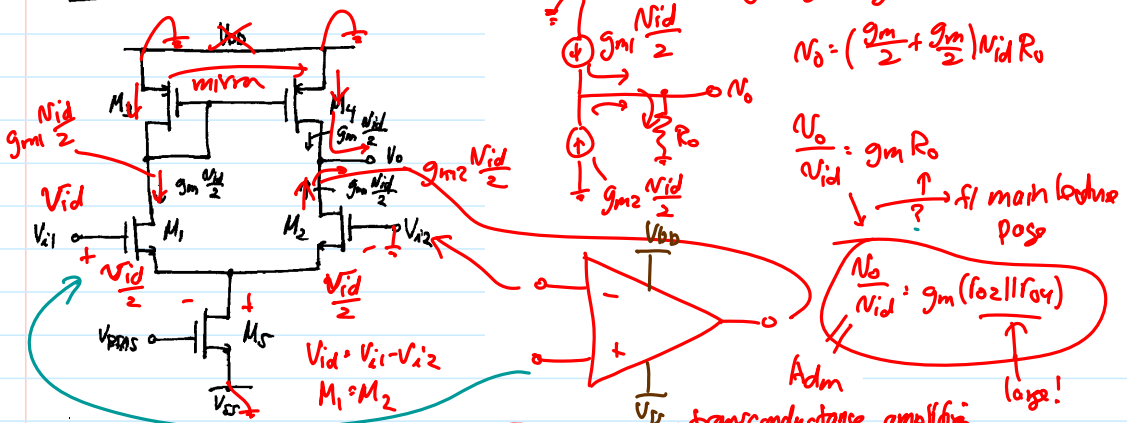MOS Differential Stage w/ Current Mirror Load



OTA → operational transconductance amplifier

CMRR -

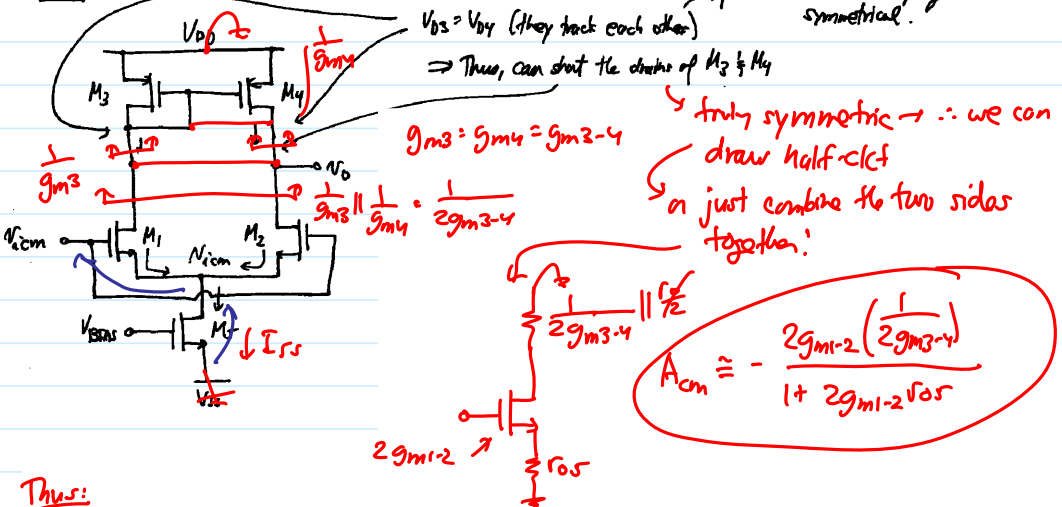

Thus:

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1-2} (r_{o1-2} || r_{o3-4}) (1 + 2g_{m1-2}r_{os}) \left( \frac{g_{m3-4}}{g_{m1-2}} \right)$$

$$CMRR = (1 + 2g_{m1-2}r_{os}) g_{m2-4} (r_{o1-2} || r_{o3-4})$$

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep  $M_5$  saturated

$$V_{icm(min)} = CMR^- = V_{SS} + V_{ovs} + V_{ovs1,2}$$

$$CMR^- = V_{SS} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox}(W/L)_5}} + V_{t1,2} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox}(W/L)_1}}$$

smallest common-mode voltage @ input w/o something gets wrong  
triode


EE 140

Diff. Pair w/ Current Mirror Load

CTN

12

High End - keep  $M_1, M_2$  saturated

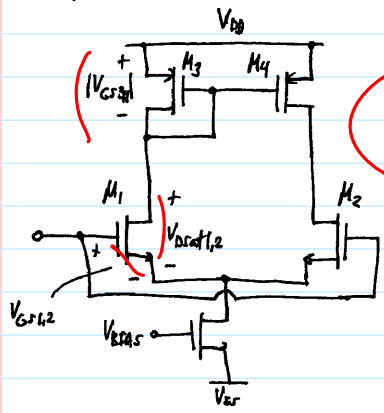

$$V_{icm(max)} = CMR \uparrow = V_{DD} - |V_{GS3,4}| - \underbrace{V_{GS1,2}}_{V_{GS1,2} + V_{\epsilon 1,2}} + V_{GS1,2}$$

$$V_{icm(max)} = CMR \uparrow = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} (W/L)_{3,4}}} |V_{\epsilon 3,4}| + V_{\epsilon 1,2}$$

EE 140

Input Offset Voltage

CTN


1

Device Mismatch Effects in Diff. Amplifiers

⇒ up to this point, we assumed that  $Q_1$  &  $Q_2$  are perfectly matched  
⇒ in actual ckt., get device mismatches due to processing variations

The Results

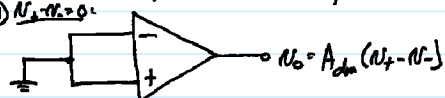①  $N_1 = N_2 = 0$ : Output not zero when Input is zero →  $N_0 \neq 0$  when  $N_{1,2} = 0!$



Ideal Case:  $N_0 = 0$

Reality:  $N_0 \neq 0$ , even if  $(N_1 - N_2) = 0!$


② Input  $I_{B1} \neq I_{B2}$  if  $Q_1$  &  $Q_2$  not matched. (for BJT & JFET only)

To model these effects, introduce:

① Input Offset Voltage,  $V_{os}$


② Input Offset Current,  $I_{os}$

Typ.  $I_{os} = 10 \text{ nA}$  for BJT

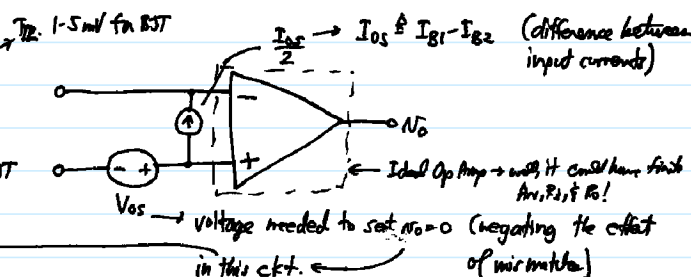

Effect of  $V_{os}$  on Op Amp Ckt. -


Example. Integrator

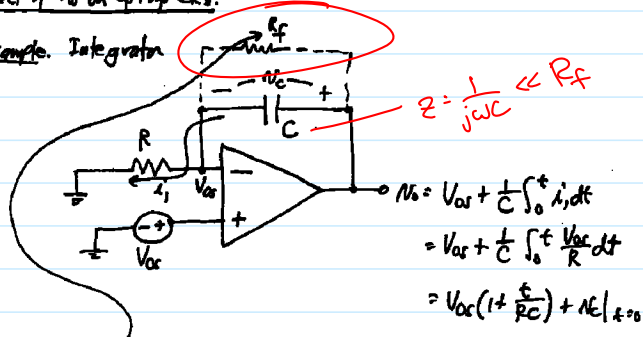

$$N_0 = V_{os} + \frac{1}{C} \int_0^t i_i dt$$

$$= V_{os} + \frac{1}{C} \int_0^t \frac{V_{os}}{R} dt$$

$$= V_{os} \left(1 + \frac{t}{RC}\right) + N_C|_{t=0}$$

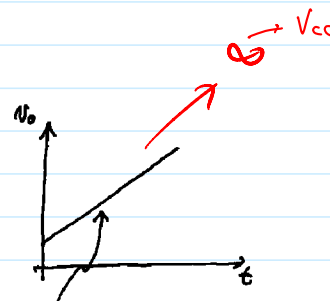

Fix: Place an  $R_f$  in shunt w/ the C

→ then  $N_0 = V_{os} \left(1 + \frac{R_f}{R}\right)$ , and railing doesn't happen

⇒ but, usually  $R_f$  is large to allow the C to dominate

the integrator Xfn Function ∴  $N_0 = V_{os} \left(1 + \frac{R_f}{R}\right)$  can be quite large ⇒ still want  $V_{os} = \text{small}$

$V_{os}$  is even more important in setting the resolution of AD converters and other precision ckt.