

Lecture 15: Finite Gain-BW

• Announcements:

- ↳ HW#6 due today; HW#7 online
- ↳ Lab#2 extended one week; due week of 3/19
- ↳ Reminder: No lecture this coming Thursday
- ↳ Makeup lecture Friday, 3/9, 3-4:30 p.m., in 277 Cory


• Lecture Topics:

- ↳ Input Offset Voltage (V_{os})
- ↳ Op Amp Finite Gain-BW
- ↳ High Gain Op Amps

• Last Time:

V_{os} of a mismatched SCP

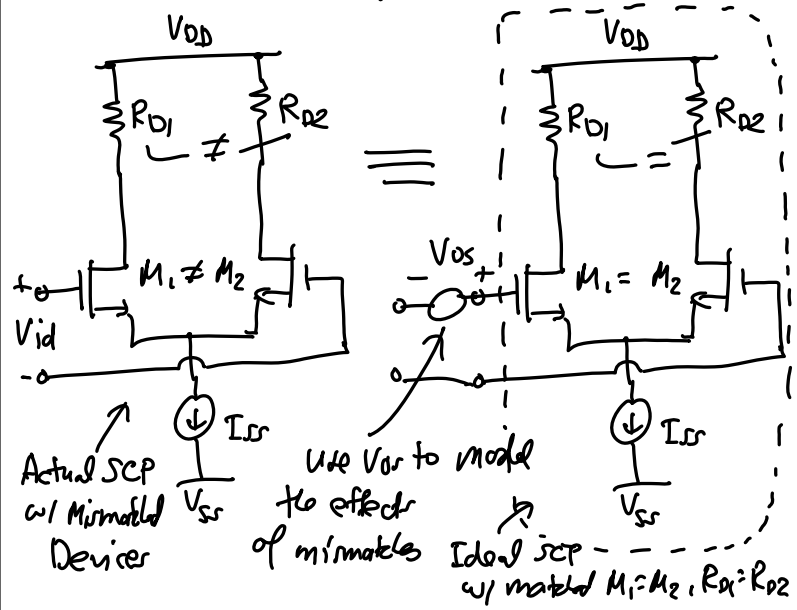
Objective: Derive an expression for V_{os} .



V_{os} arises due to variations in:

- ① $X_{paras}, M_1, \& M_2 \rightarrow \frac{W}{L} \& V_t$ vary
- ② $R_{D1} \neq R_{D2} \rightarrow$ cause variations in gain

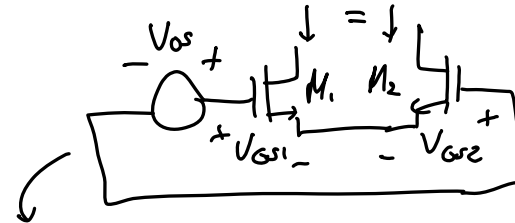Defn. V_{os} = V_{id} needed to get $V_{od} = 0V$ in this ckt.



KVL: $V_{os} - V_{GS1} + V_{GS2} = 0$

$\therefore V_{os} = V_{GS1} - V_{GS2}$

$$= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{os} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\Delta I_D = I_{D1} - I_{D2} \quad \left| \quad \Delta\left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$

$$I_D = \frac{I_{D1} + I_{D2}}{2} \quad \left| \quad \left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$$

$$\Delta V_t = V_{t1} - V_{t2} \quad \left| \quad \Delta R_D = R_{D1} - R_{D2}$$

$$V_t = \frac{1}{2}(V_{t1} + V_{t2}) \quad \left| \quad R_D = \frac{1}{2}(R_{D1} + R_{D2})$$

Rearranging:

$$\begin{array}{l|l|l} I_{D1} = I_D + \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} & V_{t1} = V_t + \frac{\Delta V_t}{2} \\ I_{D2} = I_D - \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} & V_{t2} = V_t - \frac{\Delta V_t}{2} \end{array}$$

Substituting into (1): $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}}$$

$$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right] \cdot \left[\frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right] \right]$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1+mx)^m \rightarrow 1+mnx \quad n = \text{small}$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} - 1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2}$

mismatch in I_D must be opposite that of R_D

$$\therefore \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D}$$

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ + \frac{\Delta R_D}{R_D} + \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Voltage Mismatch
Bias Dependent

Geometric Variations (i.e., layout & litho)

scale w/ overdrive
 $\frac{W}{L} \uparrow \rightarrow V_{ov} \downarrow$

These (-)'s don't help: $\frac{\Delta R_D}{R_D} = (+) \text{ or } (-)$

• Now, go through bipolar mismatch prepared material

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.
In reality, the gain is given by: $A(s) = \frac{A_0}{1 + s/\omega_b}$

open loop op amp by itself

$20 \log(A_0)$
 $20 \log(1 + T_0)$
 $20 \log(\frac{1}{\beta})$
 $20 \log(1) = 0 \text{ dB}$

ω_b $\omega_b(1 + T_0)$ ω_T

$T_0 = A_0 \beta$

$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$ (= 0 dB)

At ω_T :
 $|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + (\frac{\omega_T}{\omega_b})^2}}$ dc gain

$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\omega_T} = 1 \rightarrow \omega_T = A_0 \omega_b$
Gain-Bandwidth Product

For $\omega \gg \omega_b$:
 $A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f}$ Integrate w/ time
Constant $C = \frac{1}{\omega_T}$

The unity gain bandwidth f_T is usually specified on op amp data sheet. Knowing f_T , one can easily determine the op amp gain at a given frequency f .

Frequency Response of Closed Loop Amplifier

Example. Non-Inverting Amplifier

N_i $N_o = A(s)(N_+ - N_-)$

$N_- = N_+ - \frac{N_o}{A(s)}$
 $N_- = N_i - \frac{N_o}{A(s)}$

Find an expression for the gain as a function of frequency.

① Brute force derivation:

KCL @ ①: $\frac{N_o - N_-}{R_2} = \frac{N_-}{R_1} \Rightarrow \frac{N_o}{R_2} = N_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$

$\frac{N_o}{R_2} = (N_i - \frac{N_o}{A(s)}) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{N_o}{N_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$


$[A(s) = \frac{A_0}{1 + s/\omega_b}] \Rightarrow \frac{N_o}{N_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{s}{\omega_b} \frac{1 + \frac{R_2}{R_1}}{A_0}} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{s}{\omega_b} \frac{1 + \frac{R_2}{R_1}}{A_0 \omega_b \left(\frac{R_1}{R_1 + R_2} \right)}}$

algebra freq. shaping term

② More insightful way to do this:

Neg. FB Block Diagram

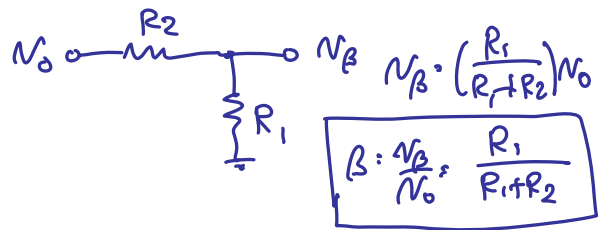$N_2 = N_i - N_\beta$
 $N_i = N_2 + N_\beta$



Recall from previous FB analysis:

$$\frac{V_o}{V_i(s)} = \frac{A(s)}{1 + \beta A(s)}$$

$$\left[A(s) = \frac{A_o}{1 + s/\omega_b} \right] \rightarrow \frac{V_o}{V_i(s)} = \frac{\frac{A_o}{1 + s/\omega_b}}{1 + \beta \left(\frac{A_o}{1 + s/\omega_b} \right)}$$

$$\frac{V_o}{V_i(s)} = \frac{A_o}{1 + \beta A_o} \cdot \frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_o)}}$$

closed loop dc gain: $\frac{A_o}{1 + \beta A_o} \approx \frac{1}{\beta}$ (if $\beta A_o \gg 1$)

freq. shaping term: $\frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_o)}}$

$\beta A_o = T_o \triangleq$ "loop gain" at $\omega = 0$ (i.e., at dc)

Plug in β :

$$\frac{V_o}{V_i(s)} \approx \frac{1}{\beta} \frac{1}{1 + \frac{s}{\omega_b \beta A_o}} = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{\omega_b A_o \left(\frac{R_1}{R_1 + R_2} \right)}}$$

What if $A_o \neq$ large?
 \rightarrow can't say $\frac{A_o}{1 + \beta A_o} \approx \frac{1}{\beta}$


- Observations:
- ① Closed loop DC gain = $\frac{A_o}{1 + \beta A_o} = \frac{A_o}{1 + T_o} \approx \frac{A_o}{T_o}$
 i.e., the closed loop gain is reduced from the open loop gain by $1 + T_o \rightarrow$ show this on graph [$T_o \gg 1$]
 - ② Alternatively, closed loop DC gain $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta}$ [$T_o \gg 1$]
 - ③ ω_{-3dB} has increased from $\omega_b \rightarrow \omega_b(1 + \beta A_o) = \omega_b(1 + T_o)$
 \hookrightarrow To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!
 - ④ Gain-BW Product = $\frac{A_o}{1 + \beta A_o} \omega_b(1 + \beta A_o) = A_o \omega_b = \omega_T$
 \therefore the Gain-BW product remains the same for the open & closed loop FB cases!

High Gain Op Amps

How can we increase gain?

- ① Cascode
- ② Cascode of Amplifiers

Telescopic Op Amp w/ Single-Ended Output

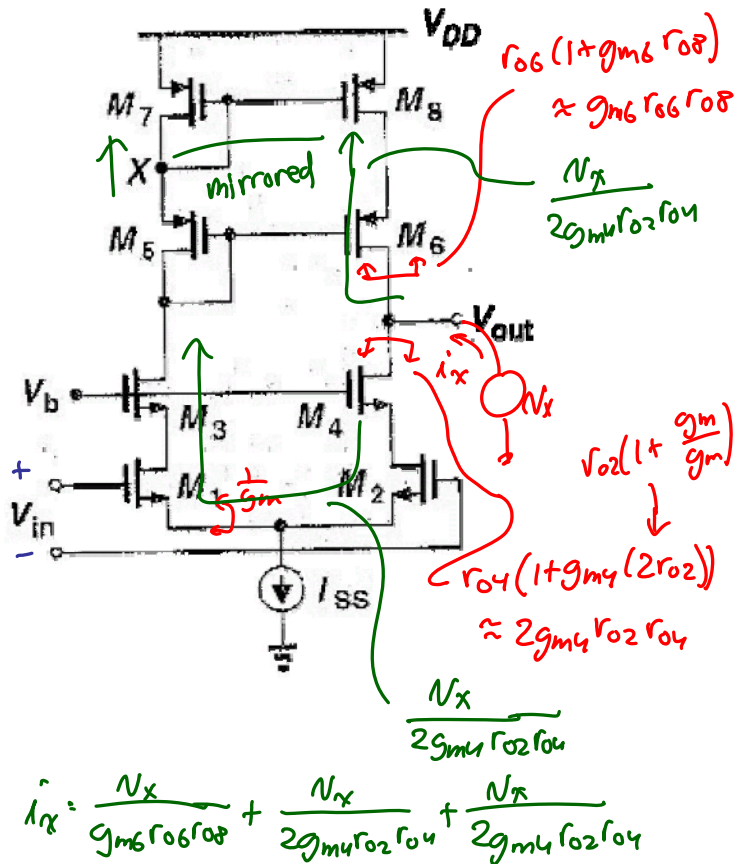

$$R_o = \frac{V_x}{i_x} = (g_{m6}r_{o6}r_{o8}) || (g_{m4}r_{o2}r_{o4}) = (g_{mp}r_{op}^2) || (g_{mn}r_{on}^2)$$

