

Lecture 18: Stability


Announcements:

- ↳ Lab#2 due week of 3/19 (next week) which is one week after the original due date
- ↳ Suggestion: Get it done this week
- ↳ Midterm Exam next Thursday, 3/22
- ↳ Review Session: Monday, 3/19, 7-9 p.m., Hogan Room (521 Cory)

Lecture Topics:

- ↳ Midterm information
- ↳ Output Stages (continued)
- ↳ Stability

Last Time: Emitter Follower (Class A)

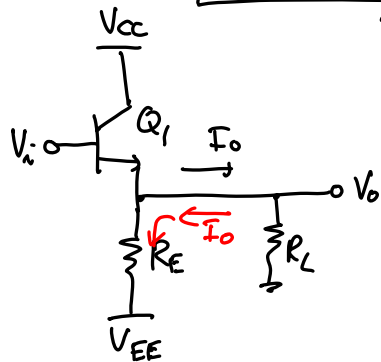

Two main cases:

① $I_o > 0$: I_o comes from Q_1
 \Rightarrow adequate I_o can be supplied so long as Q_1 stays in forward active


② $I_o < 0$: (i.e., $V_o < v_i$)

I_o must be sunk to V_{EE} through R_E

$I_o = \frac{V_o - V_{EE}}{R_E} \rightarrow |I_o|$ gets smaller as $V_o \downarrow$

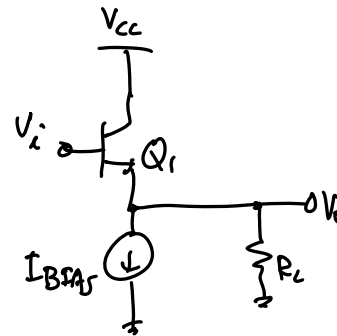
Problem!

Solution: Replace R_E w/ a current source.



Now can source I_o through Q_1 for $V_o = (+)$.
 \downarrow
 And can sink $I_o = I_{BIAS}$, when I_o stays $= I_{BIAS}$ or V_o changes.


Actual Implementation:

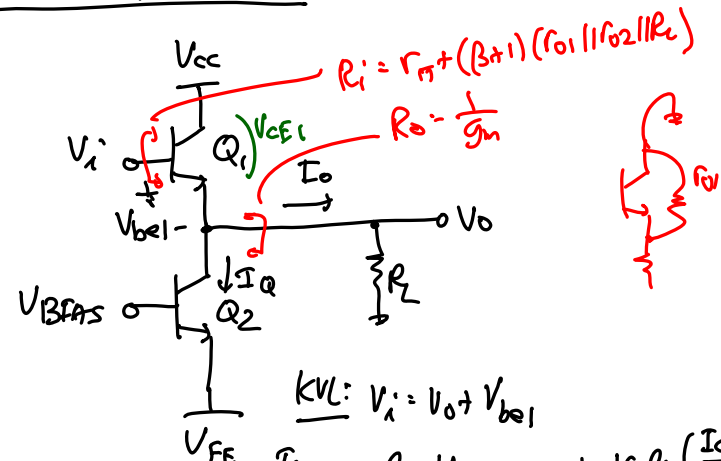

$R_i = r_{\pi 1} + (\beta + 1)(r_{o1} || r_{o2} || R_L)$
 $R_o = \frac{1}{g_m}$

KVL: $V_i = V_o + V_{be1}$
 In general: $V_{be1} \neq \text{const} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$
 (for Q_2 in F.A.R.)

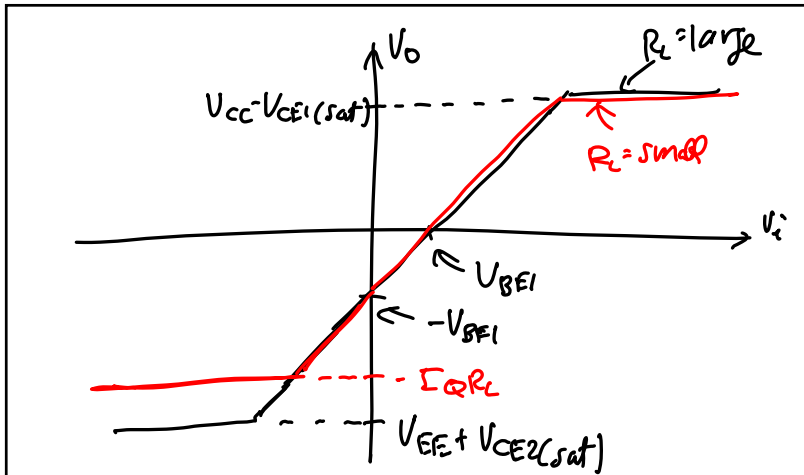$I_{C1} = I_o + I_{Q2} = I_{Q1} + \frac{V_o}{R_L}$
 $\therefore V_i = V_o + V_T \ln\left(\frac{I_{Q1} + \frac{V_o}{R_L}}{I_{S1}}\right)$



Two Cases:

Case 1: $R_L = \text{large}$

$\rightarrow I_o$ not Δ 'ing much to deliver large excursions in V_o
 $\hookrightarrow I_{C1}$ not Δ 'ing much

For $V_i = \text{large and } (+)$: Q_1 must source $I_o + I_Q$

$$V_o = V_i - V_{be1}$$

@ some pt., Q_1 will

saturate or $V_o \uparrow$

\downarrow
defines V_{omax}

$$V_{omax} = V_{CC} - V_{CE1(sat)}$$

and $V_i = V_{CC} - V_{CE1(sat)} + V_{be1}$

For $V_i = \text{large and } (-)$: V_o follow V_i until Q_2 saturates

$$V_{omin} = V_{EE} + V_{CE2(sat)} \quad \rightarrow 0.2V$$

$$V_i = V_o + V_{BE1} = V_{EE} + V_{CE2(sat)} + V_{BE1}$$

Case 2: $R_L = \text{small}$ \rightarrow ΔI_{C1} , I_o can be large!

For $V_i = (+)$ and large: Q_1 can source as much current as needed until it saturates (or it fries)

For $V_i = (-)$ and large: $V_o = +I_o R_L \rightarrow \text{min. } V_o = -I_Q R_L$

$\Rightarrow Q_1$ cuts off ($I_{C1} = 0$)

$\Rightarrow V_o$ clamps @ $-I_Q R_L$

\uparrow further decreases in $V_i \rightarrow$ no Δ in V_o
 fix by making $I_Q = \text{large}$


Problem: too much power consumption

$$P_Q = (V_{CC} - V_{EE}) I_Q \leftarrow \text{DC power consumption!}$$

\uparrow $V_{EE} = (-)$ \downarrow w/ Class A, if you want a large output swing w/ $R_L = \text{small}$, you must consume power!

Solution: **Class B Output Stage**

↳ can attain zero DC (quiescent) power

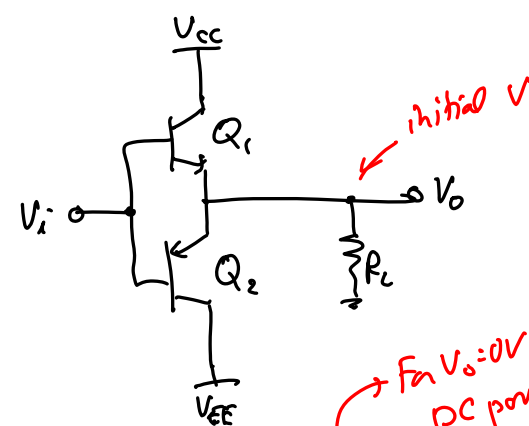

initial $V_O = 0V$


For $V_O = 0V \rightarrow$ no DC power consumption!

Operation:


$|V_i| < V_{BE(on)} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_O = 0V$

$V_{CC} > |V_i| > V_{BE(on)} \rightarrow V_O \approx V_i - V_{BE(on)}$

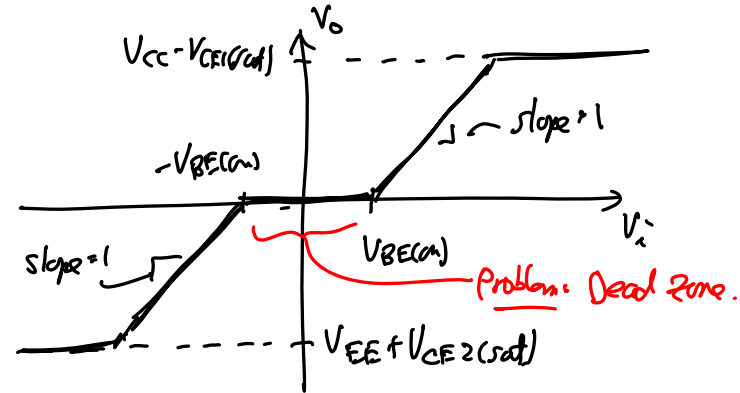$V_{Omax} = V_{CC} - V_{CE1(sat)}, V_{Omin} = V_{EE} + V_{CE2(sat)}$




Problem: Dead Zone.

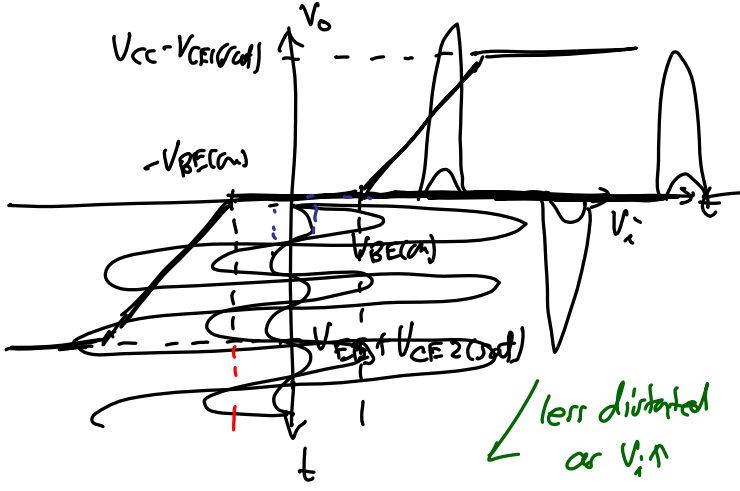

less distorted as $V_i \uparrow$

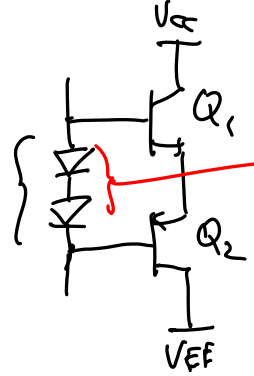To remove distortion due to the dead zone \rightarrow compromise: **Class AB**



Thus keep Q_1 & Q_2 on, but w/ much less DC power consumption than Class A

Stability & Compensation

Used to set BW.

Why is C_c needed?

causes instability!

Stability & Compensation in Op Amps


In general, op amps are used in neg. FB loops.

Reasons:

- Feedback sets the biasing → no large coupling or bypass caps needed.
- FB increases BW.
- FB increases linearity or input range. (eg., emitter degeneration is a type of FB)
- Gain determined by external FB components → more accurate than op amp gain.
- FB sets R_i and R_o .
- FB can improve temperature stability.

→ Problem: any FB loop can become unstable under certain conditions
 ↳ need to compensate the instabilities

Ex. Non-Inverting Amplifier

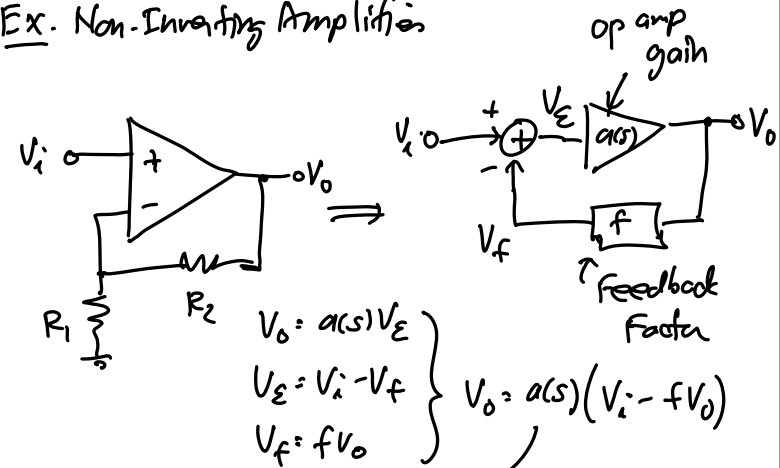

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$

Closed Loop Voltage Gain

Loop Transmission

$T(s) = a(s)f$

$T_0 = T(0)$

Instability occurs when $A(s) \rightarrow \infty$.

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1}$$

will also go unstable when denominator = (-)

In General:

If $|a(s)f| \geq 1$ when $\angle a(s)f = -180^\circ \Rightarrow$ Unstable!

↑

This is just a simplified form of
the Nyquist Criterion.