

Lecture 19: Compensation

• Announcements:

- ↳ Lab#2 due this week (and Monday next week for those in the Monday section: use the 140 box in the Cory Hall lounge)
- ↳ Midterm Exam Thursday, 3/22
- ↳ Lab#3 will be online very soon

• Lecture Topics:

- ↳ Stability (continued)
- ↳ Compensation
 - Narrowbanding
 - Pole-Splitting

• Went through Lab#3

• Last Time:

Stability & Compensation in Op Amps

causes instability!


In general, op amps are used in neg FB loops.

Reasons:

- ① Feedback sets the biasing → no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity or input range.
(eg., emitter degeneration is a type of FB)
- ④ Gain determined by external FB components → more accurate than op amp gain.
- ⑤ FB sets R_i and R_o .
- ⑥ FB can improve temperature stability.

⇒ Problem: any FB loop can become unstable under certain conditions
↳ need to compensate the instabilities

Ex. Non-Inverting Amplifier

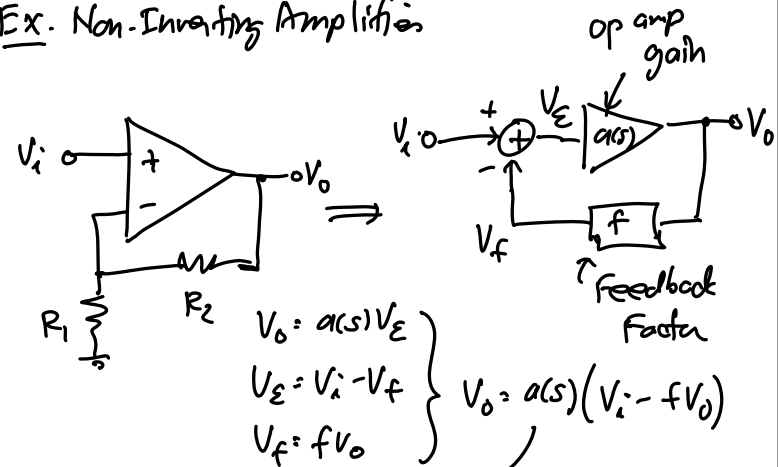

$$V_o = a(s)V_E$$

$$V_E = V_i - V_f$$

$$V_f = fV_o$$

$$V_o = a(s)(V_i - fV_o)$$

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f}$$

Labels: Closed Loop Voltage Gain, Loop Transmission, $T(s) = a(s)f$, $T_0 = T(0)$

Instability occurs when $A(s) \rightarrow \infty$.

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} \rightarrow \infty$$

will also go unstable when denominator = (-)

In General:

If $|a(s)f| \geq 1$ when $\angle a(s)f = -180^\circ \Rightarrow$ unstable

This is just a simplified form of the Nyquist Criterion.

Stability of FB Clf. Using a Single Pole Op Amp

For a single pole op amp: $a(s) = \frac{a_0}{1 - \frac{s}{p_1}}$ op amp transfer function

Thus: closed loop Xfer fun

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0 f} \frac{1}{1 - \frac{s}{p_1(1 + a_0 f)}}$$



$A_0 =$ closed loop dc gain $\rightarrow (1 + a_0 f) \approx a_0 f \times$ smaller than a_0

$$\frac{a_0}{1 + a_0 f} \approx \frac{1}{f}$$

$T_0 = a_0 f =$ loop gain (defined at dc)

$T(s) = a(s)f =$ loop transmission (defined for general freqs.)

Bode Plot: \rightarrow use to determine $\angle a(s)f$
when $|a(s)f| = 1 \rightarrow$ then determine stability

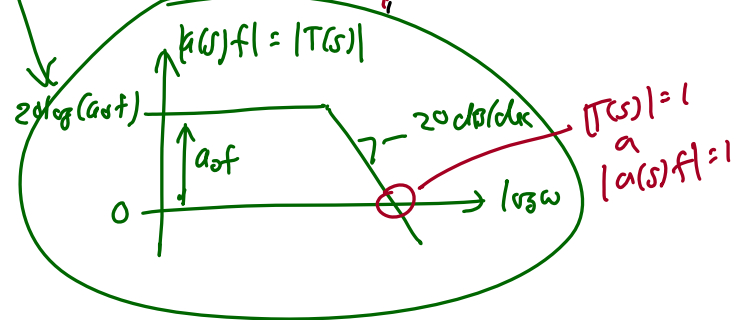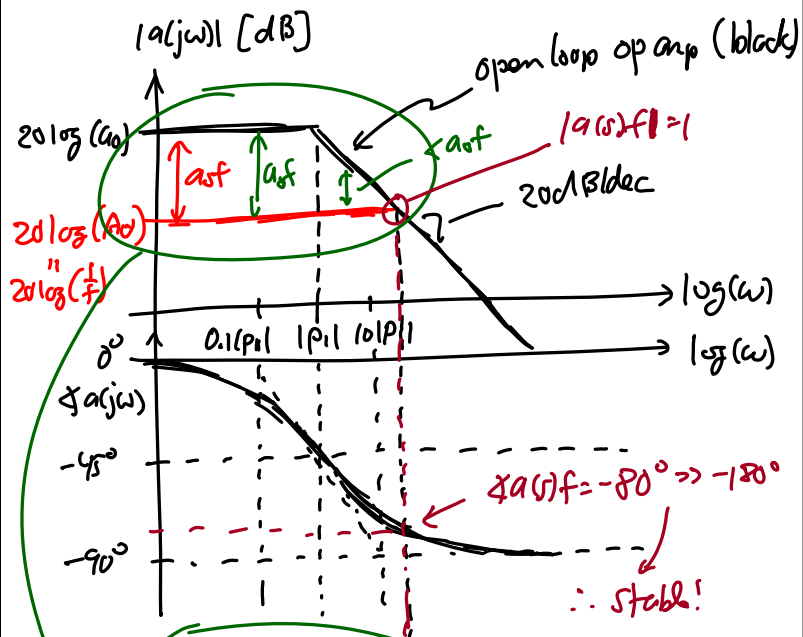

Remarks:

① For the case of a single-pole op amp, FB can never reach $\angle a(s)f = -180^\circ$ (90° is the limit)


② Thus, an op amp FB ckt. w/ $f = \text{const.}$ and using a single-pole op amp is always stable!

↓
But add a few non-dominant poles \rightarrow then instability is possible!

↓
since now, $\angle a(s)f$ can reach -180° !

↓
Can best visualize this via a Bode plot.

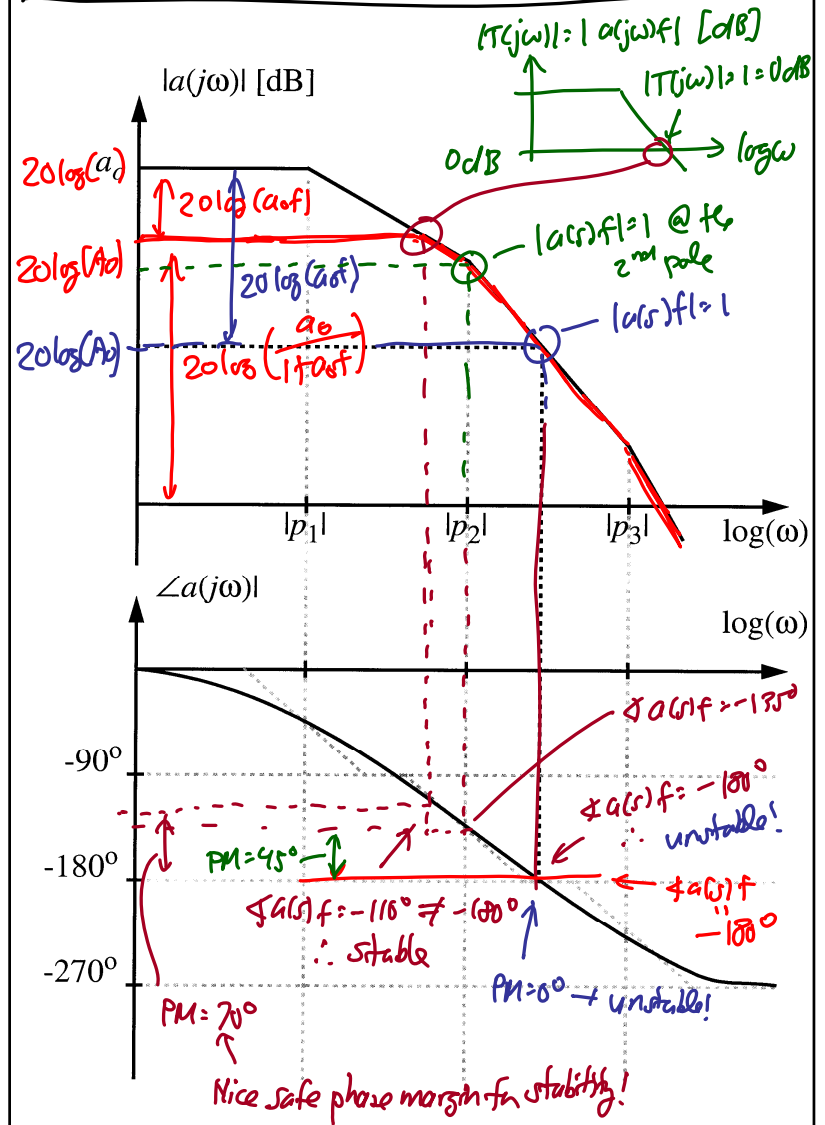Stability of a FB Ckt. Using a Multi-Pole Amp



For the more general case where $a(s)$ has multiple poles:

$\Rightarrow A(s)$ has the same additional poles

\Rightarrow i.e., @ freq. $> |p_1|$ (1st asf), the $A(s)$ curve just follows the $a(s)$ curve

$$A(s) \approx \frac{A_0}{\left(1 - \frac{s}{|p_1|(1+asf)}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)}$$

makes sense, because @ freq. $> |p_1|(1+asf)$, the loop transmission $|a(s)f| < 1 \rightarrow \therefore$ there really isn't much FB anymore

Definition:

$$\text{Phase Margin} = 180^\circ + (\angle a(j\omega)f) \text{ @ freq. where } |a(j\omega)f| = 1$$

