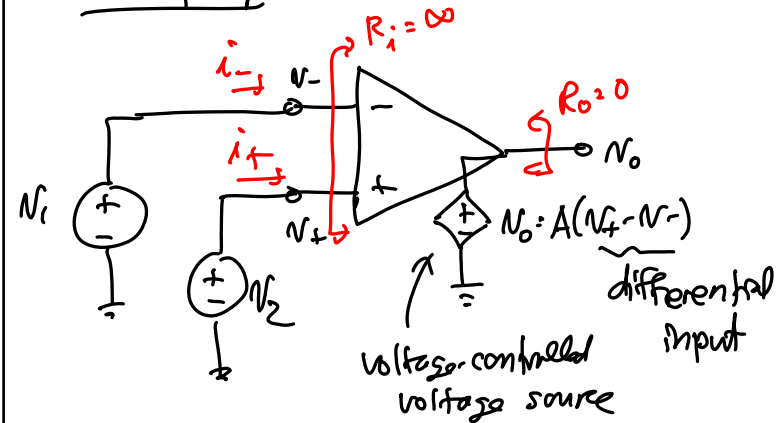


Lecture 1: Admin & Overview

- Announcements:
- **EE 140: Analog Integrated Circuits**
- **Instructor:** Prof. Clark T.-C. Nguyen
- **Screencast:** wireless mic
 - ↳ Can view lectures at either <http://itunes.berkeley.edu/> or <http://www.youtube.com/ucberkeley>
- For the course website, just google ee140
 - ↳ The website should be up and running in a couple of days
- **Office Hour Changes?:** None requested
- **Discussion sections start next week**
 - ↳ What about the TBD room for Section 102?
 - ↳ Th 2-5, specifically 4-5 (237 Cory might be open) - we will try for this; I will announce the results in the next lecture
-
- **Lecture Topics:**
 - ↳ Review
 - Ideal Op Amps
 - Non-Ideal Op Amps
 - ↳ Op Amp Examples
-
- **Go though**
 - ↳ Course information sheet
 - ↳ Syllabus
 - ↳ Grading Information and Policy
- Hand out class account sheets in class


Review of Op Amps

Ideal Op Amp:



Properties of Ideal Op Amps:

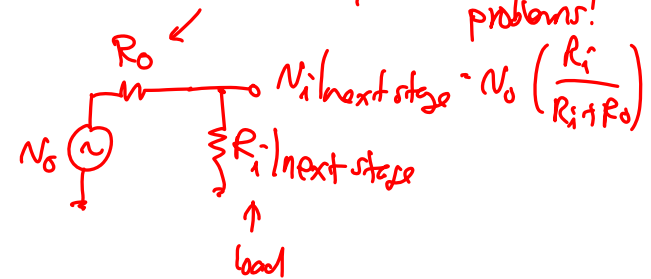- ① $R_i = \infty \rightarrow i_- = i_+ = 0$ ← if we have neg. FB!
- ② Gain, $A = \infty \rightarrow V_+ = V_-$ ↓ finite!
- ③ Infinite BW (a freq. response)
- ④ $R_o = 0 \rightarrow$ Can drive any load w/ no problems!



Inverting Amplifier

Steps:

- Verify that we have neg. FB ✓ *→ can use ideal op amp properties!*

Pos. FB Example

Aside

This continues to go ↑!

par. FB. $N_0 \rightarrow \infty$

Cannot use ideal op amp properties!

can no longer say $\frac{N_0}{A} = 0$

- $N_0 = \text{finite} \rightarrow N_+ = N_-$
get virtual ground
- $i_i = \frac{N_i}{R_1} = \frac{(N_i - 0)}{R_1} = i_2$
 $i_- = 0$
- $N_0 = -i_2 R_2 = -\left(\frac{N_i}{R_1}\right) R_2$

$$\frac{N_0}{N_i} = -\frac{R_2}{R_1}$$

- **Non-Ideal Op Amps:**
- **Actual op amps, of course, are not ideal; rather, they ...**
 - ↳ **Have finite gain, A_o**
 - ↳ **Have finite bandwidth, BW**
 - ↳ **Have finite input resistance, R_i**
 - ↳ **Have finite input capacitance, C_i**
 - ↳ **Have finite output resistance, R_o**
 - ↳ **Generates noise**
 - ↳ **Have input bias currents (because R_i is not infinite)**
 - ↳ **Have input offset currents and voltages**
 - ↳ **Have finite slew rate**
 - ↳ **Have finite output swing**
- **All of the above can be temperature dependent!**
- **A major objective of this class is understand what gives rise to the above non-idealities and to teach design strategies to get around them**

- **Then look at op amp usage examples using prepared pages**