

EE 140

BJT Modeling

CTN


1

Modeling the Bipolar Junction Transistor (BJT)

⇒ physically, BJTs are just back-to-back pn junctions

npn bipolar Xistor

ppp bipolar Xistor

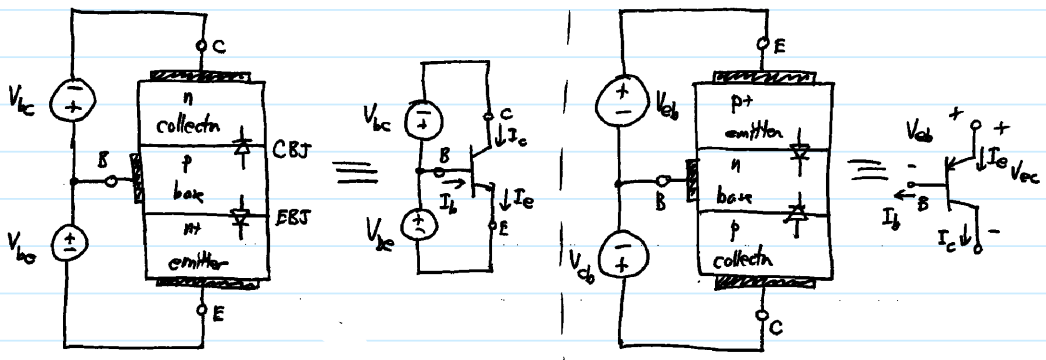


Regions of Bipolar Xistor Operation

EBJ	CBJ	Mode
R	R	Cut-off (both diodes off)
F	R	Forward Active (widely used in analog amplifier ccts)
R	F	Reverse Active
F	F	Saturation

Key: R = reverse-biased  
F = forward-biased

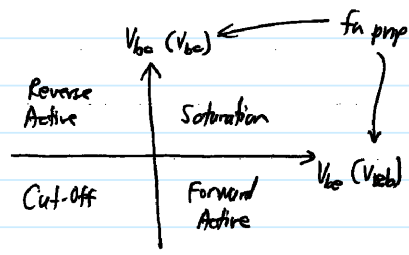⇒ can also think of this in a convenient graphical sense:  
→ for npn (pnp):




① Cut-off Region - (npn transistor)

⇒ both diodes reverse-biased

⇒ no current flows:

$I_b = 0, I_c = 0, I_e = 0$

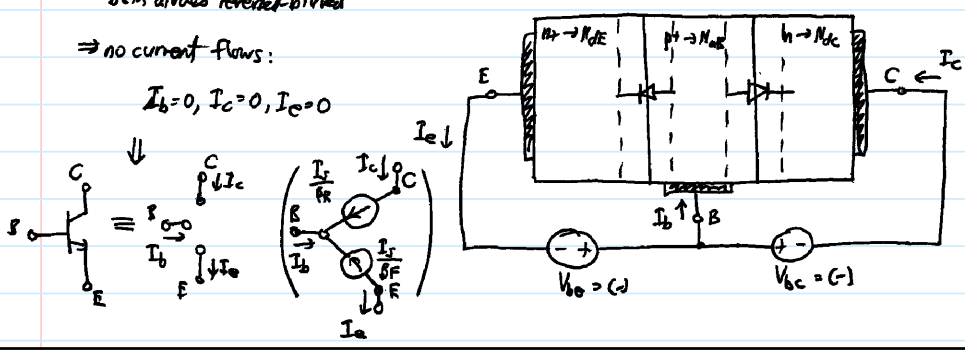

EE 140



BJT Forward-Active

CTN

2

② Forward-Active Region - (npn transistor)

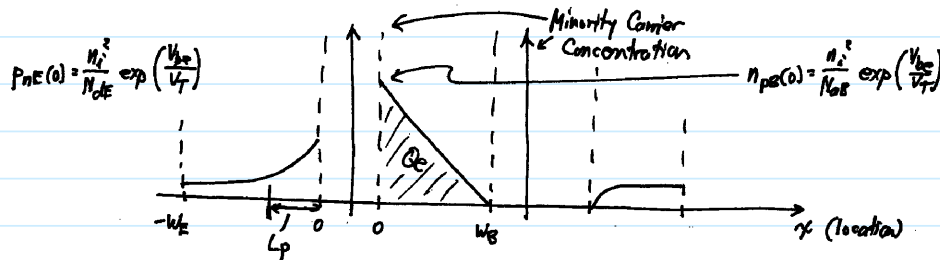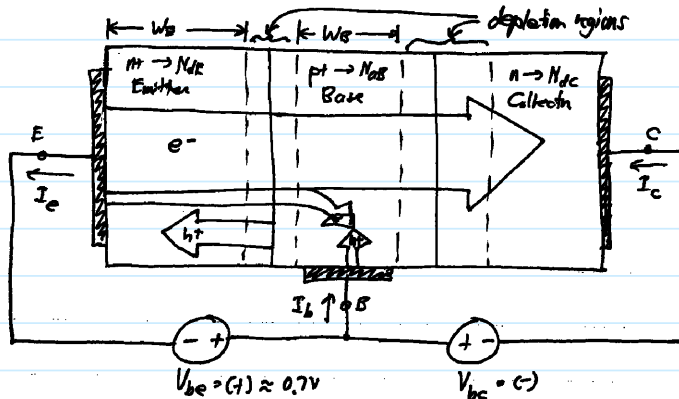⇒ BEJ Forward-Biased (i.e., diode on), BCJ Reverse-Biased (i.e., diode off)



Forward biasing of the BEJ generates three current components:

- ① e<sup>-</sup>s injected from emitter to base:  $I_{nB} = -A J_{nB}^{diff}$
  - ② h<sup>+</sup>s injected from base to emitter:  $I_{pE} = A J_{pE}^{diff}$
  - ③ recombination of e<sup>-</sup>s & h<sup>+</sup>s in base:  $I_{rB}$
- $I_C = I_{nB} = 0$   
 $I_E = I_{nB} + I_{pE} + I_{rB} = ① + ② + ③$   
 $I_B = I_{pE} + I_{rB} = ② + ③$

$$I_{nB} = -A J_{nB}^{diff} = -A q D_{nB} \frac{dn_p(x)}{dx} = -q A D_{nB} \frac{[n_{pB}(W_B) - n_{pB}(0)]}{W_B} = q A D_{nB} \frac{n_i^2}{N_B W_B} \exp\left(\frac{V_{BE}}{V_T}\right) = ① *$$

diffusion constant for e<sup>-</sup>s in B  
 slope  
 diffusion constant for h<sup>+</sup>s in E

$n_{pB}(W_B) = \frac{n_i^2}{N_B} \exp\left(\frac{V_{BC}}{V_T}\right) \approx 0$   
 $n_{pB}(0) = \frac{n_i^2}{N_B} \exp\left(\frac{V_{BE}}{V_T}\right)$

$I_C = I_{nB} \exp\left(\frac{V_{BC}}{V_T}\right)$

$$I_{pE} = A J_{pE}^{diff} = A q D_{pE} \frac{dp_n(x)}{dx} = q A D_{pE} \frac{[p_{nE}(0) - p_{nE}(-W_E)]}{W_E} = q A D_{pE} \frac{n_i^2}{N_E W_E} \exp\left(\frac{V_{BE}}{V_T}\right) = ② *$$

slope  
 $p_{nE}(0) = \frac{n_i^2}{N_E} \exp\left(\frac{V_{BE}}{V_T}\right)$   
 $p_{nE}(-W_E) \approx 0$

could also replace by diffusion length,  $L_p$  (for h<sup>+</sup> in n-type material)

EE 140

BJT Forward-Active

CTN

3

minority-carrier charge in base

$$I_{B8} = \frac{Q_{e8}}{\tau_b} = \frac{1}{\tau_b} \left[ \frac{1}{2} N_{p8}(0) W_B q A \right] = \frac{1}{2} \frac{n_i^2 W_B q A}{N_B \tau_b} \exp\left(\frac{V_{be}}{V_T}\right) = \textcircled{3} \quad *$$

minority carrier lifetime in base

Define Forward Current Gain =  $\beta_F$ :

$$\beta_F = \frac{I_c}{I_b} = \frac{\textcircled{1}}{\textcircled{3} + \textcircled{2}} = \frac{\frac{q A D_{nB} n_i^2}{N_{pB} W_B}}{\frac{1}{2} \frac{n_i^2 W_B q A}{N_{pB} \tau_b} + \frac{q A D_{nE} n_i^2}{N_{pE} W_E}} = \left[ \frac{W_B^2}{2 \tau_b D_{nB}} + \frac{D_{nE} W_B N_A}{D_{nE} W_E N_D} \right]^{-1}$$

$N_{pB}$   
 $N_{pE}$   
 $L_p$

To maximize  $\beta_F$ , want:

- ①  $W_B = \text{small}$
- ②  $N_{pE} \gg N_{pB}$  (this is why emitter is  $n^+$ )  $\rightarrow$  also leads to  $D_{pE} \ll D_{pB}$  which we also want
- ③  $\tau_b = \text{long}$  (base Si must be free of impurities/defects to prevent recombination)

More Complete Expression for  $\beta_F$ :

$$\beta_F = \underbrace{\frac{N_{pE} W_B}{D_{nE}} \cdot \frac{D_{nE}}{N_{pE} L_p}}_{\text{Injection Efficiency}} + \underbrace{\frac{1}{2} \left( \frac{W_B}{L_{nB}} \right)^2}_{\text{Volume Recombination}} + \underbrace{s \left( \frac{A_E}{A_F} \right) \left( \frac{W_B}{D_{nB}} \right)}_{\text{Surface Recombination}} + \underbrace{\frac{W_E N_{pB} W_B}{2 D_{nE} \tau_{nE}} e^{-\frac{V_{be}}{2V_T}}}_{\text{Recombination in the BE Depletion Region} \leftarrow \text{Significant @ low current levels}}$$

where:  $s$  = Surface recombination velocity

$D_i$  = Diffusion constant

$n_i$  = intrinsic carrier concentration

$N_i$  = carrier concentration


$A_E$  = total emitter area

$A_S$  = sidewall emitter area

$\tau$  = minority carrier lifetime

$L_i$  = diffusion length ( $L_i = \sqrt{D_i \tau}$ )

$W_B$  = active base width

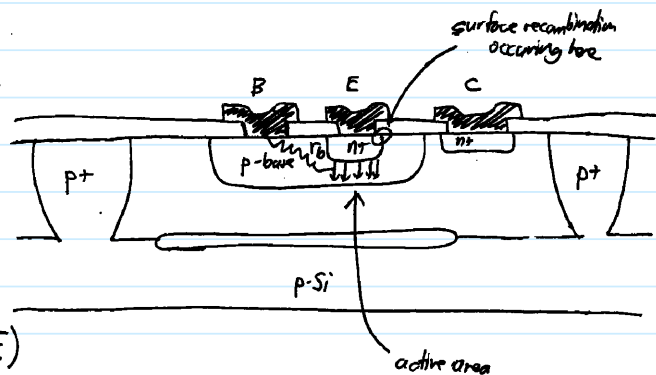


EE 140

Forward-Active LS Models

CTN

4

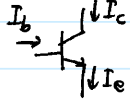So  $\beta$  relates  $I_b$  &  $I_c$ . To relate  $I_c$  &  $I_e$ , use KCL:




$$I_e = I_c + I_b = I_c + \frac{I_c}{\beta} = (1 + \frac{1}{\beta}) I_c$$


$$\Rightarrow I_c = (\frac{1}{1 + \frac{1}{\beta}}) I_e = (\frac{\beta}{\beta + 1}) I_e = \alpha I_e, \text{ where } \alpha = \frac{\beta}{\beta + 1} \Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$

Equivalent Large Signal Ckt. Models for Forward-Active BJTs

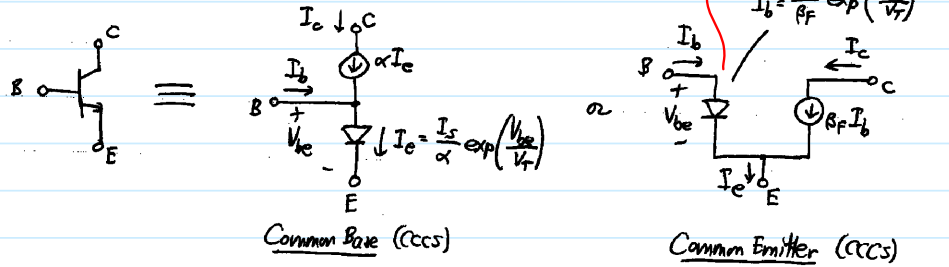
There are several of them. The most useful ones are:



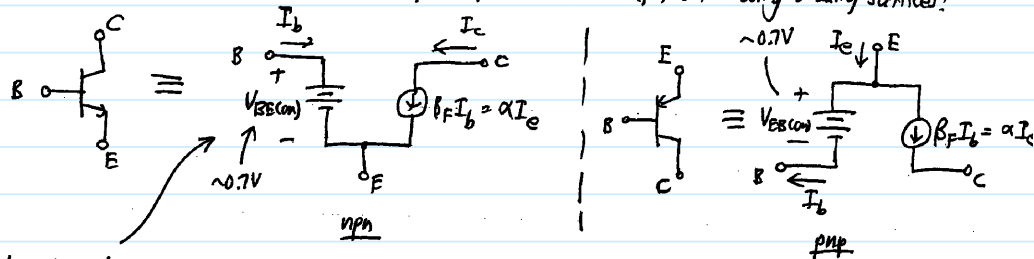But usually one doesn't have to use those complicated models. Rather, the following usually suffices:



Just as in a diode:

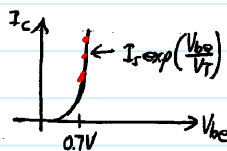

You should already be used to using approximate models like this  
 $\Rightarrow$  the more complicated models are a waste of time in comparison

③ Reverse-Active Region -

$\Rightarrow$  very similar to forward-active region except now: BEJ reverse-biased  
 BCJ forward-biased

$\Rightarrow$  one important difference:  $\beta_R \propto \frac{N_{dc} L_{nc} D_{nc}}{N_{cb} W_B D_{pc}}$   $\rightarrow$  since collector is n-  $N_{dc} \ll N_{cb} \rightarrow D_{nc} \ll D_{pc}$   
 $\therefore \beta_R$  is much smaller than  $\beta_F$   
 $\Rightarrow$  poor device performance

EE 140

BJT Saturation LS Models

CTN


5

④ Saturation Region-

BEJ forward-biased  $\rightarrow V_{BE(sat)} \sim 0.8V$  (higher than 0.7V in saturation)

BCJ forward-biased  $\rightarrow V_{BC(sat)} \sim 0.6V$

Result:

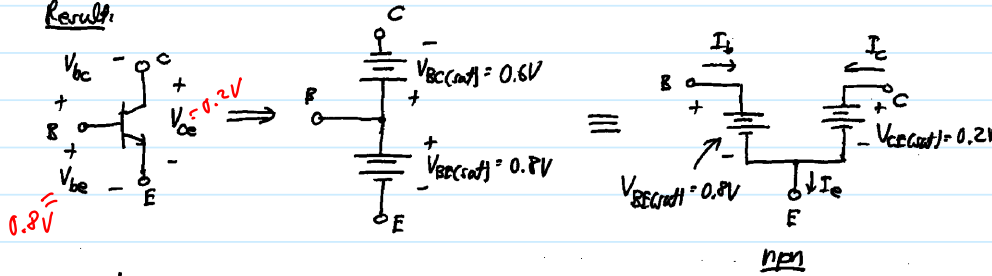

$\Rightarrow$  currents now determined by the attached elements & KCL:



$$I_e = I_b + I_c ; \text{ no longer have } I_b = \frac{I_c}{\beta} \text{ or } I_c = \alpha I_e$$

These no longer apply when BJT is in saturation.


When determining DC operating point:

- Pass (1) Assume forward-active  $\rightarrow$  check for cut-off (enough  $V_{be}$ ?)
- (2) Determine  $V_{ce}$ .
- (3) If  $V_{ce} > V_{ce(sat)} = 0.2V$ , then ok (i.e., it's forward-active) ... otherwise, must do the analysis over assuming saturation.

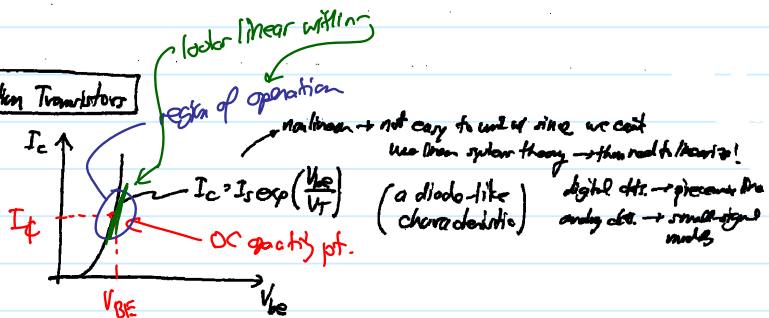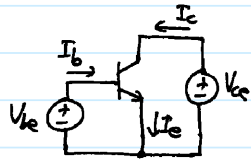IV Characteristics of Bipolar Junction Transistors



$\Rightarrow$  really most interested in  $I_c = f(I_b, V_{ce})$ :

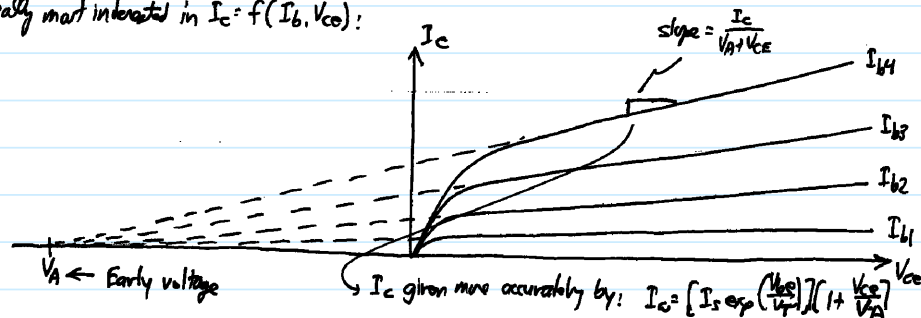


EE 140

BJT Early Effect

CTN

6

What is happening physically?

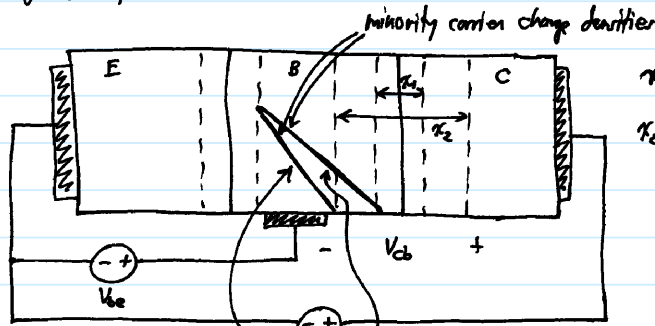

$x_1 \triangleq$  depl. region width for  $V_{ce} = V_{ce1}$

$x_2 \triangleq$  depl. region width for  $V_{ce} = V_{ce2} > V_{ce1}$

① Case:  $V_{ce} = V_{ce1} \rightarrow x_1 \rightarrow I_{c1} \propto$  slope of this curve line

② Now, increase  $V_{ce1} \rightarrow V_{ce2} \rightarrow V_{cb} \uparrow \rightarrow x_1 \uparrow$  to  $x_2 \rightarrow I_{c2} \propto$  slope of this line

$\therefore I_{c2} > I_{c1}$


Thus,  $V_{ce} \uparrow \rightarrow I_c \uparrow$  due to  $x_{depl.} \uparrow$

Result:  $I_c = f(I_b, V_{ce})$  in forward-active!

$$I_c = \left[ I_s \exp\left(\frac{V_{be}}{V_T}\right) \right] \left[ 1 + \frac{V_{ce}}{V_A} \right]$$

← This, too, is a more accurate  $I_c$  equation.

Small-Signal Models for Forward-Active Bipolar Xsistors

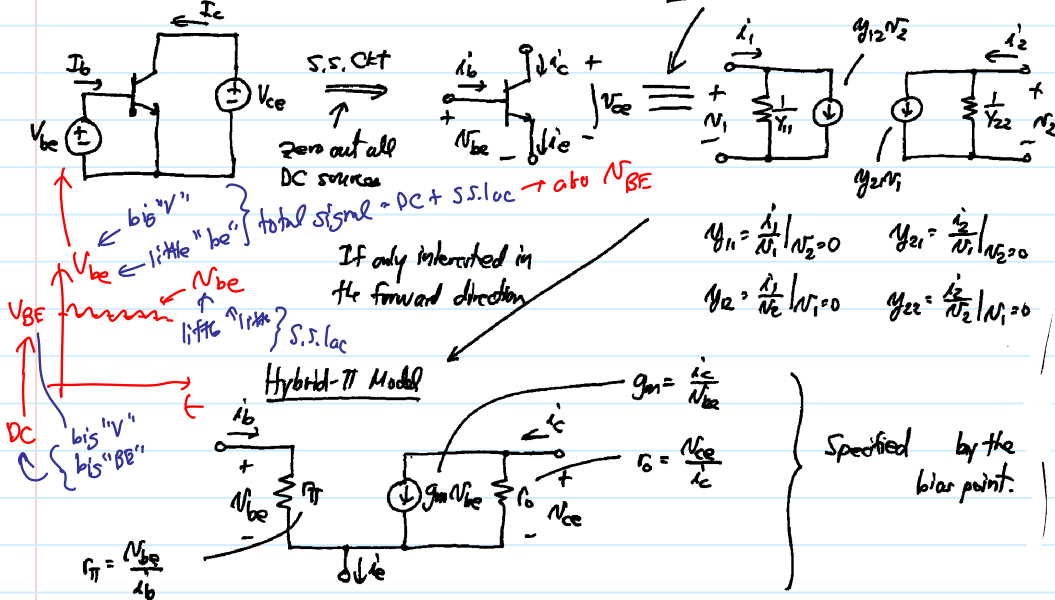

EE 140


BJT Small-Signal Model

CTN

7


Determine the S.S. elements

$$g_m = \frac{i_c}{v_{be}} = \frac{\partial I_c}{\partial v_{be}} \Big|_{Q.pt.} = \frac{\partial}{\partial v_{be}} \left[ I_s \exp\left(\frac{v_{be}}{V_T}\right) \right] \Big|_{v_{be} = V_{BE}} = \frac{I_c}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow \boxed{g_m = \frac{I_c}{V_T}}$$

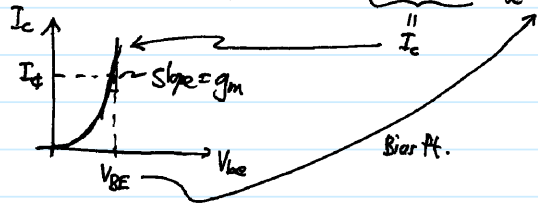

Note: function of the DC operating pt.

$$r_{\pi} = \frac{V_{be}}{i_b}$$

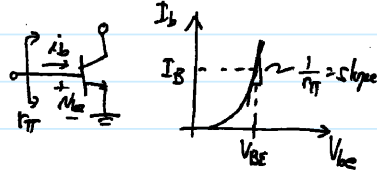


$$r_{\pi} = \frac{V_{be}}{i_b} = \frac{V_{be}}{\frac{I_c}{\beta}} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_c}{V_T}} = \frac{\beta V_T}{I_c}$$

$$\therefore \boxed{r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}}$$

Again, function of the DC operating pt.

$$r_o = \frac{V_{ce}}{i_c}$$

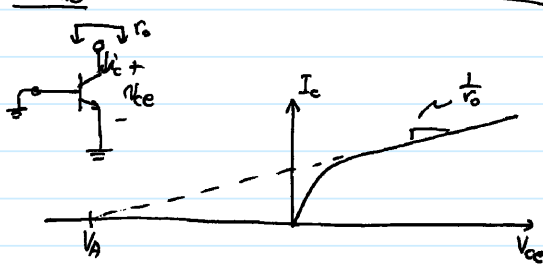

$$r_o = \frac{\partial v_{ce}}{\partial i_c} \Big|_{Q.pt.} = \left[ \frac{\partial I_c}{\partial v_{ce}} \Big|_{Q.pt.} \right]^{-1} = \left[ \frac{\partial}{\partial v_{ce}} \left( I_s \exp\left(\frac{v_{be}}{V_T}\right) \left[ 1 + \frac{v_{ce}}{V_A} \right] \right) \Big|_{v_{be} = V_{BE}} \right]^{-1}$$

$$= \left[ \frac{I_s \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A} \right]^{-1} = \left[ \frac{I_c}{V_A + V_{CE}} \right]^{-1} = \frac{V_A + V_{CE}}{I_c}$$

$$\therefore \boxed{r_o = \frac{V_A + V_{CE}}{I_c} \approx \frac{V_A}{I_c} \quad [V_A \gg V_{CE}]}$$

... and thus, we have the hybrid- $\pi$  model:



SPICE: BJT

$$\boxed{\begin{aligned} r_{\pi} &= \frac{\beta}{g_m} = \frac{V_T}{I_B} \\ g_m &= \frac{I_c}{V_T} \\ r_o &= \frac{V_A + V_{CE}}{I_c} \approx \frac{I_c}{V_A} \end{aligned}}$$

SPICE: VAF

Remarks:

- ①  $g_m$  is independent of device specifics; depends only on temperature (thru  $V_T$ ) and biasing  $I_c$
- ② small-signal model valid for  $v_{be} \ll V_T \leftarrow \approx 26\text{mV} @ 300\text{K}$

quite different from MOS, as we'll see