

Lecture 20: Narrowbanding vs. Pole-Splitting

Announcements:

- ↳ Welcome back (from Spring Break)
- ↳ Lab#3 in progress
- ↳ HW#9 online

Lecture Topics:

- ↳ Review Last Lecture
- ↳ Review of Pole/Zero Plots
- ↳ Compensation
 - Narrowbanding
 - Pole-Splitting
- ↳ Hand back graded midterm & discuss grading

Last Time: (it's been a long while, so we'll quickly review the whole last lecture)

Stability & Compensation in Op Amps

causes instability!


In general, op amps are used in neg FB loops.

Reasons:

- ① Feedback sets the biasing → no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity or input range.
(eg., emitter degeneration is a type of FB)
- ④ Gain determined by external FB components → more accurate than op amp gain.
- ⑤ FB sets R_i and R_o .
- ⑥ FB can improve temperature stability.

→ Problem: any FB loop can become unstable under certain conditions
 ↳ need to compensate the instabilities

Ex. Non-Inverting Amplifier

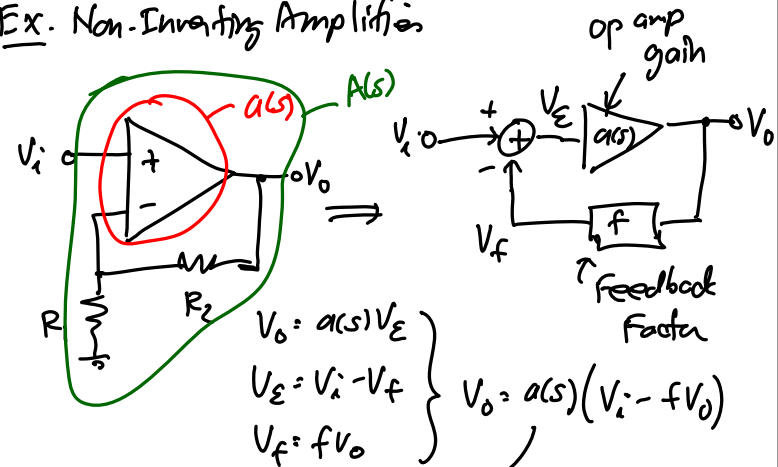

$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$

Closed Loop Voltage Gain Loop Transmission $T(s) = a(s)f$ $T_0 = T(0)$

Instability occurs when $A(s) \rightarrow \infty$.

$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} \rightarrow \infty$

$a(s)f = -1$ will also go unstable when denominator = (-)

In General:

If $|a(s)f| \geq 1$ when $\angle a(s)f = -180^\circ \Rightarrow$ unstable

This is just a simplified form of the Nyquist Criterion.

Stability of FB Claf. Using a Single Pole Op Amp

For a single pole op amp: $a(s) = \frac{a_0}{1 - \frac{s}{p_1}}$ op amp transfer function

Thus: closed loop Xfer fun



$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0f} \frac{1}{1 - \frac{s}{p_1(1+a_0f)}}$$

feedback fact \uparrow \uparrow freq. shaping term
 $A_0 =$ closed loop dc gain $\rightarrow (1 + a_0f) \approx a_0f \times$ smaller than a_0

dc $\frac{a_0}{1+a_0f} \approx \frac{1}{f}$
 $T_0 = a_0f =$ loop gain (defined at dc)
 $T(s) = a(s)f =$ loop transmission (defined for several freqs.)

Bode Plot: \rightarrow use to determine $\angle a(s)f$

when $|a(s)f| = 1 \rightarrow$ then determine stability

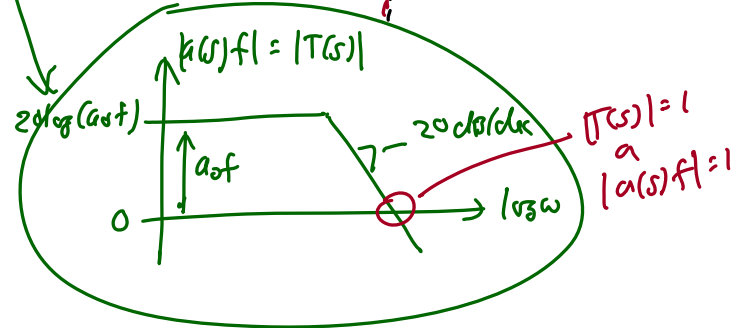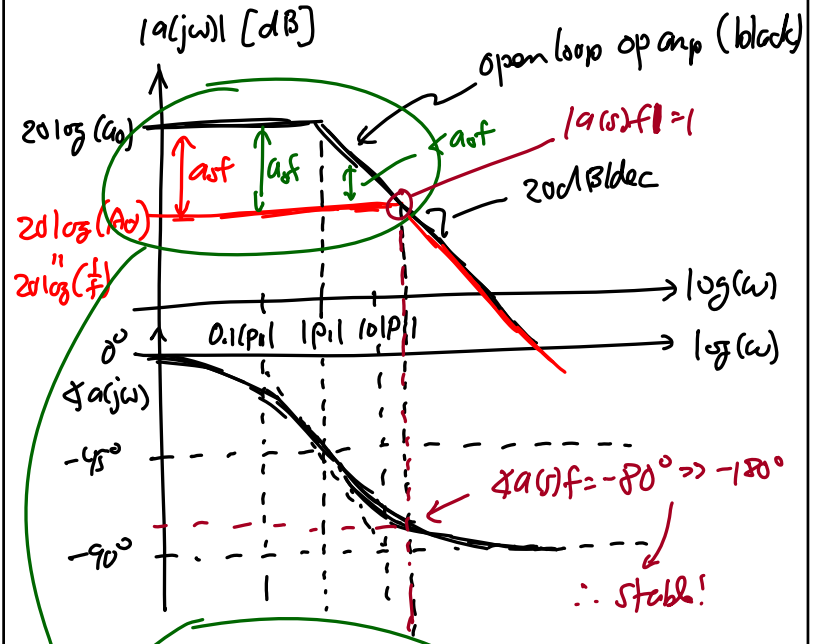

Remarks:

① For the case of a single-pole op amp, FB can never reach $\angle a(s)f = -180^\circ$ (90° is the limit)


② Thus, an op amp FB ckt. w/ $f = \text{const.}$ and using a single-pole op amp is always stable!

↓
 But add a few non-dominant poles → then instability is possible!

↓
 since now, $\angle a(s)f$ can reach -180° !

↓
 Can best visualize this via a Bode plot.

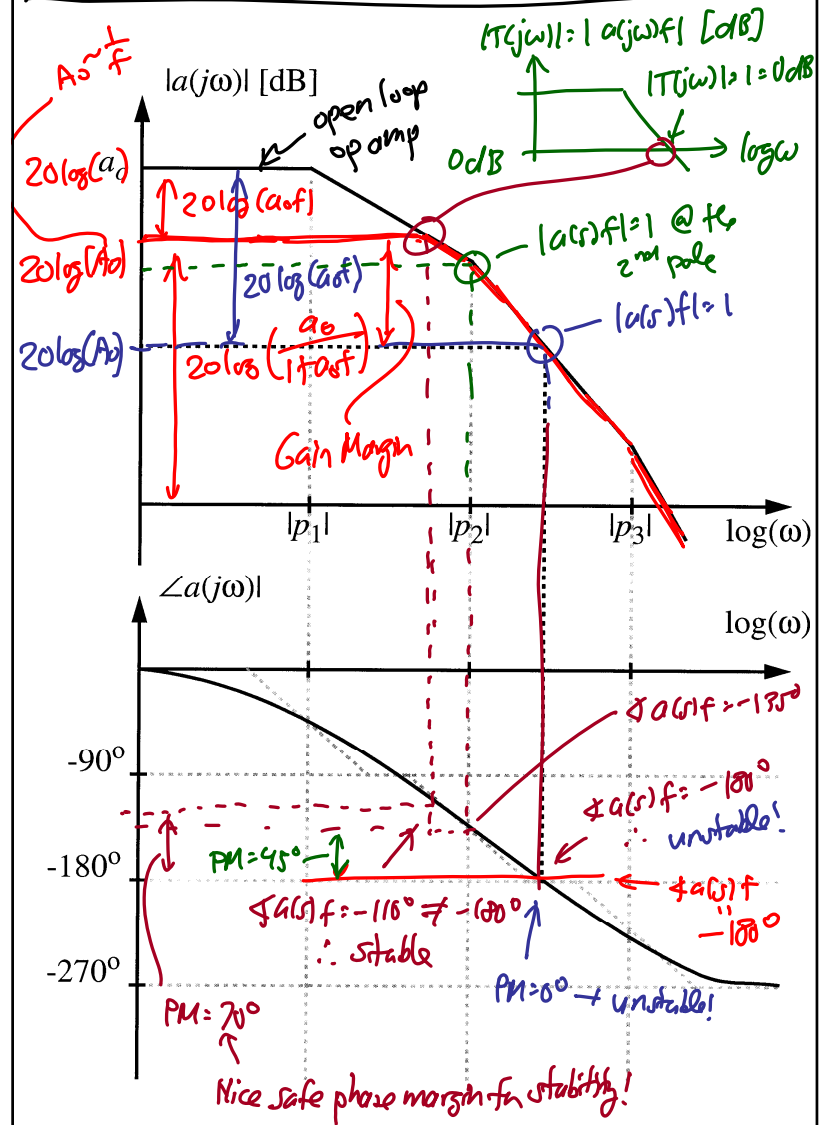Stability of a FB Ckt. Using a Multi-Pole Amp



For the more general case where $a(s)$ has multiple poles:

$\Rightarrow A(s)$ has the same additional poles

\Rightarrow i.e., @ freq. $> |p_1|$ (if asf), the $A(s)$ curve just follows the $a(s)$ curve

$$A(s) \approx \frac{A_0}{\left(1 - \frac{s}{|p_1|(1+asf)}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)}$$

makes sense, because @ freq. $> |p_1|$ (if asf), the loop transmission $|a(s)f| < 1 \rightarrow \therefore$ there really isn't much FB anymore

Definition:

$$\text{Phase Margin} = 180^\circ + (\angle a(j\omega)f) \text{ @ freq. where } |a(j\omega)f| = 1$$


\Rightarrow Phase Margin must be $> 0^\circ$ for stability

For stability: Phase Margin $> 0^\circ$

\Rightarrow But for safety, design for

Phase Margin $\geq 45^\circ$

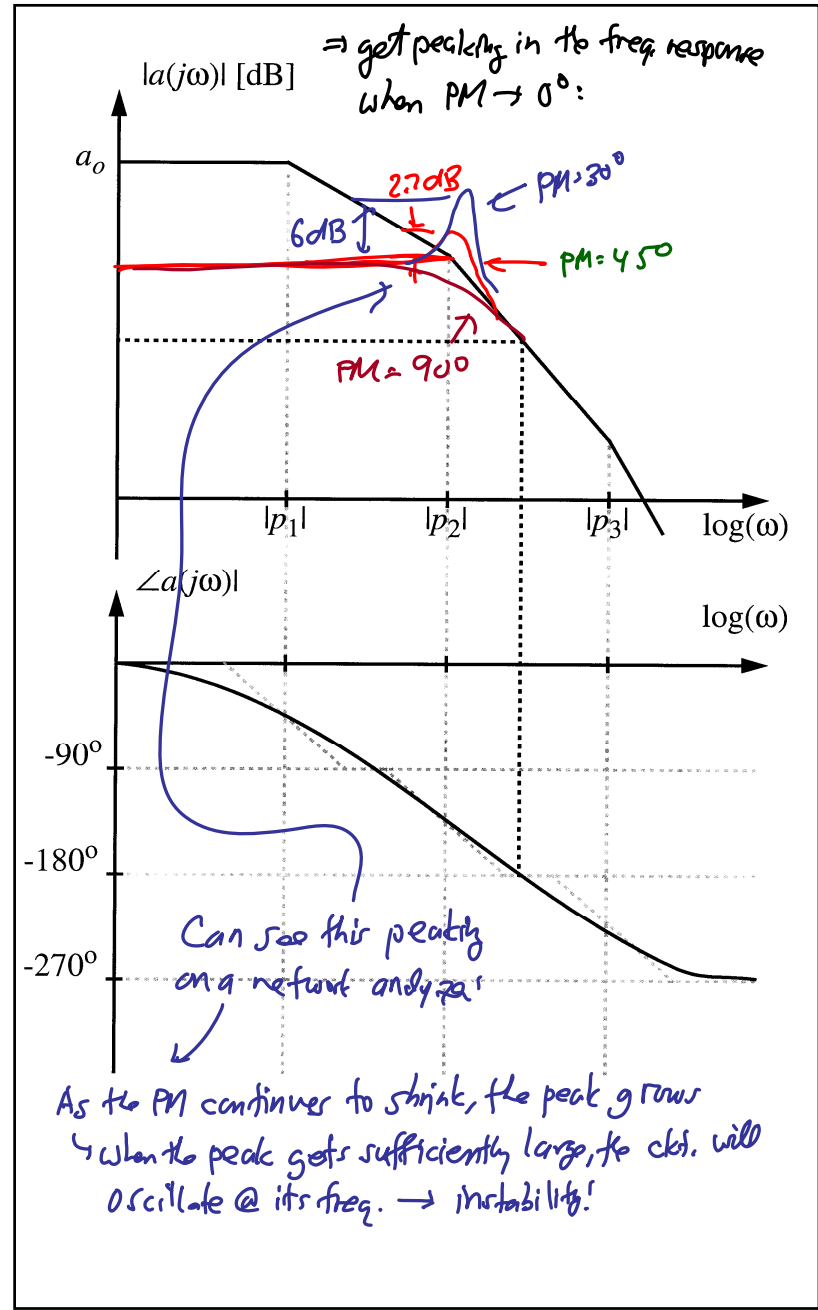offentimes, use PM $\geq 60^\circ$. (Design Criterion for Practical Design)



Definition.


Gain Margin = $|T(j\omega)|$ in dB @ freq. ω_{180}

$\angle T(j\omega) = -180^\circ$

For stability: Gain Margin < 0 dB

Comparison of Op Amps

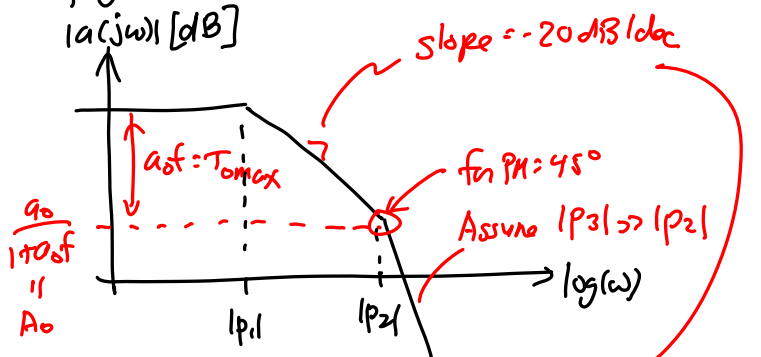To compensate, need the distance between p_1 & p_2 to be large enough to encompass the largest desired loop gain!



$20(\log|p_2| - \log|p_1|) = 20 \log(T_{\text{omax}})$

$\frac{|p_2|}{|p_1|} = T_{\text{omax}} \rightarrow |p_2| = |p_1| T_{\text{omax}}$
 Largest expected loop gain

For stability w/ $PM = 45^\circ$

Two Ways to Compensate:

- ① Narrowbanding
- ② Pole-Splitting

Narrowbanding

dominant = "0"

→ introduce a pole p_0 so that is sufficient separation between p_0 & p_1

which becomes the "new p_2 "

