


Lecture 21: Choosing Cc

Lab#3
 models

- Announcements:
 - ↳ Lab#3: Note that models have been online
- Lecture Topics:
 - ↳ Review of Pole/Zero Plots
 - ↳ Compensation: Narrowbanding & Pole-Splitting
 - ↳ Choosing Cc

• Last Time: Comparison of Op Amps

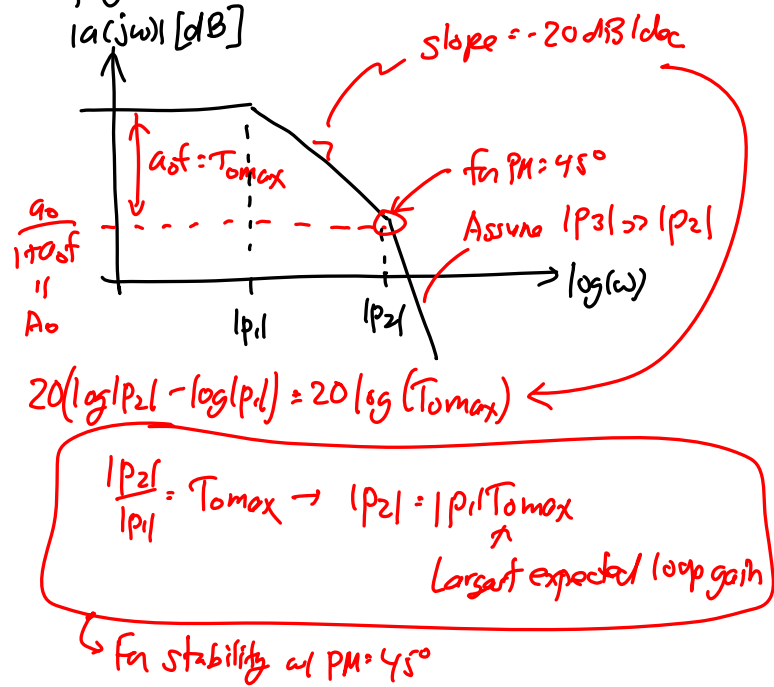To compensate, need the distance between p_1 & p_2 to be large enough to encompass the largest desired loop gain!




Two Ways to Compensate:

- ① Narrowbanding
- ② Pole-Splitting

Narrowbanding

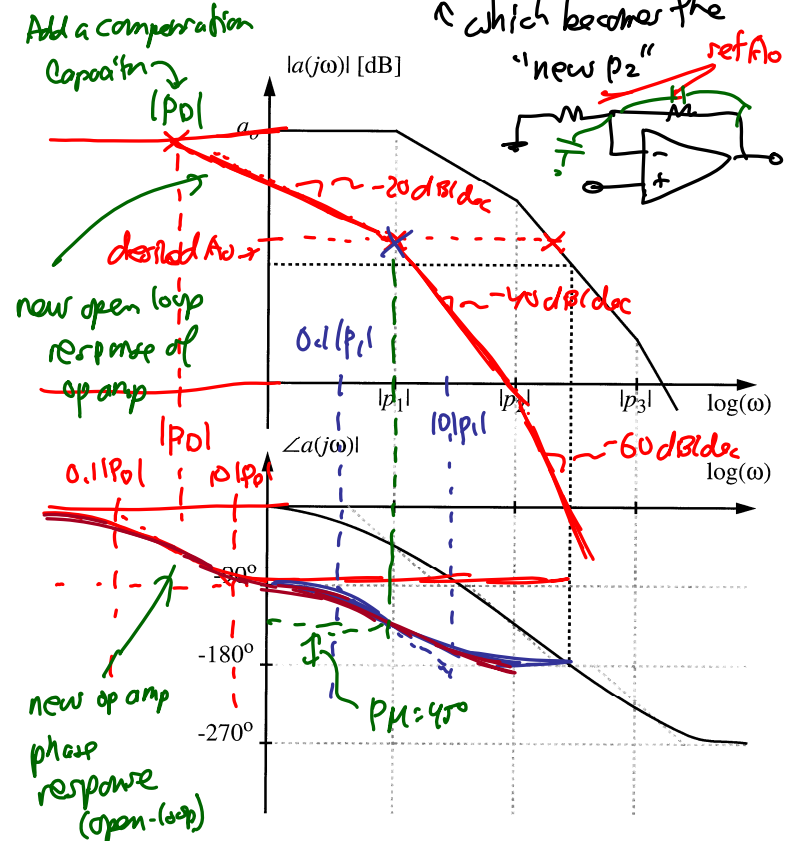dominant = "0"
 ↳ introduce a pole p_0 so that is sufficient separation between p_0 & p_1



Remarks on Narrowbanding

- ① Assumptions: p_1, p_2, p_3 don't move when p_D is introduced (often not true, but that's normal isn't that big)
- ② Summarize: choose p_D such that $|T(j\omega)| = 0 \text{ dB} = 1$ @ p_1 (which becomes the "new 2nd most dominant pole")
 ↳ this gives $PM = 45^\circ$ (for $|p_2| \gg |p_1|$ & $|p_3| \gg |p_2|$)
- ③ Why do this? Wouldn't it be much better to just move the original $|p_1|$ (i.e., pole-split)

↳ Do it when you have no other choice, e.g., when you have a packaged op amp & have access only to a few terminals, not the optimum compensation node.

④
$$|p_D| = \frac{|p_1|}{T_{\text{omax}}}$$
 ← maximum expected/needed loop gain

Problem:


- ① often, $|p_D| \ll |p_1| \therefore f_{-3\text{dB}}$ BW of the op amp will be very small
- ② $\omega_{\text{closed loop}} = |p_1|$ which isn't that large

Solution: Pole-Splitting

↳ move $|p_1|$ down & either keep $|p_2|$ still
 ↳ after doing this: or move $|p_2|$ up simultaneously

① $\omega_{-3\text{dB}} = |p_1'|$ ② $\omega_{\text{closed loop}} = |p_2'|$

Pole-Splitting

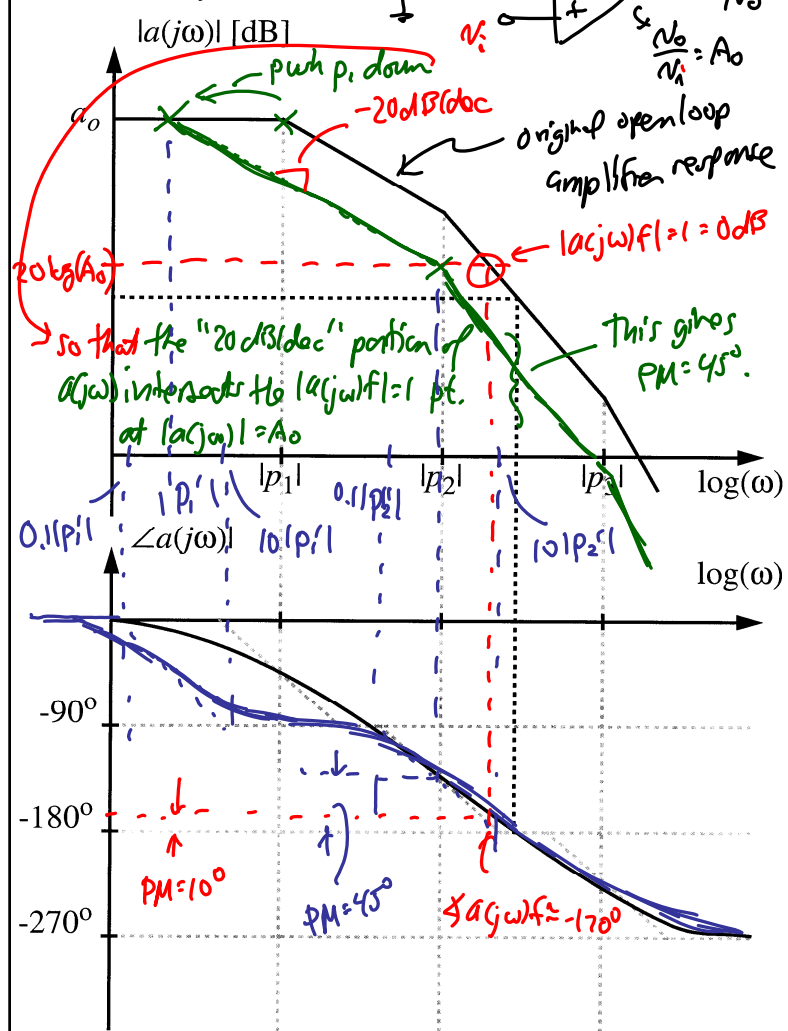


Assumption (for above): p_2 doesn't move


Remarks for Pole-Splitting

① For pole-splitting, $|p_{1,1}| = \frac{|p_{21}|}{T_{0max}}$

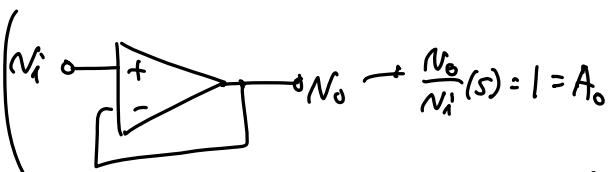Unity-Gain Stable Op Amp → e.g., 741 op amp



monolithically compensated w/ an internal C_c to be stable when $A_o = 1$
 $|A(j\omega)|$ [dB]

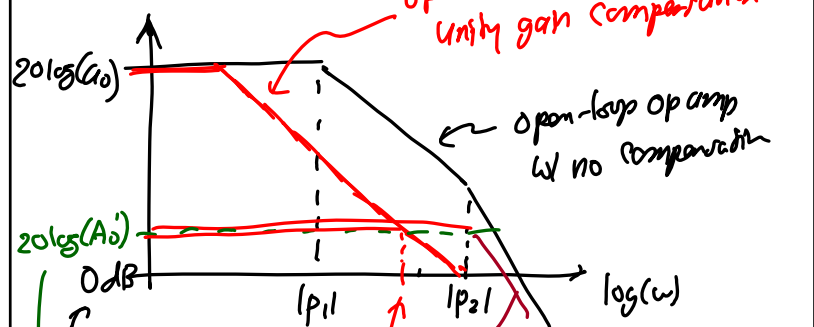

open-loop op amp w/ unity gain compensation

open-loop op amp w/ no compensation

Wide for unity gain compensated op amp




What if this was the lowest gain you needed > 1 ?

→ Could have done this! → compensate for the A_o you need → get higher BW! (vs. unity gain comp.)

Choosing C_c (assume no RHP zeroes $\{ |p_{31}| \gg |p_{21}| \}$)

→ assume $\frac{1}{sC_c} \ll$ surrounding impedance @ high freq.

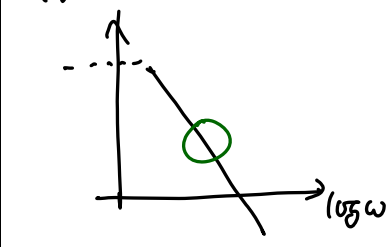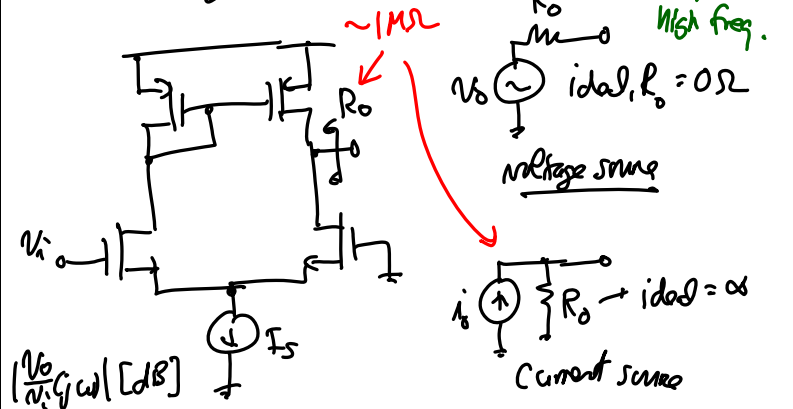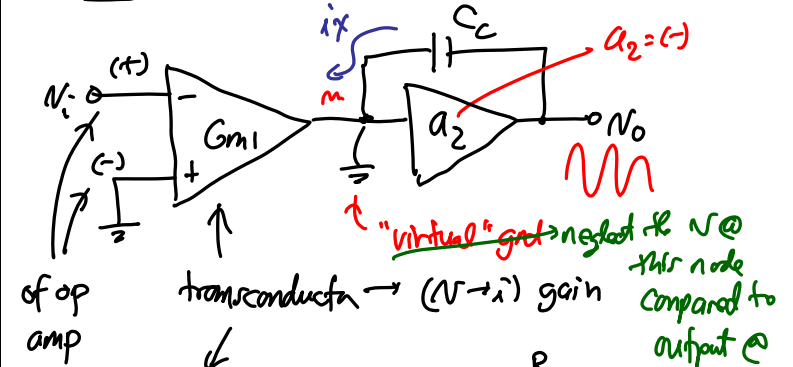① Case: Two-Stage Amplifier, Miller compensation



$$V_o = \frac{i_{ix}}{sC_c} \left. \begin{array}{l} i_{ix} = G_{m1} V_i \\ V_o = \frac{G_{m1}}{sC_c} V_i \end{array} \right\} \rightarrow \frac{V_o}{V_i}(s) = \frac{G_{m1}}{sC_c}$$

does not hold here
 but does hold here
 This is all that matters for Phase Margin deformation!

$$\left| \frac{V_o}{V_i}(j\omega) \right| = \frac{G_{m1}}{\omega C_c} \Rightarrow \text{this should equal } A_o \text{ @ the freq. } \omega \text{ corresponding to the target phase margin}$$

For $PM = 45^\circ$:

$$\omega_{ult} = \omega @ |a(j\omega)| = 1$$

"ult" = "unity loop transmission"
 $|a(j\omega)| = 1$

For $PM = 45^\circ \rightarrow \omega_{ult} = \omega_2 \approx$ freq. of the 2nd pole in the $a(j\omega)$ transfer fun.

$$\left| \frac{V_o}{V_i}(j\omega_2) \right| = A_o = \frac{G_{m1}}{\omega_2 C_c} \rightarrow C_c = \frac{G_{m1}}{\omega_2 A_o}$$

For $PM = 45^\circ$
 (provided $|p_3| \gg |p_2|$)

For $PM = 60^\circ$:

$$\omega_{ult} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{V_o}{V_i}(j \frac{\omega_2}{1.73}) \right| = A_o = \frac{G_{m1}}{(\frac{\omega_2}{1.73}) C_c}$$

$$C_c = \frac{1.73 G_{m1}}{\omega_2 A_o} \leftarrow \text{For } PM = 60^\circ$$

② Case: Two Stage Amplifier, Shunt C_c Compensation

of op amp
 of the transconductance