

Lecture 22: CMOS Op Amp Compensation

• Announcements:

- ↳ HW#9 due today
- ↳ HW#10 online: shorter than usual, since you also have your project (Lab#3) to work on

• Lecture Topics:



- ↳ Choosing C_c (cont.)
- ↳ CMOS 2-Stage Op Amp Poles & Zeros
- ↳ RHP Zero
- ↳ Nulling the RHP Zero

• Last Time:


Choosing C_c (assume no RHP zeroes $\nmid p_3 \rmid \gg \nmid p_2 \rmid$)

\Rightarrow assume $\frac{1}{SC_c} \ll$ surroundly impedance @ high freq.

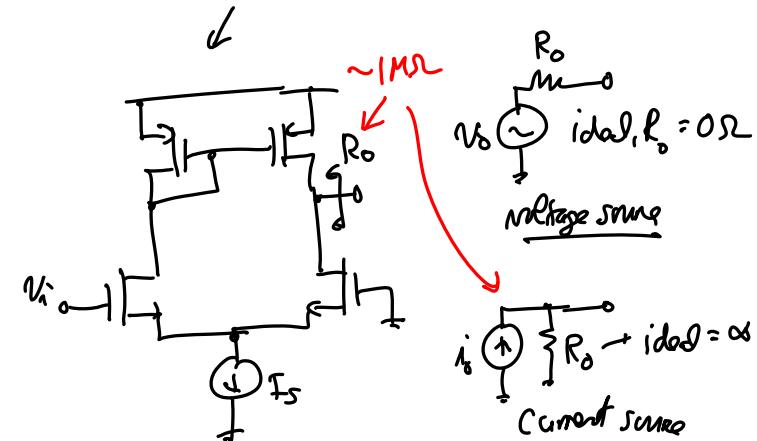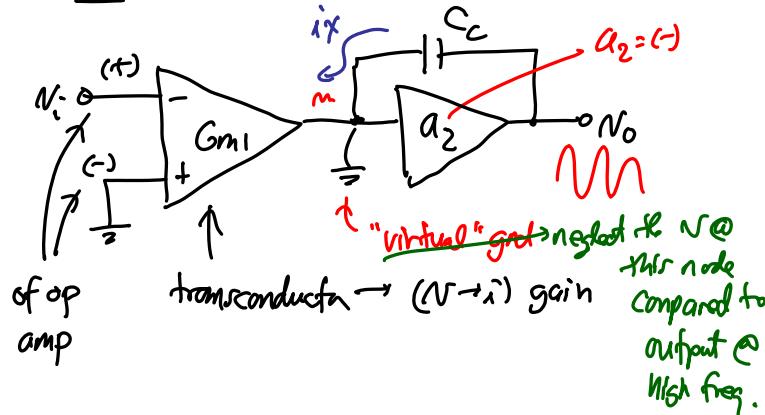① Case: Two-Stage Amplifier, Miller Compensation


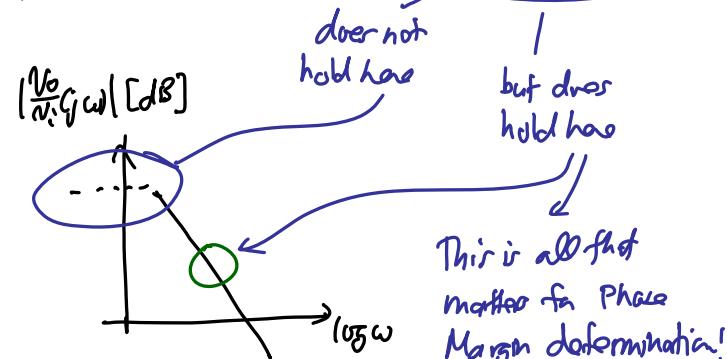
$$V_o = \frac{i_x}{SC_c} \quad i_x = G_{m1} V_i \quad \left\{ \begin{array}{l} V_o = \frac{G_{m1}}{SC_c} V_i \\ \frac{V_o}{V_i(j\omega)} = \frac{G_{m1}}{SC_c} \end{array} \right. \rightarrow \frac{V_o}{V_i(j\omega)} = \frac{G_{m1}}{SC_c}$$




$$\left| \frac{V_o}{V_i(j\omega)} \right| = \frac{G_{m1}}{WC_c} \Rightarrow \text{this should equal } A_o \text{ @ the freq. } \omega \text{ corresponding to the target phase margin}$$

For PM = 45°:

$$\omega_{ult} = \omega @ |A(j\omega)f| = 1$$

"ult" = "unity loop transmission"
 $|A(j\omega)f| = 1$
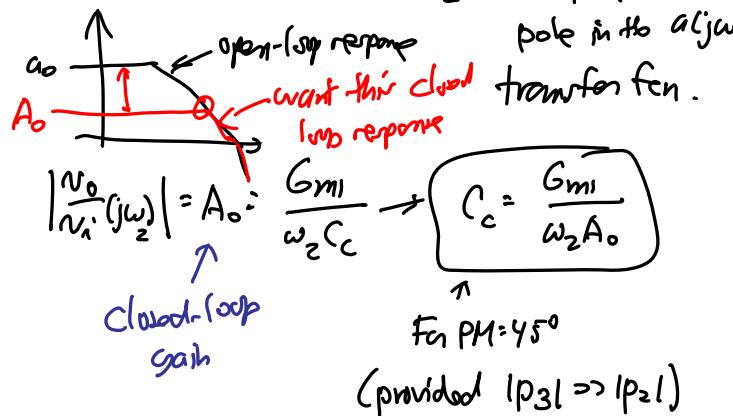
$$For PM = 45^\circ \rightarrow \omega_{ult} : \omega_2 \leftarrow \text{freq. of } f_L \text{ at } 2\omega$$




For PM = 60°:


$$\omega_{ult} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{V_o}{V_i} \left(j \frac{\omega_2}{1.73} \right) \right| = A_o \cdot \frac{G_m}{\left(\frac{\omega_2}{1.73} \right) C_c}$$

$$C_c = \frac{1.73 G_m}{\omega_2 A_o} \quad \leftarrow \text{For PM} = 60^\circ.$$

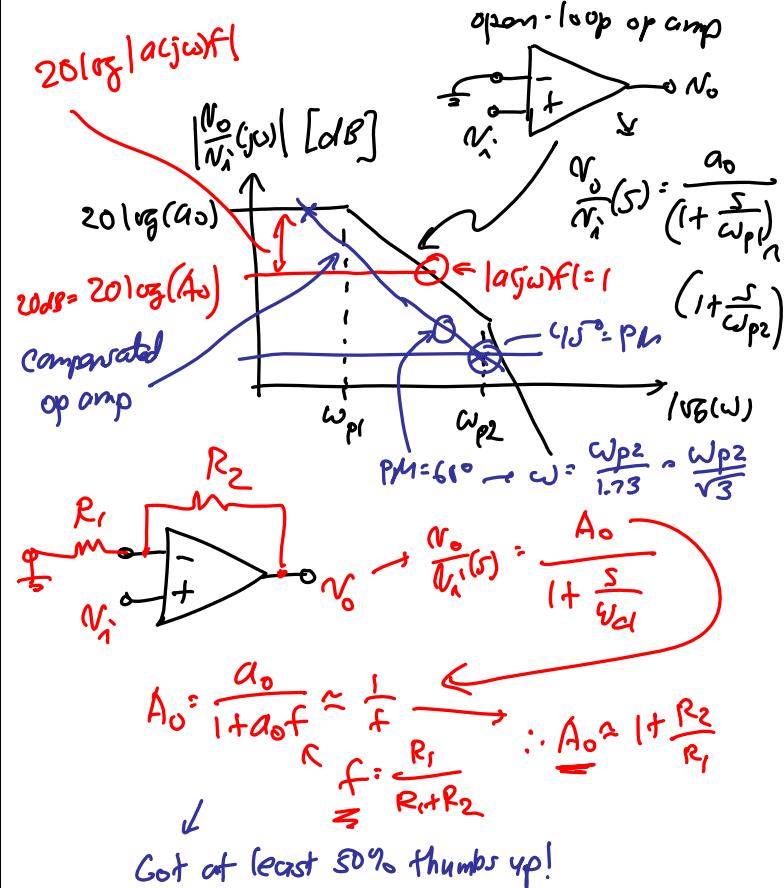Review: To make sure everyone understands



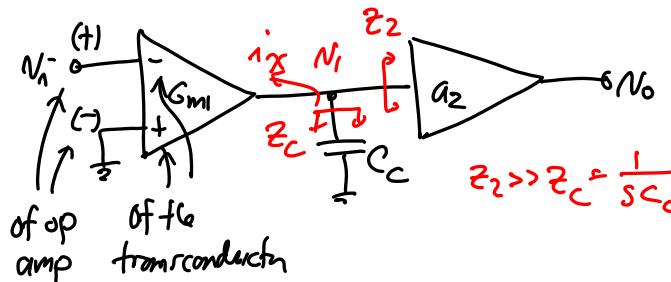② Case 2: Two-Stage Amplifiers, Shunt C_c Compensation



$$\left. \begin{aligned} N_1 &= -\frac{G_{m1} N_i}{sC_c} \\ N_0 &= a_2 N_1 \end{aligned} \right\} N_0 = -\frac{G_{m1} a_2}{sC_c} N_i$$

$$\therefore \frac{N_0}{N_i(s)} = -\frac{G_{m1} a_2}{sC_c} \quad \left. \begin{aligned} &\text{Closed loop gain} \\ &\text{A}_o \text{ must again} \\ &\text{intersect this curve} \end{aligned} \right\}$$

@ the right w_{ulf} for a given PM

For PM = 45°:


$$\left| \frac{N_0}{N_i(j\omega_{ulf})} \right| = A_o = \frac{G_{m1} a_2}{\omega_{ulf} C_c} \quad \left. \begin{aligned} &\left(\text{For PM} = 45^\circ : \omega_{ulf} = \omega_2 \right) \\ &C_c = \frac{G_{m1} a_2}{\omega_2 A_o} \end{aligned} \right\}$$

For PM = 60°:

$$C_c = \frac{1.73 G_{m1} a_2}{\omega_2 A_o} \quad \text{for PM} = 60^\circ.$$

Case ③: Single-Stage Amplifier, Shunt C_c Compensation

e.g., telescopic cascode op amp

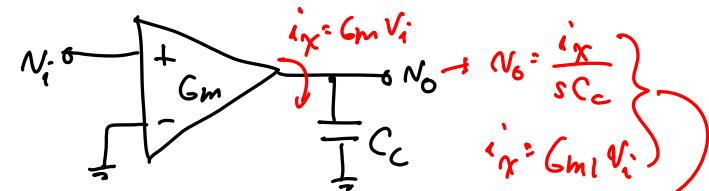

$$\frac{N_0}{N_i(s)} = \frac{G_{m1}}{sC_c} \quad \leftarrow \text{same as case ①!}$$



Thus

$$C_c = \frac{G_{m1}}{\omega_2 A_o} \quad \leftarrow \text{PM} = 45^\circ$$

$$C_c = \frac{1.73 G_{m1}}{\omega_2 A_o} \quad \leftarrow \text{PM} = 60^\circ$$

This is the final ω_2 after C_c is inserted.

CMOS 2-Stage Op Amp Compensation

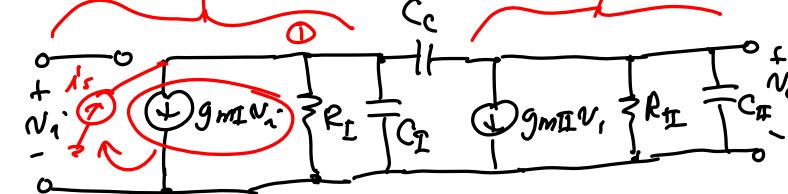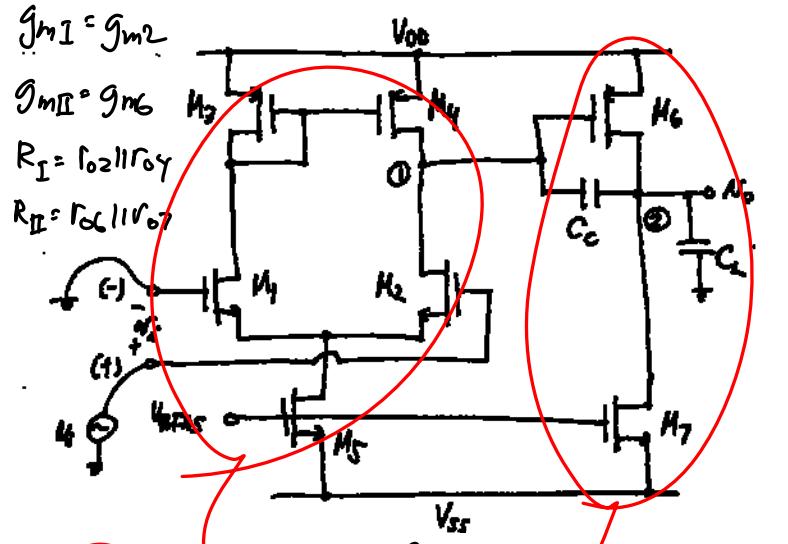

$$KCL \textcircled{1}: i_s = \frac{N_1}{R_I} + sC_I V_i + (N_1 - N_2) sC_c$$

$$KCL \textcircled{2}: g_{mII} V_i + \frac{N_2}{R_{II}} + sC_{II} V_o + (N_2 - N_3) sC_c = 0$$

$$\frac{N_2}{i_s} = \frac{(g_{mII} + sC_c) R_I R_{II}}{(g_{mII} + sC_c) R_I R_{II}} \leftarrow N(s)$$

$$D(s) \rightarrow \frac{\{1 + s[(C_{II} + C_c) R_{II} + (C_I + C_c) R_I + g_{mII} R_I R_{II} C_c]\}}{+ s^2 R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$\frac{N_o}{i_s}(s) = \frac{N(s)}{D(s)}$ → This $X(s)$ func has 2 poles & one zero.

The zero: $N(s) > 0 \rightarrow z = s$ $\boxed{z = \frac{g_{mII}}{C_c}}$ ← (+) and real

The poles:

$$D(s) = \left(1 - \frac{s}{P_1}\right) \left(1 - \frac{s}{P_2}\right) = 1 - s\left(\frac{1}{P_1} + \frac{1}{P_2}\right) + \frac{s^2}{P_1 P_2}$$

$$[P_2 \gg P_1] \approx 1 - \frac{s}{P_1} + \frac{s^2}{P_1 P_2}$$

i.e., there is a dominant pole

thus:

$$P_1 = -\frac{1}{(C_{II} + C_c) R_{II} + (C_I + C_c) R_I + g_{mII} R_I R_{II} C_c}$$

$$A_r C_c \uparrow \rightarrow P_1 \downarrow \approx -\frac{1}{g_{mII} R_I R_{II} C_c}$$

For the 2nd pole:


$$P_1 P_2 = \frac{1}{R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$$C_c \uparrow \rightarrow P_2 \uparrow$$


$$P_2 = -\frac{g_{mII} C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \rightarrow A_r C_c \uparrow$$

$$P_2 \approx -\frac{g_{mII}}{C_I + C_{II}}$$

higher than before ∵

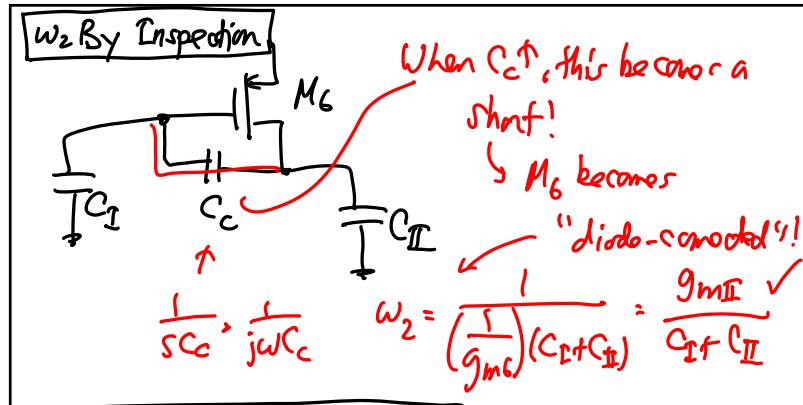

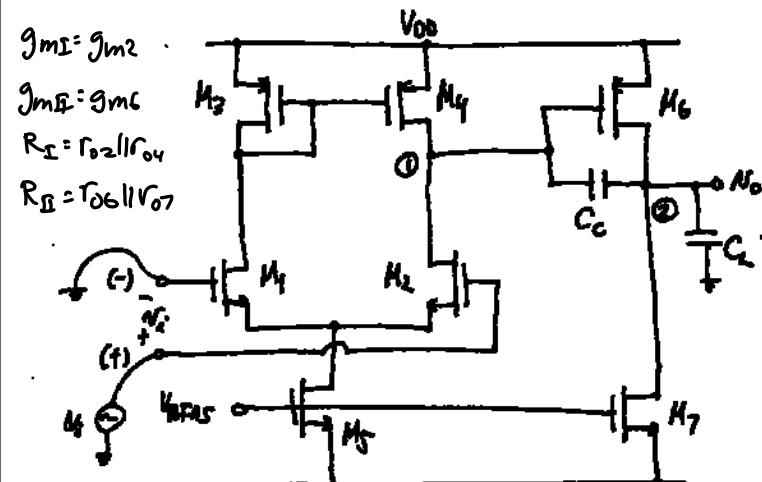CMOS 2-Stage Op-Amp Compensation (Summary)



From our previous analysis:

$$\omega_1 = \frac{1}{g_{mI} R_I R_{II} C_c} \quad [C_c \gg C_I \text{ and } C_{II}] \quad [C_L \gg C_I]$$

$$\omega_2 = -\frac{g_{mII} C_c}{C_I C_{II} + C_c(C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{mI}}{C_L}$$

$$z = +\frac{g_{mII}}{C_c} \leftarrow \text{RHP zero (this will cause problems)}$$