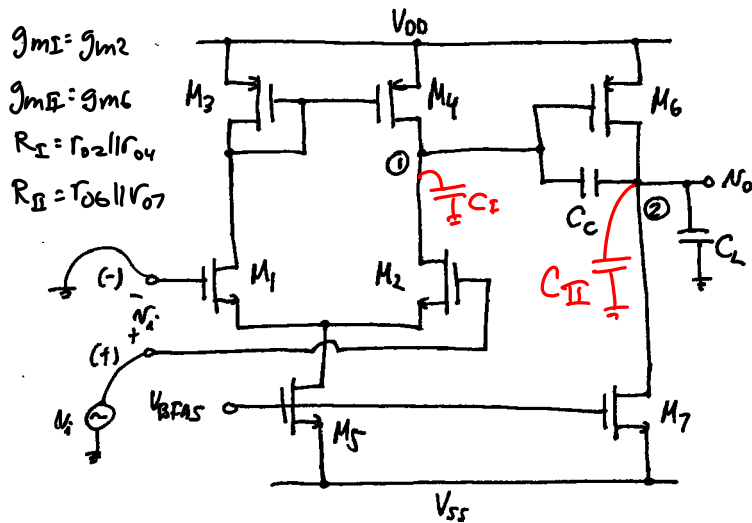


Lecture 23: Practical Compensation

- Announcements:
- Design Project Checkpoint:
 - ↳ Due Monday, April 23, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (or linear if an MOS resistor)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
- Lecture Topics:
 - ↳ RHP Zero
 - ↳ Nulling the RHP Zero

Last Time:

CMOS 2-Stage Op Amp Compensation (Summary)



from our previous analysis:

$$p_1 = -\frac{1}{g_{mII} R_I R_{II} C_C} \quad [C_C \gg C_I \text{ or } C_{II}] \quad [C_L \gg C_I]$$



$$p_2 = -\frac{g_{mII} C_C}{C_I C_{II} + C_C(C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{m6}}{C_L}$$

$$z = +\frac{g_{mII}}{C_C} \leftarrow \text{RHP zero (this will cause problems)}$$

Remarks:

- ① Note that as $C_C \uparrow \rightarrow p_1 \downarrow \rightarrow 0$
- ② As $C_C \uparrow \rightarrow p_2 \uparrow \rightarrow p_2 = \frac{g_{mII}}{C_I + C_{II}}$
- ③ With $C_C = 0$ (i.e., before compensation)
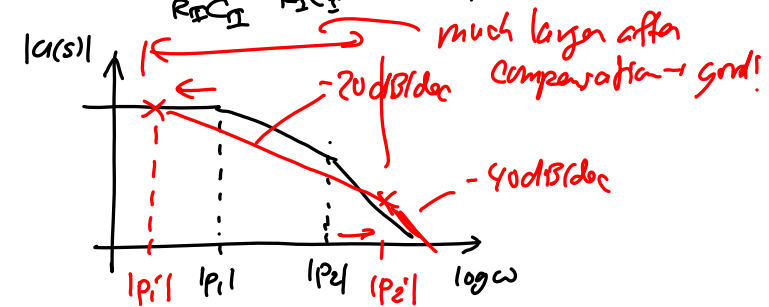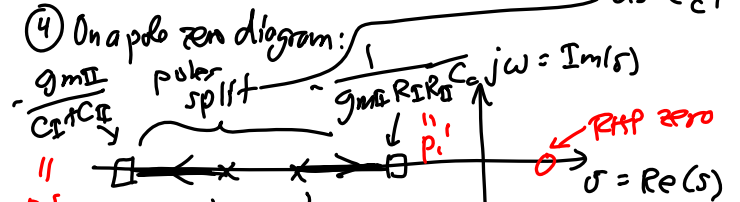
$$p_1 = -\frac{1}{R_I C_I}, \quad p_2 = -\frac{1}{R_{II} C_{II}} \quad \text{as } C_C \uparrow$$



- Go through RHP zero handout: Lec12x

Where Does the RHP zero come from?

Feedforward Current

$$\frac{V_o}{v_i} = -\frac{g_{m2}}{g_{m6}}$$

Negative! (should be (+))
→ Thus → instability!

Observation:
The Miller effect (for compensation) requires the FB path around M_6 → BUT: the feedforward path (that causes the zero) isn't needed!

Solution: ① kill the feedforward path
② keep the feedback path

The Ckt.

Apply KCL:

$$P_1 \approx -\frac{1}{g_{m2} R_1 R_2 C_c} \quad (\text{same as before})$$

$$P_2 \approx -\frac{g_{m2} C_c}{C_{II}(C_I + C_c)} \approx -\frac{g_{m2}}{C_{II}} \quad [C_c \gg C_I]$$

$$P_3 \approx \frac{-1}{R_0 [C_I C_c / (C_I R_c)]} \approx -\frac{1}{R_0 C_I}$$


Series combination of C_I & C_c .

$$z \approx -\frac{1}{R_0 C_c} \leftarrow \text{LHP zero!} \rightarrow \text{Good!}$$

Remarks:

- ① An additional pole $P_3 = -\frac{1}{R_0 C_I}$ has been created! But since R_0 is small (for a buffer) and C_I is small, P_3 is at a very high freq. → contributes very little phase @ ω_{ut} , where $|T(j\omega)| = 1$.
- ② A LHP zero now emerges, $z_1 = -\frac{1}{R_0 C_c}$.
This helps stability as discussed before.
(by contributing (+) phase shift → PMN)

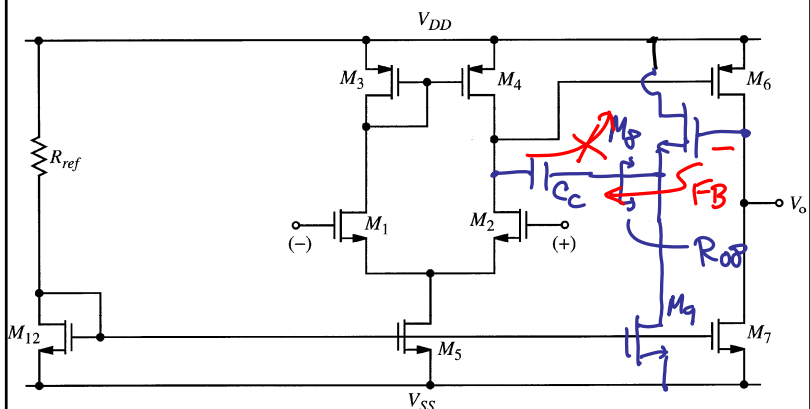Actual Implementation of Buffer-Based Zero Cancellation




$R_{null} \approx \frac{1}{g_{m8}} = \frac{1}{\sqrt{2\mu_n C_{ox}} \left(\frac{W}{L}\right)_8 I_{D8}}$ ← Want this sufficiently small to drive $|p_3| \uparrow$

① make $(W/L)_8$ big $X \rightarrow area \uparrow$
② use large enough I_{D8}

Solution: a better technique! $X \rightarrow power \uparrow$

Nulling Resistor in Series w/ C_c

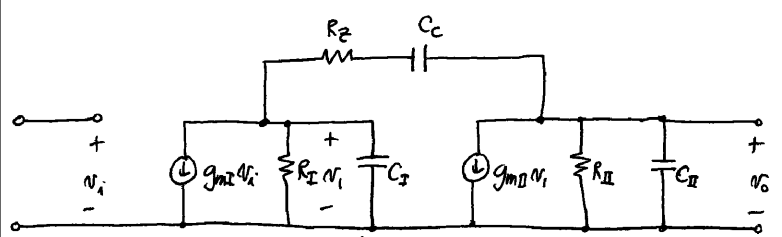

Doing KCL: $P_1 \approx -\frac{1}{g_{m1}R_1R_2C_c}$
 $P_2 \approx \frac{-g_{m2}C_c}{C_1C_2 + C_c(C_1 + C_2)}$

} Same as before

$p_3 = -\frac{1}{R_2C_I}$ ← pole due to R_2

$z_1 = \frac{1}{C_c \left(\frac{1}{g_{m8}} - R_2\right)}$ ← relocated zero (function of R_2)

Note: The position of the zero depends on the value of the "nulling" resistor R_2 .


- { If $R_2 < \frac{1}{g_{m8}}$ then z_1 is in the RHP
- { If $R_2 > \frac{1}{g_{m8}}$ then z_1 " " " LHP!

↳ This is good! → can convert the zero to a LHP zero!

$H(s) = \frac{(s-z_1)}{(s-p_1)}$
If $z_1 = p_1$

can even stick it on top of a pole → null it!

The Root Locus:

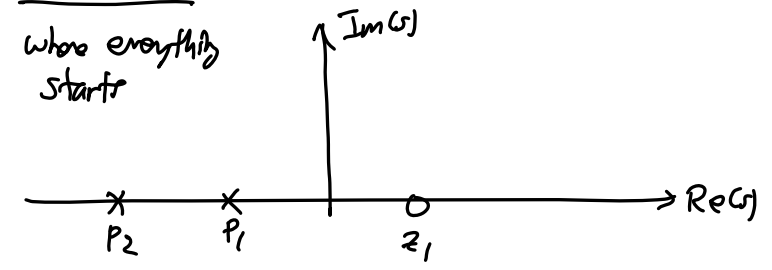

Now, introduce R_2 :

Zero Placement Strategies

① Eliminate $z_1 \rightarrow$ move it to ∞ :

$$z_1 = C_c \left(\frac{1}{g_{mII}} - R_2 \right) \rightarrow \infty \text{ when } R_2 = \frac{1}{g_{mII}}$$

After doing this: $p_3 \approx -\frac{g_{mII}}{C_I}$ usually, $C_I \gg C_c$
 $p_2 \approx -\frac{g_{mII}}{C_{II}}$ since $C_{II} = C_c$.

so these poles are often very far apart.
 (but be careful)

This is good... but we could do better...

② Eliminate p_3 by placing z_1 on top of it:

$$z_1 = p_3 = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} = -\frac{1}{R_2 C_I}$$

$$R_2 = \frac{1}{g_{mII} \left(1 - \frac{C_I}{C_c} \right)}$$

After this:

- ① p_3 gone; p_1, p_2 left
- ② Now, can place ω_{uit} @ p_2 and really get $PM = 45^\circ$ (w/o worrying about the influence of p_3)