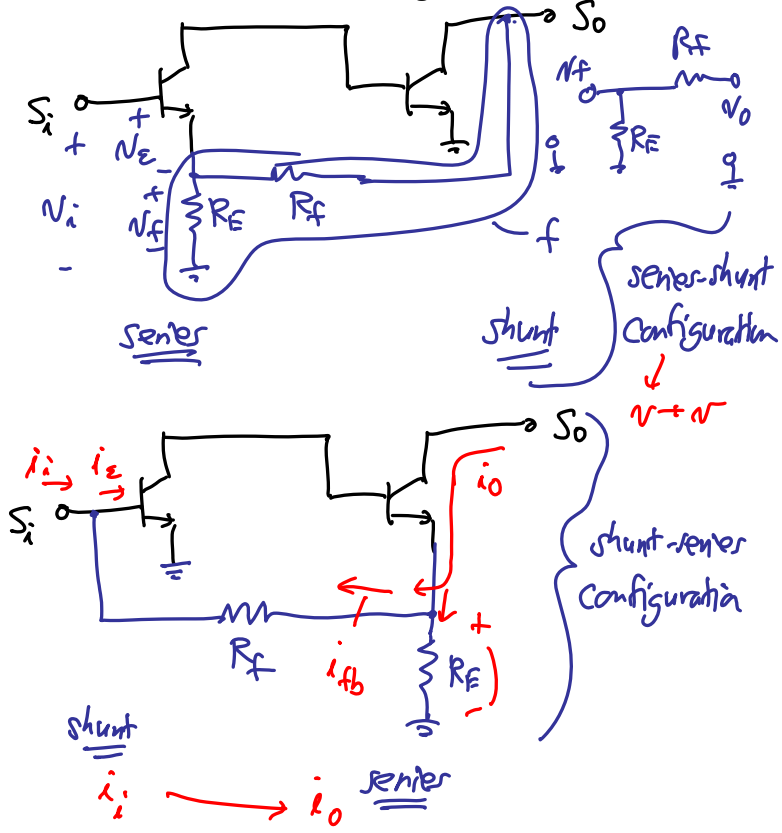


Lecture 26: Feedback Z

- Announcements:
- HW#11 due today; project due next Friday
- HW#12 online: your last HW, due during RRR week
 - ↳ Yes, I know, yet another homework
 - ↳ But this will help you for your final exam
- Lecture Topics:
 - ↳ Effect of FB on Z_i and Z_o
 - ↳ Feedback Loading

• Last Time: Feedback Configurations



Feedback Configurations


Variable	Connection	Connection	Variable
voltage	series	series	current
current	shunt	shunt	voltage

$n \rightarrow i$ (blue arrow)
 $i \rightarrow n$ (green arrow)
 $i \rightarrow i$ (red arrow)
 $n \rightarrow n$ (red arrow)

Effect of FB on Z_i & Z_o

Ex. Series-Shunt FB

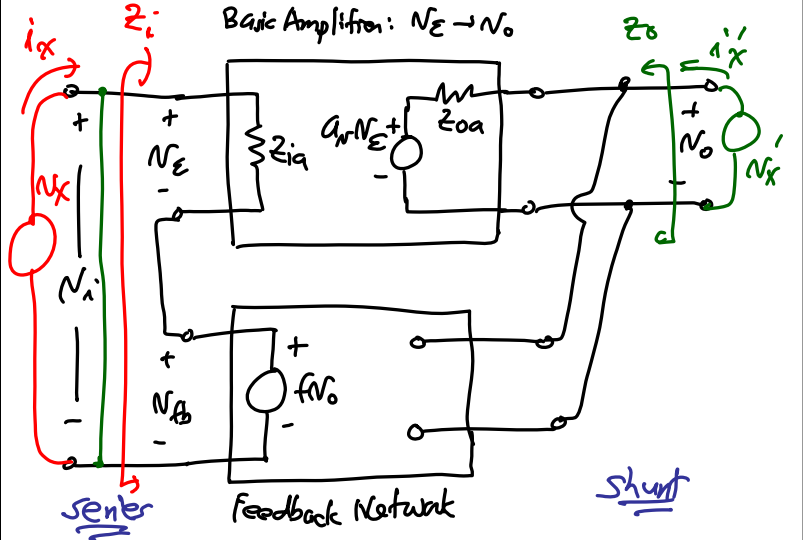Assumption: FB network has ideal impedances
 ↳ i.e., it does not load the basic amplifier



Find the T.F. -

$$\left. \begin{aligned} V_o &= a_v V_i - V_{fb} \\ V_o &= a_v V_o \\ V_{fb} &= f V_o \end{aligned} \right\} \Rightarrow \frac{V_o}{V_i} = \frac{a_v}{1 + a_v f} \quad \checkmark \quad (\text{as expected})$$

Find $Z_i = \frac{V_x}{i_x}$:

$$V_x = V_o + V_{fb} = V_o + f V_o = V_o(1 + f a_v)$$

$$i_x = \frac{V_o}{Z_{ia}} \quad \text{orig. open-loop input impedance}$$

$$Z_i = \frac{V_x}{i_x} = \frac{V_o(1 + f a_v)}{\frac{V_o}{Z_{ia}}} = Z_{ia}(1 + f a_v) = Z_i$$

closed-loop input impedance

When use series connection @ input

Input impedance raised by $(1 + a_v f)$!

↓

If $Z_i \uparrow \rightarrow$ better voltage amplifier!

Find $Z_o = \frac{V_x'}{i_x'}$: (w/ input shorted)

$$V_o + V_{fb} = V_o + f a_v V_o = 0 \rightarrow V_o = -f a_v V_x'$$

$$i_x' = \frac{V_x' - a_v V_o}{Z_{oa}} = \frac{V_x' - a_v (-f a_v V_x')}{Z_{oa}} = \frac{V_x'(1 + a_v^2 f)}{Z_{oa}}$$

orig. open-loop output impedance

$$\frac{V_x'}{i_x'} = \frac{Z_{oa}}{1 + a_v f} = Z_o$$

closed-loop output impedance Z_o

↓

lowered a factor of $(1 + a_v f)$


Again, makes for a better voltage amplifier!

Overall, series-shunt FB improves the impedance characteristics of a $v \rightarrow v$ amplifier:

$Z_i \uparrow, Z_o \downarrow$ due to FB

Ex: Shunt-Series FB

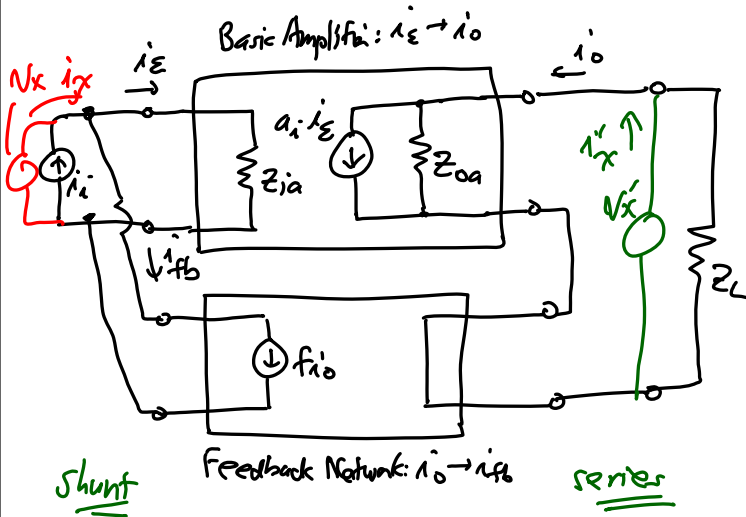⇒ Again, assume the FB network does not load the amplifier



Find the T.F.:

$$i_o = a_i i_\epsilon$$

$$i_\epsilon = i_x - i_{fb} = i_x - f i_o$$

$$\frac{i_o}{i_x} = \frac{a_i}{1 + a_i f}$$

open-loop current gain

loop gain

Similar form to the V+V case, except now for i → i.

Find $Z_i = \frac{V_x}{I_x}$: open-loop input impedance

$$\frac{V_x}{I_x} = \frac{Z_{ia}}{1 + a_i f} = Z_i$$

loop gain

⇒ Again, a shunt connection reduces impedance by a factor of $(1 + a_i f)$!

Find $Z_o = \frac{V_x}{I_x}$:

$$\frac{V_x}{I_x} = Z_{oa} (1 + a_i f) = Z_o$$

Series connection raises the impedance by a factor of $(1 + a_i f)$!

Shunt-Series

Everything together makes for a better i → i amplifier!


Summary. $T = \text{loop gain}$

- ① series connection: $Z \rightarrow Z(1+T)$
- ② shunt connection: $Z \rightarrow \frac{Z}{(1+T)}$

• Now go through the handout on feedback loading

Determine the FB loading of an Amplifier


Example: Non-Inverting Amplifier

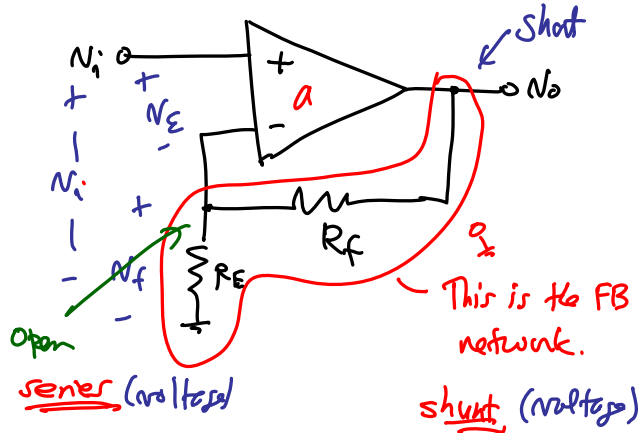


Objective: Use $A_o = \frac{a_v}{1 + a_v f}$ to get A_o .
 closed loop gain \leftarrow open loop gain
 feedback factor

In order to use this equation, we must know
 (i) $a_v \hat{=}$ gain of the amplifier
 (ii) $f \hat{=}$ gain of the feedback (also, called the feedback factor)

In general:

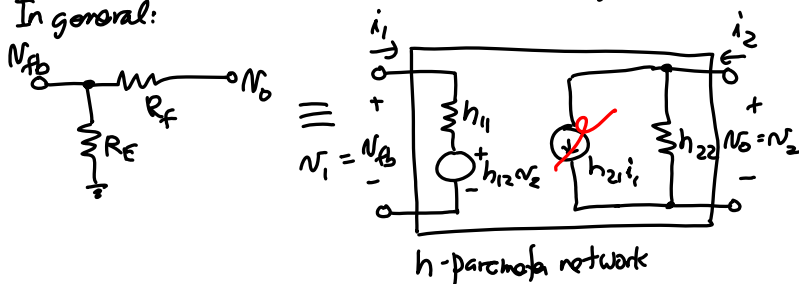


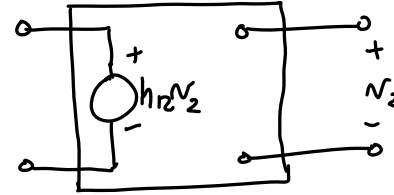But to simplify things, we would like to be able to represent the feedback network by just:




- Where: ① The small h_{21} is neglected.
- ② All impedances have been moved out of the f-network and moved to the a_v -network.

Pictorially:

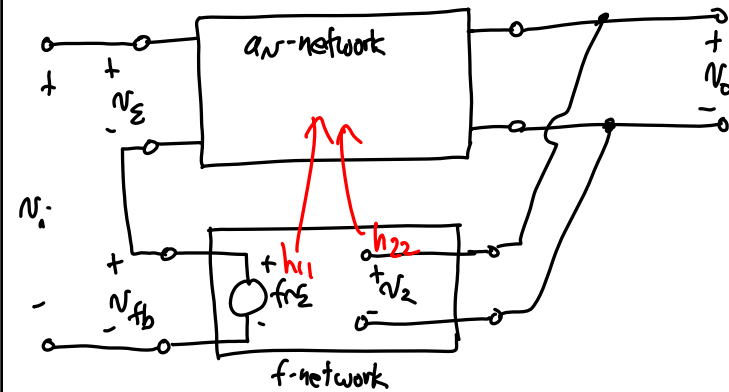

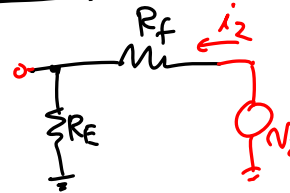The FB Network: (find the h-parameter representation)



h-parameter Network (just a reminder)

Port Equations:

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$i_2 = h_{21}i_1 + h_{22}V_2$$

Elements:

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

$$h_{22f} = \left. \frac{i_2}{V_2} \right|_{i_1=0} = \frac{1}{R_E + R_F}$$

↑
This is a conductance.

(This is the loading @ port 2, i.e., at the amplifier output port)

$$h_{12f} = \left. \frac{V_1}{V_2} \right|_{i_1=0} = \frac{R_F}{R_E + R_F} = f$$

(feedback gain factor)

$$h_{11f} = \left. \frac{V_1}{i_1} \right|_{V_2=0} = R_E || R_F$$

(This is the loading at port 1, i.e., at the amplifier's input port.)

So we have: