

Lecture 27: Feedback By Inspection

Announcements:

- ↳ Lab#3 (your project) due on Friday, May 4, at 6 p.m., in the EE140 box
- ↳ Passed out Feedback Inspection Handout (last time) but covered it today
- ↳ Passed out Final Information Sheet and sample Final Exams (from 2009 & 2011)


Lecture Topics:

- ↳ Feedback Loading
- ↳ Open-Loop Amp w/ Feedback Loading
- ↳ Feedback By Inspection
- ↳ Final Exam Info & Course Wrap Up

Last Time: Open-Loop Amp w/ Feedback Loading

Determine the FB loading of an Amplifier

Example: Non-Inverting Amplifier

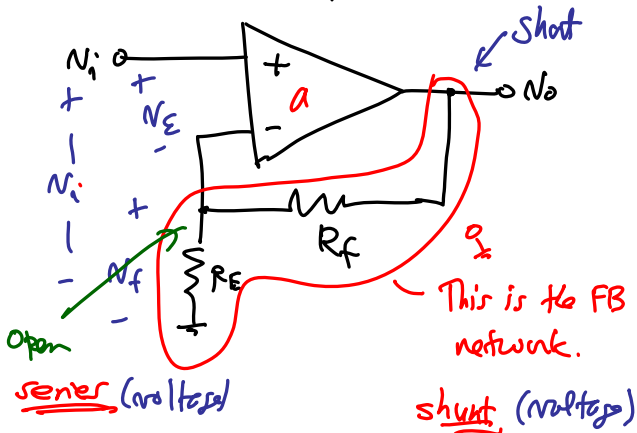


closed loop gain
 $A_o = \frac{a_N}{1 + a_N f}$
 open-loop gain
 feedback factor


Objective: Use $A_o = \frac{a_N}{1 + a_N f}$ to get A_o .

In order to use this equation, we must know
 (i) $a_N \triangleq$ gain of the amplifier
 (ii) $f \triangleq$ gain of the feedback (also, called the feedback factor)

In general:


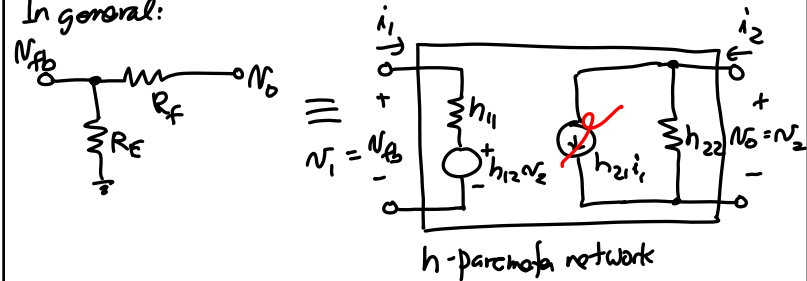


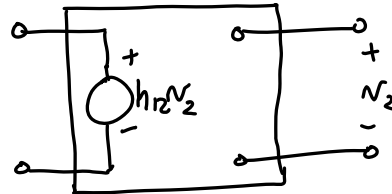
But to simplify things, we would like to be able to represent the feedback network by just:



- where:
- ① The small h_{21} is neglected.
 - ② All impedances have been moved out of the f-network and moved to the a_N -network.

↳ Pictorially:

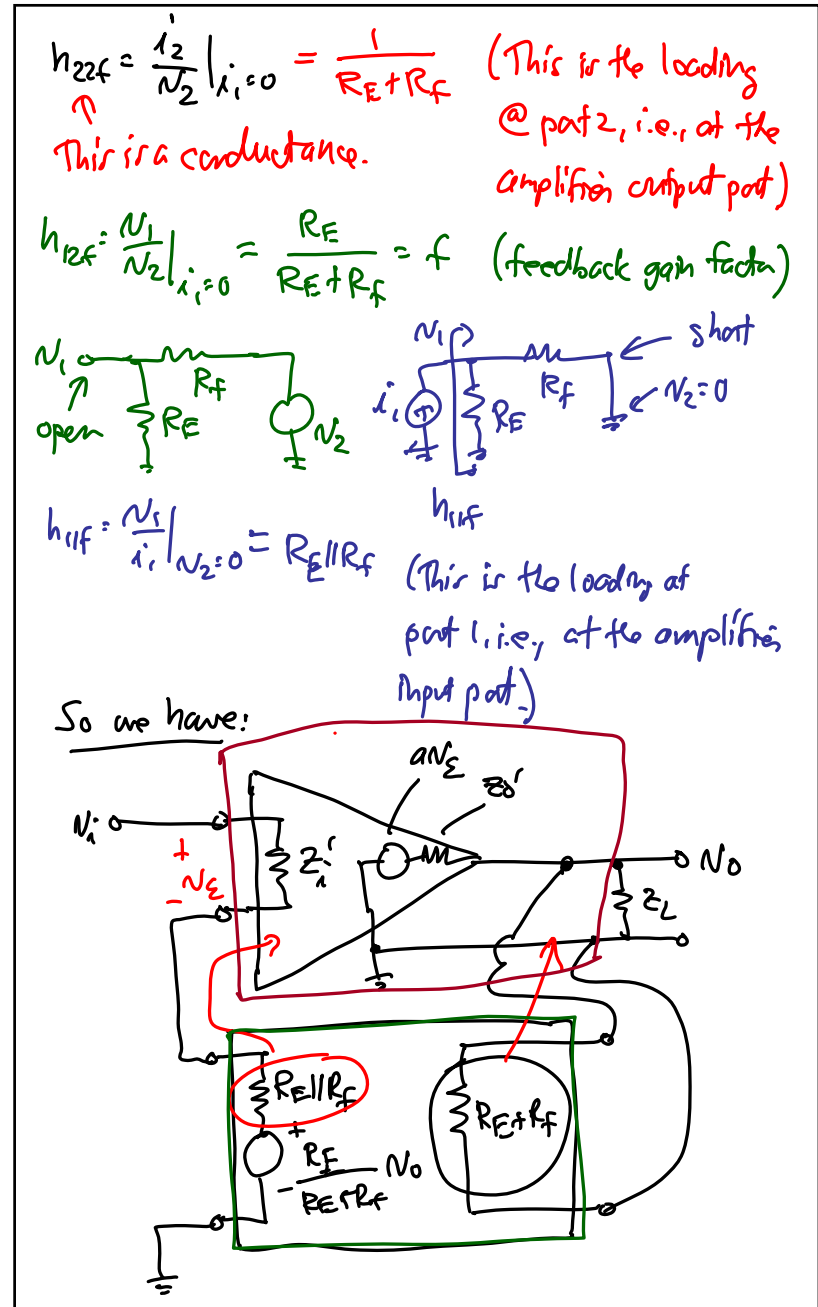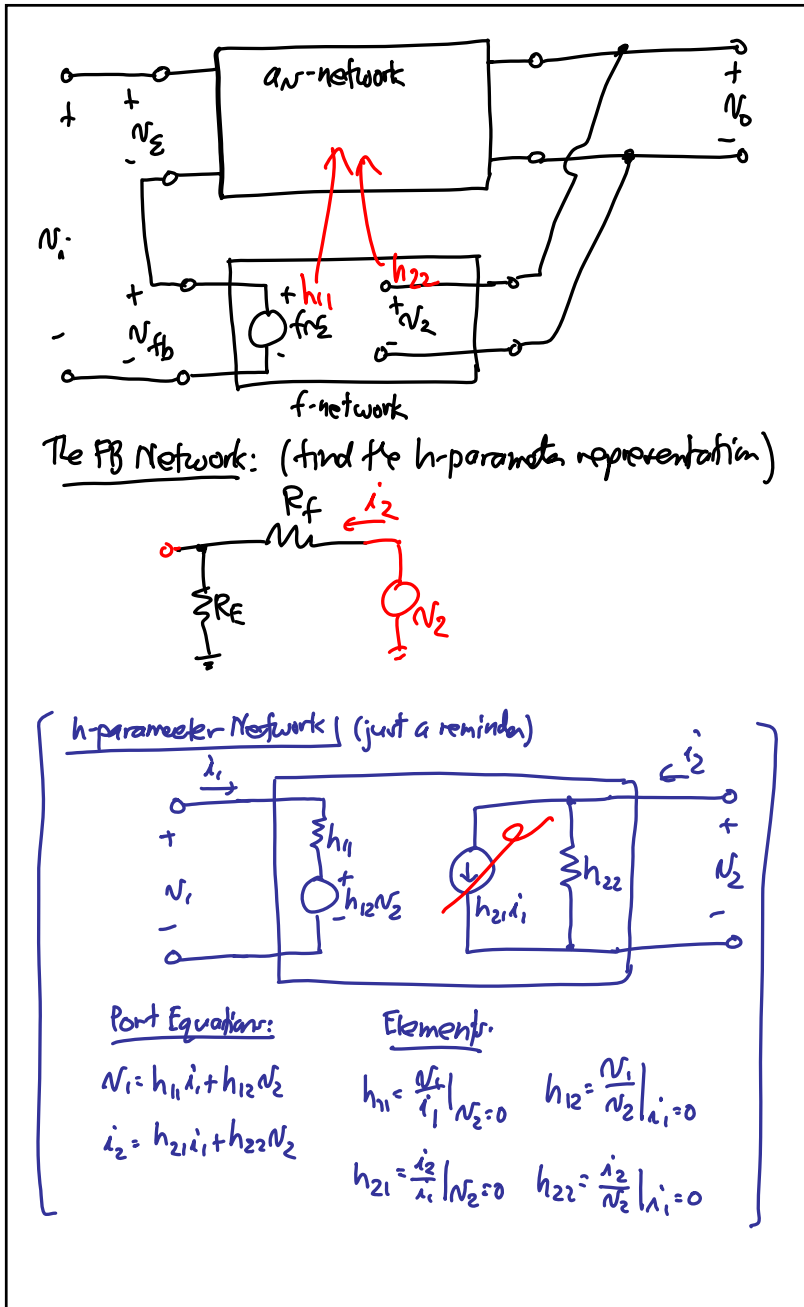

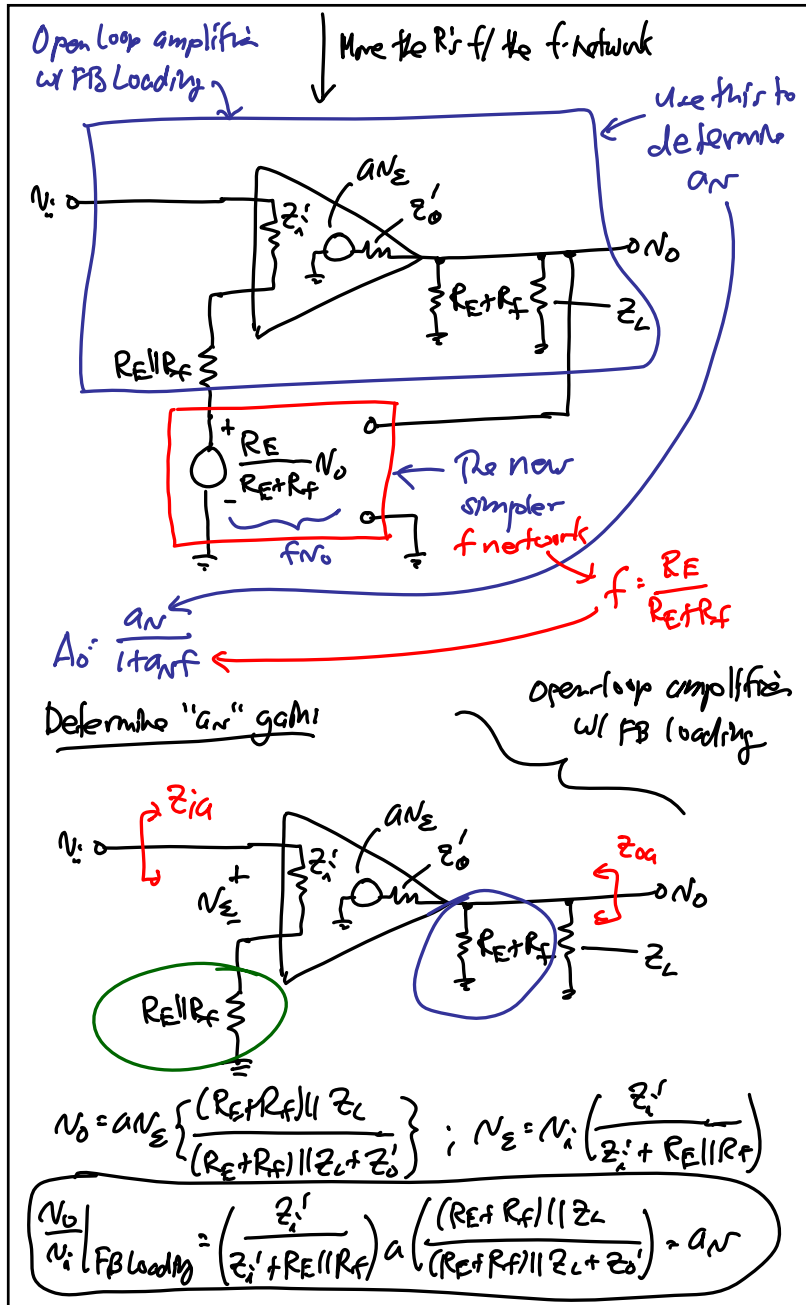

We know: $f = \frac{R_E}{R_E + R_F}$

Get closed-loop gain, A_o : for $a_N \gg 1$

$$A_o = \frac{N_o}{N_i} = \frac{a_N}{1 + a_N f} \approx \frac{1}{f} = 1 + \frac{R_F}{R_E}$$

Must use this if a_N not large.

What about R_i & R_o ?

\Rightarrow For the open-loop amp w/ FB loading:

$Z_i = Z_i' + RE || RF \xrightarrow{\text{series}} Z_i = (Z_i' + RE || RF)(1 + a_N f)$

$Z_o = Z_o' || (RE + RF) || Z_L \xrightarrow{\text{shunt}} Z_o = \frac{Z_o' || (RE + RF) || Z_L}{1 + a_N f}$

What about ω_{-3dB} ?

$$\omega_{-3dB} |_{\text{closed-loop}} = [\omega_{-3dB} |_{\text{open-loop amp}}] \times (1 + a_N f) \text{ w/ FB loading}$$

- Go through the "Inspection Analysis of Feedback Circuits" handout
- In the end, if one can determine the open loop gain with FB loading and feedback factor, then the rest of the problem becomes simple
- Study the table in the handout

To determine loading by FB:

Input Loading: ① Determine the feedback type @ the output. (Here, it's shunt.)
② Break the loop @ the output.
③ For shunt, ground the loose end.

Output Loading:

① Determine the feedback type @ the input. (Here, it's series.)
② Break the loop @ the input.
③ For series, open the loose end.
(If shunt, short it.)

Example. Transresistance Amplifier

① Determine type of FB: → determine type of gain
② Biasing:
 $I_{FB} = I_{B1} \leftarrow f_{m1} \approx 0$ ← Note: Don't do this if $R_f = \text{large}$
 $I_{C2} \approx I_{E2} = \frac{V_{BE(2)}}{R_{E2} || R_L}$; $I_{C1} = \frac{V_{CC} - 2V_{BE(1)}}{R_{C1}}$
③ What kind of gain?
shunt-shunt FB → $i \rightarrow v$ gain
 \therefore we're looking for $R_m = \frac{v_o}{i_i} = \frac{r_m}{1 + r_m f}$
④ Determine r_m : (open loop w/ FB loading)
 $r_m = R_{C1} || (R_{E2} || R_L || R_f) || (R_{E2} || R_L) || R_f$

Get Gain:

$$\frac{N_0}{i_i} = \frac{N_0}{i_i} \cdot \frac{N_1}{N_1} \cdot \frac{N_2}{N_2} = \frac{N_0}{i_i} \Big|_{OL \ w/ \ FB \ loading} = r_m$$


$$N_0 = i_i (r_{\pi} || R_f) \rightarrow \frac{N_0}{i_i} = r_{\pi} || R_f$$

$$\frac{N_2}{N_1} = -g_m (R_{C1} || [r_{\pi 2} + (B+1)(R_{E2} || R_L || R_f)])$$

$$\frac{N_0}{N_2} \approx 1$$

$$r_m = \frac{N_0}{i_i} \Big|_{OL \ w/ \ FB \ loading} = -g_m (r_{\pi} || R_f) [R_{C1} || (\quad)] = r_m$$

Find f:

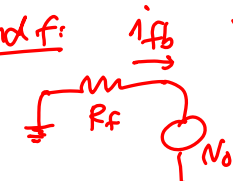

$$f = \frac{i_{fb}}{N_0} = -\frac{1}{R_f}$$

Thus:

$$T = r_m f = (-g_m (r_{\pi} || R_f) [R_{C1} || (\quad)]) \left(-\frac{1}{R_f} \right)$$

$$T \approx r_m f = g_m R_{C1} \left(\frac{r_{\pi} || R_f}{R_f} \right) \quad [if \ r_m f \gg 1]$$

Finally, set all parameters:

$$R_m = \frac{r_m}{(1 + T)} \approx \frac{1}{f} = -R_f \Rightarrow R_m = -R_f$$


$$R_i = \frac{R_{in} |_{\omega / FB \ loading}}{1 + r_m f} = \frac{r_{\pi} || R_f}{1 + g_m R_{C1} \left(\frac{r_{\pi} || R_f}{R_f} \right)} = R_i$$

large \therefore this = r_{π}

$$R_o = \frac{R_{out} |_{\omega / FB \ loading}}{1 + r_m f} = \frac{\frac{r_{\pi 2} + R_{C1}}{\beta + 1} || R_{E2} || R_f || R_L}{1 + g_m R_{C1} \left(\frac{r_{\pi} || R_f}{R_f} \right)} = R_o$$

Find ω_{-3dB} :

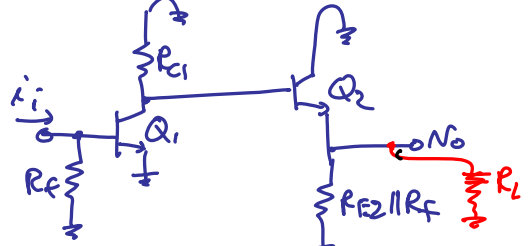① Find the ω_{-3dB} of the open-loop amplifier w/ FB loadings, i.e., of this: \rightarrow use OCTC analysis



② Multiply by (1+T):

$$\omega_{-3dB} |_{closed-loop} = (1+T) \times \omega_{-3dB} |_{OL \ w/ \ FB \ loading}$$

- What's next?
- **EE 240: Advanced Analog Integrated Circuits**
- Analysis and optimized design of integrated analog systems and building blocks. Specific topics include operational and wide-band amplifiers, gain-bandwidth and power considerations, analysis of noise in integrated circuits, low noise design, feedback, precision passive elements, analog switches, comparators, CMOS voltage references, non-idealities such as matching and supply/IO/substrate coupling. The course will include a significant design project applying the techniques taught in class to implement the analog front-end of a high-speed serial link.
- **EE 142: Integrated Circuits for Communication**
- Analysis and design of electronic circuits for communication systems, with an emphasis on integrated circuits for wireless communication systems. Analysis of noise and distortion in amplifiers with application to radio receiver design. Power amplifier design with application to wireless radio transmitters. Radio-frequency mixers, oscillators, phase-locked loops, modulators, and demodulators.
- **EE C245: Introduction to MEMS**
- Physics, fabrication, and design of micro-electromechanical systems (MEMS). Micro and nanofabrication processes, including silicon surface and bulk micromachining and non-silicon micromachining. Integration strategies and assembly processes. Transduction strategies and mechanical circuits. Electronic position-sensing circuits and electrical and mechanical noise. CAD for MEMS. Design project is required.