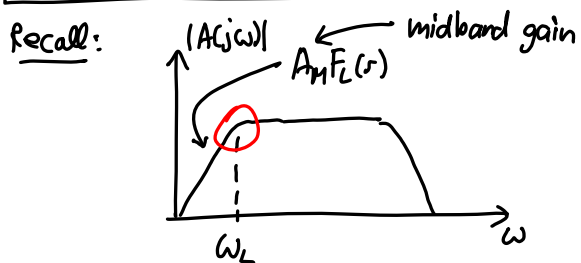


Lecture 7: Frequency Response Inspection Analysis II

- Announcements:
- This is our make-up lecture for next Tuesday
- No lecture next Tuesday, but there will be lecture next Thursday
- Lecture Topics:
 - ↳ Frequency Response Examples (cont.)
 - ↳ Short Ckt Time Constant (SCTC) Analysis
 - ↳ Example Low Freq. Response Determination
 - ↳ Start Active Loads

 • Last Time:

Low Freq. Amplifier Response Using Short Circuit Time Constant Analysis (SCTC)



In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}, \quad n_z = \# \text{ poles} = \# \text{ zeros}$$

We can express the coefficient e_1 by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn}$$

For the case of a dominant pole:

↳ i.e., the highest freq. pole

} Similar analysis to that used for OCTC...

$$F_L(s) \cong \frac{s}{s + \omega_L} = \frac{s}{s + e_1} \rightarrow e_1 \cong \omega_{p1} = \omega_L$$

$$\omega_L \cong e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{j,s}} = \sum_j \frac{1}{\tau_{j,s}}$$

where $C_j \triangleq$ various large ($> 10 \text{ nF}$) capacitors in the ckt. (e.g., the bypass caps.)

$R_{j,s} \triangleq$ driving point resistance seen between the terminals of C_j determined with:

For readability, can go to Sedra & Smith

① all large capacitors short-circuited, except C_j , which is replaced by the test voltage source for R determination


② all independent sources eliminated (i.e., short voltage sources, open current sources)

③ open all H.F. capacitors (i.e., small caps in the pF range, or $< 1 \text{ nF}$)


Again, for the case where there are no dominant poles, a reasonable approximation is:

$$\omega_L \cong \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$

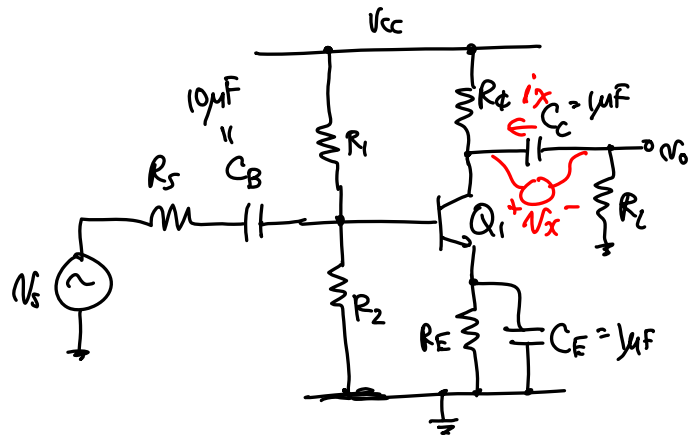Ex. Determine the L.F. Response of the C.E. Amplifier



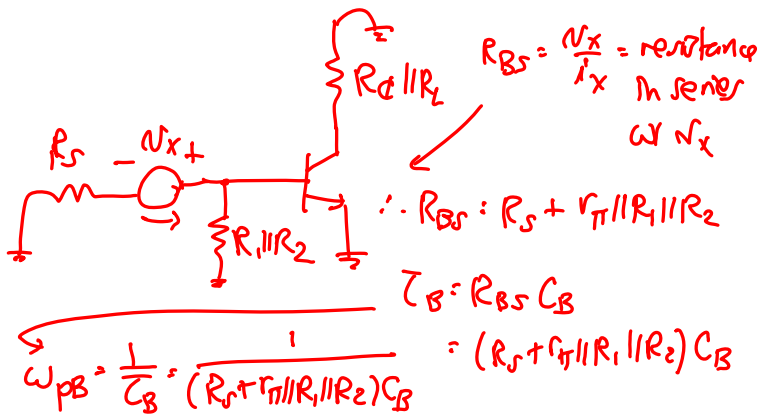
(a) Find τ due to C_B : short ckt. C_c & C_E



(b) τ due to C_c : short ckt. C_B & C_E
 → again, it will be R in series

$\tau_c = (R_c + r_{o1} || R_c) C_c$
 $\approx R_c \rightarrow \omega_{pC} = \frac{1}{\tau_c} = \frac{1}{(R_c + R_c) C_c}$

(c) τ due to C_E : short C_B & C_c

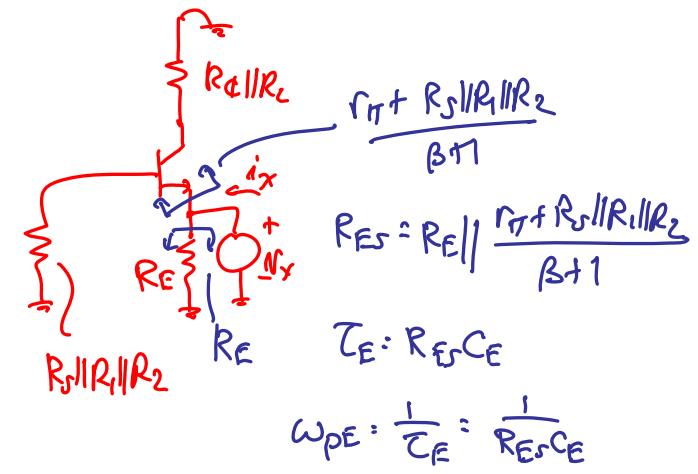

and finally:

$\omega_L = \omega_{pB} + \omega_{pC} + \omega_{pE}$



Active Loads

⇒ Why use them? → Gain $= \frac{V_{o}}{V_{i}} = -g_m R_D$

For $\frac{V_o}{V_i} \uparrow$, must:

- 1) Raise $g_m \rightarrow$ raise I_D
- 2) increase $R_D \rightarrow$ some problem

Problems: $V_{R_D} \uparrow$
 $V_{oD} \rightarrow V_{psv} \downarrow$

MOS saturated \rightarrow linear \rightarrow lose gain!

also, area!

Layout: (for resistors)

polysil $\sim 1k\Omega$

⇒ what could be ideal?

to set this up active load!

Types of Active Loads → want a current source

Diode-Connected Enhancement Load:

to drive X'sistor

Depletion Load:

ancient & we can't consider this

Diode-Connected PMOS Load:

PMOS Current Source Load:

Norton Equivalent: ideal when $R_S = \infty$

Diode-Connected Enhancement Load

S.S. Ckt. \Rightarrow (do by inspection)

"Diode-Connected"

$R_L = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} = \frac{1}{g_m + g_{mb}}$
 $\approx 1-10k\Omega$
 $\approx \frac{1}{g_m}$

How about this?

S.S. Ckt. (hybrid- π)

$i_x = -g_m V_{gs} + g_{ds}(-V_{gs}) - g_{mb} V_{bs}$
 $= g_m (V_x - i_x R_D) + g_{mb} V_x$

$R_S = \frac{V_x}{i_x} = \frac{1 + g_m R_D}{g_m + g_{mb}} = \frac{1}{g_m + g_{mb}} + \frac{R_D}{1 + \eta}$

$\approx \frac{1}{g_m + g_{mb}} + R_D$

$R_S \approx \frac{1 + R_D}{1 + \eta}$

... and from the top:

S.S. Ckt. hybrid- π

do the analysis

$R_D = \frac{V_x}{i_x} = \frac{1}{g_m} + (1 + \eta) R_S \approx \frac{1}{g_m} + R_S$

Thus:

$$a_v = \frac{N_0}{N_s} \cdot \frac{N_2}{N_1} \cdot \frac{N_0}{N_2}$$

$$= (1) (-g_{m1} (r_{o1} || r_{o2})) \frac{g_{m4} (r_{o3} || r_{o4})}{1 + (g_{m4} + g_{mb4}) (r_{o3} || r_{o4})}$$

$$\therefore a_v = -g_{m1} (r_{o1} || r_{o2}) \left[\frac{g_{m4}}{g_{m4} + g_{mb4}} \right]$$

$C_H = C_{gd1} (1 + g_{m1} (r_{o1} || r_{o2}))$
 big! big! \therefore

$\tau_0 = [C_{gs1} + C_{gd1} (1 + g_{m1} (r_{o1} || r_{o2}))] R_s$ huge!

$\tau_2 = (C_{gd1} + C_{db1} + C_{gd2} + C_{db2} + C_{gs4}) (r_{o1} || r_{o2})$

These dominate!

$$\tau_3 = (C_{db3} + C_{gd3} + C_{sb4}) \left[\frac{1}{g_{m4} + g_{mb4}} \right]$$

$$\tau_{gs4} = C_{gs4} \left[\frac{(r_{o1} || r_{o2}) + (r_{o3} || r_{o4})}{1 + (g_{m4} + g_{mb4}) (r_{o3} || r_{o4})} \right] \times$$

from inspection formula
 but \rightarrow there's a zero, too, in MOS

$\frac{2}{g_{m4} + g_{mb4}}$

$$\omega_H = \frac{1}{\tau_0 + \tau_2 + \tau_3 + \tau_{gs4}}$$