

Lecture 8: Active Loads

Announcements:


- ↪ No Prof. Nguyen Office Hours on Monday or Thursday next week (on travel)
- ↪ There WILL BE lecture Tuesday, next week
- ↪ But NO LECTURE Thursday, next week???
- ↪ Make-up lecture will probably be Friday in a room and time TBA

Lecture Topics:

- ↪ Analysis of actively loaded circuits (continued)
- ↪ Current Sources

Last Time:


Ex. Multistage Actively Loaded MOS Ckt.

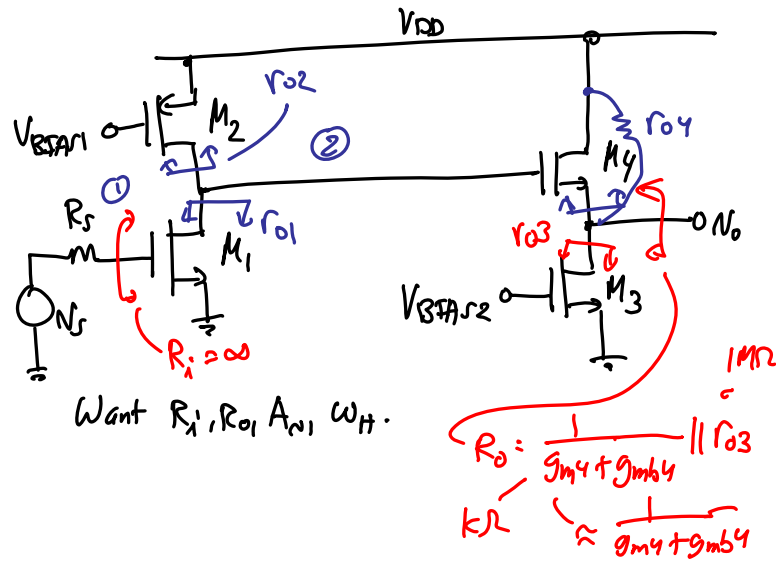

$$a_v = \frac{v_o}{v_s} = \frac{v_{o2}}{v_{o1}} \cdot \frac{v_o}{v_{o2}}$$

$$= (1) \cdot (-g_{m1} (r_{o2} || r_{o1})) \cdot \frac{g_{m4} (r_{o3} || r_{o4})}{1 + (g_{m4} + g_{mb4}) (r_{o3} || r_{o4})}$$

$$\therefore a_v \approx -g_{m1} (r_{o1} || r_{o2}) \left[\frac{g_{m4}}{g_{m4} + g_{mb4}} \right]$$

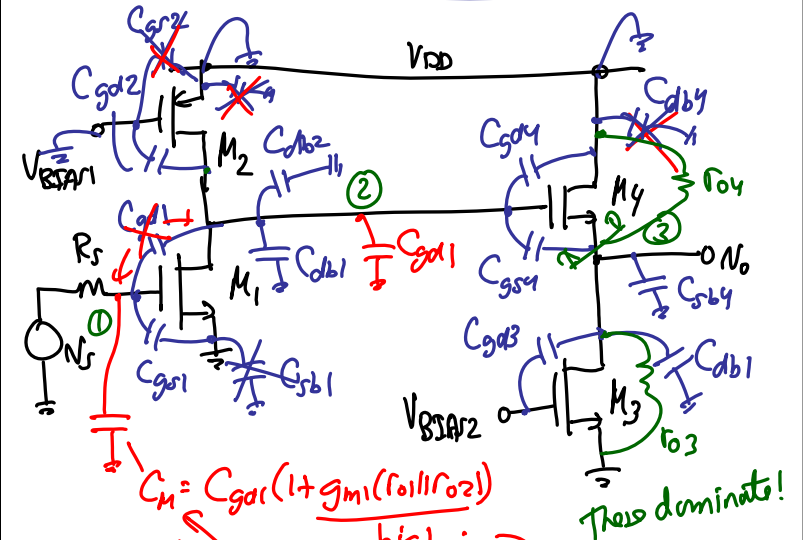

$$\tau_{O1} = [C_{gs1} + C_{gd1}(1 + g_{m1}(r_{o1} || r_{o2}))] R_s \quad \leftarrow \text{huge!}$$

$$\tau_{O2} = (C_{gd1} + C_{db1} + C_{gd2} + C_{db2} + C_{gd4})(r_{o1} || r_{o2})$$

$$\tau_{\textcircled{3}} = (C_{db3} + C_{gs3} + C_{sb4}) \left[\frac{1}{g_{m4} + g_{mb4}} \right]$$

$$\tau_{gs4} = C_{gs4} \left[\frac{(r_{o1} || r_{o2}) + (r_{o3} || r_{o4})}{g_{m4} + g_{mb4}} \right] \quad \times$$

from inspection formula
 but \rightarrow there's a zero, too, in MOS

$$\omega_H = \frac{1}{\tau_{\textcircled{1}} + \tau_{\textcircled{2}} + \cancel{\tau_{\textcircled{3}}} + \cancel{\tau_{gs4}}}$$

Ex. Carcode Drive & Load

$$R_o = r_{o2} (1 + (g_{m2} + g_{mb2}) r_{o1}) || r_{o3} (1 + (g_{m3} + g_{mb3}) r_{o4})$$

$$\sim g_{m2} r_{o1} r_{o2} \quad \sim g_{m3} r_{o3} r_{o4}$$

$$\sim \frac{g_m r_o^2}{2} \text{ } \} \text{ huge!}$$

$r_o \approx \frac{1}{\lambda I_D}$
 $g_{m0} \sim 100$ $500k\Omega \rightarrow 1M\Omega \rightarrow 100M\Omega$

This is actually could be significant, but let's ignore for now

Get gain: $\frac{V_o}{V_s} = \frac{N_0}{N_s} \cdot \frac{N_2}{N_1} \cdot \frac{N_3}{N_2} = \frac{N_0}{N_s}$

$\frac{N_0}{N_s} = (1) \left(-g_{m1} \left(\frac{1}{g_{m2} + g_{mb2}} \right) \right) \left(\frac{1}{g_{m3} + g_{mb3}} \right) R_o$

$= -g_{m1} R_o$

same as C.S., but w/ $R_o = \text{huge!}$

Get the dominant pole: (use OCF analysis)

$V_{GS1} - \text{Generator}$
As we will see, this node won't move much! (voltage)

Current source load

$C_M = (1 - \frac{1}{A}) C_{gd1} = 2C_{gd1}$

$C_M = (1 - \frac{1}{A}) C_{gd1} = 2C_{gd1}$

$\tau_1 = (2C_{gs1} + C_{gs1}) R_s$

$\tau_2 = (2C_{gd1} + C_{db1} + C_{sb2} + C_{gs2}) \left(\frac{1}{g_{m2} + g_{mb2}} \right)$

$\tau_3 = (C_{gd2} + C_{db2} + C_{db3} + C_{gd3}) R_o$

$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3}$

might need to include if R_o large

dominant!

$\omega_H = \frac{1}{\tau_3}$

large distance

$\omega_{p1} = \omega_H$

ω_{p2}

ω_H

short

$\frac{1}{2}$

C_3 no longer flat!

$\omega \uparrow \rightarrow \downarrow$

$\frac{V_o}{V_s} \approx 1$

$R_o \parallel \frac{1}{j\omega C_3}$

R_s

M_2

M_1

C_2

C_3

2nd pole (3rd pole),

$$\omega_{p2} = \frac{1}{\tau_0 + \tau_0}$$

over for Current Sources ...

Transistor Current Sources

How can a transistor implement a current source?

Ideal Current Source \Rightarrow Actual Current Source \Rightarrow Bipolar Forward-Active Transistor Current Source

$R_0 = \infty \rightarrow$ ideal

exponential

$$I_0 = I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

Very stable if $V_{BE} = \text{const.}$ & $V_A = \text{large}$

Note that V_{BE} must be very accurate due to exponential \rightarrow to several sig. figs.

e.g., $V_{BE} = 0.68745V$

Can this really be accurate to many sig. figs.?

Again, very stable if $V_{BE} = \text{const.}$ & $\lambda = \text{small}$

Problem: need to generate a stable V_{BE}

Saturated MOS Transistor Current Source

$$I_0 = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{BEAS} - V_t)^2 (1 + \lambda V_{DS})$$


We now focus on methods for generating V_{BSAS} .
But how do we get this degree of precision using a transistor ckt?

Solution: \rightarrow

Replica Biasing (a simple & effective approach)

- ① Generate the desired current.
 - ② Push the current through a χ istor and allow it to reach a stable bias pt.
 - ③ Use this stable bias pt. as V_{BSAS}
- \rightarrow this can be very precise!

One simple approach:

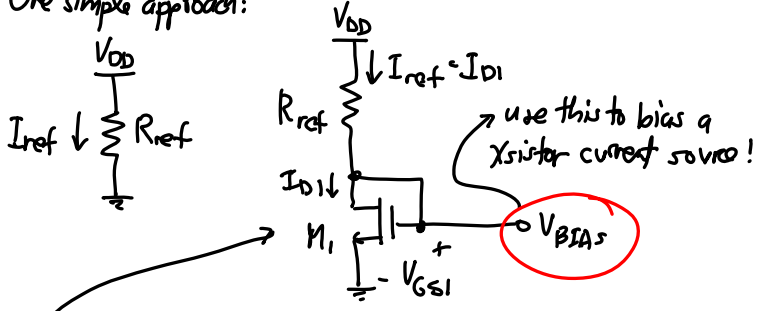


A diode-connected χ istor is always in saturation and will basically bias itself to support the needed current!

$$I_{ref} = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$$

\uparrow
 V_{BSAS}

Now, can distribute this V_{BSAS} to the gates of many MOS transistor current sources!

Ex. Simple MOS Current Source

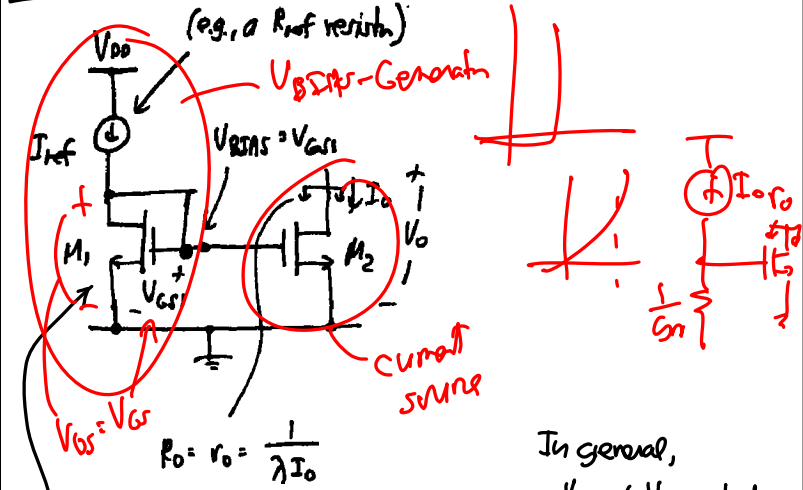

In general,
Diode-connected χ istor \rightarrow saturation:
 $I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{BSAS} - V_t)^2 (1 + \lambda V_{DS1})$
 $I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{BSAS} - V_t)^2 (1 + \lambda V_{DS2})$
if λ is small, then little difference in I_{D1} & I_{D2}

① Case: matched M_1 & $M_2 \Rightarrow I_O = I_{ref}$

② Case: M_1 & M_2 scaled wr to each other

$$\Rightarrow I_O = I_{ref} \frac{(W/L)_2}{(W/L)_1}$$

\Rightarrow use $L_1 = L_2$ for better accuracy, then:

$$\frac{I_O}{I_{ref}} = \frac{W_2}{W_1}$$

Note: for better accuracy, should use multiple copies of one device when scaling currents \rightarrow reduces edge effects!

Ex: Layout for a Doubling Current Source

A single V_{BSAs} generator can now serve numerous current sources:

How about bipolar?

Simple Bipolar Current Source

KCL here to get $I_{C2} = f(I_{ref})$

Current sources

VBSAs-Generator

Assume Q_1 & Q_2 are matched. i.e., $V_A = \infty$

$V_{BE1} = V_{BE2} \rightarrow I_{C1} = I_{C2} = I_O$ (neglecting V_A 's)

KCL: $I_{ref} = I_{C1} + I_{B1} + I_{B2} = I_{C1} \left(1 + \frac{2}{\beta}\right)$

$\therefore I_{C1} = I_{C2} = I_O = \frac{I_{ref}}{1 + \frac{2}{\beta}} \rightarrow I_O \approx I_{ref}$

and $I_{ref} = \frac{V_{cc} - V_{BE(on)}}{R_{ref}}$ $R_{O1} = R_{O2}$ can say error $\sim \frac{2}{\beta}$

Again, a single V_{BSAs} generator can serve many current sources throughout the IC chip:

Use a single V_{BSAs} for all curr.!

$I_{ref} = I_{C1} + I_{B1} + I_{B2} + I_{B3} + \dots + I_{Bn}$

[Identical X 's exist] $\Rightarrow I_{ref} = I_{C1} \left(1 + \frac{n}{\beta}\right)$

$\Rightarrow I_O = I_{C1} = \frac{I_{ref}}{\left(1 + \frac{n}{\beta}\right)}$

Problem: error $\sim \frac{n}{\beta}$ increases as n (I_O divider from I_{ref} , and % deviation depends on n .)

This was not the case for MOS!

How can one reduce the error?

To reduce the error term, use a **Buffered V_{BE} Generator**

Add a buffer resistor to attenuate base currents from resistor current sources.

This can now drive the base currents of many bipolar-transistor current sources (i.e., active loads).

$$I_{ref} = I_{C1} + I_{B1A}$$

$$I_{B1A} = \frac{I_{B1} + I_{B2} + \dots + I_{Bn}}{\beta + 1} \approx \frac{n I_{C1}}{\beta(\beta + 1)}$$

[Assuming identical X -sistors]

binomial approx.

$$I_{ref} = I_{C1} \left(1 + \frac{n}{\beta(\beta + 1)} \right)$$

$$I_0 = I_{C2} = \frac{I_{ref}}{1 + \frac{n}{\beta(\beta + 1)}} \approx I_{ref} \left(1 - \frac{n}{\beta^2} \right)$$

Note: Now, $I_{ref} = \frac{V_{cc} - 2V_{BE(on)}}{R_{ref}}$

Problem: For power savings reasons, oftentimes very small bias currents are needed, on the order of $5\mu A$. This might force for large an R_{ref} in the above bipolar V_{BE} generator.

Ex. $I_C = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$

1x device

10x emitter

10x device

i.e., larger emitter area: \rightarrow layout like this to get more accurate ratio.

If Q_1 is 10x larger than Q_2 .

$$\therefore I_{S1} = 10 I_{S2} \rightarrow I_0 \approx I_{ref}/10$$

$$\therefore I_0 = \frac{V_{cc} - V_{BE(on)}}{10 R_{ref}} \rightarrow R_{ref} = \frac{V_{cc} - V_{BE(on)}}{10 I_0}$$

this helps to lower R_{ref} , but is it enough?

Ex. $I_0 = 5\mu A$, $V_{cc} = 30V$

$$R_{ref} \approx \frac{30}{5\mu} = 600k\Omega \leftarrow \text{That's way too big!}$$

(Yes, there's only one of them on the chip, but this takes up too much space!)

The Low Current Solution: **Widlar Current Source**

\Rightarrow scale $I_{C2} = I_0$ by reducing V_{BE2} (relative to V_{BE1}):

Do this by emitter degenerating Q_2 via R_2

$I_{C2} = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) < I_{C1}$

$$V_{BE1} = V_{BE2} + V_{R_2} = V_{BE2} + \frac{1}{\alpha} I_{C2} R_2 \approx V_{BE2} + I_{C2} R_2$$

$$I_{C2} R_2 = V_{BE1} - V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$I_{C2} R_2 = V_T \ln \frac{I_{C1}}{I_{C2}} \quad (\text{Assuming } Q_1 \text{ \& } Q_2 \text{ are matched.})$$

$$I_0 R_2 = V_T \ln \frac{I_{ref}}{I_0}$$

Rule of Thumb: $V_{R_2} = I_{C2} R_2$

V_{R_2}	$I_{C2} = I_0$
18 mV	$\frac{1}{2} I_{ref}$
42 mV	$\frac{1}{5} I_{ref}$
60 mV	$\frac{1}{10} I_{ref}$
120 mV	$\frac{1}{100} I_{ref}$

→ Just example again

Ex: scale by 100x using Widlar source

$$V_{BE1} - V_{BE2} = 120 \text{ mV} \rightarrow R_2 = \frac{120 \text{ mV}}{5 \mu\text{A}} = 24 \text{ k}\Omega$$

$$I_{ref} = 500 \mu\text{A} \rightarrow R_{ref} = \frac{30 \text{ V}}{500 \mu\text{A}} = 60 \text{ k}\Omega$$

More reasonable than 600kΩ before.
 If want smaller, scale by 100x instead.

Another advantage of the Widlar: larger $R_0 \therefore$ a more ideal current source:

$$R_0 = r_{o2} (1 + g_{m2} R_2)$$