

**Lecture 10: High Swing Current Sources**

**Announcements:**

- ↪ HW#3 due today
- ↪ HW#4 online
- ↪ Lab#2 online
- ↪ Monday Labs: due to holiday next week, shift to the following Monday
- ↪ Monday Lab#1's are due in the 140 Box on Tuesday next week
- ↪ No lecture during our regular time on Thursday
- ↪ Make-up lecture still TBA ... either Thursday evening or Friday sometime, I hope

**Lecture Topics:**

- ↪ Output Swing (Headroom)
- ↪ High Swing Current Sources
- ↪ Current Source Matching Considerations

**Last Time:**

- Reviewed current sources using prepared lecture material
- Finished with Widlar current sources

over

**Issue: Output Swing (Headroom)**  $arriving V_{GS} = \frac{V_{DD}}{2}$

$N_{ov} = |V_{GS2} - V_{ov2}|$

$V_{ovswing} = V_{ovmax} - V_{ovmin}$

**$I_D$  vs.  $V_{DS}$  Characteristics:**

linear  $\rightarrow$  saturation

slope:  $\frac{1}{r_o} = \text{small} \therefore r_o = \text{big!}$

gain  $\sim g_m r_o = \text{big}$

$V_{ovsat} = V_{GS} - V_{t}$  (for long-channel)

different for short channel

slope:  $\frac{1}{r_o'} = \text{large} \therefore r_o' = \text{small}$

$\therefore \text{gain} \sim g_m r_o' = \text{small}$

$V_{ovsat} = V_{GS1} - V_{t1} = V_{ov} = \Delta V = V_{ov}$

overdrive voltage

for long-channel devices

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{t})^2$$

$$V_{ovsat} = V_{ov} = \Delta V = V_{DD} - V_{GS} - V_{t} = \sqrt{\frac{2 I_D}{\mu_n C_{ox} (\frac{W}{L})}} = V_{ov}$$

The min. voltage that still keeps  $M_1$  as a good current source (i.e.,  $R_o = \text{large}$ )

$$V_{om1h} = V_{Dsat} = V_{ov1}$$

$\therefore$  the output swing:

$$V_{o, \text{swing, pp}} = V_{DD} - V_{ov1} - V_{ov2}$$

↑  
peak-to-peak

Noise

$v_{i, \text{noise}}$

$V_{ov2} = |V_{GS2} - V_{Dsat2}|$

$V_{o, \text{swing}} = V_{om1h} - V_{om1l}$

Dynamic Range = DR =  $\frac{\text{maximum output signal}}{\text{minimum input signal}}$

simple current source  $\rightarrow$  one  $K_n$  ratio

determined by output swing

determined by noise!

Ex. Cell Phone

very clear to you

higher  $R_o$

What about better current sources, like the Cascode current source?

$V_{ov3} = 2V_{ov2}$

$V_{ov1h} = 2V_{ov}$

current source  $\rightarrow$  large  $R_o$

How can we generate these?



