

Lecture 10: High Swing Current Sources I

• Announcements:

↳ HW#4 due tomorrow

↳ HW#5 online soon

↳ Lab#2 online

— This is a hardware lab, so you will need to use the lab to make measurements

— You are all being added to the access list for 353 Cory

↳ Those taking 240A will soon get additional HW assignments to supplement the regular ones


• Lecture Topics:

↳ Output Swing (Headroom)


↳ High Swing Current Sources

• Last Time:



Issue: Output Swing (Headroom)

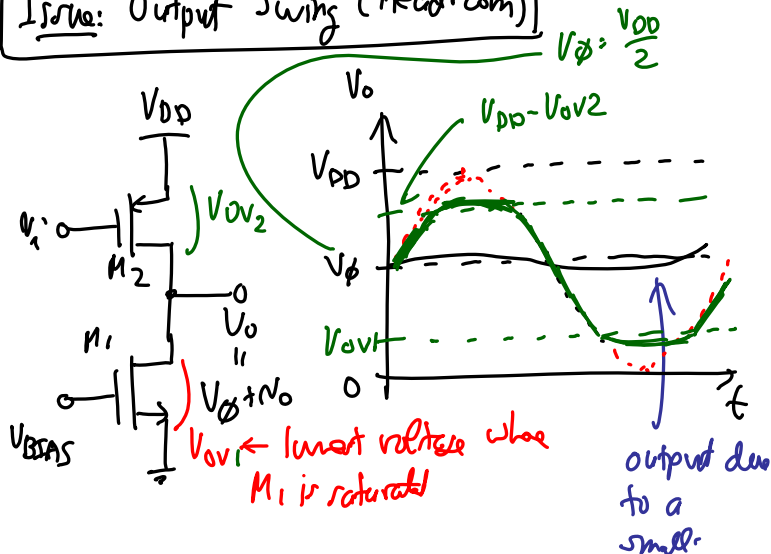

I_D vs. V_{DS} Characteristic:

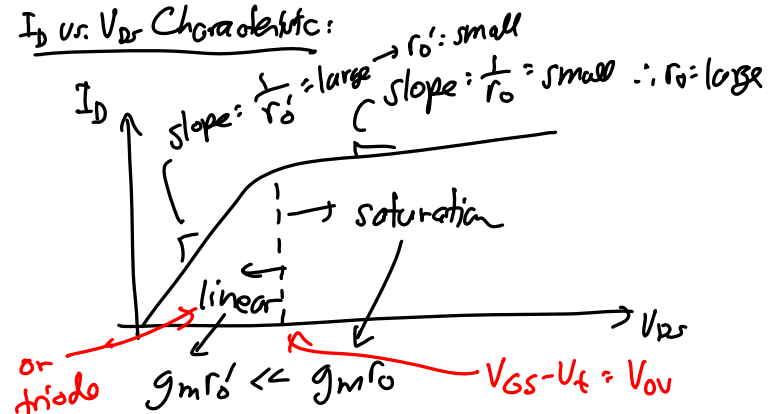

Ex: Cell Phone

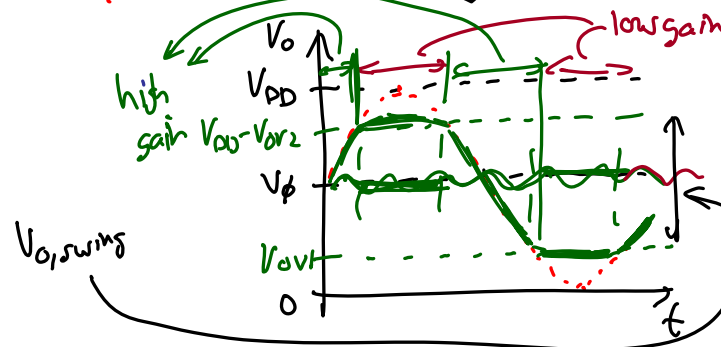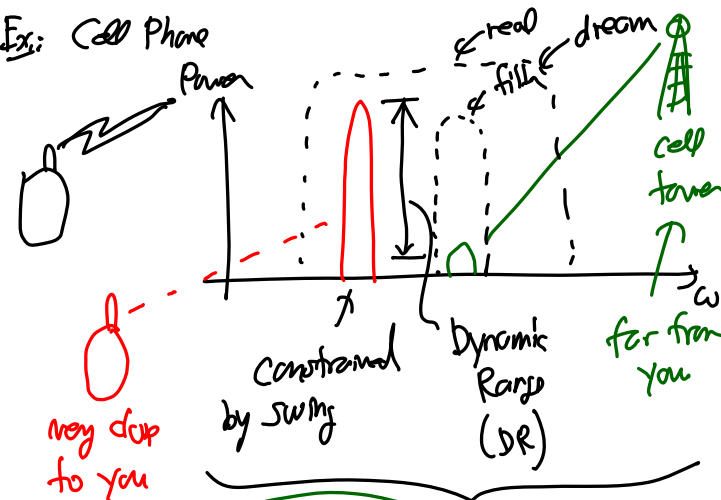

What is V_{ov} ?

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{ov} = \Delta V = V_{GS} - V_t = \sqrt{\frac{2 I_D}{\mu_n C_{ox} (\frac{W}{L})}} = V_{ov}$$

'overdrive'
voltage

The min. voltage that still keeps M_1 as a good current source (i.e., R_o large, M_1 saturated)

$$V_{omn} = V_{ov}$$

\therefore the output swing:


$$V_{o, swing, pp} = V_{DD} - V_{ov1} - V_{ov2}$$

↑
peak-to-peak

What about better current sources? (i.e., w/ higher R_o)

Ex. Cascode current source load + cascode drive

What is $V_{o, swing}$?

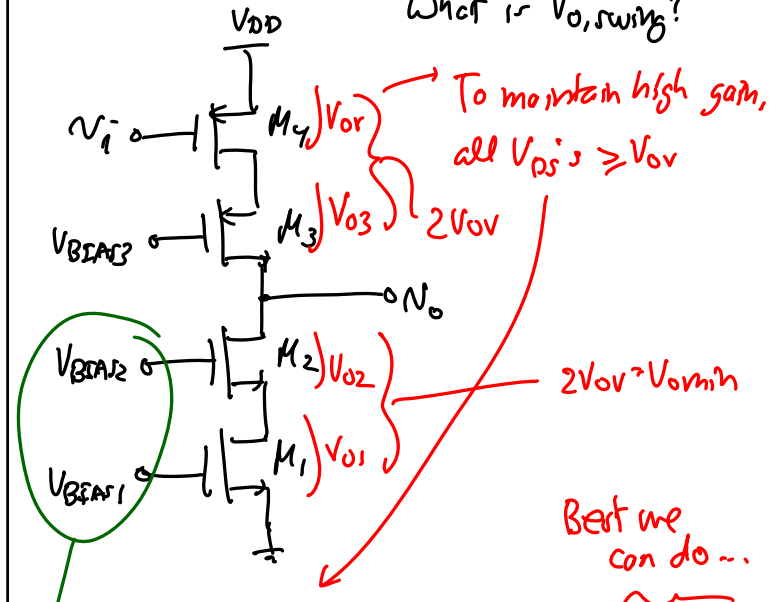

$$V_{o, swing} = V_{DD} - V_{ov1} - V_{ov2} - V_{ov3} - V_{ov4} = V_{DD} - 4V_{ov}$$



$$\approx 2 - 4(0.2) = 1.2V$$

How do we generate those?

Answer: make a V_{BIAS} -generator


simplest way: replica bias

(i.e., use a simple cascode)

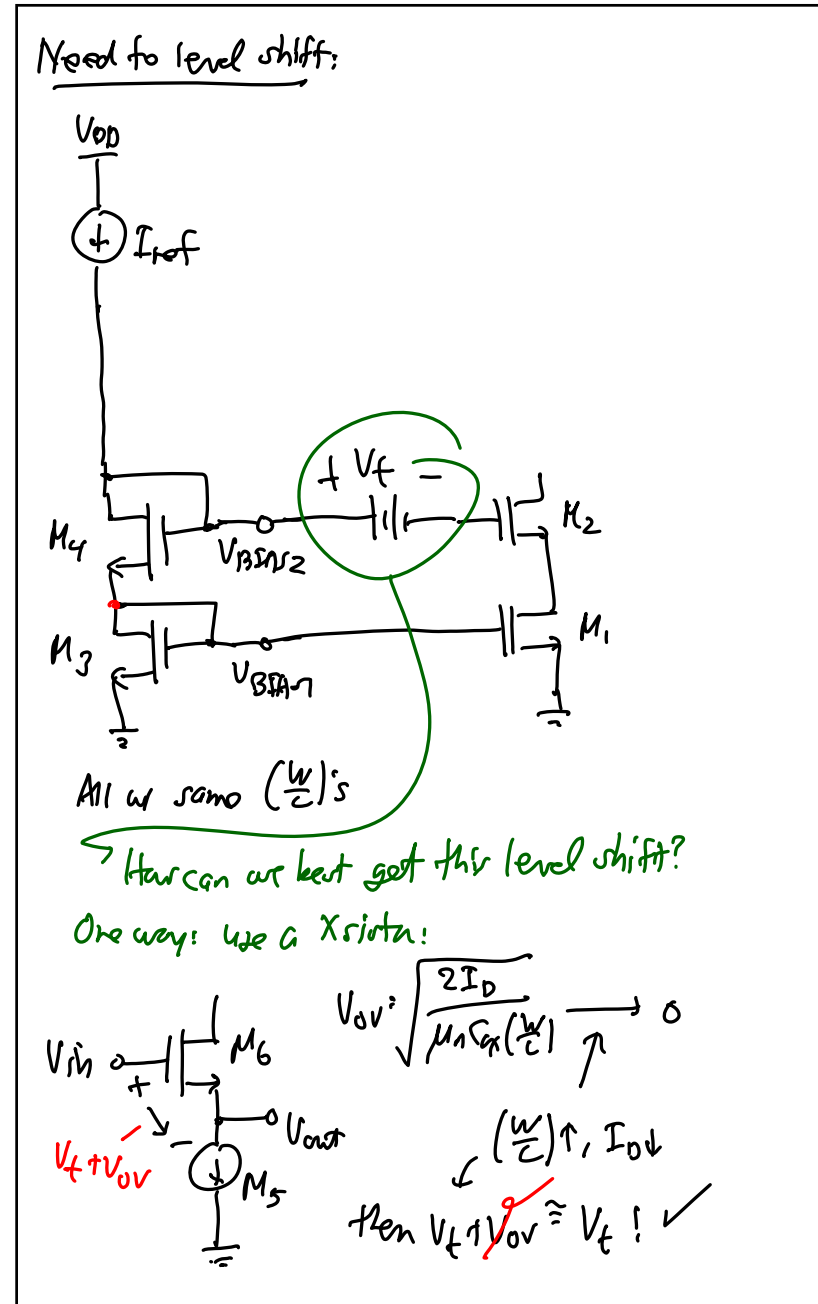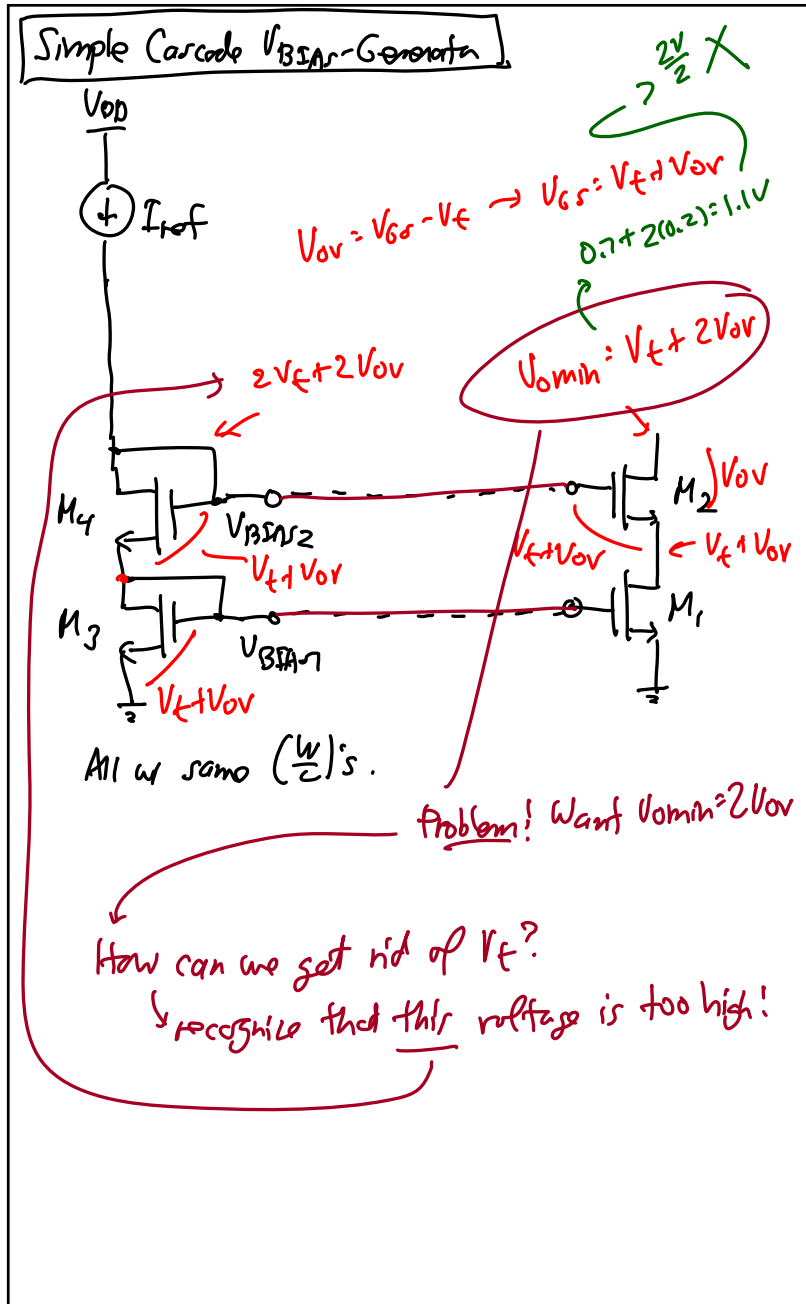



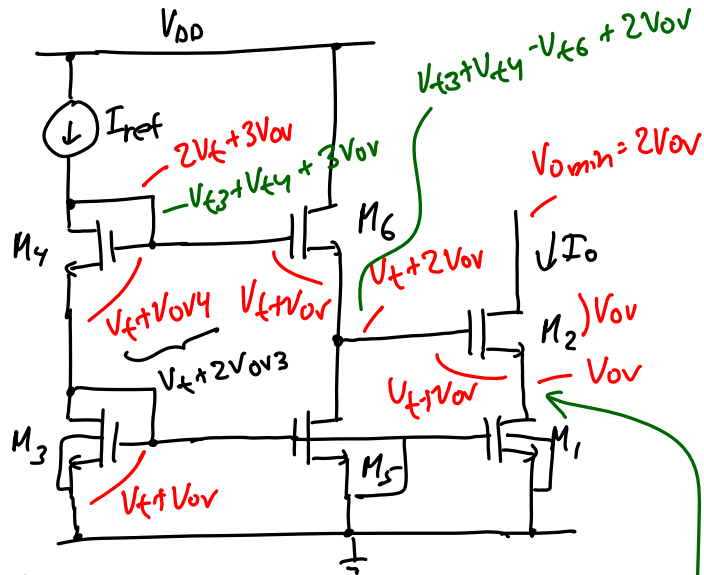Problem: Body effect M_4, M_6, M_2
increases their V_t 's



$$V_{t4} \approx V_{t6} \rightarrow \begin{cases} V_{S4} = V_t + V_{ov} \\ V_{S6} = V_t + 2V_{ov} \end{cases} \Rightarrow V_{t6} > V_{t4}$$

$$V_t = V_{t0} + \gamma \sqrt{V_{S4} + \phi}$$

Could be a problem if it makes $V_{DS1} < V_{ov}$
($M_1 \rightarrow$ triode)

What exactly is the voltage here?

$$V_{t3} + V_{t4} - V_{t6} - V_{t2} + V_{ov}$$

$$\underbrace{(V_{t4} - V_{t6})}_{(-)} + \underbrace{(V_{t3} - V_{t2})}_{(-)} + V_{ov} < V_{ov}$$

$\therefore M_1$ is not saturated!

BIG PROBLEM!

Solutions:

① Tie the wells of M_4, M_6, M_2 to their sources.

$$V_t = V_{t0} + \gamma \sqrt{V_{S4}} = V_{t0}$$

But don't want to do this \rightarrow too much die area consumed \rightarrow cost \uparrow


② Bias M_4 so that $V_{GS4} \approx V_t + 2V_{ov}$

$$\text{e.s., } V_{GS4} = V_t + 3V_{ov}$$

\downarrow

$$\left(\frac{W}{L}\right)_4 = \frac{1}{9} \left(\frac{W}{L}\right)_3$$

\rightarrow safety margin!

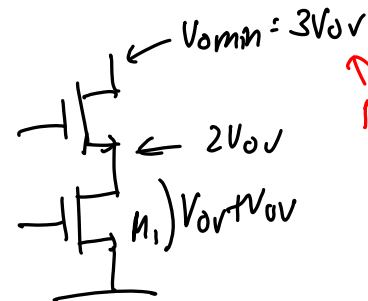

Not optimum, but safe $\rightarrow M_1$ stays in saturation

Issue: $I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $\lambda \uparrow$ as channel length \downarrow

If $V_{DS1} \neq V_{DS3}$

$I_O = \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS3})} I_{ref} \rightarrow I_O \neq I_{ref}$

Solution: Use alternative biasing scheme.

Alternate Biasing Scheme for Cascode

