

Lecture 14: Vos & Finite Gain-BW

• Announcements:

- ↳ HW#6 due tomorrow
- ↳ HW#7 online soon
- ↳ Pre-Lecture materials online
- ↳ Midterm will be on the date specified in your syllabus: Thursday, March 21, 3:30-5 p.m. in 390 Hearst Mining Building


• Lecture Topics:

- ↳ Input Offset Voltage (Vos)
- ↳ Op Amp Finite Gain-BW

• Last Time:

Vos of a mismatched SCP


Objective: Derive an expression for Vos.

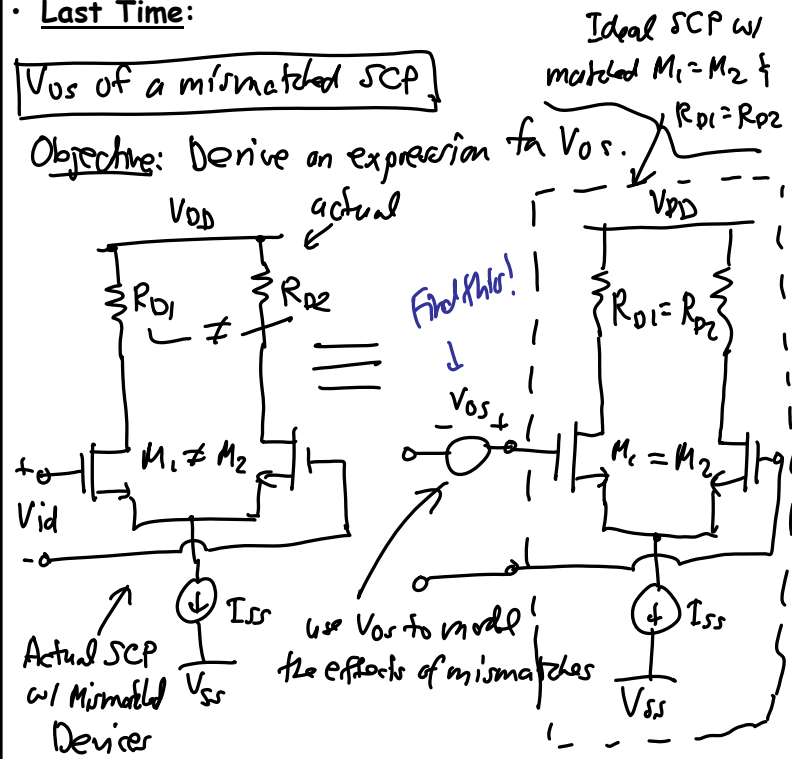

Vos arises due variations in:

- ① X_{offset} for M_1 & $M_2 \rightarrow \frac{W}{L} \{ V_t \text{ vary}$
- ② $R_{D1} \neq R_{D2} \rightarrow$ cause variation in gain

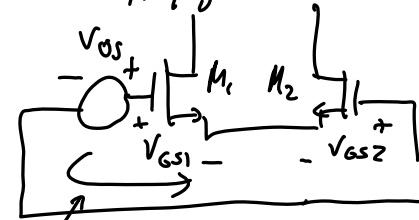Definition: $V_{OS} = V_{id}$ needed to get $V_{od} = 0V$ when applying $0V$ to both inputs



KVL: $V_{OS} - V_{GS1} + V_{GS2} = 0$

$$\therefore V_{OS} = V_{GS1} - V_{GS2} = V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\begin{aligned} \Delta I_D &= I_{D1} - I_{D2} & \Delta\left(\frac{W}{L}\right) &= \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2 \\ I_D &= \frac{I_{D1} + I_{D2}}{2} & \left(\frac{W}{L}\right) &= \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right] \end{aligned}$$

$$\begin{aligned} \Delta V_t &= V_{t1} - V_{t2} & \Delta R_D &= R_{D1} - R_{D2} \\ V_t &= \frac{1}{2}(V_{t1} + V_{t2}) & R_D &= \frac{1}{2}(R_{D1} + R_{D2}) \end{aligned}$$

Rearranging:

$$\begin{array}{l|l|l} I_{D1} = I_D + \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} & V_{t1} = V_t + \frac{\Delta V_t}{2} \\ I_{D2} = I_D - \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} & V_{t2} = V_t - \frac{\Delta V_t}{2} \end{array}$$

Substituting into (1): $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}}$$

$$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right] \rightarrow \frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right]$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1+x)^m \xrightarrow{\eta \text{ small}} 1 + m\eta$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} - 1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{OS} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2}$

mismatch in I_D must be opposite that of R_D

$$\therefore \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D} \quad \text{Pay no attention to these signs}$$

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ - \frac{\Delta R_D}{R_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Mismatch

Scale mismatch

Geometric Variations (i.e., layout)

Bias Independent

small I_D or $\frac{W}{L} T$

$$\sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}}$$

$$V_{to} + \gamma(f(V_{OS}))$$

Easily possible for


$$\frac{\Delta R_D}{R_D} = (-) ; \frac{\Delta(W/L)}{(W/L)} = (-)$$

• Now, go through bipolar mismatch prepared material

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.

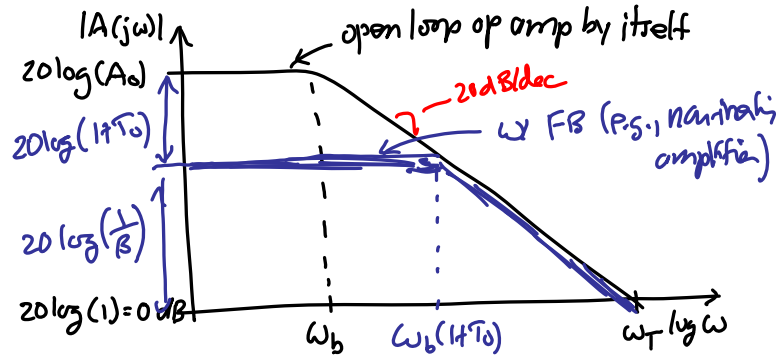In reality, the gain is given by: $A(s) = \frac{A_0}{1 + s/\omega_b}$



$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$ (= 0 dB)

At ω_T :

$$|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + (\frac{\omega_T}{\omega_b})^2}}$$

$$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \omega_T = A_0 \omega_b$$

Gain-Bandwidth Product


For $\omega \gg \omega_b$:

$$A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f} \quad \left[\begin{array}{l} \text{Integrate w/ time} \\ \text{Constant } T = \frac{1}{\omega_T} \end{array} \right]$$

The unity gain bandwidth f_T is usually specified on op amp data sheets. Knowing f_T , one can easily determine the op amp gain at a given frequency f .

Frequency Response of Closed Loop Amplifiers

Example. Non-Inverting Amplifier

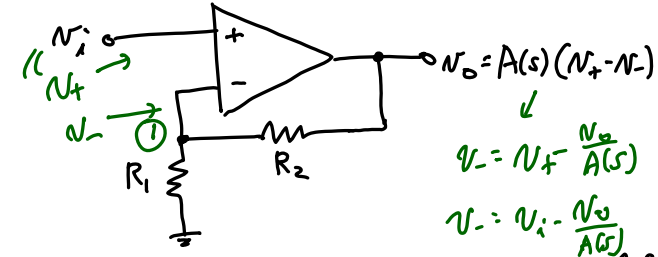

Find an expression for the gain as a function of frequency.


① Brute force derivation:


$$\text{KCL } \textcircled{1}: \frac{N_o - N_-}{R_2} = \frac{N_-}{R_1} \rightarrow \frac{N_o}{R_2} = N_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{N_o}{R_2} \left(N_i - \frac{N_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{N_o}{N_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$$

$$\left[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{N_o}{N_i}(s) = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b} \left(\frac{R_1 + R_2}{R_1} \right)}$$

② More insightful way to do this:

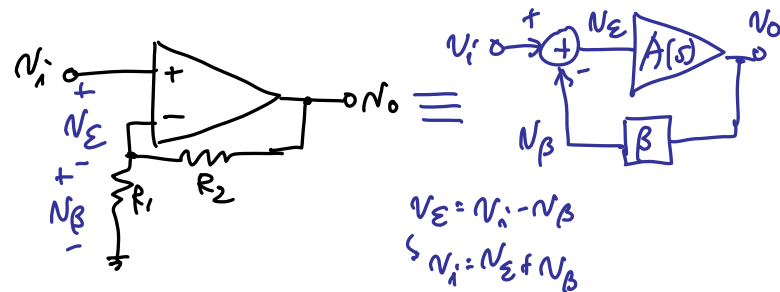

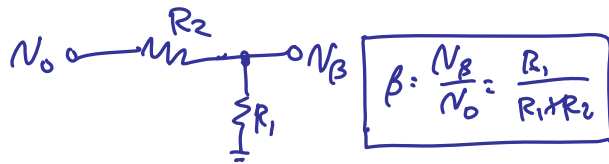

Recall from previous FB analysis:

$$\frac{V_o}{V_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$\left[A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{V_o}{V_i}(s) = \frac{A_o}{1 + \beta \left(\frac{A_o}{1 + \frac{s}{\omega_b}} \right)}$$

if $\beta A_o \gg 1 \rightarrow \frac{1}{\beta}$

$$\frac{V_o}{V_i}(s) = \frac{A_o}{1 + \beta A_o} \cdot \frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_o)}}$$

"closed loop dc gain" term frequency shaping term

Plug in β :

$$\frac{V_o}{V_i}(s) \cong \frac{1}{\beta} \cdot \frac{1}{1 + \frac{s}{\omega_b \beta A_o}} = \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{1}{1 + \frac{s}{\omega_b A_o \left(\frac{R_1}{R_1 + R_2} \right)}} = \frac{V_o}{V_i}(s)$$

Observations:

① Closed loop DC gain = $\frac{A_o}{1 + \beta A_o} = \frac{A_o}{1 + T_o} \approx \frac{A_o}{T_o}$
 i.e., the closed loop gain is reduced from the open loop gain by $1 + T_o \rightarrow$ show this on graph
 $[T_o \gg 1]$

② Alternatively, closed loop DC gain $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta} \quad [T_o \gg 1]$

③ ω_{-3dB} has increased from $\omega_b \rightarrow \omega_b(1 + \beta A_o) = \omega_b(1 + T_o)$
 To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!

④ Gain-BW Product = $\frac{A_o}{1 + \beta A_o} \omega_b(1 + \beta A_o) = A_o \omega_b = \omega_T$
 \therefore the Gain-BW product remains the same for the open & closed loop FB cases!