

### Lecture 15: High Gain Op Amps

#### Announcements:

- ↪ Midterm will be on the date specified in your syllabus: Thursday, March 21, 3:30-5 p.m. in 390 Hearst Mining Building
- ↪ No lecture the day of the midterm
- ↪ HW#7 due this coming Friday
- ↪ HW#8 will be available Thursday and due Tuesday next week (I know, but this will help you on the midterm)

#### Lecture Topics:

- ↪ High Gain Op Amps
- ↪ Slew Rate

#### Last Time:

- First pass on feedback

#### Observations:

- ① Closed loop DC gain =  $\frac{A_o}{1+\beta A_o} = \frac{A_o}{1+T_o} \approx \frac{A_o}{T_o}$   
 i.e., the closed loop gain is reduced from the open loop gain by  $1+T_o \rightarrow$  show this on graph  $[T_o \gg 1]$

- ② Alternatively, closed loop DC gain  $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta} \quad [T_o \gg 1]$

- ③  $\omega_{-3dB}$  has increased from  $\omega_b \rightarrow \omega_b(1+A_o\beta) = \omega_b(1+T_o)$


- ④ Gain-BW Product =  $\frac{A_o}{1+\beta A_o} \omega_b(1+\beta A_o) = A_o \omega_b = \omega_T$   
 $\therefore$  the Gain-BW product remains the same for the open & closed loop FB cases!

### High Gain Op Amps

How can we increase gain?

- ① Cascode
- ② Cascode Amplifiers
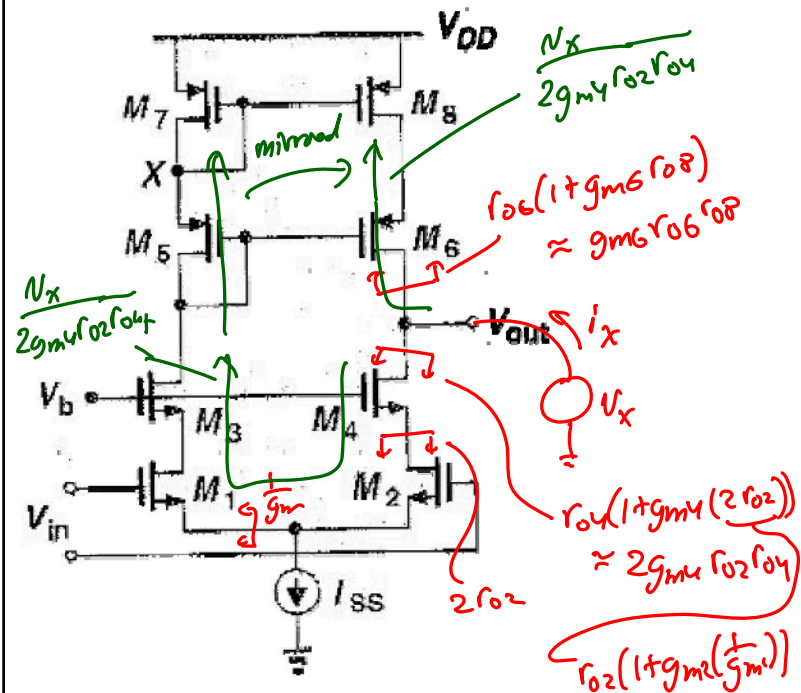
### Telescopic Op Amp w/ Single-Ended Output




Get  $R_o$ :

$$i_x = \frac{N_x}{g_{m6} r_{o6} r_{o8}} + \frac{N_x}{2g_{m4} r_{o2} r_{o4}} + \frac{N_x}{2g_{m1} r_{o2} r_{o4}}$$

$$\frac{i_x}{N_x} = \frac{1}{g_{m6} r_{o6} r_{o8}} + \frac{1}{g_{m4} r_{o2} r_{o4}}$$
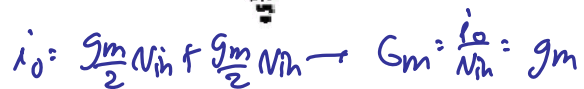
$$R_0 = (g_{mfp} r_p^2) \parallel (g_{mvr} r_{ov}^2)$$



hugo R! hugo R!  
Gern → BIG!

[illegible]

↳ Contributor dominant pole:  $\omega_H = \frac{1}{R_{oC_L}}$



① Limited output swing:

Vomih:  $V_{ovs5} + V_{ov2} + V_{ov4}$

Vorsung: Vomer-Vornrin

Problem, Not enough swing!  
(too many transistors stacked)

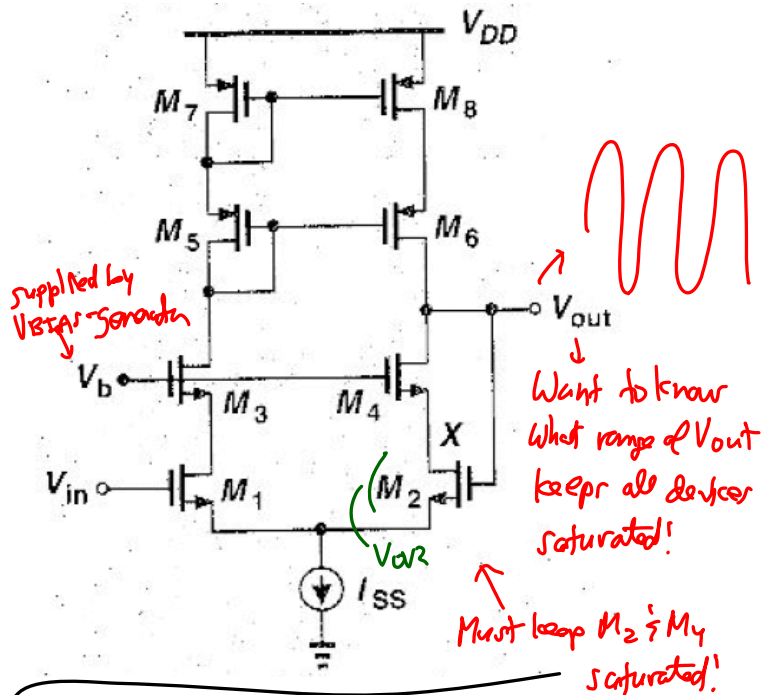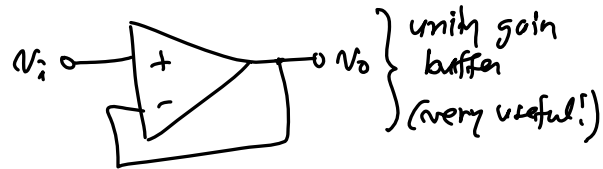Problem (2): Difficult to tie input to output!




M4: Need  $V_{out} \geq V_b - V_{GS4} + V_{OV4} = V_b - V_{t4} - V_{OV4} + V_{OV4}$

$$\therefore V_{out} \geq V_b - V_{t4}$$

M2: Need  $V_{out} \leq V_X - V_{GS2} + V_{t2} + V_{OV2}$

$$V_{out} \leq V_b - V_{t4} - V_{OV4} + V_{t2} \approx V_b - V_{OV4}$$


$V_{t2} \approx V_{t4}$

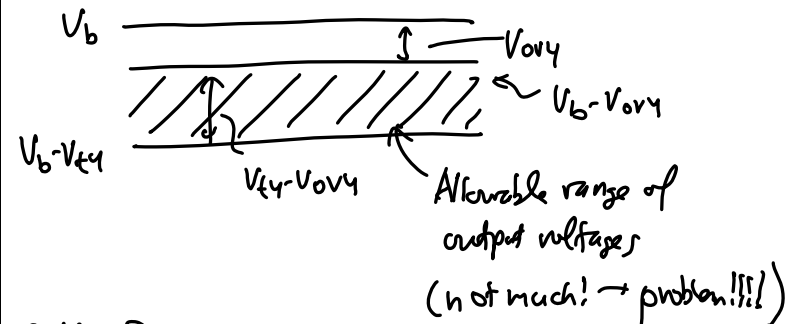

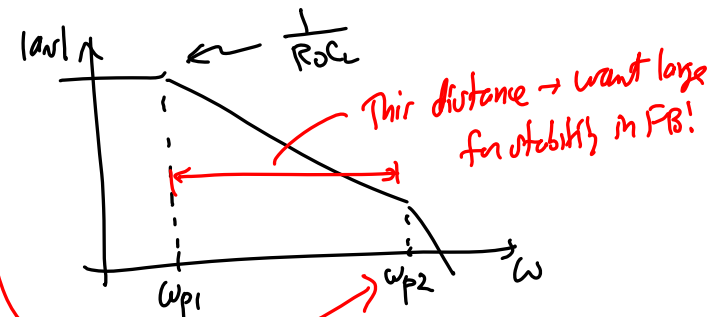Problem (3):


Low freq. non-dominant pole associated w/ "mirror" node  $\rightarrow$  will hurt stability in a FB ckt!  
(we'll cover this later)

Soln. fully-differential, fully-balanced op amp



Another Soln: 2-stage op amp

Classic 2-Stage Op Amp

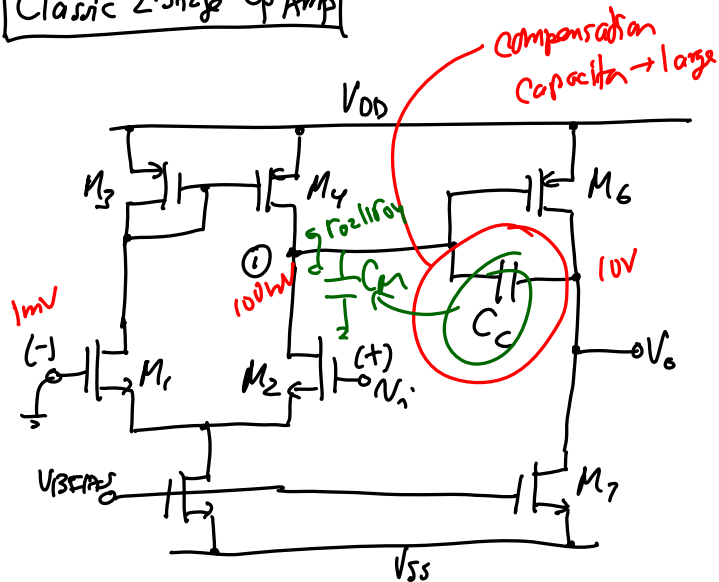


Gain:

1st Stage:  $a_{v1} = \frac{V_{o1}}{V_i} = -g_{m2}(r_{o2} || r_{o4})$

2nd Stage:  $a_{v2} = \frac{V_o}{V_{o1}} = -g_{m6}(r_{o6} || r_{o7})$

$a_v = a_{v1} a_{v2} = g_{m2}(r_{o2} || r_{o4}) g_{m6}(r_{o6} || r_{o7})$

Freq. Response:

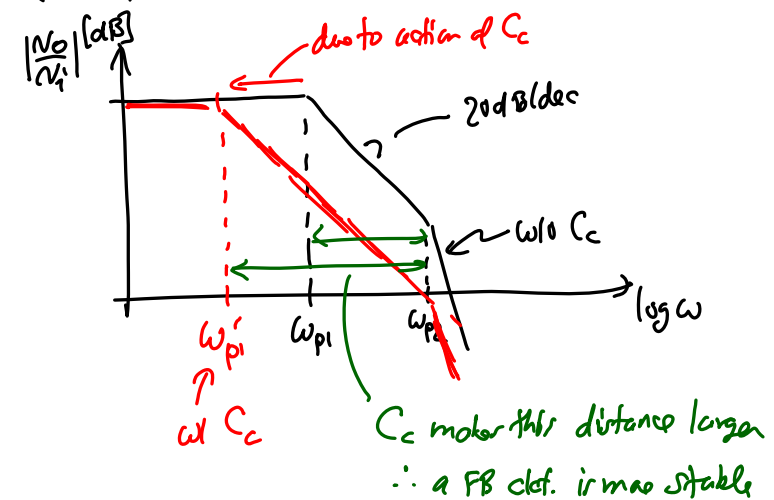

Dominant Pole:

$$\omega_{p1} \approx \omega_H = \frac{1}{(r_{o2} || r_{o4}) (1 + g_{m6}(r_{o6} || r_{o7})) C_c}$$

Miller Effect

Output Swing:

$V_{oswing} = V_{DD} - V_{SS} - |V_{ov6}| - V_{ov7}$