

### Lecture 17: Output Stages

#### Announcements:


- ↳ Midterm's graded - will pass back at the end of lecture
- ↳ HW#9 will be online on Thursday
- ↳ Lab#2 due this Friday
  - Grade depends heavily on the report
  - Make sure you spend enough effort on the report per your TA's requirements
- ↳ Lab#3 update online (update for 240A folks)
- ↳ No lecture next Tuesday - we will make this up by going 2 hours the next three lectures

#### Lecture Topics:

- ↳ Stability

#### Last Time:

#### Settling Time

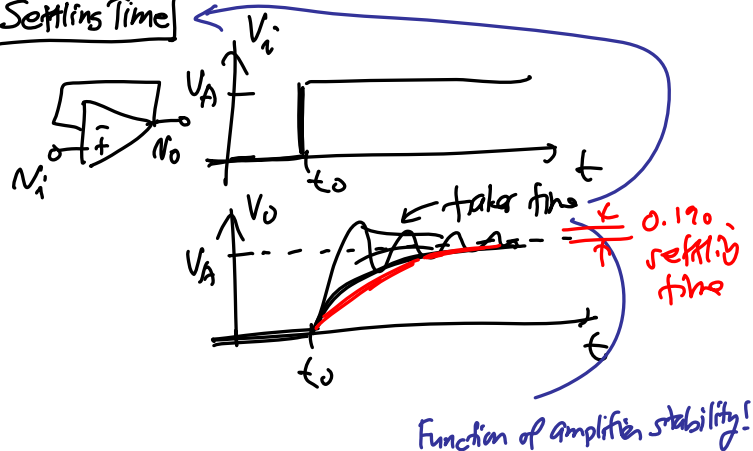


#### Stability & Compensation in Op Amps

In general, op amps are used in neg. FB loops. → can cause instability!

#### Reasons:


- ① Feedback sets the biasing → no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity or input range.  
(e.g., emitter degeneration is a type of FB)
- ④ Gain determined by external FB components → more accurate than op amp gain.
- ⑤ FB sets  $R_i$  and  $R_o$ .
- ⑥ FB can improve temperature stability.

#### Stability & Compensation

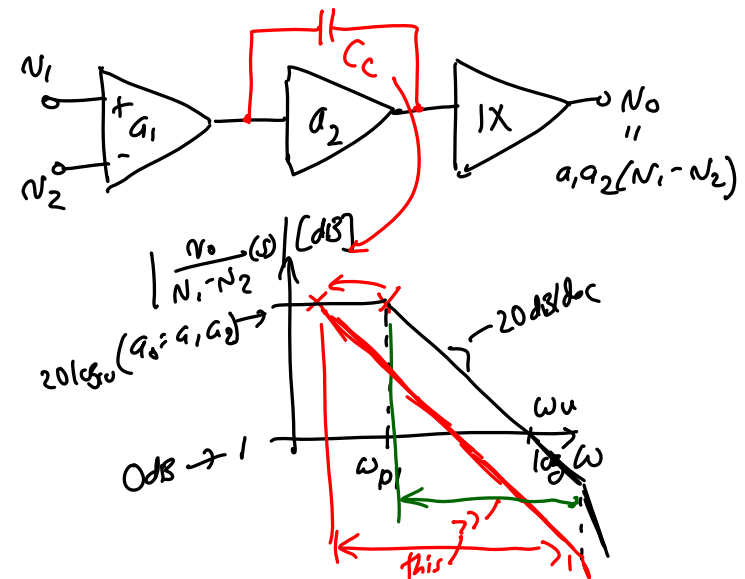

Where does instability come from? practical  
 $\Rightarrow$  any neg. FB becomes unstable under certain conditions  $\rightarrow \therefore$  must compensate to suppress instability!

Ex. Non-Inverting Amplifier

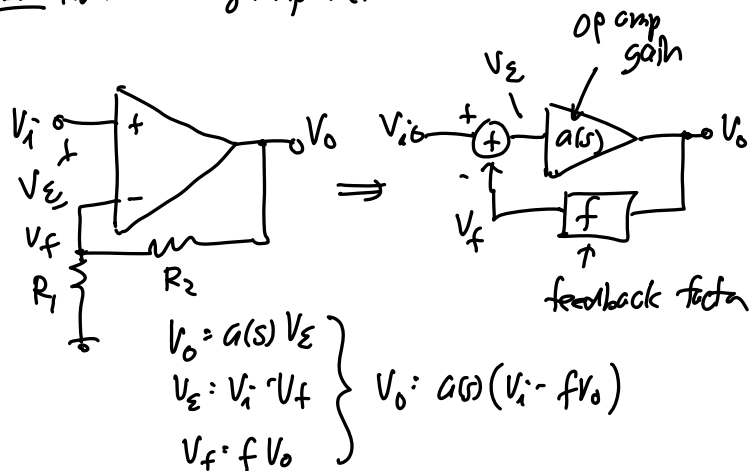

$$V_o = a(s) V_e$$

$$V_e = V_i - V_f$$

$$V_f = f V_o$$

$$V_o = a(s) (V_i - f V_o)$$

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$

closed loop gain

Loop Transmission:  $T(s) = a(s)f$   
 $\downarrow$  fcn of freq.

Instability occurs when  $A(s) \rightarrow \infty!$

@ dc: loop gain =  $a_0 f = T_0$

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} = \frac{a(s)}{0} \rightarrow \infty$$

$a(s)f = -1$  will also go unstable if denominator is (-)

In General

If  $|a(s)f| \geq 1$  when  $\angle a(s)f = -180^\circ \Rightarrow$  Instability

This is a simplified form of the Nyquist Criterion

Stability of a FB Ckt. Using a Single-Pole Op Amp

For a single pole op amp:  $a(s) = \frac{a_0}{1 - \frac{s}{p_1}}$  op amp transfer function

Thus: closed loop T.F.

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0 f} \frac{1}{1 - \frac{s}{p_1 (1 + a_0 f)}}$$

BW increases

$A_0$ : closed loop dc gain  
 $\rightarrow (1 + a_0 f)$  smaller than  $a_0$   
 $\approx \frac{1}{f}$   
 Freq. Shaping Term

$T_0 = a_0 f$  = loop gain (defined @ dc)

$T(s) = a(s)f$  = loop transmission (defined for general frequencies)

