

Lecture 19: Compensation

• Announcements:


- ⇒ HW#9 online
- ⇒ Lab#2 due this Friday
  - Grade depends heavily on the report
  - Make sure you spend enough effort on the report per your TA's requirements
- ⇒ Lab#3 update online (update for 240A folks)
- ⇒ No lecture next Tuesday; this lecture is 2 hours to compensate
- ⇒ Two lectures after next Tuesday also 2 hours

• Lecture Topics:

- ⇒ Compensation

• Last Time:


Stability & Compensation

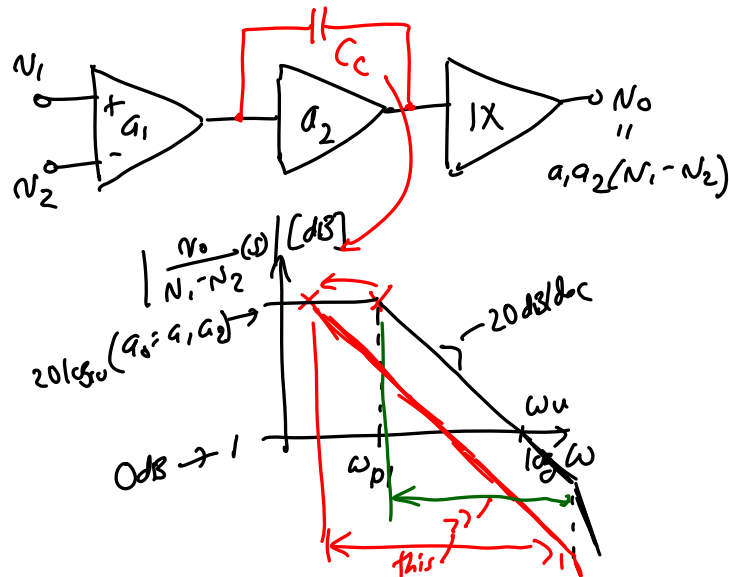

Where does instability come from? practical

⇒ any neg. FB becomes unstable under certain conditions → ∴ must compensate to suppress instability!

Ex. Non-Inverting Amplifier

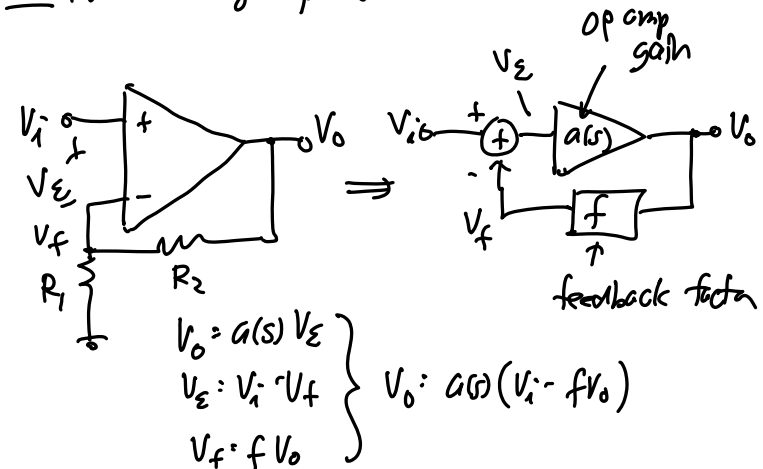

$$A(s) = \frac{V_o}{V_i}(s) = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$

↑  
closed loop gain

Loop Transmission:  $T(s) = a(s)f$   
fcn of freq.

Instability occurs when  
 $A(s) \rightarrow \infty$ !

@ dc: loop gain =  $a_0 f = T_0$

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} = \frac{a(s)}{0} \rightarrow \infty$$

↑  
 $a(s)f = -1$  will also go unstable if denominator is (-)

In General

If  $|a(s)f| \gg 1$  when  $\angle a(s)f = -180^\circ \Rightarrow$  Instability

This is a simplified form of the Nyquist Criterion.

Stability of a FB Ckt. Using a Single-Pole OpAmp

For a single pole op amp:  $a(s) = \frac{a_0}{1 - \frac{s}{p_1}} \equiv$  op amp transfer function

Thus: closed loop T.F.

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0 f} \frac{1}{1 - \frac{s}{p_1(1 + a_0 f)}}$$

BW increases

$A_0$ : closed loop dc gain  
 $\rightarrow (1 + a_0 f)$  smaller than  $a_0$   
 $\approx \frac{1}{f}$   
 Freq. Shaping Term

$T_0 = a_0 f$  = loop gain (defined @ dc)


$T(s) \cdot a(s)f$  = loop transmission (defined for general frequencies)

Bode Plot:  $\rightarrow$  use to determine

$\angle a(s)f$  when  $|a(s)f| = 1 \rightarrow$  then can

determine stability
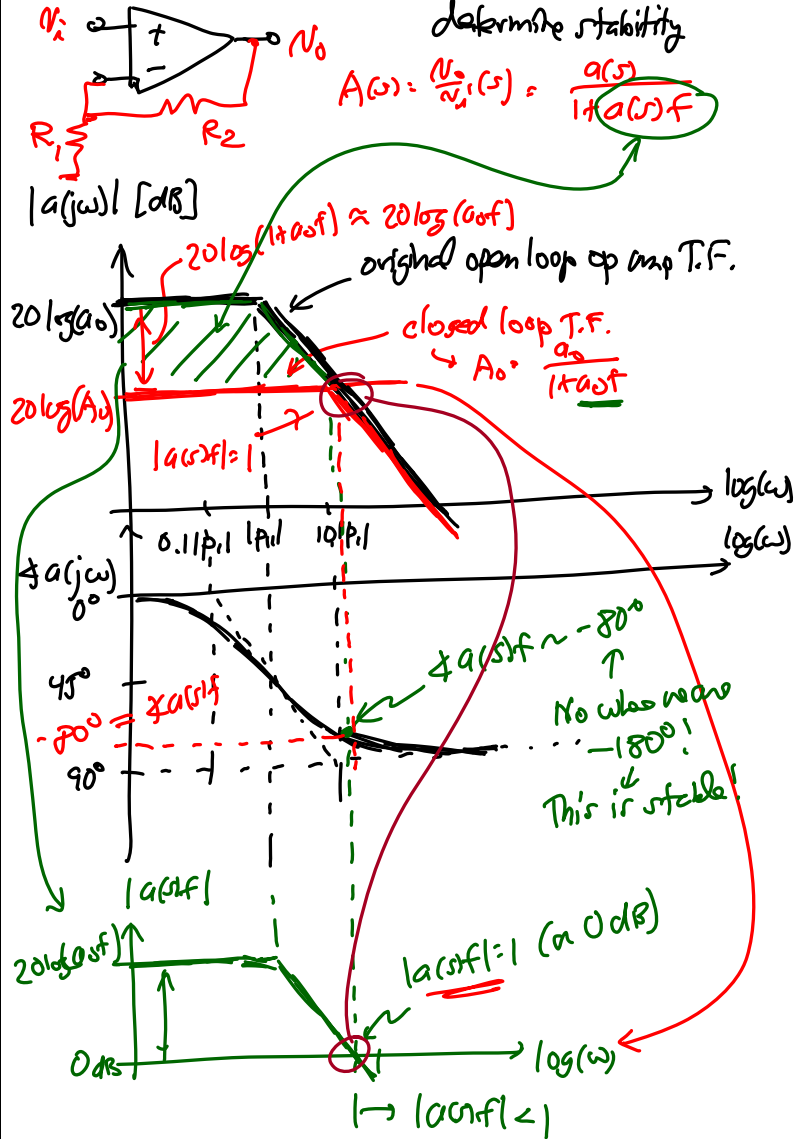
$$A(s) = \frac{V_o}{V_i}(s) = \frac{a(s)}{1 + a(s)f}$$




Remarks:

$\omega$   $f = \text{const.}$

① For the case of a single-pole op amp, FB can never reach  $\angle a(s)f = -180^\circ$ . ( $90^\circ$  is the limit.)

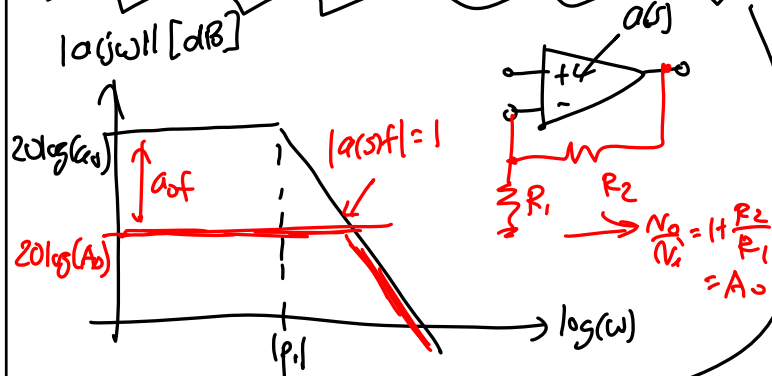② Thus, a single-pole op amp in FB w/  $f = \text{const.}$ , i.e.,  $f \neq \text{function of } s=j\omega$ , is always stable!




But in reality, op amp also has non-dominant poles!  $\rightarrow$   $\angle a(s)f \rightarrow -180^\circ$

Can investigate  
stability!

Use again a Bode plot to investigate.

Stability of a FB Ckt. using a mul.

Assume. dominant pole:  $p_1$ , non-dominant poles:  $p_2$   
 $|p_3|, |p_4| \gg |p_2|$

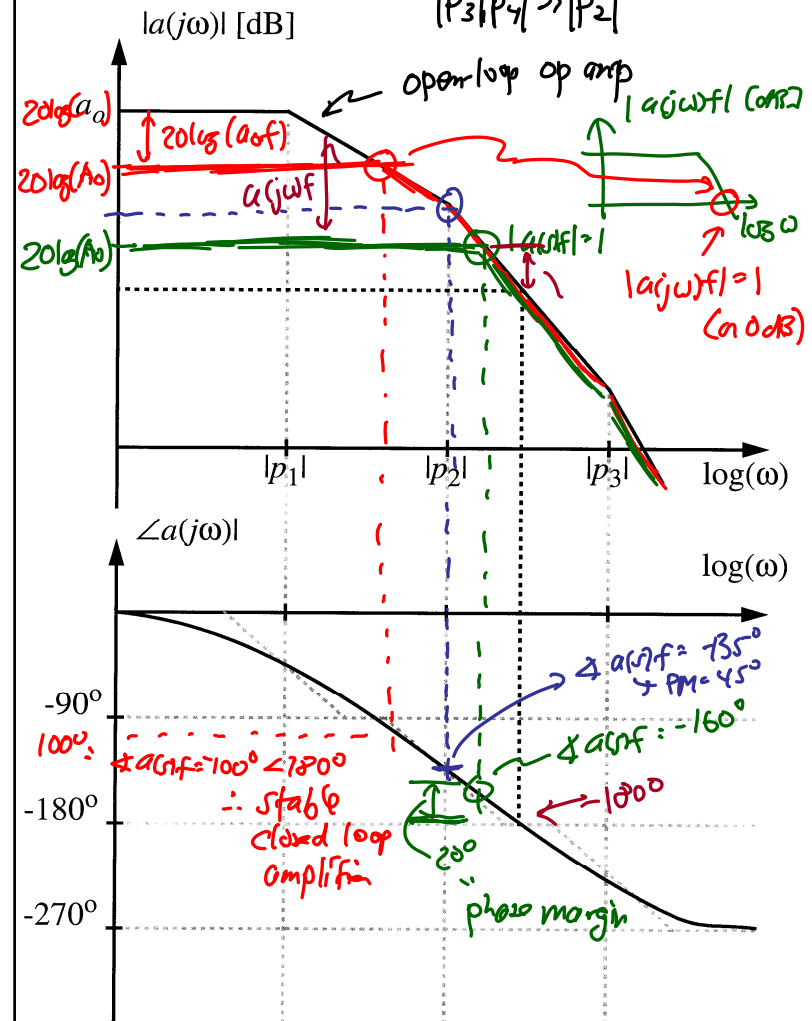

For the more general case where  $a(s)$  has multiple poles:

$\Rightarrow A(s)$  has the same additional poles ( $f = \text{const.}$ )

$\Rightarrow$  i.e., @ freq  $\omega > |p_1|$  (1st of), the  $A(s)$  curve just follows the  $a(s)$  curve

$$A(s) \approx \frac{A_0}{\underbrace{\left(1 - \frac{s}{|p_1|(1+\alpha f)}\right) \left(1 - \frac{s}{|p_2|}\right) \left(1 - \frac{s}{|p_3|}\right)}_{\text{But can also get peaking}}}$$

Definitions:

$$\begin{aligned} \text{Phase Margin} &= 180^\circ + (\angle a(j\omega))_f \text{ @ freq. where } |a(j\omega)|=1 \\ &= 180^\circ - 160^\circ = 20^\circ \\ &= 180^\circ - 100^\circ = 80^\circ \end{aligned}$$


$\Rightarrow$  phase margin must be  $> 0^\circ$  for stability

For stability:  $\text{Phase Margin} > 0^\circ$

$\Rightarrow$  for design safety, design for


$\text{Phase Margin} \geq 45^\circ$

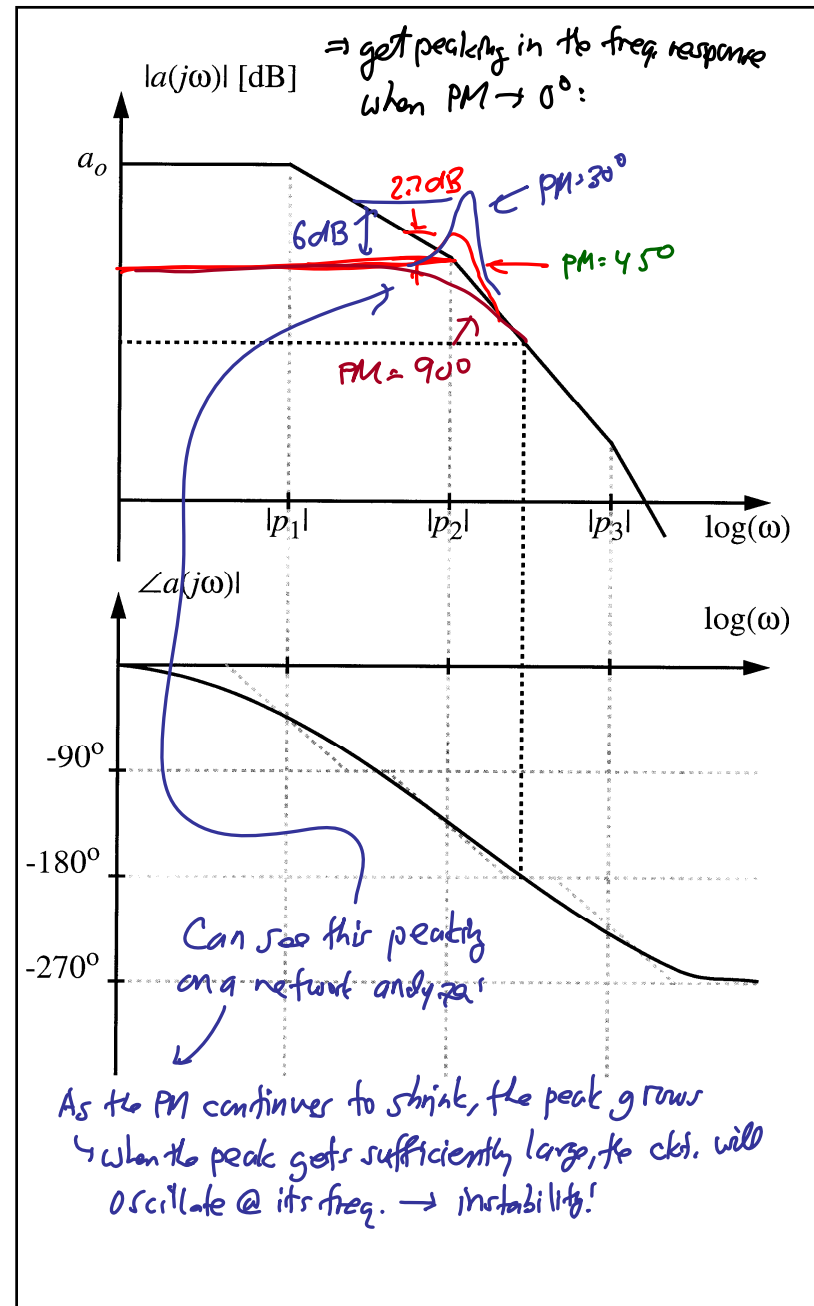$\Rightarrow$  even safer (for settling time):  $\text{PM} \geq 60^\circ$




Definition.

Gain Margin =  $|a(j\omega)f|$  in dB @ freq. where  
 $\angle a(j\omega)f = -180^\circ$

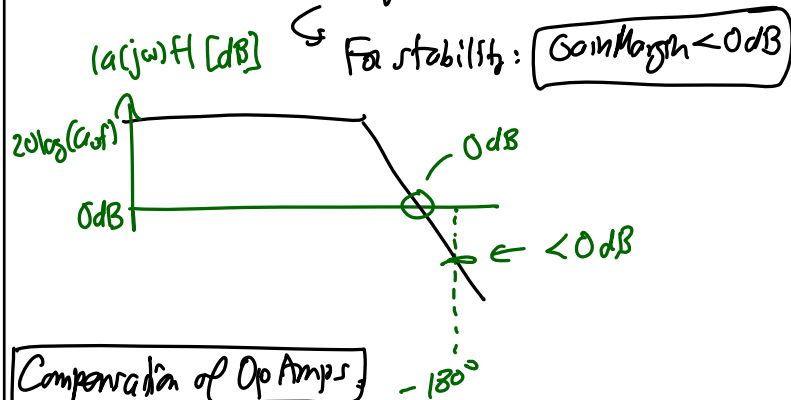

Compensation of Op Amps:

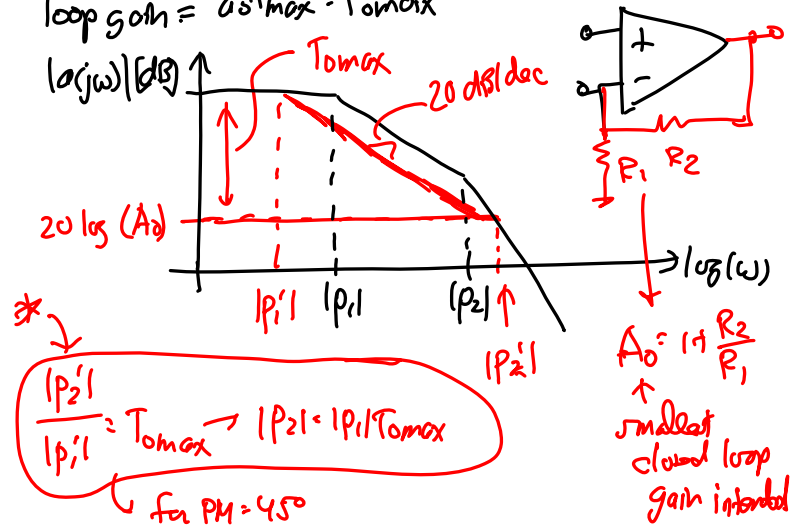To compensate, need distance between  $p_1$  &  $p_2$  to be large enough to encompass the largest desired loop gain =  $A_0f_{\text{max}} = T_{\text{omax}}$



$$20(\log|p_2'| - \log|p_1'|) = 20\log(T_{\text{omax}})$$


$$20\log\left(\frac{|p_2'|}{|p_1'|}\right) = 20\log(T_{\text{omax}})$$

\*

Two Ways to Compensate:

- ① Narrowbanding
- ② Pole splitting

over

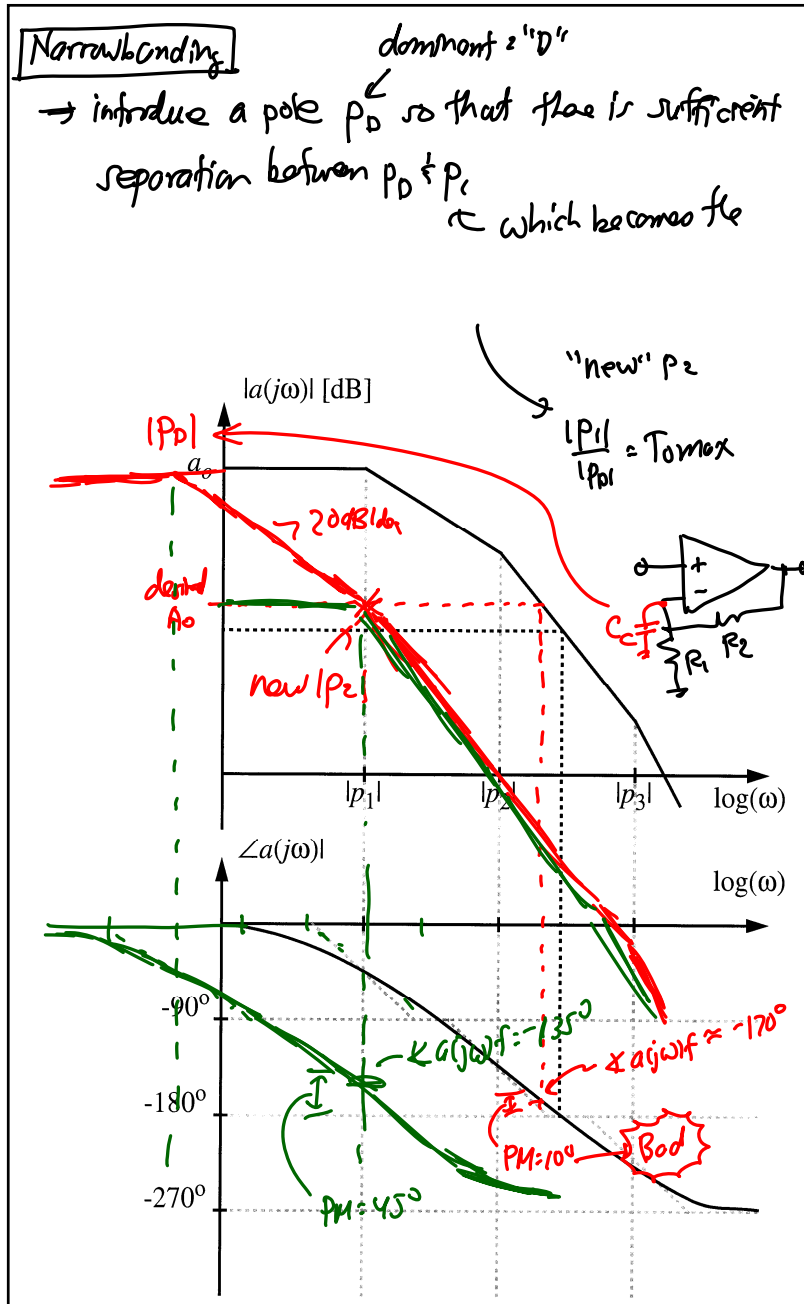

Remarks on Narrowbanding

- ① Assumption:  $p_1, p_2, p_3$  don't move when  $p_D$  is introduced (often not true, but that's minimal isn't that big)
- ② Summarize choose  $p_D$  such that  $|T(j\omega)| = 0\text{dB} = 1$  @  $p_1$  (which becomes the 'new 2<sup>nd</sup> most dominant pole')  
 ↳ this gives  $PM = 45^\circ$  (for  $|p_2| \gg |p_1|$  &  $|p_3| \gg |p_2|$ )
- ③ Why do this? Wouldn't it be much better to just move the original  $|p_1|$  (i.e., pole-split)
- ↳ Do it when you have no other choice, e.g., when you have a packaged op amp & have access only to a few terminals, not the optimum compensation node.

④  $|p_D| = \frac{|p_1|}{T_{\text{omax}}}$  ← maximum expected/needed loop gain

Problem:

- ① often,  $|p_D| \ll |p_1| \therefore f_{-3dB}$  BW of the op amp will be very small
- ②  $\omega_{\text{closed loop}} = |p_1|$  which isn't that large

Solution: Pole-Splitting

- ↳ move  $|p_1|$  down & either keep  $|p_2|$  still  
 ↳ or move  $|p_2|$  up simultaneously
- ↳ after doing this:
- ①  $\omega_{-3dB} = |p_1|$
  - ②  $\omega_{\text{closed loop}} = |p_2|$

