


Lecture 20-21: Choosing C_c

- Announcements:
 - This lecture will be 2 hours (2nd lecture to make up for missing Tuesday)
 - Next lecture will also be 2 hours
 - HW#9 due tomorrow
 - HW#10 online soon
- Design Project Checkpoint:
 - ↳ Due Monday, April 22, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (or linear if an MOS resistor)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
- Lecture Topics:
 - ↳ Review of Pole-Zero Plots
 - ↳ Choosing C_c
 - ↳ CMOS Op Amp Compensation

• Last Time:

Two Ways to Compensate:

- ① Narrowbanding
- ② Pole Splitting

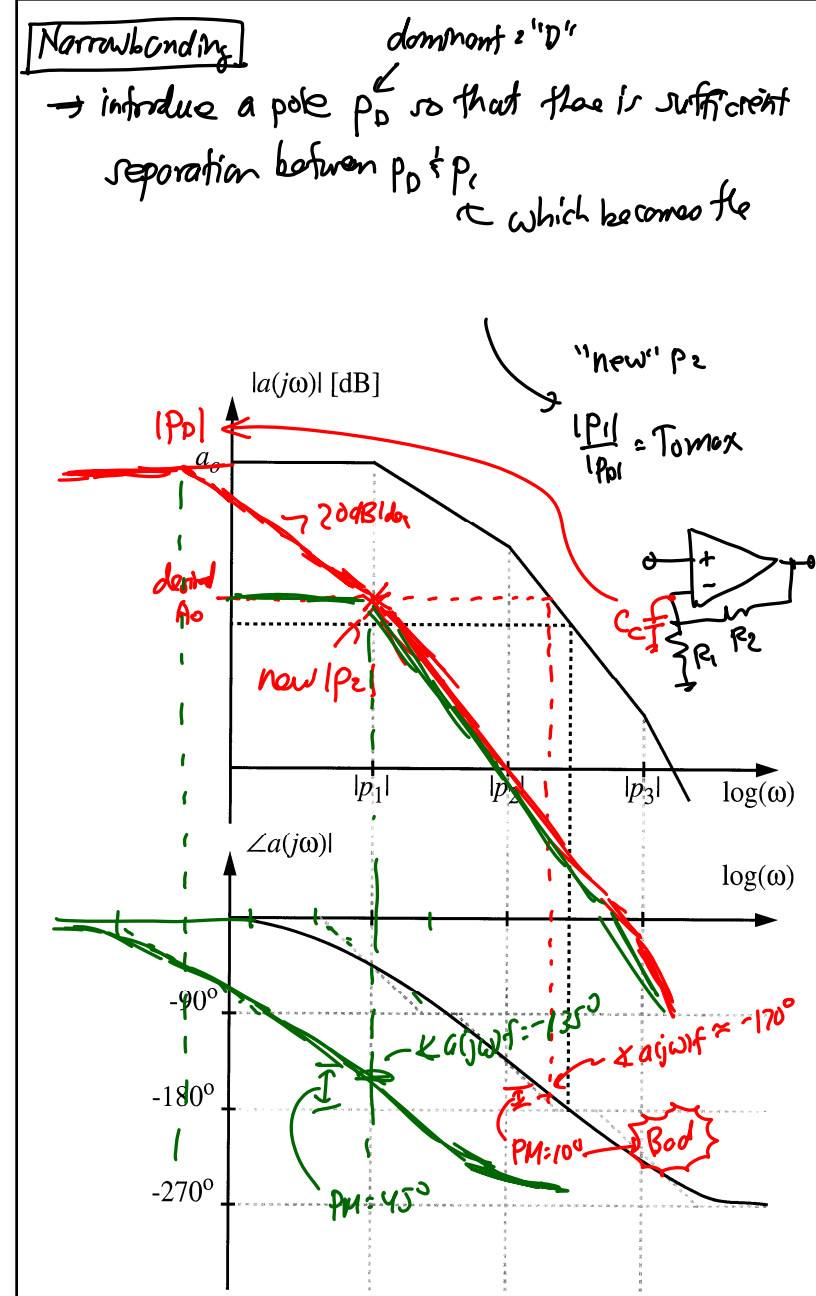

Remarks on Narrowbanding

- ① Assumption: p_1, p_2, p_3 don't move when p_0 is introduced (often not true, but that's minimal isn't that big)
- ② Summarize: choose p_0 such that $|T(j\omega)| = 0 \text{ dB} = 1$ @ p_1 (which becomes the "new 2nd most dominant pole")
 ↳ this gives $\text{PM} = 45^\circ$ (for $|p_2| \gg |p_1|$ & $|p_3| \gg |p_2|$)
- ③ Why do this? Wouldn't it be much better to just move the original $|p_1|$ (i.e., pole-split)

↳ Do it when you have no other choice, e.g., when you have a packaged op amp & have access only to a few terminals, not the optimum compensation node.

④ $|p_0| = \frac{|p_1|}{T_{\text{omax}}}$ ← maximum expected/needed loop gain

Problem:


- ① often, $|p_0| \ll |p_1| \therefore f_{3\text{dB}}$ BW of the op amp will be very small
- ② $\omega_{\text{closed loop}} \approx |p_1|$ which isn't that large



Solution: Pole-Splitting

- ↳ move $|p_1|$ down & either keep $|p_2|$ still
 ↳ or move $|p_2|$ up simultaneously
 ↳ after doing this:
- ① $\omega_{3\text{dB}} = |p_1'|$
 - ② $\omega_{\text{closed loop}} = |p_2'|$

Pole-Splitting



⇒ assume p_2 does not move

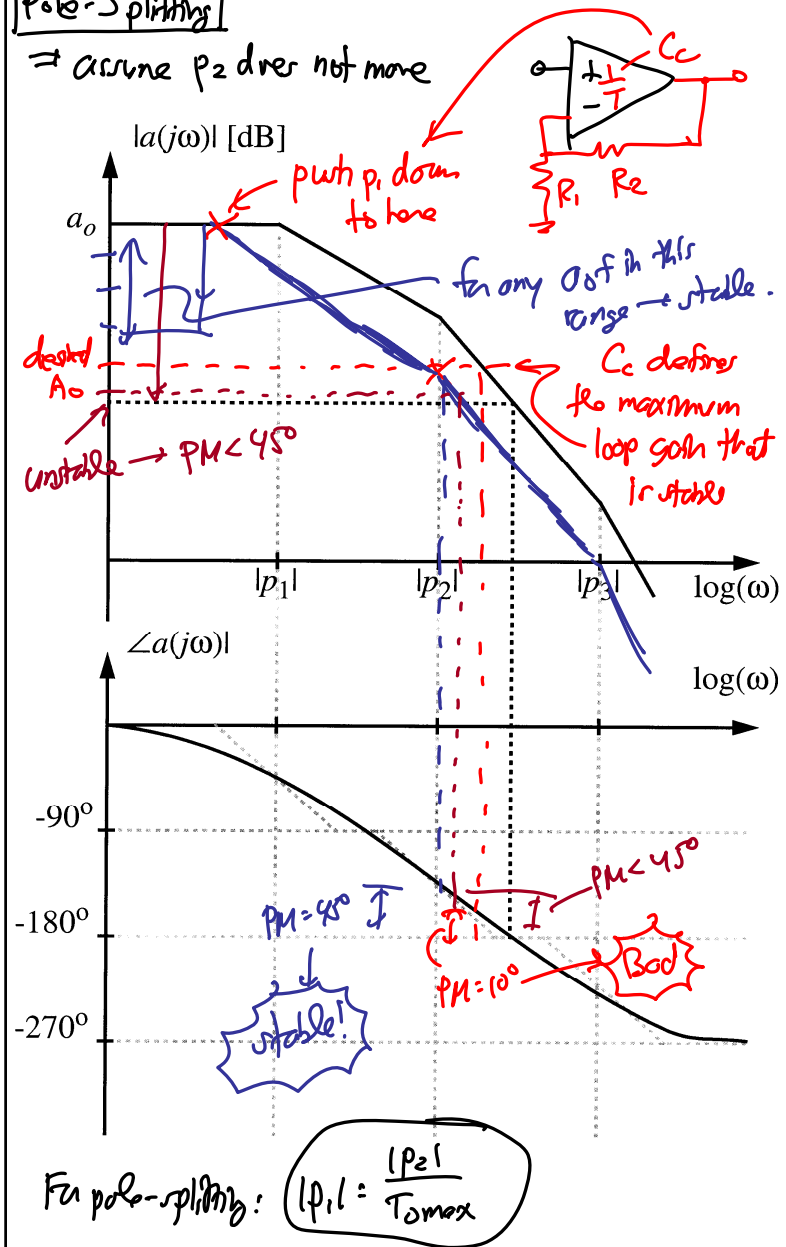

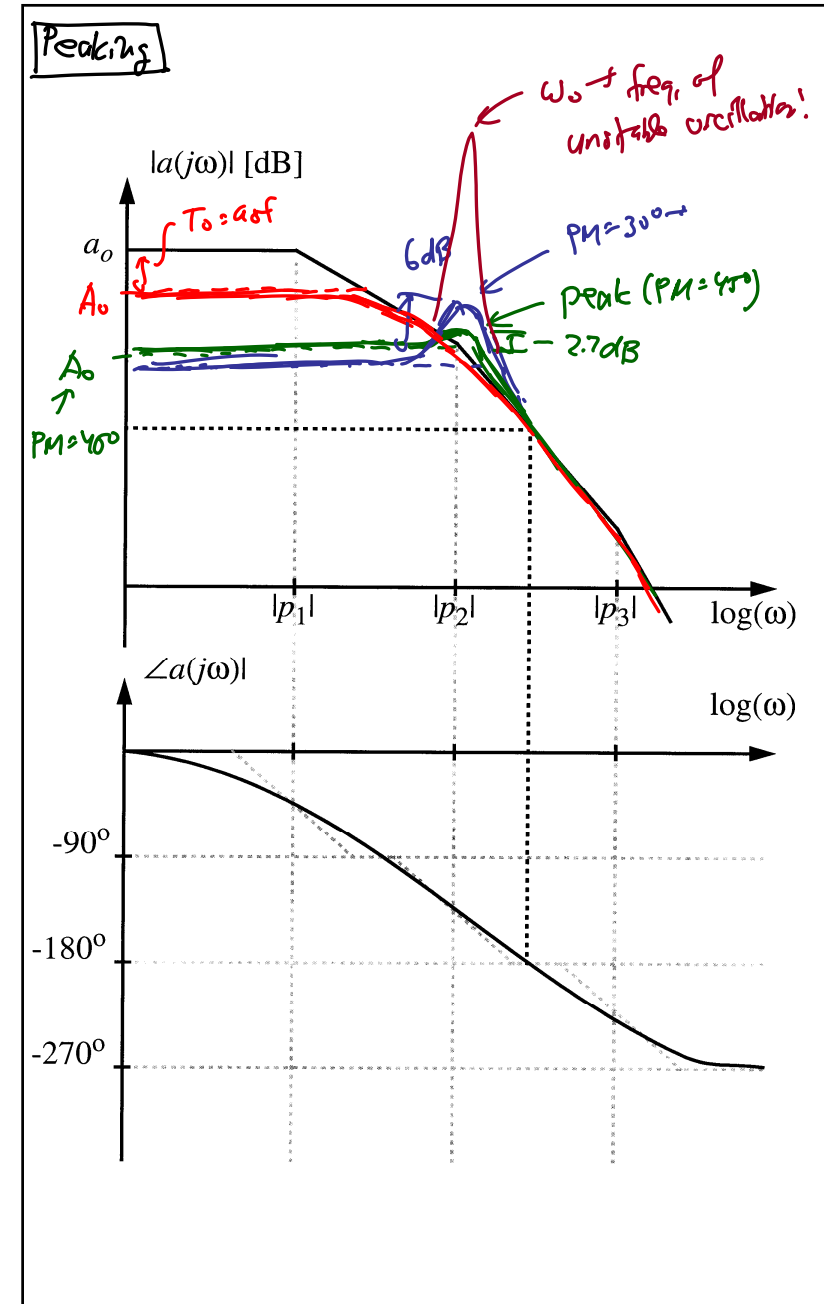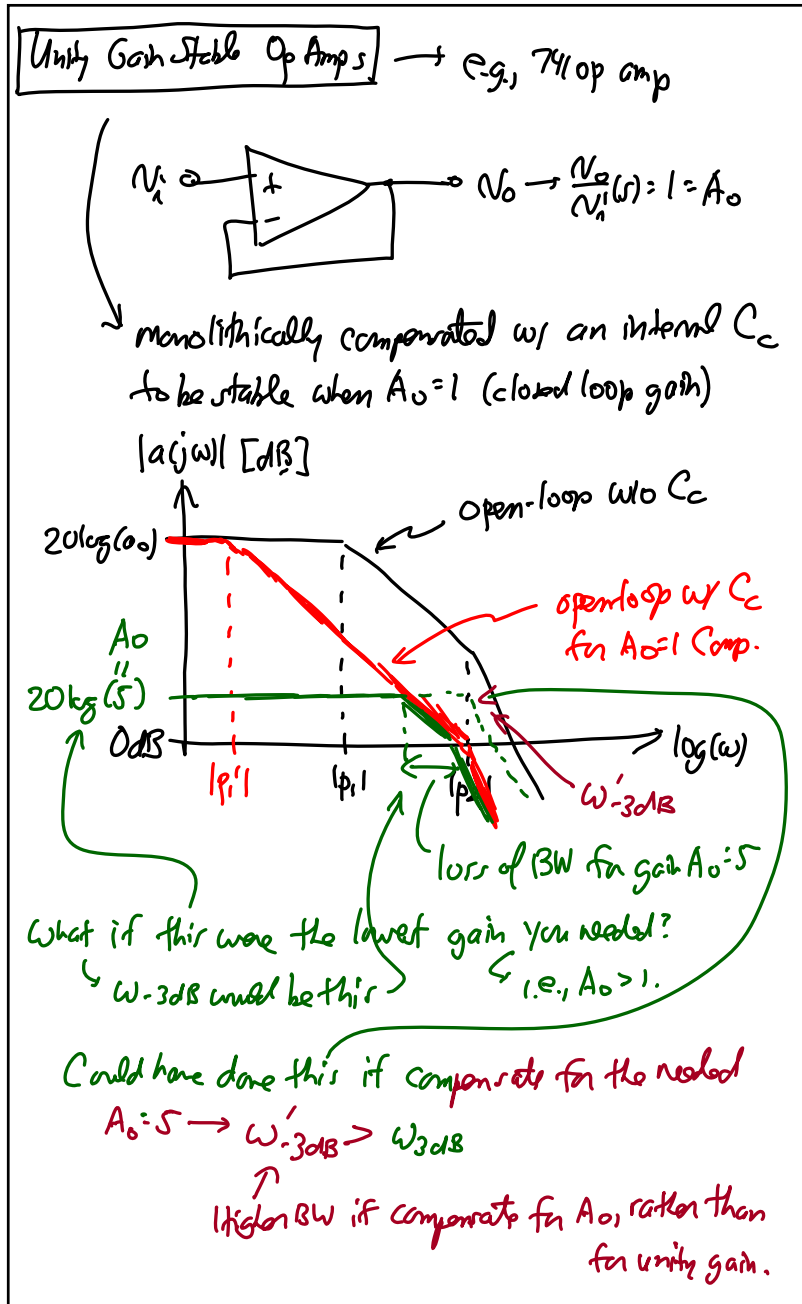

Choosing C_c (assume no RHP zeros & $|p_3| \gg |p_2|$)
 \Rightarrow assume $\frac{1}{sC_c} \ll$ surrounding impedances @ high freq.

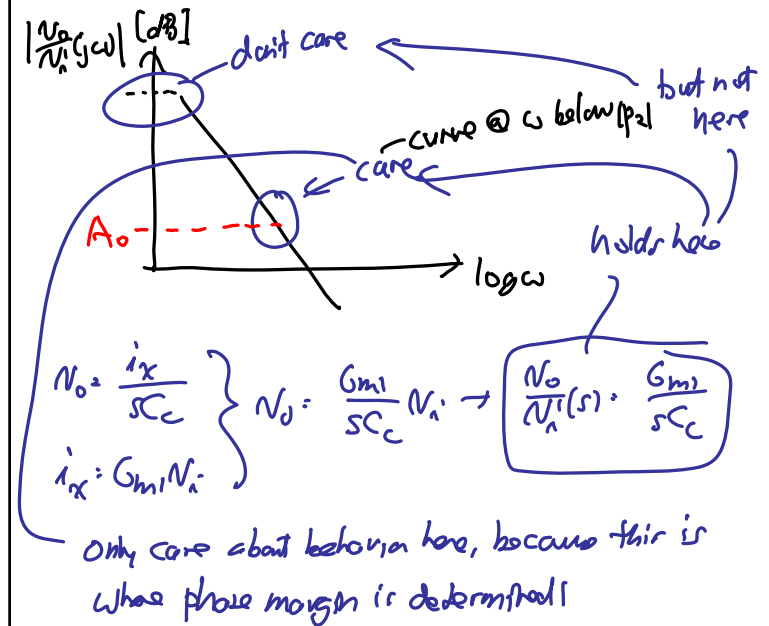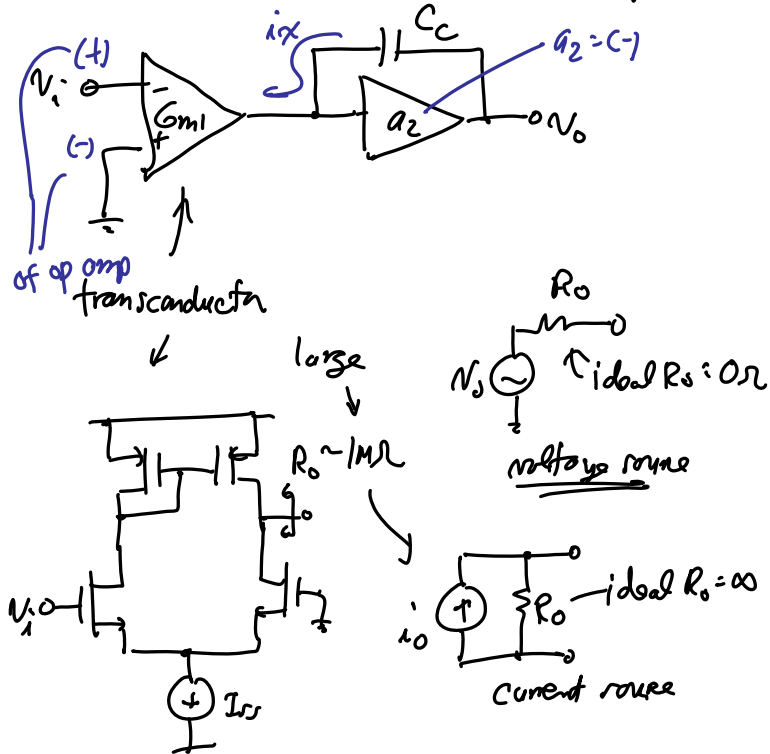① Case ①: Two-stage Amplifier, Miller Compensation



$|N_o/V_i(jw)| = \frac{G_{m1}}{\omega C_c} \Rightarrow$ this should equal A_o @ f_0 freq. corresponding to the target phase margin

For PM = 45°:

$\omega_{ult} = \omega @ |a(jw)f| = 1$

"ult" = "unity loop transmission"


For PM = 45° $\rightarrow \omega_{ult} = \omega_2 \leftarrow$ freq. of the 2nd pole of the open loop $a(jw)$ transfer fn.

$$\left| \frac{V_o}{V_i}(j\omega_2) \right| = A_o = \frac{G_{m1}}{\omega_2 C_c} \rightarrow C_c = \frac{G_{m1}}{\omega_2 A_o}$$

desired closed-loop gain

For $PM = 45^\circ$
(provided $|p_3| \gg |p_2|$)
(also $|p_2| \gg |p_1|$)


For $PM = 60^\circ$:
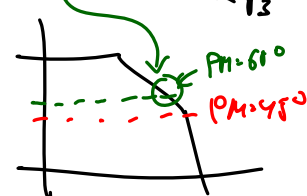
$$\omega_{ult} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{V_o}{V_i}(j\omega_{ult}) \right| = A_o = \frac{G_{m1}}{\left(\frac{\omega_2}{1.73}\right) C_c}$$


$$C_c = \frac{1.73 G_{m1}}{\omega_2 A_o}$$

For $PM = 60^\circ$

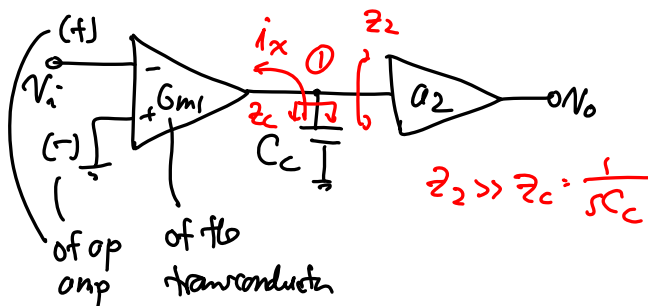② Case: Two-Stage Amplifier, Shunt C_c Compensation



$$\left. \begin{aligned} V_i &= -\frac{G_{m1} V_i}{sC_c} \\ V_o &= a_2 V_i \end{aligned} \right\} V_o = -\frac{G_{m1} a_2}{sC_c} V_i$$

$$\therefore \frac{V_o}{V_i}(s) = -\frac{G_{m1} a_2}{sC_c}$$

closed-loop gain A_o must again intersect this curve @ the right ω_{ult} for the needed PM

For $PM = 45^\circ$:

$$\left| \frac{V_o}{V_i}(j\omega_{ult}) \right| = A_o = \frac{G_{m1} a_2}{\omega_2 C_c} \rightarrow C_c = \frac{G_{m1} a_2}{\omega_2 A_o}$$


[For $PM = 45^\circ$, $\omega_{ult} = \omega_2$]

For $PM = 45^\circ$

For $PM = 60^\circ$:

$$C_c = \frac{1.73 G_{m1} a_2}{\omega_2 A_o} \leftarrow \text{For } PM = 60^\circ$$

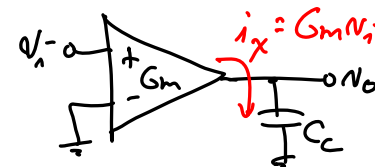Case ③: Single-Stage Amplifier, Shunt C_c Compensation
e.g., telescopic cascode op amp



$$N_o = \frac{i_x}{sC_c}$$

$$i_x = G_m N_i$$

$$\left. \begin{array}{l} N_o = \frac{i_x}{sC_c} \\ i_x = G_m N_i \end{array} \right\} \frac{N_o}{N_i}(s) = \frac{G_m}{sC_c} \leftarrow \text{same as case ①! (Miller comp.)}$$

Thus:

$$C_c = \frac{G_m}{\omega_2 A_o} \leftarrow PM = 45^\circ$$

$$C_c = \frac{1.73 G_m}{\omega_2 A_o} \leftarrow PM = 60^\circ$$

CMOS 2-Stage Op Amp Compensation

$$g_{mI} = g_{m2}$$

$$g_{mII} = g_{m6}$$

$$R_I = r_{o2} || r_{o4}$$

$$R_{II} = r_{o6} || r_{o7}$$

$$KCL \text{ ①: } i_s = \frac{N_i}{R_I} + sC_I N_i + (N_i - N_o)sC_c$$

$$KCL \text{ ②: } g_{mII} N_i + \frac{N_o}{R_{II}} + sC_{II} N_o + (N_o - N_i)sC_c = 0$$

$$\frac{N_o}{i_s} = \frac{(g_{mII} - sC_c) R_I R_{II}}{1 + s[(C_{II} + C_c) R_{II} + (C_I + C_c) R_I + g_{mII} R_I R_{II} C_c] + s^2 R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$$\frac{V_o}{V_i}(s) = \frac{N(s)}{D(s)} \rightarrow \text{This Xfer fcn has 2 poles \& one zero.}$$

The zero: $N(s) = 0 \rightarrow z = \frac{g_{mII}}{C_c} \leftarrow (+) \& \text{ real}$

The poles:

$$D(s) = \left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right) = 1 - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

$[p_2 \gg p_1] \rightarrow \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$
i.e., there is a dominant pole

Thus:

$$p_1 = - \frac{1}{(C_{II} + C_c)/R_{II} + (C_I + C_c)/R_I + g_{mII} R_I R_{II} C_c}$$


As $C_c \uparrow \rightarrow p_1 \downarrow \approx - \frac{1}{g_{mII} R_I R_{II} C_c} = p_1$

for the 2nd pole:

$$p_1 p_2 = \frac{1}{R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$$

$$p_2 = - \frac{g_{mII} C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \xrightarrow{+ \text{As } C_c \uparrow} \approx p_2 = - \frac{g_{mII}}{C_I + C_{II}}$$

ω_2 By Inspection

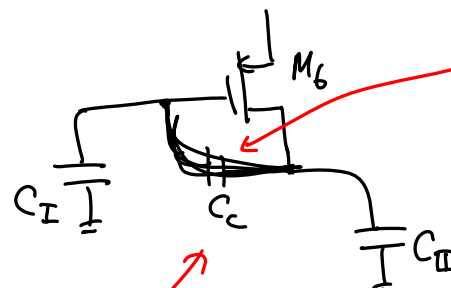

$$\frac{1}{sC} = \frac{1}{j\omega C} \rightarrow 0$$

$$\omega_2 = \frac{1}{\left(\frac{1}{g_{mII}}\right)(C_I + C_{II})} = \frac{g_{mII}}{C_I + C_{II}} \checkmark$$

