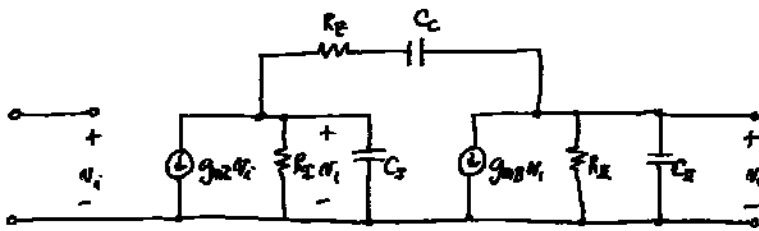


Lecture 23: RHP Zero, Slew Rate, Settling Time

- Announcements:
- This lecture will be 2 hours (1st lecture to make up for missing Thursday)
- So next two lectures will also be 2 hours, with video of at least the last half hour posted online
- HW#11 has been online
- Lecture Topics:
 - ↳ Nulling the RHP Zero (finish compensation)
 - ↳ Slew Rate (revisited)
 - ↳ Settling Time

• Last Time:

Solution: Nulling Resistor in Series w/ C_c



Doing KCL:

$$p_1 \approx -\frac{1}{g_{mII} R_I R_O C_c}$$

$$p_2 \approx -\frac{g_{mII} C_c}{C_I C_{II} + C_c (C_I + C_{II})} \approx -\frac{g_{mII}}{C_{II}}$$

} Same as before

$$p_3 = -\frac{1}{R_2 C_I} \leftarrow \text{pole due to } R_2$$

$$z_1 = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} \leftarrow \text{relocated zero (function of } R_2 \text{)}$$

Note: The position of the zero depends upon the value of the "nulling resistor" R_2

$$\begin{cases} \text{If } R_2 < \frac{1}{g_{mII}}, \text{ then } z_1 \text{ is in the RHP } \times \\ \text{If } R_2 > \frac{1}{g_{mII}}, \text{ then } z_1 \text{ is in the LHP } \checkmark \end{cases}$$

↳ This is great! → Can convert the zero to a LHP zero!


Can even stick the zero on top of a pole!

↳ much better PM...

$$H(s) = \dots \frac{(s - z_1)}{(s - p_1)}$$

If $z_1 = p_1$

The Root Locus:

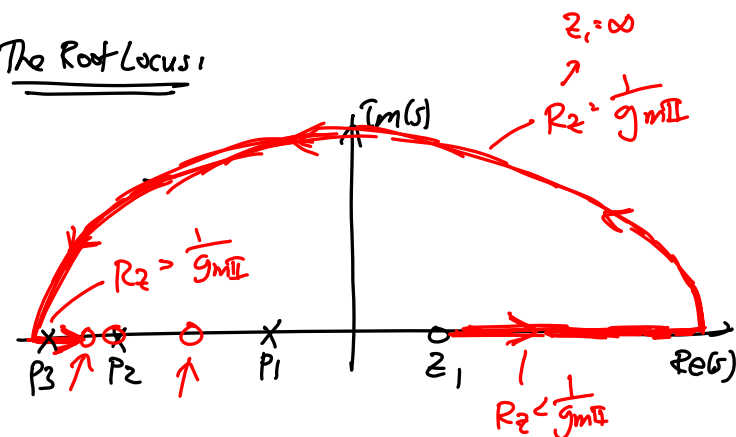

Project Design → Lab #3

Ad Hoc Procedure:

- Write down all eqns. for all needed specs.
↓ then study dependencies, e.g.

$$a_0 = \text{gain} = f(I_D, \lambda, \dots) \sim \frac{1}{\sqrt{I_D}}$$

- Choose C_c


$$\omega_u = \text{unity gain freq.} = \frac{g_{mII}}{C_c}$$

$$|p_2| = -\frac{g_{mII}}{C_L}$$


choose to be

- Choose I_D 's → SR

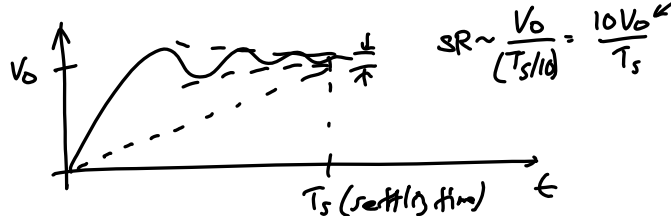- Determine ψ 's (governed by swing & input range)



240A Folks:

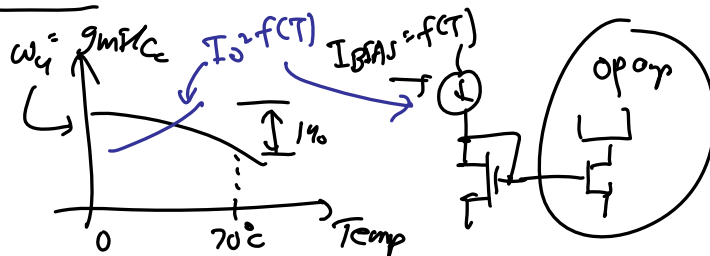

Zero Placement Strategies

- Eliminate z_1 → move it to ∞ :

$$z_1: \frac{1}{C_c(\frac{1}{g_{mII}} - R_2)} \rightarrow \infty \text{ when } R_2 = \frac{1}{g_{mII}}$$

$$R_2 = \frac{1}{g_{mII}}$$

local cap.

After doing this:

$$p_3 \approx -\frac{g_{mII}}{C_I}$$

$$p_2 \approx -\frac{g_{mII}}{C_{II}}$$

usually, $C_{II} \gg C_I$,
so these poles are
far apart...
...but be careful...

This is good,
but we can do better!

- Eliminate p_3 by placing z_1 on top of it:

$$z_1: p_3 = \frac{1}{C_c(\frac{1}{g_{mII}} - R_2)} = -\frac{1}{R_2 C_I}$$

$$R_2 = \frac{1}{g_{mII}(1 - \frac{C_I}{C_c})}$$

After this:

- p_3 gone, p_1 & p_2 left over

no excess phase shift fr z_1 on p_3


- Now, can place ω_{ult} @ p_2 & expect PM = 45°

...but, we can still do better ...

③ Eliminate p_2 by placing z_1 on top of it:

$$z_1 = p_2 \Rightarrow \frac{1}{C_c \left(\frac{1}{g_{mII}} R_2 \right)} = - \frac{g_{mII}}{C_{II}}$$
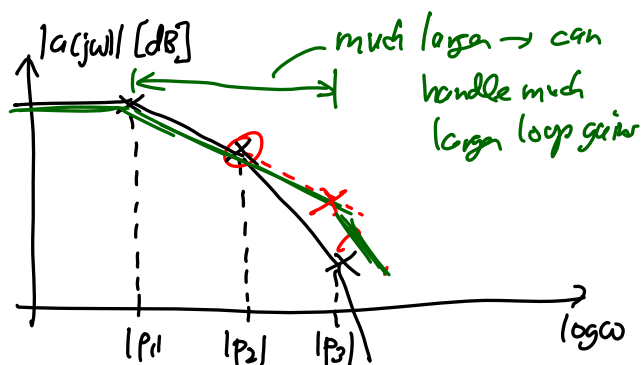
$$R_2 = \left(\frac{C_c + C_{II}}{C_c} \right) \left(\frac{1}{g_{mII}} \right) = \frac{1}{g_{mII}} \left(1 + \frac{C_{II}}{C_c} \right)$$



\Rightarrow w/ this choice of R_2 :

$$p_3 = - \frac{1}{R_2 C_I} = - \frac{1}{\left(\frac{C_c + C_{II}}{C_c} \right) \left(\frac{1}{g_{mII}} \right) C_I} C_I$$

\downarrow
 $p_3 = - \frac{g_{mII} C_c}{C_I (C_c + C_{II})}$

This becomes the new p_2 !

For $PM = 45^\circ$

$$C_c = \frac{g_{mI}}{|p_3| A_o} = \frac{g_{mI}}{g_{mII}} \frac{C_I (C_c + C_{II})}{C_c A_o}$$

\uparrow the "new" $|p_2|$

For $PM = 45^\circ$

$$C_c \cong \sqrt{\frac{g_{mI}}{g_{mII}} \frac{C_I C_{II}}{A_o}}$$

For $PM = 60^\circ$:

$$C_c = \frac{1.73 g_{mI}}{|p_3| A_o} \rightarrow C_c = \sqrt{\frac{1.73 g_{mI}}{g_{mII}} \frac{C_I C_{II}}{A_o}}$$

\uparrow For $PM = 60^\circ$


$[C_I \ll C_{II}]$

Remark. If settling time is important, then approach ③ may not be the best approach. The reason is that if the zero is not exactly equal to the pole, then a "doublet" ensues, which actually can hurt the settling time.

\uparrow
Discussed in a handout to be posted on the course website. \rightarrow also, discussed in Razavi, problem 10.19.

Actual Implementation

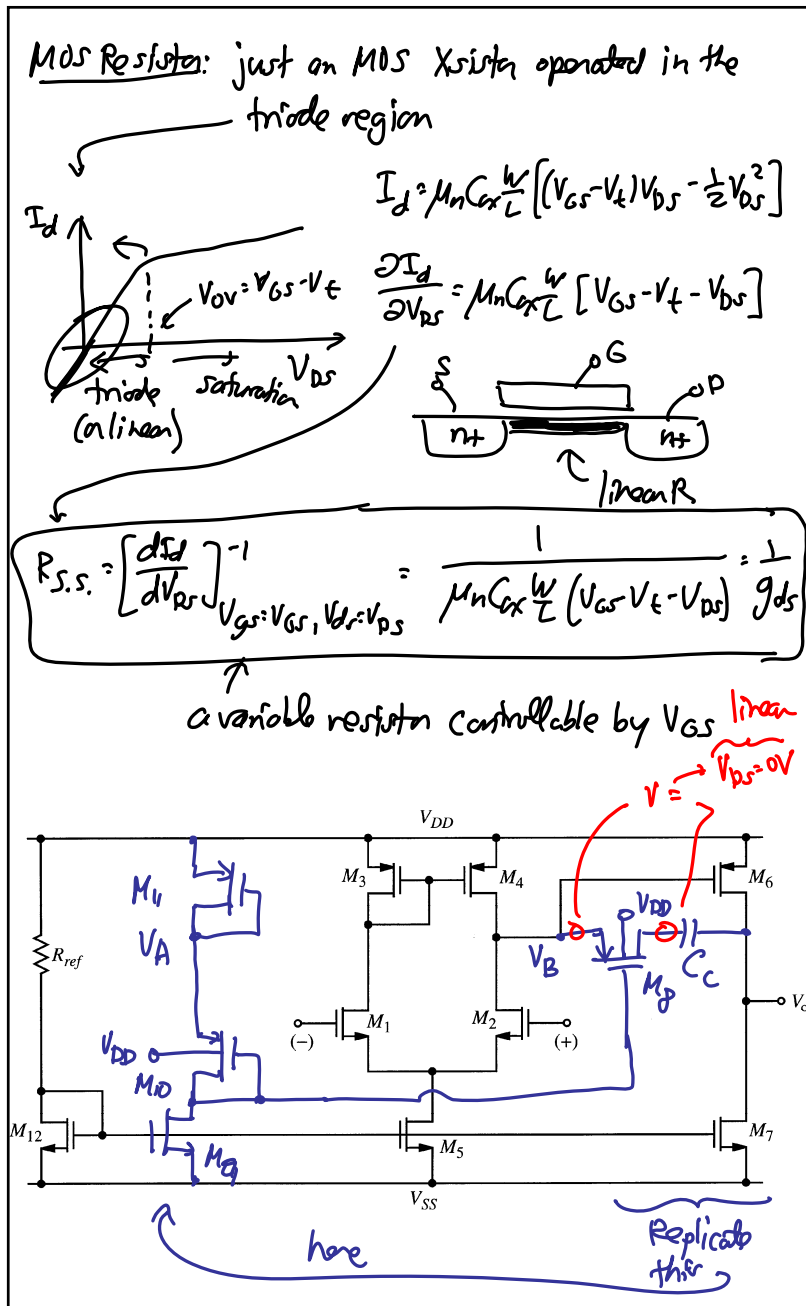\Rightarrow resistors are too big! $\rightarrow \therefore$ implement the R_2 using a much smaller triode (or linear) region MOS transistor



$$V_{DS} = 0V \Rightarrow R_p = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p \underbrace{(V_{GS} - V_{t,p})}_{|V_{ov,p}|}}$$

Design.

Need $V_A = V_B \rightarrow |V_{GS1}| = |V_{GS6}|$, know that $|V_{t1}| = |V_{t6}|$

$$[V_{ov1} = V_{ov6}] \Rightarrow \sqrt{\frac{2I_{D11}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_1}} = \sqrt{\frac{2I_{D6}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_6}}$$

$$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_6 \frac{I_{D11}}{I_{D6}} = \left(\frac{W}{L} \right)_6 \frac{I_{D10}}{I_{D6}} \rightarrow V_A = V_B$$

Also need $|V_{GS10}| = |V_{GS8}|$

& because $V_A = V_B \rightarrow V_{S10} = V_{S8}$, also know $|V_{t10}| = |V_{t8}|$

$$\therefore |V_{ov10}| = |V_{ov8}| \Rightarrow \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_{10}}}$$

Thus:

$$R_p = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_{10}}}} = \frac{\sqrt{\mu_p C_{ox} \left(\frac{W}{L} \right)_{10}}}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p \sqrt{2I_{D10}}}$$

equating this to the needed R_2

Case: Eliminate p_2 by placing z_1 on top of it

$$R_z: \frac{C_c + C_L}{g_{m6} C_c} = \frac{\sqrt{\mu_p C_{ox}} (W/L)_{10}}{\mu_p C_{ox} (\frac{W}{L})_8 \sqrt{2} I_{D10}}$$



$$\sqrt{2 \mu_p C_{ox}} (W/L)_6 I_{D6} \Rightarrow \left(\frac{W}{L} \right)_8 = \sqrt{\left(\frac{W}{L} \right)_6 \left(\frac{W}{L} \right)_{10} \frac{I_{D6}}{I_{D10}} \cdot \left(\frac{C_c}{C_c + C_L} \right)}$$

Case: move $z_1 \rightarrow \infty$

$$R_z: \frac{1}{g_{m6}} \Rightarrow \left(\frac{W}{L} \right)_8 = \sqrt{\left(\frac{W}{L} \right)_6 \left(\frac{W}{L} \right)_{10} \frac{I_{D6}}{I_{D10}}}$$

over \curvearrowright

Slew Rate (f/ before)

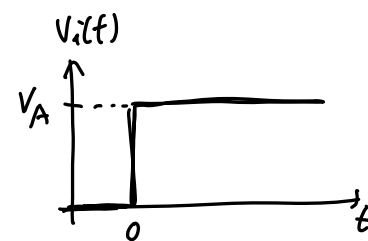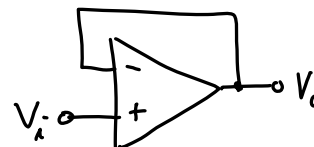

Using Laplace Xform Theory:

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + \frac{s}{\omega_1}} = \frac{1}{1 + s\tau_1}$$




\sim single (dominant) pole

$$V_i(s) = \frac{V_A}{s}$$


$$V_o(s) = \frac{V_A}{s(1 + s\tau_1)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_1}}$$

\Updownarrow Inverse Laplace Xform

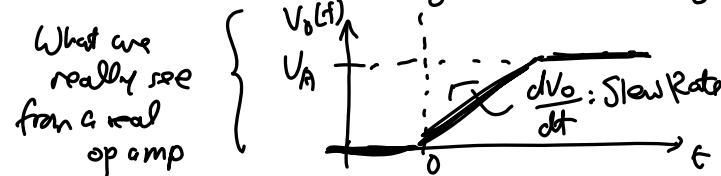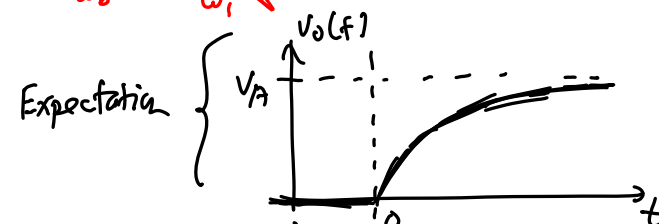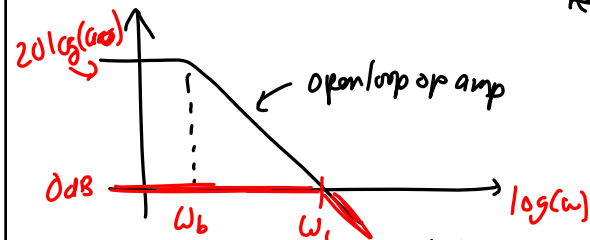
$$V_o(t) = V_A(1 - e^{-t/\tau_1}) \leftarrow \text{expected response}$$



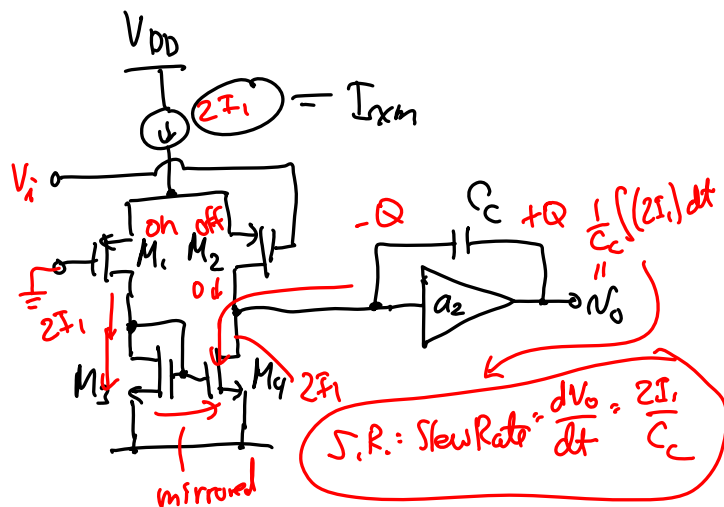Reason: 1st or 2nd stage of op amp cannot source enough current to mimic the slope (or speed) of a fast rising input signal



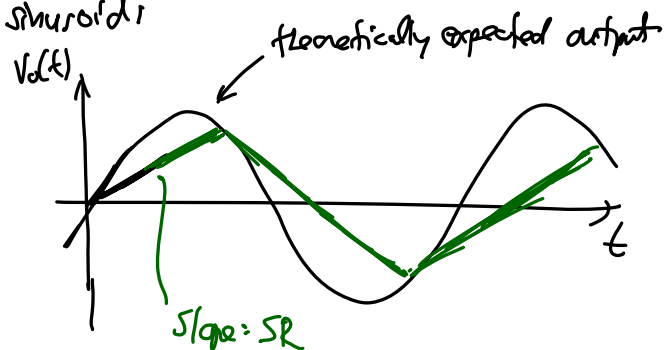If apply a very fast (i.e., high frequency), large amplitude sinusoid:



In terms of design variables:

$$SR = \frac{dV_o}{dt} = \frac{I_{xm}}{C_c} \uparrow \left(\frac{I_{xm}}{G_{m1}} \omega_{ult} A_o = SR \right)$$

$$C_c = \frac{G_{m1}}{\omega_{ult} A_o}$$

$$\omega_{ult} = \omega @ |a(j\omega)f| = 1$$

To Increase SR:

- ① Decrease G_{m1} ← transconductance of 1st stage
- ② Increase ω_{ult} ← increase ω_2
limited by the Xstart freq. range
- ③ Use a larger A_o , if possible.
closed loop gain (only if permitted by the application)

over ↻

① Emitter or Source Degeneration @ the Input Stage:



- ① R_E mismatched $\rightarrow V_{OS} \uparrow$
 \searrow must limit value of R_E to limit V_{OS}
- ② $R_E \uparrow \rightarrow \text{gain} \downarrow$ (SR-gain trade-off)
- ③ R_E contributes noise (thermal) \rightarrow

FETs: $\frac{g_m}{I_D} \approx \frac{2}{V_{GS} - V_t}$ $\sim 0.2V$

For BJTs: $\frac{g_m}{I_C} = \frac{1}{V_T} \leftarrow \sim 25 \text{ mV}$

$$\frac{\text{FET SR}}{\text{BJT SR}} = \frac{\frac{I_D}{g_{mF}} \omega_{ult}}{\frac{I_C}{g_{mB}} \omega_{ult}} = \frac{\frac{V_{GS} - V_t}{2}}{V_T} = \frac{V_{GS} - V_t}{2V_T} \approx \frac{260}{26} \approx 10$$

Limitations:

- ① Higher V_{DS}