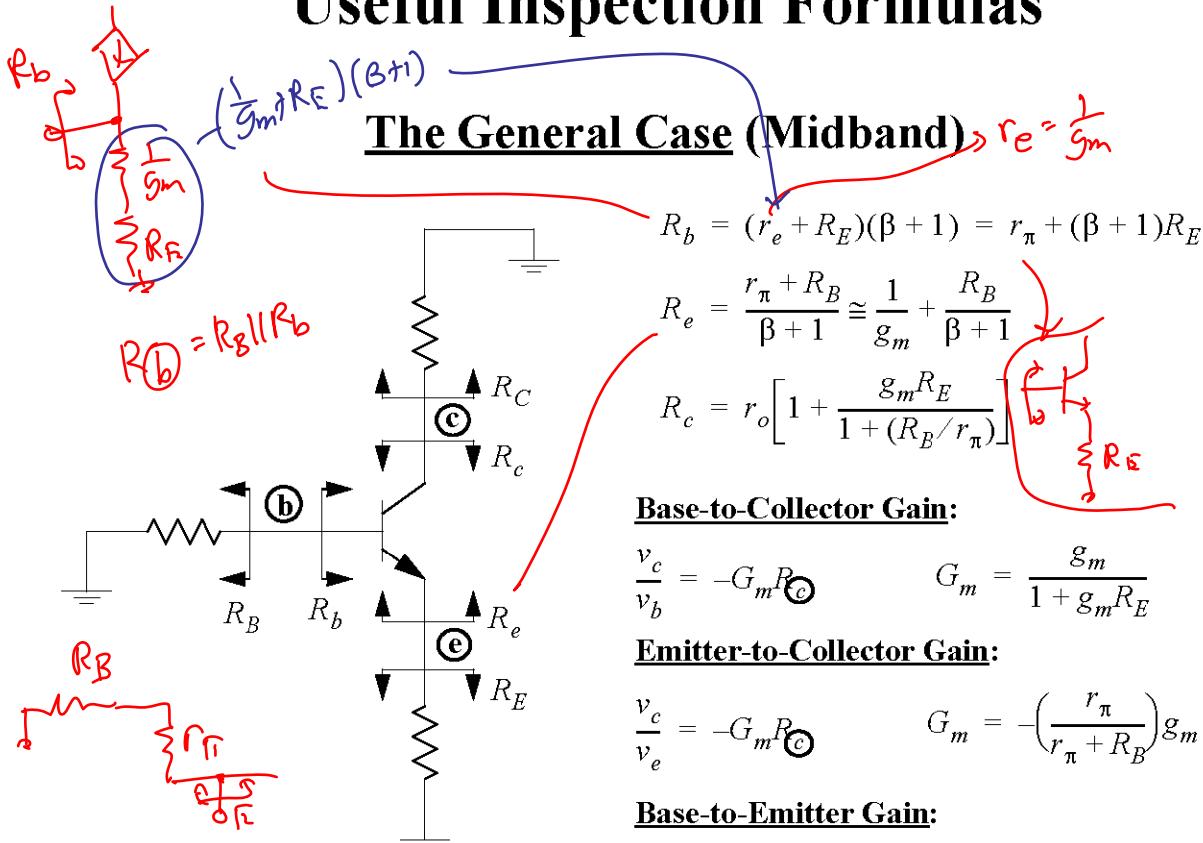


Useful Inspection Formulas




Node Resistances:

$$R_{\odot} = R_C \parallel R_c$$

$$R_{\odot} = R_E \parallel R_e$$

$$R_{\oslash} = R_B \parallel R_b$$

High Frequency Analysis

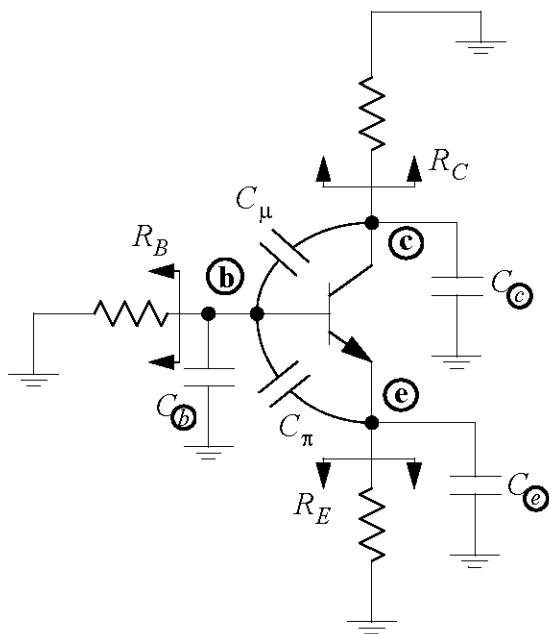

$$\omega_H = \frac{1}{\tau_b + \tau_c + \tau_e + \tau_{\mu o} + \tau_{\pi o}}$$

$$\tau_b = C_B R_{\oslash}$$

$$\tau_c = C_C R_{\odot}$$

$$\tau_e = C_E R_{\odot}$$

$$\tau_{\pi o} = C_\pi R_{\pi o}$$


$$\tau_{\mu o} = C_\mu R_{\mu o}$$

$$R_{\pi o} = r_\pi \parallel \frac{R_B + R_E}{1 + g_m R_E}$$


$$R_{\mu o} = R_{\oslash} + R_{\odot} + G_m R_{\odot} R_{\oslash}$$

Frequent Cases (Midband)

Common Emitter

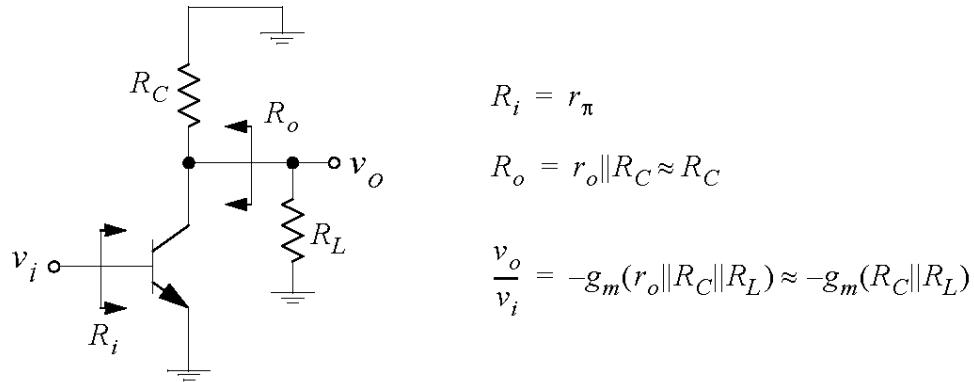

Common Collector (Emitter Follower)

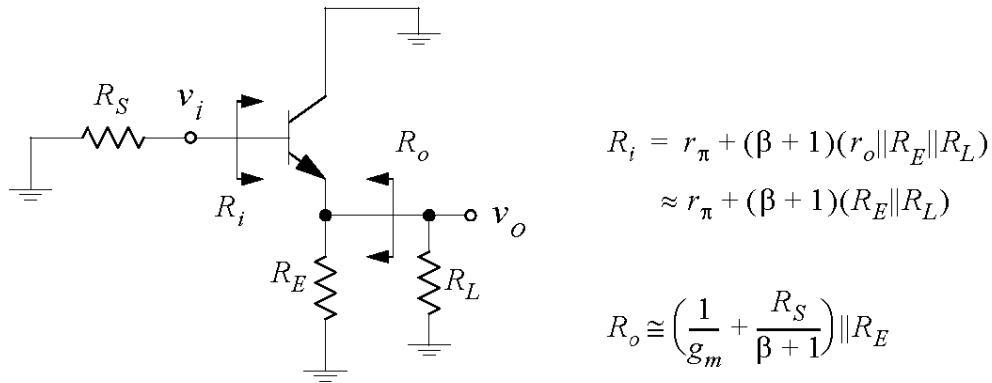

$$\frac{v_o}{v_i} = \frac{(r_o \parallel R_E \parallel R_L)}{(r_o \parallel R_E \parallel R_L) + r_e} = \frac{(\beta + 1)(r_o \parallel R_E \parallel R_L)}{(\beta + 1)(r_o \parallel R_E \parallel R_L) + r_\pi} \approx \frac{(\beta + 1)(R_E \parallel R_L)}{(\beta + 1)(R_E \parallel R_L) + r_\pi}$$

Common Base

