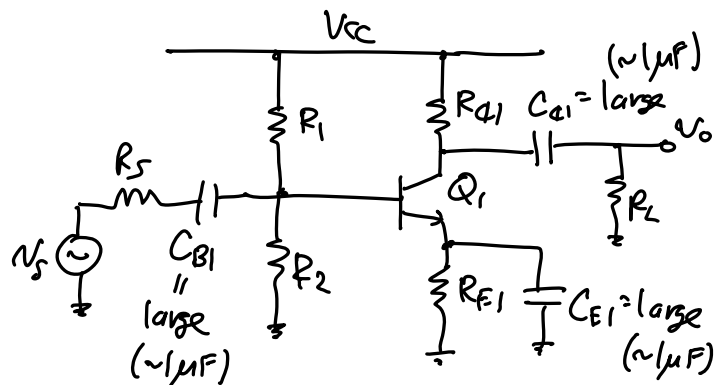


Lecture 4: Inspection Analysis

- Announcements:
- Inspection formula sheet handed out in class
 - ↳ It's also online
- HW#1 due tomorrow at 8 a.m. in the EE140/240A box near 125 Cory
- No labs this week
- -----
- Lecture Topics:
 - ↳ Procedure for Small Signal Analysis
 - ↳ Inspection Formulas
 - ↳ 1-Tx Amplifier Examples
- -----

Procedure for Small-Signal Analysis


Ex. Discrete Common-Emitter Ckt.





Want R_i , R_o , & $g_{mth} = \frac{V_o}{V_s}$.

Procedure:


- ① Find the DC operating pt. — get voltages & currents at all nodes & all branches, respectively
- ② Determine the small-signal (s.s.) parameter for devices in the signal path (e.g., g_m , r_{π} , ...)
- ③ Convert the full ckt. to the S.S. ckt.
 - ⇒ zero out the dc sources
 - DC voltage source → short
 - DC current source → open
 - ⇒ short out large capacitors
- ④a If needed, replace the Xs for w/ its model (e.g., hybrid- π , T, ...)
 - ⇒ this should NOT be needed often
 - ⇒ when is it needed? → generally, in cases where there is feedback! →
- ④b Analyze by inspection based on prior S.S. analysis experience!
 - ↓
 - This should be 99% of the time
 - Don't draw the hybrid- π model!

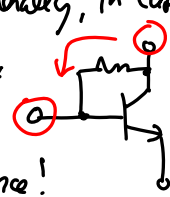

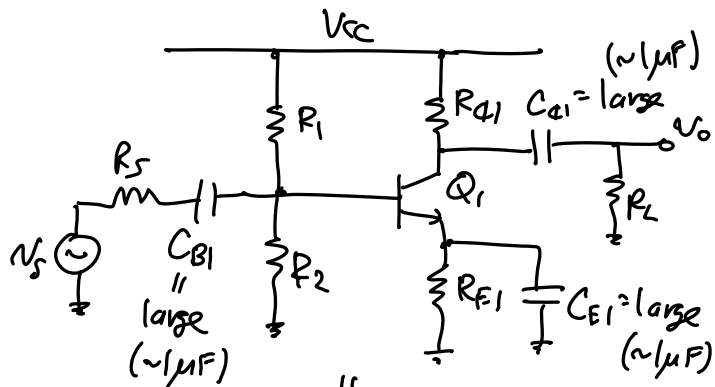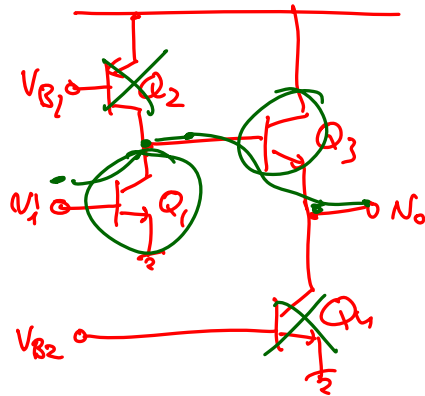Signal paths (to answer a question that came up)



Connect to S.S. clcf.

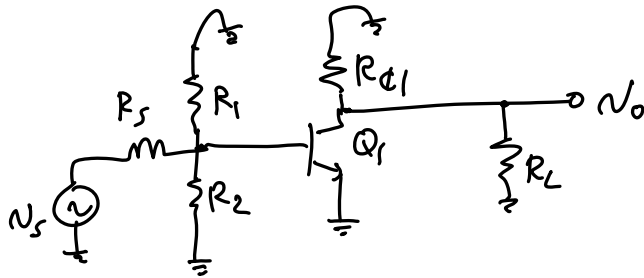


Nomenclature:


$V_{\phi} \leftarrow DC$
"copied"

$V_C \rightarrow$ full signal
 N_C $V_C = V_{\phi} + N_C$


$N_C \leftarrow$ small-signal

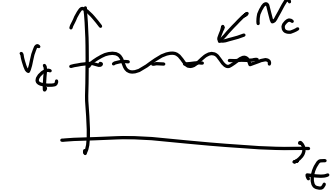

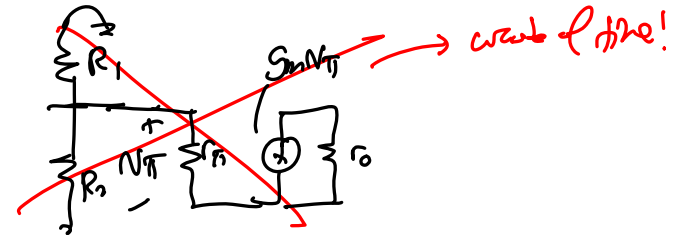What did I not do? Didn't draw the hybrid- π




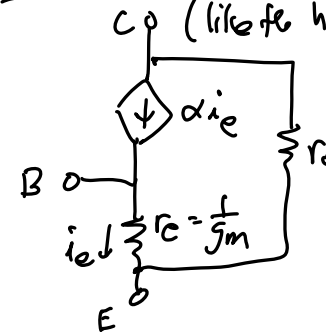T-Model - S.S. equiv. clcf. for a transistor
(like the hybrid- π model \rightarrow equivalent)




- Now, go through the inspection analysis sheet
 - Show how some things are a bit easier to visualize w/ the T-model
 - Others easier to visualize with the hybrid-pi
- Then, back to the small-signal analysis example:

S.s. Ckt.

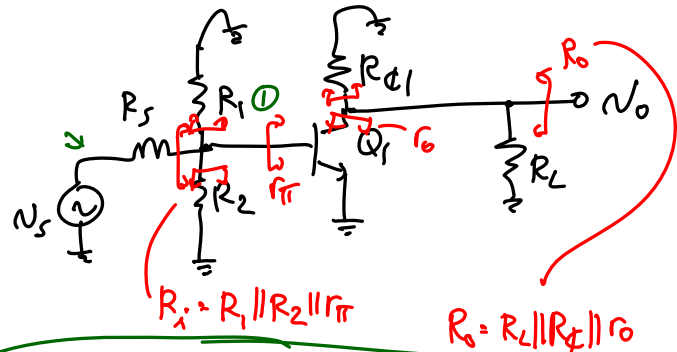


$$G_{\text{cm}} = \frac{N_o}{N_s} = \frac{V_o}{V_s} \cdot \frac{V_o}{V_o} = \left(\frac{R_1 || R_2 || r_{\pi}}{R_1 || R_2 || r_{\pi} + R_s} \right) g_{m1} (R_{\phi 1} || R_L)$$

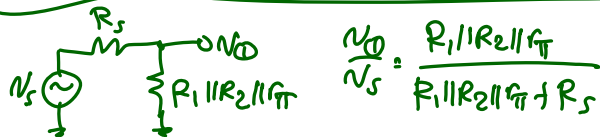

$$\frac{V_o}{V_o} = -G_m R_{\phi} = -g_{m1} (r_{o1} || R_{\phi 1} || R_L) \approx -g_{m1} (R_{\phi 1} || R_L)$$

$$G_m = \frac{g_{m1}}{1 + g_{m1} R_{EE}} = g_{m1} \quad R_{\phi} = R_{\phi 1} || r_{o1} || R_L$$

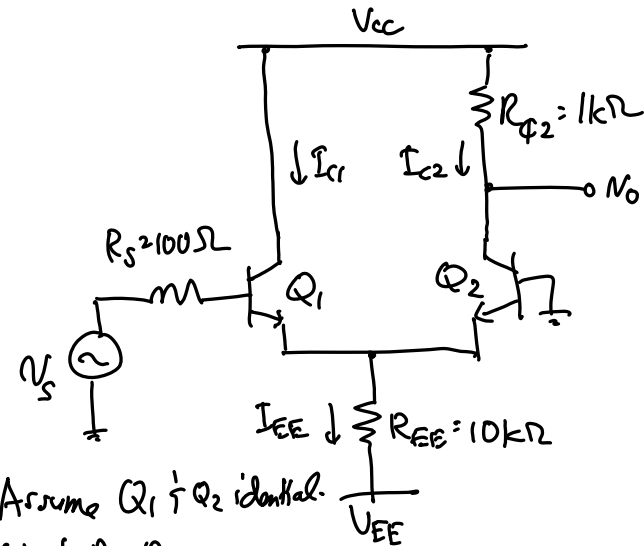Inspection Analysis of a Multi-Transistor Ckt.




Assume Q_1 & Q_2 identical.
Want R_i, R_o, g_{cm} .

First, get DC operating pt.

$$I_{C1} = I_{C2} = \frac{I_{EE}}{2} \rightarrow r_{\pi 1} = r_{\pi 2} = r_{\pi}$$

$$r_{o1} = r_{o2} = r_o$$

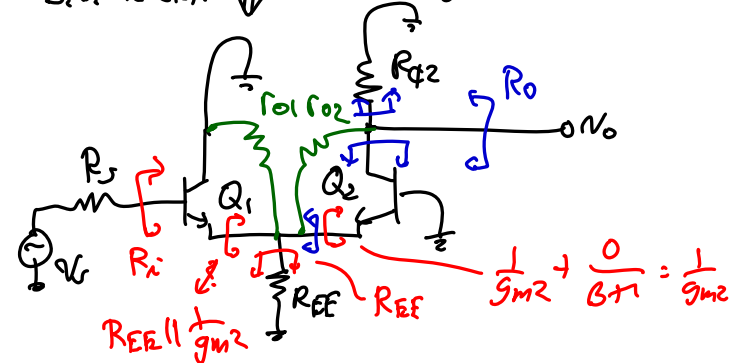S.s. ac ckt. \downarrow $g_{m1} = g_{m2} = g_m$



$$R_i = r_{\pi} + (\beta+1)R_E$$

$$= r_{\pi} + (\beta+1) \left(R_{EE} \parallel \frac{1}{g_{m2}} \right)$$

$\parallel r_{o1} \parallel r_{o2}$
for completeness!
(but usually
they are big, so
can be ignored!)

$$R_o = R_{\phi 2} \parallel r_{o2} \left(1 + \frac{g_{m2} \left(\frac{1}{g_{m1}} \right)}{1 + \beta} \right) = R_{\phi 2} \parallel 2r_{o2} \approx R_{\phi}$$

$$R_{EE} \parallel \left(\frac{1}{g_{m1}} + \frac{R_S}{\beta+1} \right) \parallel r_{o1} \parallel r_{o2}$$

Assume r_{o1} & r_{o2} are very large.

Also, given that R_S is small, which it usually is...