

**EE 140/240A**


**Inspection Analysis**

**CTN**

**1**

## Useful Inspection Formulas

### The General Case (Midband)

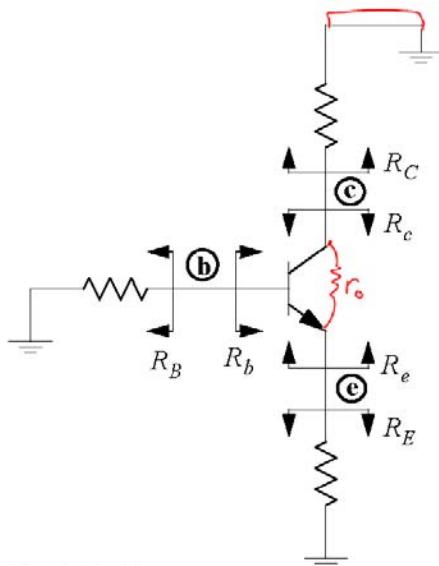

$$R_b = (r_e + R_E)(\beta + 1) = r_\pi + (\beta + 1)R_E$$

$$R_e = \frac{r_\pi + R_E}{\beta + 1} \cong \frac{1}{g_m} + \frac{R_E}{\beta + 1} \quad (r_o \gg R_E)$$

$$R_c = r_o \left[ 1 + \frac{g_m R_E}{1 + (R_E/r_\pi)} \right] \quad (g_m R_E \ll \beta_0)$$

$\hookrightarrow R_E = \text{small} \ll r_o$

#### Base-to-Collector Gain:

$$\frac{v_c}{v_b} = -G_m R_c \quad G_m = \frac{g_m}{1 + g_m R_E}$$

#### Emitter-to-Collector Gain:

$$\frac{v_c}{v_e} = -G_m R_c \quad G_m = -\left( \frac{r_\pi}{r_\pi + R_E} \right) g_m$$

#### Base-to-Emitter Gain:

$$\frac{v_e}{v_b} = \frac{R_E \parallel r_o}{R_E \parallel r_o + r_e}$$


#### Node Resistances:

$$R_{\textcircled{C}} = R_C \parallel R_c$$

$$R_{\textcircled{E}} = R_E \parallel R_e$$

$$R_{\textcircled{B}} = R_B \parallel R_b$$

## High Frequency Analysis

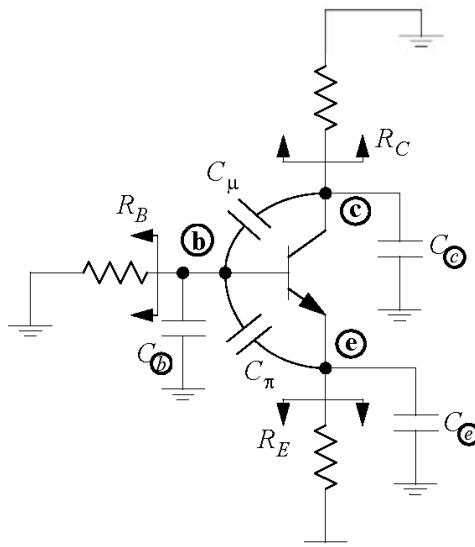

$$\omega_H = \frac{1}{\tau_{\textcircled{B}} + \tau_{\textcircled{C}} + \tau_{\textcircled{E}} + \tau_{\mu o} + \tau_{\pi o}}$$

$$\tau_b = C_{\textcircled{B}} R_{\textcircled{B}}$$

$$\tau_{\pi o} = C_\pi R_{\pi o}$$

$$\tau_c = C_{\textcircled{C}} R_{\textcircled{C}}$$

$$\tau_{\mu o} = C_\mu R_{\mu o}$$

$$\tau_e = C_{\textcircled{E}} R_{\textcircled{E}}$$

$$R_{\pi o} = r_\pi \parallel \frac{R_B + R_E}{1 + g_m R_E}$$

$$R_{\mu o} = R_{\textcircled{B}} + R_{\textcircled{C}} + G_m R_{\textcircled{C}} R_{\textcircled{B}}$$