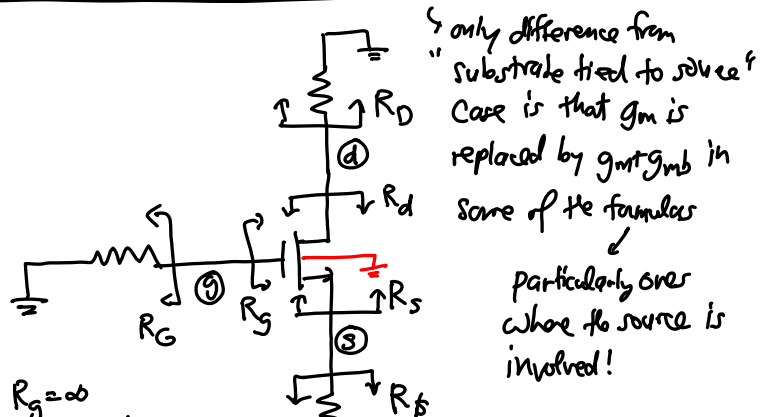


## Lecture 6w: Frequency Response Inspection Analysis I

## Lecture 6: Frequency Response Inspection Analysis

- Announcements:
- HW#2 due tomorrow at 8 a.m.
- HW#3 now online
- Lecture Topics:
  - ↳ Amplifier Bode plot
  - ↳ Open Circuit Time Constant (OCTC) Analysis
  - ↳ Frequency Response Inspection Analysis

• Last Time:Mos Inspection Formulas w/ Substrate Grounded

$$R_G = \infty$$

$$R_S = \frac{1}{g_m + g_{mb}}$$

$$R_D = r_o [1 + (g_m + g_{mb}) R_f]$$

$$\frac{v_d}{v_g} = -G_m R_D, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_f}$$

$$\frac{v_d}{v_s} = -G_m R_D, \quad G_m = -(g_m + g_{mb})$$


Remark: When the substrate is tied to the source,  $g_{mb} = 0$ .

Poles & Zeros → Bode Plots

$$v_i \rightarrow A(s) \rightarrow v_o$$

$$A(s) = \frac{v_o}{v_i}(s) = \frac{a_0}{(1 + \frac{s}{\omega_b})(1 + \frac{s}{\omega_{p2}})(1 + \dots)}$$


$\omega_{p1}$

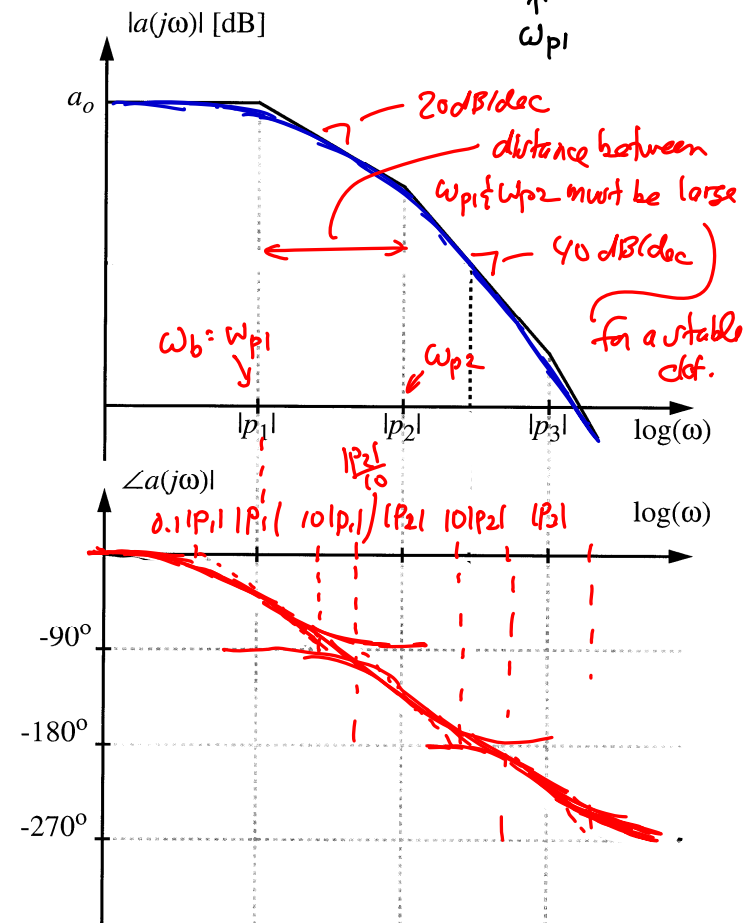

## Lecture 6w: Frequency Response Inspection Analysis I
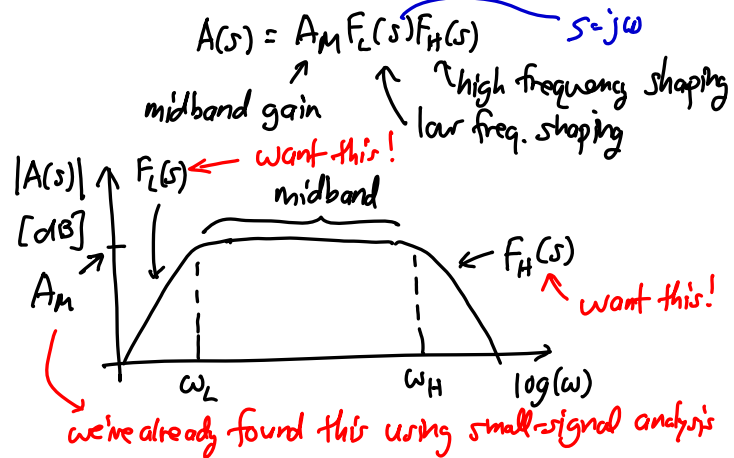
## Freq. Response

Recall that the transfer function of a general amplifier can be expressed as a function of frequency via:



## High Freq. Response Determination Using Open Ckt. Time Constant (OCTC) Analysis

In general:

$$F_H(s) = \frac{1 + a_1 s + a_2 s^2 + \dots + a_{n_z} s^{n_z}}{1 + b_1 s + b_2 s^2 + \dots + b_{n_p} s^{n_p}}, \quad n_p > n_z$$

$$= \frac{\prod_{j=1}^{n_z} \left(1 - \frac{s}{z_j}\right)}{\prod_{i=1}^{n_p} \left(1 - \frac{s}{p_i}\right)} = \frac{\prod_{j=1}^{n_z} \left(1 + \frac{s}{\omega_{zj}}\right)}{\prod_{i=1}^{n_p} \left(1 + \frac{s}{\omega_{pi}}\right)}$$

$\text{Im}(s)$   $\text{Re}(s)$

from which:

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn_p}} = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{k=1}^{n_p} \tau_{pk}$$

$\uparrow$  coeff. of the 1<sup>st</sup> order term

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{n_p} \tau_{pi} = \sum_j C_j R_{jo} = \sum_j \tau_{jo}$$

where  $C_j$  are capacitors in the H.F. ckt., i.e., small ones  
 $R_{jo} \triangleq$  driving pt. resistance seen between the terminals of  $C_j$  determined with

- ① all small ( $< 1nF$ ) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e.,  $> 1\mu F$  or  $> 1nF$ )

In calculating the H.F. response, we use the dominant pole approximation:

(i)  $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pn_p}$

(ii)  $F_H(s) \approx \frac{1}{1 + \frac{s}{\omega_H}}$

(ii)  $b_1 \approx \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \approx \frac{1}{b_1} = \frac{1}{\sum_j \tau_{jo}} = \frac{1}{\sum_j C_j R_{jo}}$


When there is no dominant pole, an approximate expression for  $\omega_H$  is:

$$\omega_H \approx \sqrt{\frac{1}{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots - \frac{1}{\omega_{z1}^2} - \frac{1}{\omega_{z2}^2} - \dots}}$$


(just FYI)

- Now, go to inspection formula sheet and go over how to use the frequency response parts


Example H.F. Analysis (C.E. Ckt.)

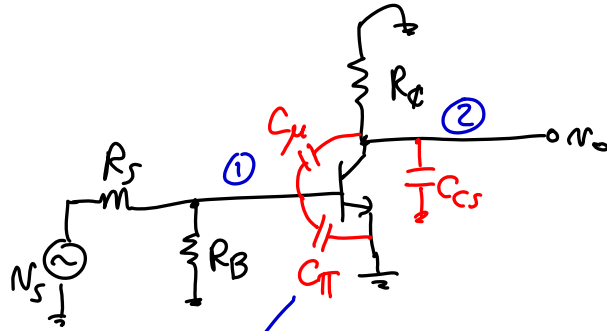

Find  $\tau_{\text{in}}$ :

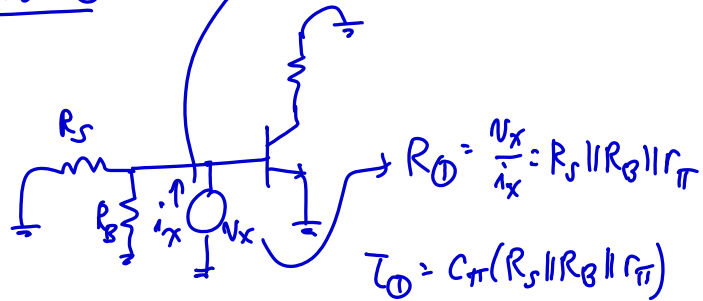


Find  $\tau_{\text{out}}$ :

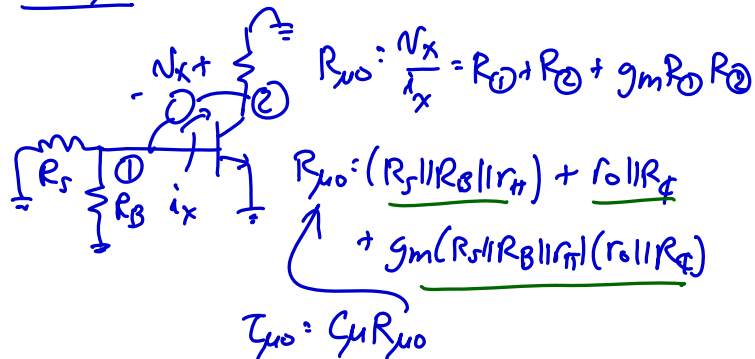

Find  $\tau_{\text{out}}$ :  $\tau_{\text{out}} = C_{\text{out}} R_{\text{out}}$

$$\omega_H = \frac{1}{\tau_{\text{in}} + \tau_{\text{out}} + \tau_{\text{mu}}}$$

Now, use Miller's Theorem:

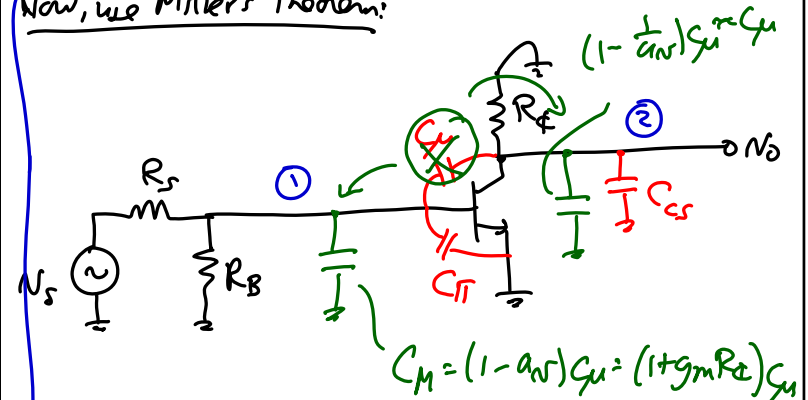

$$\tau_{\text{in}} = (R_s || R_1 || R_2 || r_{\pi}) (C_{\pi} + C_{\mu} (1 + g_m R_L))$$

$$\tau_{\text{out}} = R_L (C_{\mu} + C_{\text{cs}})$$

$$\omega_H = \frac{1}{\tau_{\text{in}} + \tau_{\text{out}}}$$

Same as

Multi-Stage Ex.

Assume large

$$\tau_1 = (R_s / 2\pi) C_{\pi 1}$$

$$\tau_{\pi 1} = C_{\pi 1} \left( r_{\pi 1} \parallel \frac{R_s + \frac{1}{g_{m2}}}{1 + g_{m1} \left( \frac{1}{g_{m2}} \right)} \right)$$

$$\tau_2 = C_{\pi 2} \left( \left( \frac{1}{g_{m1}} + \frac{R_s}{\beta + 1} \right) \parallel \frac{1}{g_{m2}} \parallel R_{EE} \right)$$

$$\tau_3 = (C_{cs2} + C_{ce2}) R_{f2}$$

$$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3 + \tau_{\pi 1}}$$

MOS Two-Stage Amplifier

$C_{\pi 1} = C_{gs1} (1 + g_{m1} R_{D1})$

$$\tau_1 = [C_{gs1} + C_{gs1} (1 + g_{m1} R_{D1})] R_s$$

$$\tau_2 = [C_{gs1} + C_{db1} + C_{gs2}] (R_{D1} \parallel R_{D1})$$

$$\tau_3 = C_{sb2} \left( \frac{1}{g_{m2} + g_{mb2}} \parallel R_{S2} \right)$$

because no signal occurs  $C_{gs2}$  w/ 2nd stage gain  $N_x \approx 1$


$$\tau_{gs2} = C_{gs2} \left( \frac{R_{D1} + R_{S2}}{(1 + (g_{m2} + g_{mb2}) R_{S2})} \right)$$

$$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3 + \tau_{gs2}}$$

## Lecture 6w: Frequency Response Inspection Analysis I

## Low Freq. Amplifier Response Using Short Circuit Time Constant Analysis (SCTC)

Recall:

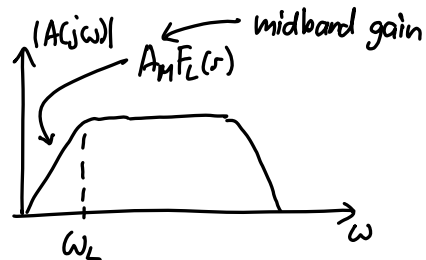

In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}, \quad n_z = \# \text{ poles} = \# \text{ zeros}$$

We can express the coefficient  $e_1$  by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn_z}$$

For the case of a dominant pole:

↳ i.e., the highest freq. pole

$$F_L(s) \approx \frac{s}{s + \omega_L} = \frac{s}{s + e_1} \rightarrow e_1 \approx \omega_{p1} = \omega_L$$

$$\therefore \omega_L \approx e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{js}} = \sum_j \frac{1}{\tau_{js}}$$

where  $C_j \triangleq$  various large ( $> 10 \text{ nF}$ ) capacitors in the ckt. (e.g., the bypass caps.) $R_{js} \triangleq$  driving point resistance seen between the terminals of  $C_j$  determined with:

For reading, can go to Sedra &amp; Smith

- ① all large capacitors short-circuited, except  $C_j$ , which is replaced by the test voltage source for  $R$  determination


② all independent sources eliminated (i.e., short voltage sources, open current sources)

③ open all H.F. capacitors (i.e., small caps in the pF range, or  $< 1 \text{ nF}$ )


Again, for the case where there are no dominant poles, a reasonable approximation is:

$$\omega_L \approx \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$

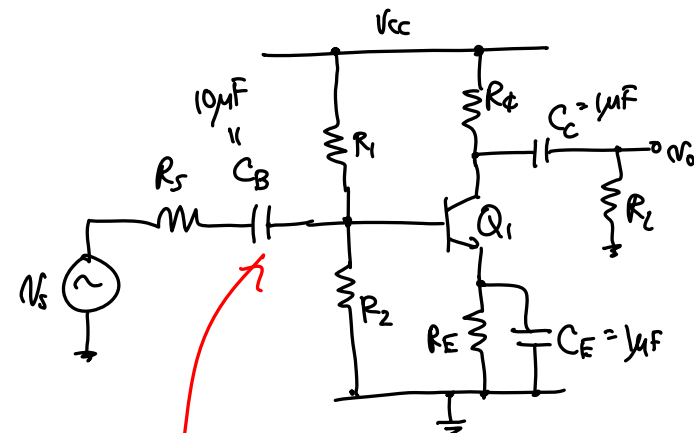Ex: Determine the L.F. response of the C.E. Amplifier



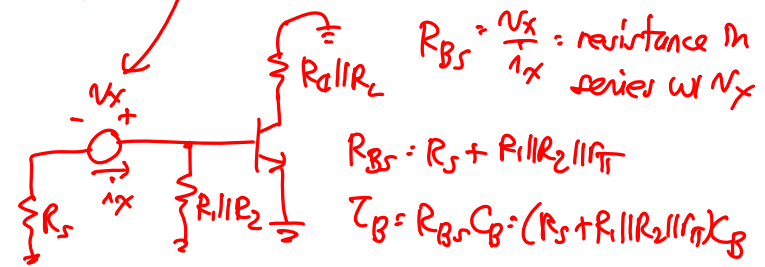(a)  $\tau$  due to  $C_B$ : short ckt.  $C_C \neq C_E$



$$\omega_{PB} = \frac{1}{C_B} = \frac{1}{(R_1 + R_1 || R_2 || r_{\pi}) C_B}$$