

Lecture 9: Supply & Temperature Independent Biasing

• Announcements:

- ↳ Lab#1's due next week in your lab section (on Friday, Feb. 29)
- ↳ Lab#2 will be online this week
  - This is a hardware lab, so you will need to use the lab to make measurements
  - You are all being added to the access list for 353 Cory
- ↳ Those taking 240A will soon get additional HW assignments to supplement the regular ones

• Lecture Topics:

- ↳ Widlar Current Source
- ↳ Supply & Temperature Independent Biasing
- ↳ Output Swing (Headroom)
- ↳ High Swing Current Sources


• Last Time:

- Reviewed current sources using prepared lecture material
- Now finish this (with Widlar current sources)

over

To reduce the error term, use a

Buffered  $V_{BE}$  Generator

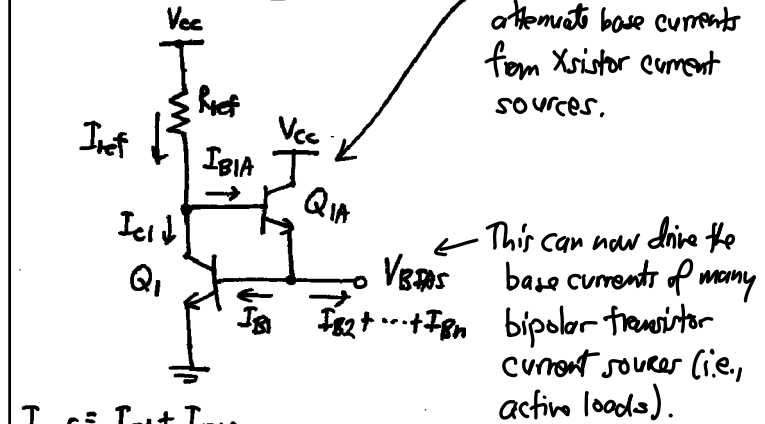

$$I_{ref} = I_{C1} + I_{B1A}$$

$$I_{B1A} = \frac{I_{B1} + I_{B2} + \dots + I_{Bn}}{\beta + 1} = \frac{n I_{C1}}{\beta(\beta + 1)}$$


[Assuming identical Xsistors]


$$I_{ref} = I_{C1} \left( 1 + \frac{n}{\beta(\beta + 1)} \right)$$

$$\rightarrow I_o = I_{C2} = \frac{I_{ref}}{1 + \frac{n}{\beta(\beta + 1)}} \approx I_{ref} \left( 1 - \frac{n}{\beta^2} \right)$$

Note: Now,  $I_{ref} = \frac{V_{cc} - 2V_{BE(on)}}{R_{ref}}$

Problem: For power savings reasons, oftentimes very small bias currents are needed, on the order of  $\mu A$ . This is might force for large an  $R_{ref}$  in the above bipolar  $V_{BEAS}$  generator.

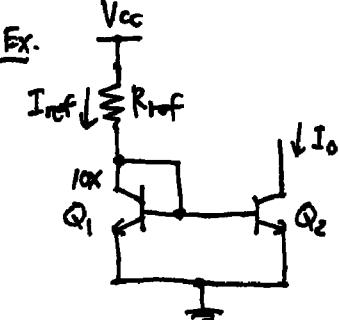Ex. 

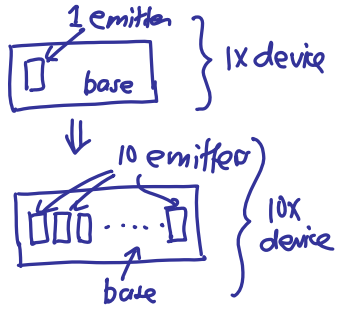


i.e., larger emitter area:  $\rightarrow$  layout like this to get more accurate ratio.

If  $Q_1$  is 10x larger than  $Q_2$ .  
 $\therefore I_{S1} = 10 I_{S2} \rightarrow I_0 \approx I_{ref}/10$   
 $\therefore I_0 = \frac{(V_{cc} - V_{BE(on)})}{10 R_{ref}} \rightarrow R_{ref} = \frac{V_{cc} - V_{BE(on)}}{10 I_0}$   
 $\uparrow$  this helps to lower  $R_{ref}$ , but is it enough?

Ex.  $I_0 = 5 \mu A$ ,  $V_{cc} = 30V$   
 $R_{ref} \approx \frac{30}{5 \mu A} = 600 k\Omega$   $\leftarrow$  That's way too big!  
 (Yes, there's only one of them on the chip, but this takes up too much space!)

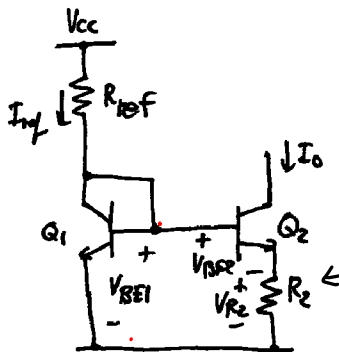The Low Current Solution: **Widlar Current Source**  
 $\Rightarrow$  scale  $I_{C2} = I_0$  by reducing  $V_{BE2}$  (relative to  $V_{BE1}$ ):  
 Do this by emitter degenerating  $Q_2$  via  $R_2$



$V_{BE1} = V_{BE2} + V_{R2} = V_{BE2} + \frac{1}{\alpha} I_{C2} R_2 \approx V_{BE2} + I_{C2} R_2$   
 $I_{C2} R_2 = V_{BE1} - V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$   
 $I_{C2} R_2 = V_T \ln \frac{I_{C1}}{I_{C2}} \quad [\text{Assuming } Q_1 \neq Q_2 \text{ are matched}]$   
 $I_0 R_2 = V_T \ln \frac{I_{ref}}{I_0}$

Rule of Thumb:  $V_{R2} = I_{C2} R_2$   $\frac{I_{C2} \cdot I_0}{\frac{1}{2} I_{ref}}$   
 18 mV  $\frac{1}{2} I_{ref}$   
 42 mV  $\frac{1}{5} I_{ref}$   
 60 mV  $\frac{1}{10} I_{ref}$   
 120 mV  $\frac{1}{100} I_{ref}$


$\rightarrow$  Sub example again

Ex. scale by 100x using Widlar source  
 $V_{BE1} - V_{BE2} = 120 mV \rightarrow R_2 = \frac{120 mV}{5 \mu A} = 24 k\Omega$   
 $\downarrow$   
 $I_{ref} = 500 \mu A \rightarrow R_{ref} = \frac{30V}{500 \mu A} = 60 k\Omega$   
 $\uparrow$   
 More reasonable than 600k $\Omega$  before.  
 If want smaller, scale by 100x instead.

Another advantage of the Widlar: larger  $R_0 \therefore$  a more ideal current source:  
 $R_0 = r_{o2} (1 + g_{m2} R_2)$
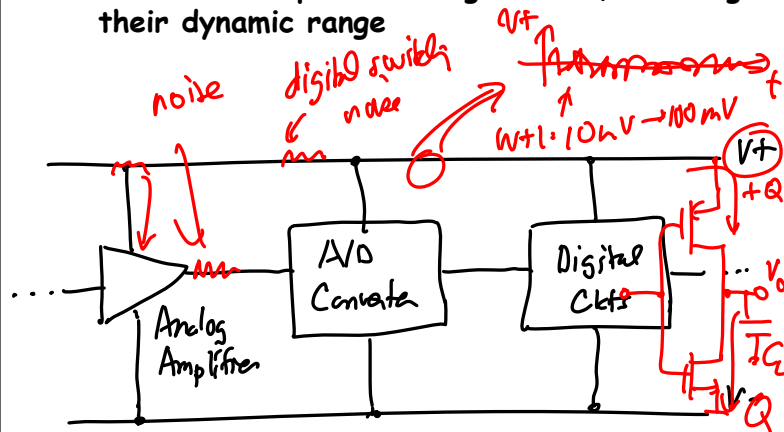
### Supply & Temperature Independent Biasing

- Why is it necessary?
- For battery-operated systems, battery voltages vary over time
  - ↳ Amplifier gains change
  - ↳ Power consumption changes
  - ↳ Frequency of oscillators changes
  - ↳ In summary: long-term stability degrades
  - ↳ Large uncertainty in biasing translates to overdesign that wastes power
- Same issues as above when temperature varies with time
- Short-term supply variations
  - ↳ In mixed signal circuits, i.e., both analog and digital together, digital switching generates noise on the supply lines
  - ↳ Noise can couple to analog circuits, reducing their dynamic range




Definition. Sensitivity of  $Y$  to  $x$

$$S_x^Y = \frac{\frac{\Delta Y}{Y}}{\frac{\Delta X}{X}} = \frac{X}{Y} \frac{\Delta Y}{\Delta X} = \frac{X}{Y} \frac{\partial Y}{\partial X}$$

For supply independence, we want  $S_{V_{CC}}^{I_0} = 0$ .

### Simple Current Source

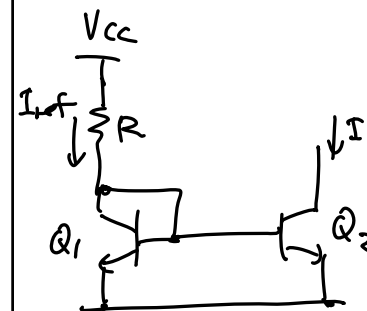

Neglecting base currents:

$$I_0 \approx I_{ref} = \frac{V_{CC} - V_{BE(on)}}{R}$$

$$I_0 \approx \frac{V_{CC}}{R} \quad (V_{CC} \gg V_{BE(on)})$$

Then:

$$S_R^{I_0} = \frac{R}{I_0} \frac{\partial I_0}{\partial R} = \frac{R^2}{V_{CC}} \left( -\frac{V_{CC}}{R^2} \right) \Rightarrow S_R^{I_0} = -1$$

$$S_{V_{CC}}^{I_0} = \frac{V_{CC}}{I_0} \frac{\partial I_0}{\partial V_{CC}} = R \left( \frac{1}{R} \right) \Rightarrow S_{V_{CC}}^{I_0} = 1$$

∴ a 10% change in  $V_{CC}$  leads to 10% change in  $I_0$ .  
(terrible!)

Widlar Current Source (Any better?) ( $\ln I_{ref} - \ln I_0$ )

$V_T \ln \frac{I_{ref}}{I_0} = I_0 R_2$

Differentiate w/r to  $V_{cc}$ :

$$V_T \left( \frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} - \frac{1}{I_0} \frac{\partial I_0}{\partial V_{cc}} \right) = R_2 \frac{\partial I_0}{\partial V_{cc}}$$

↓ math

$$\frac{\partial I_0}{\partial V_{cc}} = \frac{V_T}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \frac{I_0}{(R_2 + \frac{V_T}{I_0})}$$

$\therefore S_{V_{cc}}^{I_0} = \frac{V_{cc}}{I_0} \frac{\partial I_0}{\partial V_{cc}} = \frac{V_T \left( \frac{V_{cc}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \right)}{I_0 R_2 + V_T}$

$\Rightarrow S_{V_{cc}}^{I_0} = \left( \frac{1}{1 + \frac{I_0 R_2}{V_T}} \right) S_{V_{cc}}^{I_{ref}}$

Since  $I_{ref} \approx \frac{V_{cc} - V_{BE(sat)}}{R_1} \approx \frac{V_{cc}}{R_1} \Rightarrow S_{V_{cc}}^{I_{ref}} \approx 1$

$$\therefore S_{V_{cc}}^{I_0} \approx \frac{1}{1 + \frac{I_0 R_2}{V_T}}$$

For  $I_{ref} = 1\text{mA}$ ,  $I_0 = 10\mu\text{A}$ ,  $R_2 = 11.9\text{k}\Omega$ , then

$10\% \Delta \ln V_{cc} \rightarrow 1.39\% \Delta \ln I_0$

(better than simple current source)

How can we do better? → Use another voltage reference:


- ✓ ①  $V_{BE}$  → base-emitter junction voltage
- ②  $V_Z$  → Zener diode
- ③  $V_t$  → threshold voltage (MOS)
- ✓ ④  $V_T = \frac{kT}{q}$  → thermal voltage
- ✓ ⑤  $E_g$  → bandgap

If we can eliminate this '1',  
 then  $S_{V_{cc}}^{I_o} = 0 \rightarrow$  need to eliminate  $I_{ref}$   
 dependence on  $V_{cc}$

This is pretty damn sad!  $S_{V_{CC}}^{I_{ref}} \rightarrow S_{V_{CC}}^{I_0} \approx 0$

- 240A folks: read Gray & Meyer
  - ↳ Sections 4.4.2 through 4.4.3
  - ↳ These cover supply and temperature independent biasing, including bandgap references
  - ↳ Can also read Razavi, Chpt. 11, on bandgap references

Issue: Output Swing (Headroom)

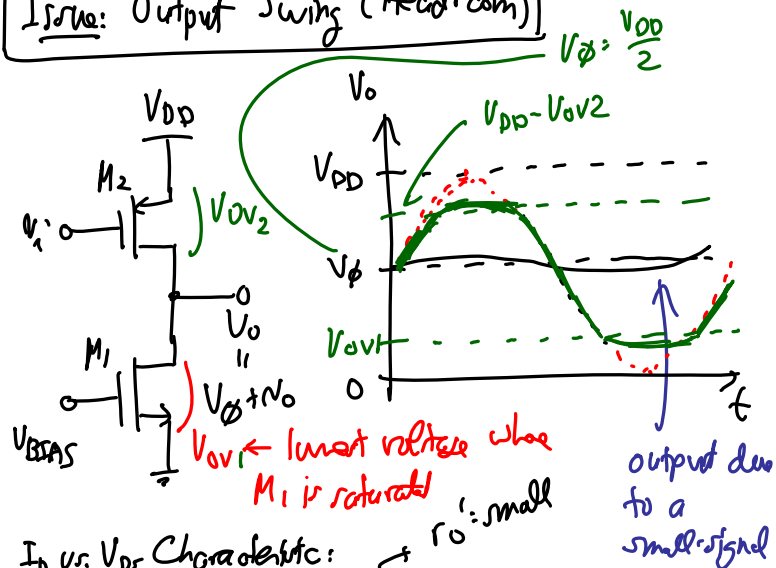

$I_D$  vs.  $V_{DS}$  Characteristic:

