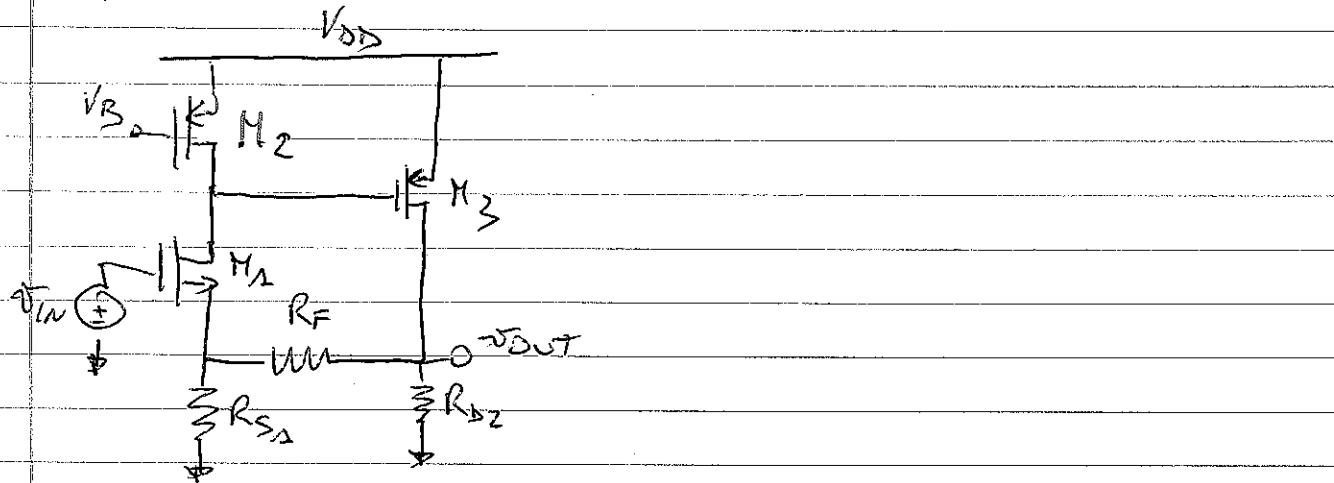


DISCUSSION 13




? Type of feedback

Series - shunt. The circuit aims at providing an ideal voltage reading at the input and at lowering the impedance of the output node to provide as ~~as~~ ideal of an output voltage as possible.

Q A.C.L.

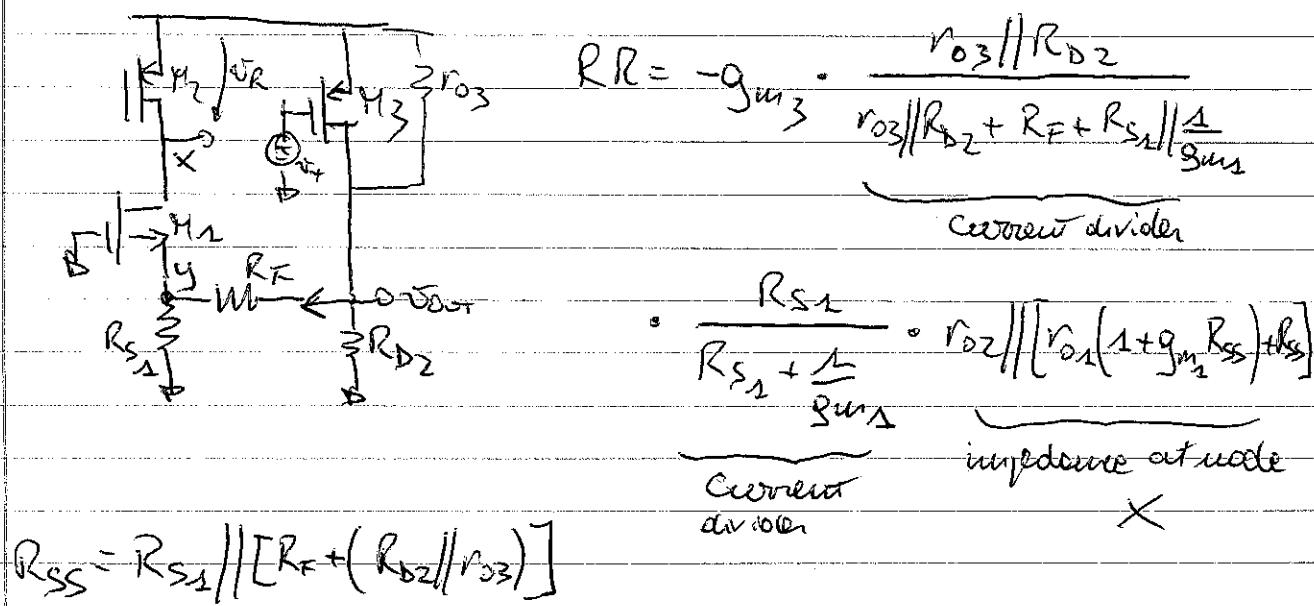- R.R. - set the  $\text{Q}_{\text{op}}$  at the gate of M<sub>3</sub>



$$-A_{\text{D}} = 1 + \frac{R_F}{R_{S1}}$$

The source of  $M_1$  needs to follow the gate, to have  $v_{GS_{M1}} = 0$  not to create infinite current in  $M_1$  ( $g_{m1} \rightarrow \infty$ ). So  $v_y = v_n$

Also, no current flows in  $M_2$ , otherwise it would create a drop on the  $v_{DS_{M2}}$  and a finite  $v_{GS_{M2}}$ , which would cause infinite current at the output because  $g_{m2} \rightarrow \infty$ .

$$\Rightarrow v_o = v_y + v_{RF} = v_{in} + R_F \frac{v_{in}}{R_{S1}} = \left(1 + \frac{R_F}{R_{S1}}\right) v_{in}$$

$$-A_{\text{O}} = 0$$

Since the input is fed to a deactivated device, no signal can flow to the output.

$$\Rightarrow A_{CL} = \frac{A_{\text{D}}}{1 + \frac{1}{RR}}$$

### Input impedance

The input impedance  $R_{in} \rightarrow \infty$  because the input is fed to the gate of a MOS

## Output impedance

Using Blackman's formula

$$Z_{\text{out}} = Z_{\text{out}}(\alpha=0) \frac{1+RR_{\text{SHORT}}}{1+RR_{\text{OPEN}}}$$


$$Z_{\text{out}}(\alpha=0) = r_o \parallel R_{D2} \parallel [R_F + (R_{S2} \parallel \frac{1}{g_m})]$$

$$RR_{\text{SHORT}} \approx 0$$

$$RR_{\text{OPEN}} = RR$$

The short output aims at lowering the output impedance.

Now with Two-port

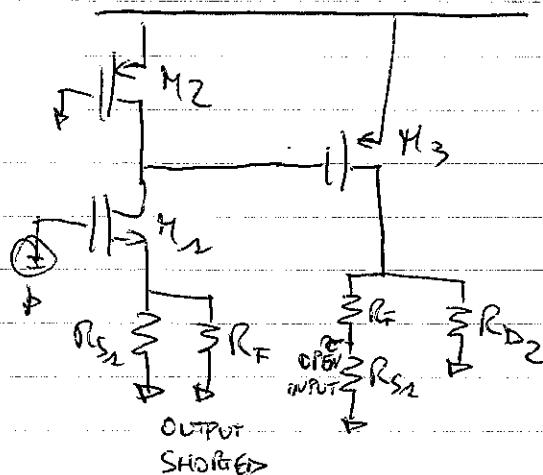

$$f = h_{12f} = \left. \frac{v_2}{v_1} \right|_{i_2=0} = \frac{R_{S2}}{R_{S2} + R_F}$$

$$\alpha = \frac{g_{m1}}{1 + g_{m1} R_{S2} / R_F} \cdot r_o \parallel [r_o \parallel (1 + g_{m1} R_{S2} / R_F) + R_{S2} / R_F]$$

$$- g_{m3} \cdot [r_o \parallel R_{D2} / (R_{S2} + R_F)]$$


$$\alpha T_{ce} = \frac{a}{1+af}$$

$$Z_{in} = n$$

$$Z_{out} = Z_{out}(a=0) \cdot \frac{1}{1+af} \quad \text{Slewing connection}$$

x ————— x

Now we modify the circuit as follows

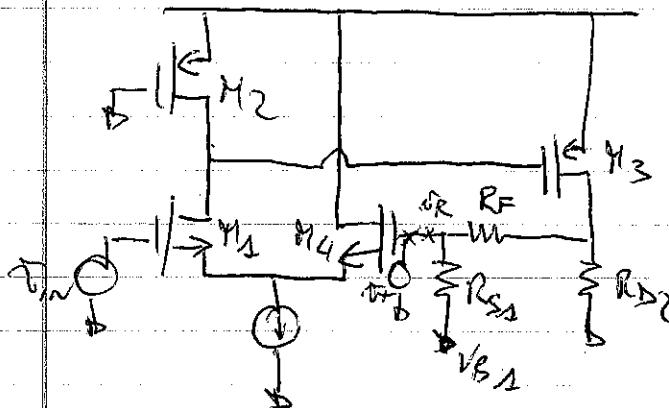


We have added a source-follower M4 to the circuit. This helps to make the current indeed uni-directional.

$$RR = \frac{g_{m4}}{1 + g_{m4} \cdot \frac{1}{RS_2}} \cdot r_{o2} \parallel [r_{o1}(1 + g_{m2} \cdot \frac{1}{g_{m4}})]$$

$$\cdot -g_{m3} \cdot R_{D2} \parallel R_{D3} \parallel R_{S2} + R_F \cdot \frac{R_{S1}}{R_{S1} + R_F}$$

$$A_V = 1 + \frac{R_F}{R_{S2}} \quad A_o = 0$$

Now with two port analysis

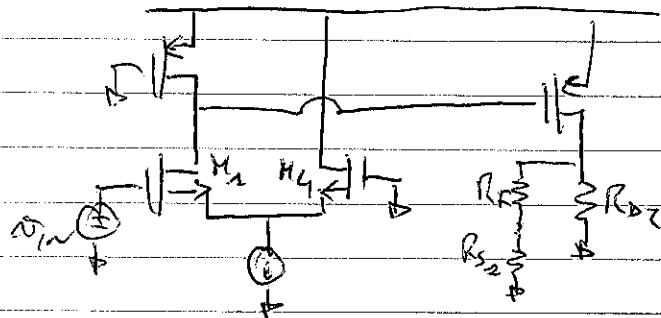

$$a = \frac{g_{m1}}{1 + g_{m1} \cdot \frac{1}{g_{m4}}} \cdot r_{o2} \parallel [r_{o3} \left( 1 + g_{m1} \cdot \frac{1}{g_{m4}} \right)] \\ - g_{m3} \cdot R_{D2} \parallel r_{o3} \parallel (R_{S2} + R_T)$$

$$f = \frac{R_{S1}}{R_{S1} + R_F}$$

$$\Rightarrow \text{Now } RR = af !$$

This shows that the approaches coincide when the circuit is truly fully differential! Otherwise, two-port method is just an approximation, while RR gives the exact answer.

