

Name Francis Scott

SID \_\_\_\_\_

Prob.	Score
1,2,3	/24
4,5	/20
6	/18
7,8	/20
9	/22
10, 11	/20
12	/20
13	/12
Total	/156

1. [8] In a vacuum tube, the plate (or anode) current is a function of the plate voltage (output) and the grid voltage (input).  $I_p = k(V_p + \mu V_g)^{3/2}$  where  $\mu$  is a function of the tube geometry.

a. Calculate  $g_m = \frac{\partial I_p}{\partial V_g} = \frac{3}{2} k (V_p + \mu V_g)^{1/2} \mu$

b. Calculate  $g_o = 1/r_o = \frac{\partial I_p}{\partial V_p} = \frac{3}{2} k (V_p + \mu V_g)^{1/2}$

c. Calculate the intrinsic gain from parts a and b

$-g_m/g_o = -\mu$  *missily minus ok*

d. Can you find intrinsic gain more easily by examining the equation for current? Explain.

$\rightarrow I_p = \text{const} \Rightarrow V_p + \mu V_g = \text{const} \Rightarrow \frac{V_p}{V_g} = -\mu$

2. [6] Your friend has designed a two stage Miller compensated op-amp, and is using a unity gain buffer in series with the compensation capacitor. He can't remember if it is supposed to point left or right, or which side of the capacitor it's supposed to be on.

a. Why use the buffer at all? What is its purpose?


*prevent feedforward current causing RHP zero*

b. Does it point left or right? Why?

*Left. Provide feedback, not forward*

 c. Which side of the capacitor should it be on? Why?

*Right. Stage 1 needs to see a capacitor to  $V_{out}$*



3. [10] You are designing a single-stage CMOS op-amp to be used in feedback to achieve a gain of 50. The gain must be accurate to 1% from DC to 20 Mrad/s. The load is a 1pF capacitor. You are restricted to biasing your transistors with overdrives between 100mV and 1V, and they look reasonably quadratic in that range.

a. What is the minimum open-loop gain and dominant pole location of the op-amp?

$f = \frac{1}{50} \quad \frac{1}{A_f} < 1\% \quad A > \frac{50}{1\%} = 5K$   *$\omega_p = 5K \omega_p \geq 20 \text{ Mrad/s}$*

b. What is the minimum unity gain frequency of the op-amp?

$(5K)(20 \text{ Mrad/s}) = 100 \text{ Mrad/s}$

c. What is the minimum transconductance of the input transistors?

$g_m \geq \omega_u C_L = (10^7 \text{ rad/s})(10^{-12} \text{ F}) = 0.1 \text{ S}$

d. What is the minimum current in each of the input transistors?

$I_b = \frac{g_m V_{ov}}{2} = \frac{(0.1)(0.1)}{2} = 5 \text{ mV}$

4. [10] An NMOS-input common source amplifier with a PMOS load is biased so that the NMOS transconductance is ten times greater than the PMOS transconductance.

a. What is the ratio of the PMOS gate noise power,  $\bar{v}_{n,P}^2$ , to the NMOS gate noise power,  $\bar{v}_{n,N}^2$ ?

$$\bar{v}_n^2 \sim \frac{1}{g_m} \quad \frac{\bar{v}_{n,P}^2}{\bar{v}_{n,N}^2} = \frac{g_{m,n}}{g_{m,p}} = 10$$

b. What is the ratio of the gain from the PMOS gate to the output,  $A_{VP}$ , to the gain from the NMOS gate to the output,  $A_{VN}$ ?

$$A_V \sim g_m \quad \frac{A_{V,P}}{A_{V,N}} = \frac{1}{10}$$

c. What is the total noise power spectral density in Volts squared per Hz at the output, in terms of  $\bar{v}_{n,P}$ ,  $A_{VP}$ ,  $\bar{v}_{n,N}$ , and  $A_{VN}$ ?

$$\bar{v}_{n,P}^2 A_{VP}^2 + \bar{v}_{n,N}^2 A_{VN}^2$$

d. What is the total noise power spectral density in Volts squared per Hz at the output in terms of just  $\bar{v}_{n,N}$ , and  $A_{VN}$ ?

$$(10 \bar{v}_{n,N}^2) \left(\frac{1}{10} A_{VN}\right)^2 + \bar{v}_{n,N}^2 A_{VN}^2 = 1.1 \bar{v}_{n,N}^2 A_{VN}^2$$

e. What is the total noise power spectral density in Volts squared per Hz at the **input** in terms of just  $\bar{v}_{n,N}$ , and  $A_{VN}$ ?

$$1.1 \bar{v}_{n,N}^2$$

5. [10] With the following selection of op-amp topologies, and assuming  $V_{TN} = -V_{TP} = 1V$ ,  $V_{DD} = 5V$

1. NMOS input diff pair with current mirror load
2. PMOS input diff pair with current mirror load
3. NMOS input 2 stage Miller compensated
4. PMOS input 2 stage Miller compensated
5. NMOS input folded cascode
6. PMOS input folded cascode

List which op-amps will work with which applications. If none, write none.

a) Switched capacitor amplifier with one input grounded -1 none

6

b) Unity gain buffer from 0 to 5V

none

c) Comparator making comparisons near  $V_{DD}$

3, 5 or none or 5

d) Unity gain buffer for signals near mid-rail, with capacitive load

all

e) Non-inverting amplifier with gain of 10 driving a 1k $\Omega$  resistive load

4 or none

6. [18] The figure below is a current mirror op-amp. Assuming a 0 to 5V supply,  $V_{TN} = -V_{TP} = 1V$ , and all transistors with the same number are the same size, and that  $g_{m}r_o \gg 1$  for all combinations.

a. What is the gain from a differential input (across the gates of 1A/B) to the voltage between the gates of 2A/B?

$$-\frac{g_{m1}}{g_{m2}} \quad \frac{g_{m1}}{g_{m2}} = \frac{1}{1} \quad -1$$

b. What is the gain from the gate of 4A to the gate of 5A?

$$-\frac{g_{m4}}{g_{m5}}$$

c. If a differential input causes a differential current  $i_d$  in 1A and  $-i_d$  in 1B, what is the current at the output if the output is held at small signal ground (e.g., in a  $G_m$  calculation)?

$$* 2 \frac{g_{m4}}{g_{m2}} i_d \quad 2 i_d - 1 \quad i_d - 2$$

d. What is the low frequency voltage gain?

$$\frac{g_{m4}}{g_{m2}} g_{m1} (r_{o4} \parallel r_{o5}) \quad \text{missing } \frac{g_{m4}}{g_{m2}} \quad -$$

e. What is the input common mode range (min and max)?

$$\min = V_{TN} + |V_{OV3}| + |V_{OV1}|$$

$$\max = V_{DD} - |V_{TP}| + V_{TN} + |V_{OV2}| = V_{DD} - |V_{OV2}|$$

f. What is the output swing (min and max)?

$$[V_{OV5}, V_{DD} - V_{OV4}]$$

g. What is the frequency of the dominant pole?

$$\omega_{pout} = \frac{1}{(r_{o4} \parallel r_{o5}) C_L}$$

h. Considering only  $C_{gs}$ , what is the frequency response of  $G_m$ ? (i.e. where are the other poles and zeros?)


$$-G_m = \frac{g_{m1}}{2} \frac{g_{m4}}{g_{m2}} \left( \frac{1}{1 + s/\omega_{pm2}} \right) \left[ 1 + \frac{1}{1 + s/\omega_{pm5}} \right]$$

$$\omega_{pm2} = \frac{g_{m2}}{C_{gs2} + C_{gs4}} \quad \omega_{pm5} = \frac{g_{m5}}{2 C_{gs5}}$$

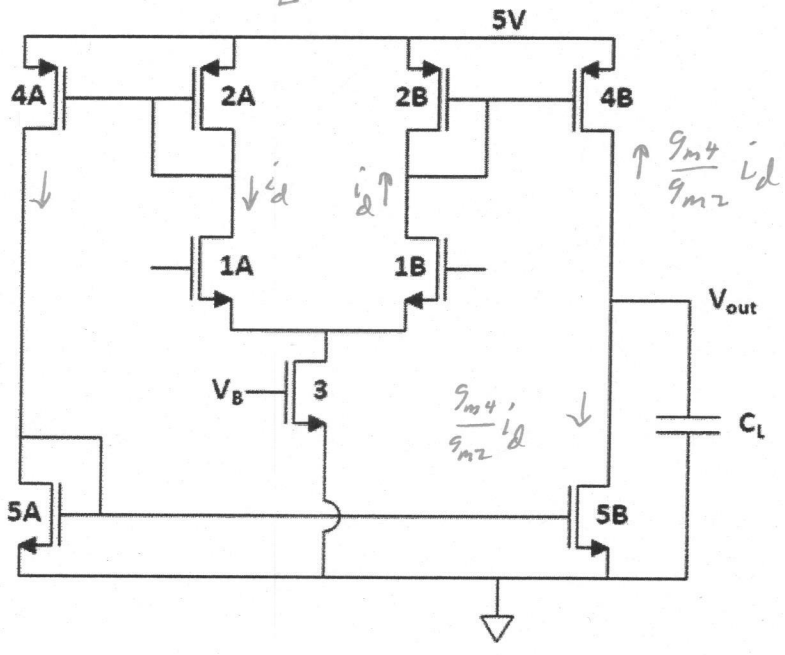
i. If you were not happy with the phase margin of this op-amp in unity gain feedback, where would you add capacitance?

At  $C_L$

turns into a doublet  $2 \left( \frac{1 + s/(2\omega_{pm5})}{1 + \frac{s}{\omega_{pm5}}} \right)$



 7. [8] The transistor below has  $V_{TN}=1V$ ,  $C_{gs}=5pF$ ,  $C_{gd}=1pF$ ,  $R_{ON}=1k\Omega$ ,



a. If the clock is high, how long does it take for  $V_C$  to settle from 100mV to 100μV?

[2]  $\tau = RC = 10^3 \cdot 10^{-9} = 1\mu s$  -1 other than  $7\tau$

[2]  $0.1\% \Rightarrow 7\tau = 7\mu s$

b. If the clock goes low (relatively slowly) when  $V_C$  has settled to 10mV, what is the impact on  $V_C$  during that transition? Give an explanation and a number in Volts.

[2] transistor turns off at  $\phi_1 = V_{tn} = 1V$   $\Delta V = + \frac{Q_i}{1nF} = 1mV$  [2]  
 $Q_i = -V_{tn} C_{gd} \approx (1V)(1pF) = -1pC$

8. [12] In the switched capacitor circuit below (bookkeep charge)

[1] a. What is the voltage on V- during  $\phi_1$ ? 0

b. What is the charge on the right side of  $C_A$  and  $C_B$  during  $\phi_1$ ?

$Q_{AR,1} = -V_{inA} C_A$   $Q_{BR,1} = 0$

[1] c. What is the voltage on V- during  $\phi_2$ ? 0

d. What is the charge on the right side of  $C_A$  and  $C_B$  during  $\phi_2$ ?

$Q_{AR,2} = 0$   $Q_{BR,2} = -V_{inB} C_B$

e. Where does the charge difference between parts b and d go?


to the left plate of  $C_F$

[4] f. What is the change in  $V_{out}$  during one cycle of both clocks?


$\Delta Q_{ABR} = -V_{inA} C_A + V_{inB} C_B$

$V_{out} = 0 + \frac{-\Delta Q_{ABR}}{C_F} = \frac{V_{inA} C_A - V_{inB} C_B}{C_F}$

all sign errors  
total -1

 

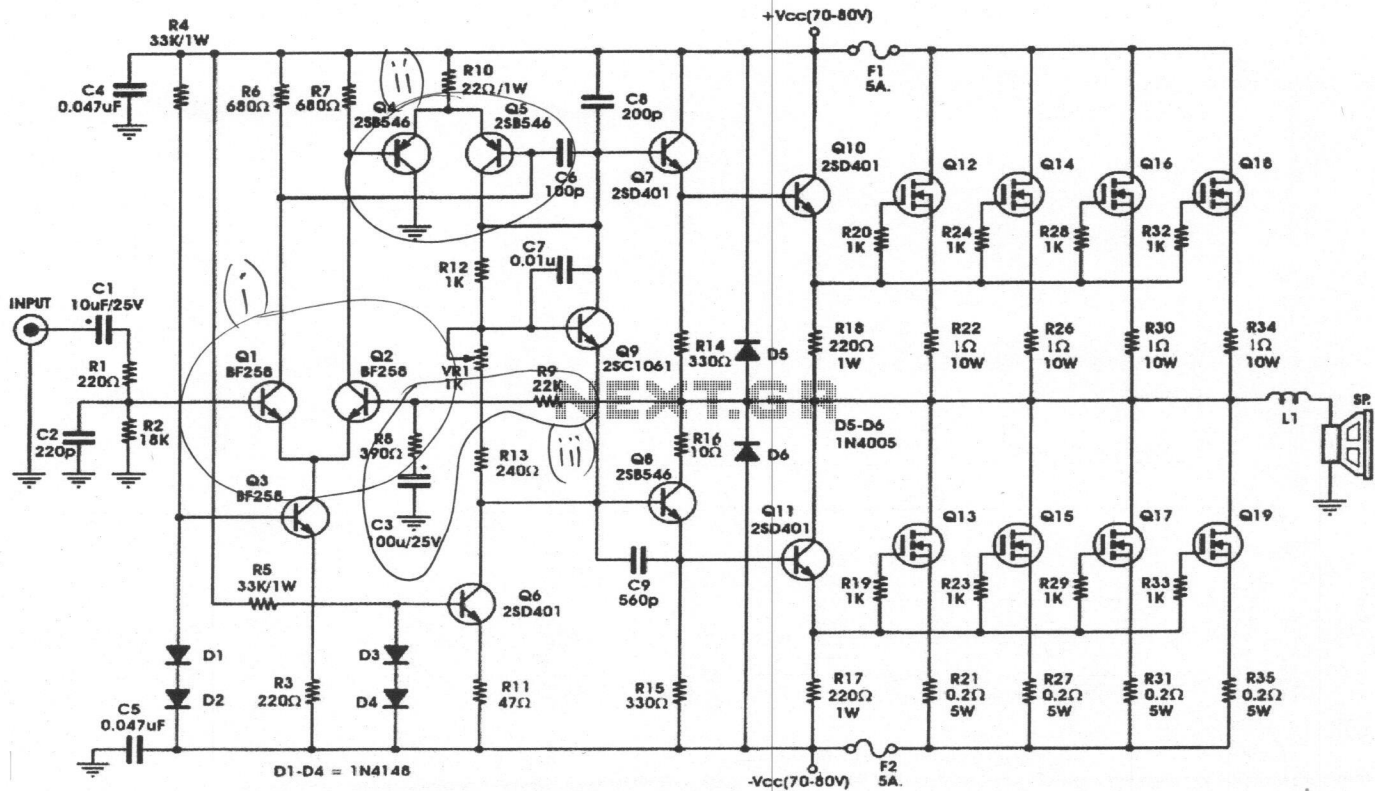(Cypress Semiconductor PSoC Application Note)



(<http://championed.info/circuit-diagram/audio-amplifier-circuit-diagram.html>)

9. [22] In the audio amplifier above, ignore the very weird output stage driving the speaker, and

2 pts each

- Circle and label the
  - input diff pair
  - 2<sup>nd</sup> stage diff pair
  - feedback network from the output to V-
- Roughly what is the voltage on R3?

$$0.7 \text{ V}$$

c. Roughly what is the current through R3?  $\frac{0.7 \text{ V}}{220 \Omega} \approx 3 \text{ mA}$

d. Roughly what is the  $g_m$  of Q1?  $g_m = \frac{I_c}{V_T} = \frac{1.5 \text{ mA}}{26 \text{ mV}} \approx 50 \text{ mS}$

e. Roughly what is the differential gain of the 1<sup>st</sup> stage  $A_{v1} = g_m r_o = (50 \text{ mS})(680 \Omega) \approx 35 \text{ V/V}$

f. Roughly what is the differential to single-ended gain of the 2<sup>nd</sup> stage?

$$A_{v2} = \frac{g_m r_{o5}}{2}$$

g. What is the DC feedback factor?


$$f = 1$$

h. What is the audio-frequency feedback factor?  $\frac{R_8}{R_8 + R_9}$

i. What RC time constant determines the lower end of the audio frequency range in the feedback network, and what is that frequency?

$$R_8 \cdot C_3 \quad \frac{1}{400 \Omega \cdot 100 \mu\text{F}} \approx 25 \text{ rad/s}$$

 10. [12] You have a bandgap that provides a stable 1.2V reference, and a 5 to 6V supply. For other analog components in a system, you need buffered reference voltages of 0.3V and 4.8V. There is very little current load on those reference voltages. Sketch the op-amp circuits that you would use to generate these voltages, and then draw the schematic of the amplifiers. Be careful of input and output voltages! You may assume that internal op-amp bias voltages are generated elsewhere.



- +1 - Low  $V_{CM} \rightarrow$  PMOS input
- +1 - Resistive feedback  
 $\rightarrow$  Must be 2 stages
- +1 - High output  
 $\rightarrow$  Cascodes must be high swing

2 pts each

11. [8] The curves below were taken from an N-type FET made at Berkeley with a single carbon nanotube gate and a single molecule of semiconductor, MoS<sub>2</sub> for the body and source/drain. Amazing!

("MoS<sub>2</sub> transistors with 1-nanometer gate lengths", Science, October 2016)

- a. This N-type device has a negative threshold voltage. Roughly what is it?

$-2V$  [-2.5 -2]

- b. If the width of the device is 1  $\mu m$ , roughly what is the transconductance when  $V_{GS} = -1V$  and  $V_{DS} = 2.5V$ ?


$\frac{5 \mu A}{0.5V} = 10^{-5} S$  [10  $\mu S$  15  $\mu S$ ]

- c. Roughly what is the output resistance at the same bias point?


$\frac{1.5V}{6 \mu A} = 250 k\Omega$  [150  $k\Omega$  350  $k\Omega$ ]

- d. What is the intrinsic gain at this bias point?

$-2.5 V/V$


 


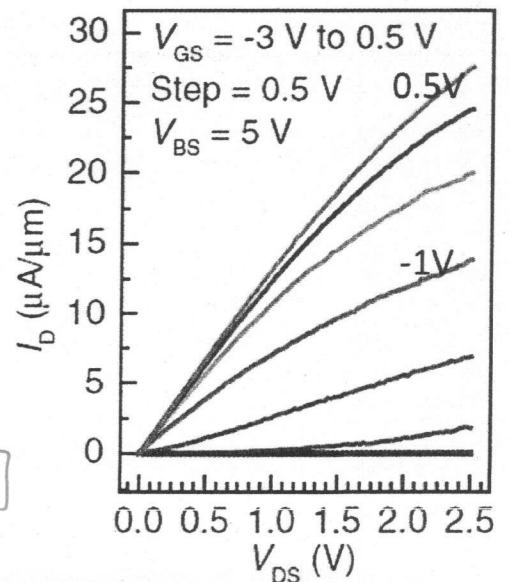- +1 - Low  $V_{CM} \rightarrow$  PMOS
- +1 - Must reach within 300mV of ground
- +3 for correct amp schematics



  12. [20] For the "gain boosting" sub-circuit in the figure to the below, assuming that the output is at the drain of M2 (load impedance not shown) and that  $g_m r_o \gg 1$ .


- 4 a. Draw the DC small signal model appropriate for a calculation of  $R_o$ .



- 2 b. Calculate  $R_o$ , the output resistance seen looking into the drain of M2

$$R_o = V_t / i_t \approx g_m r_o^2 A$$

 - 4 c. Draw the DC small signal model appropriate for a calculation of  $G_m$




- 2 d. Calculate  $G_m$ , the transconductance from the input  $V_i$  to the drain of M2

$$G_m \approx g_{m1}$$

- 2 e. If the load impedance were a mirror image made with PMOS devices, how would the gain compare to a similar cascode amplifier without the op-amps? *Increases by A times*

 - 2 f. If the op-amp gain has a single pole  $\omega_{pA}$ , sketch the impedance looking into the drain of M2 vs. frequency ignoring all other poles, zeros, caps, etc.



- 2 g. Compare the impedance above to a load capacitor. Under what conditions will the op-amp frequency response not have a substantial impact on the bandwidth of the overall amplifier?





*Pole from  $R_o C_L$  should be less than  $\omega_{pA}$*

- 2 h. What op-amps would be appropriate from the list in problem 5?

*2, 6*

*4 maybe OK, but stability concerns*

 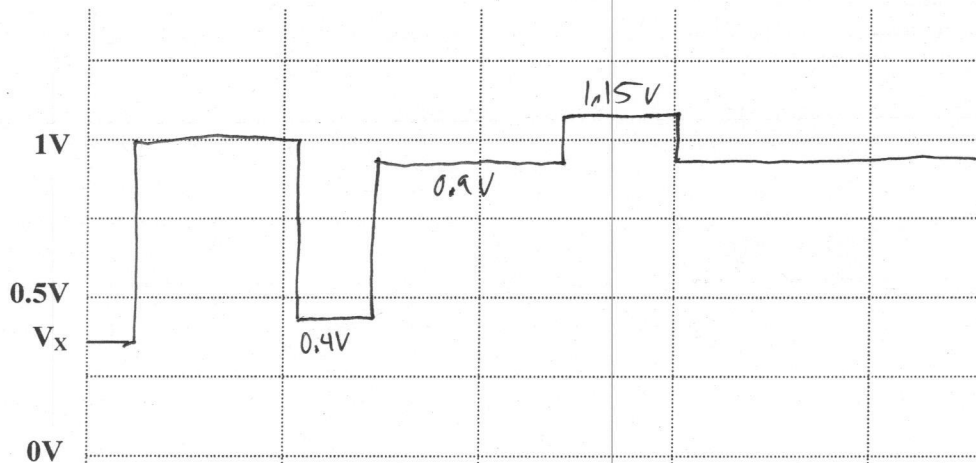  13. In the following 2 bit ADC circuit, LD and CMP are non-overlapping clocks. There is a SAR circuit which drives  $b_1$  and  $b_0$  based on LOW. Assume that the RC time constants are fast compared to the time scale below.  $V_{ref}=1V$ .  $b_1$  and  $b_0$  are either 0 or 1V.
- a. What binary value should the SAR report when  $V_{in}=0.6V$ ? 10 2 pts
- b. Assuming  $V_{in}=0.6V$ , carefully sketch the waveforms on  $V_x$  and LOW, and continue the waveforms for  $b_1$  and  $b_0$  on the graph provided below.



5 regions, 2 pts each