

EECS140 Midterm 2
Spring 2017


Name _____

SID _____

Prob.	Score
1a-e	/10
1f-1	/25
2, 3	/30
4	/15
Total	/80

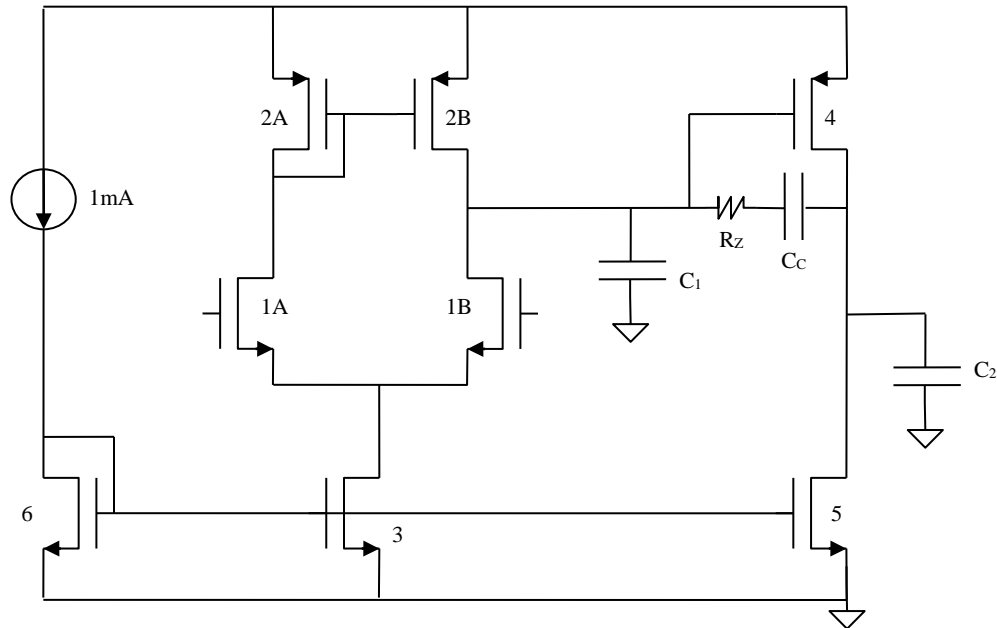1) Unless otherwise indicated, you may make the following assumptions:

- All transistors are biased in saturation with $V_{ov}=0.2V$
- $V_{DD}=3V$, $V_{tn}=1V$, $V_{tp}=-1V$
- M3, and M6 are identical, M5 is 10 times wider
- All capacitors are assumed to be zero except C_c , C_1 , and C_2 .



- What is the common mode input range (min and max)?
- What is the output swing (min and max)?
- If $C_1=0$, $C_2=1$ pF, and $C_c=1$ pF, what is the positive slew rate?
- If $C_1=0$, $C_2=2$ pF, and $C_c=1$ pF, what is the negative slew rate?
- If $C_1=0$, $C_2=1,000$ pF, and $C_c=1$ pF, what is the negative slew rate?

A different amplifier with the same topology has the following parameters. You may ignore the pole/zero doublet from the mirror.

$g_{m1,2}$	R_{o1}	g_{m4}	R_{o2}	C_1	C_C	C_2
1mS	1M	1mS	100k	10p	1p	100p

- f. If $C_C=0$ (magically we will assume no C_{gd4} for this part only), what are the uncompensated poles?

$\omega_{p1,u} =$	$\omega_{p2,u} =$
-------------------	-------------------

On the following pages,

- g. what is the location of the RHZ zero?
- h. plot the magnitude of the second stage gain
- i. plot the overall impedance seen at the first stage output (including R_{o1} , C_1 , C_C , and any effects of Miller multiplication),
- j. plot the magnitude of the first stage gain,
- k. plot the magnitude and phase of the overall gain. **Label any poles and zeros clearly.**
- l. Estimate the phase margin for this value of C_C .


$\omega_z =$

PM =


- m. What is the maximum feedback factor and closed loop gain for which the amplifier has a 45 degree phase margin?

f =	$A_{cl} =$
-----	------------


1h) Second stage gain – $|A_{v2,0}|$

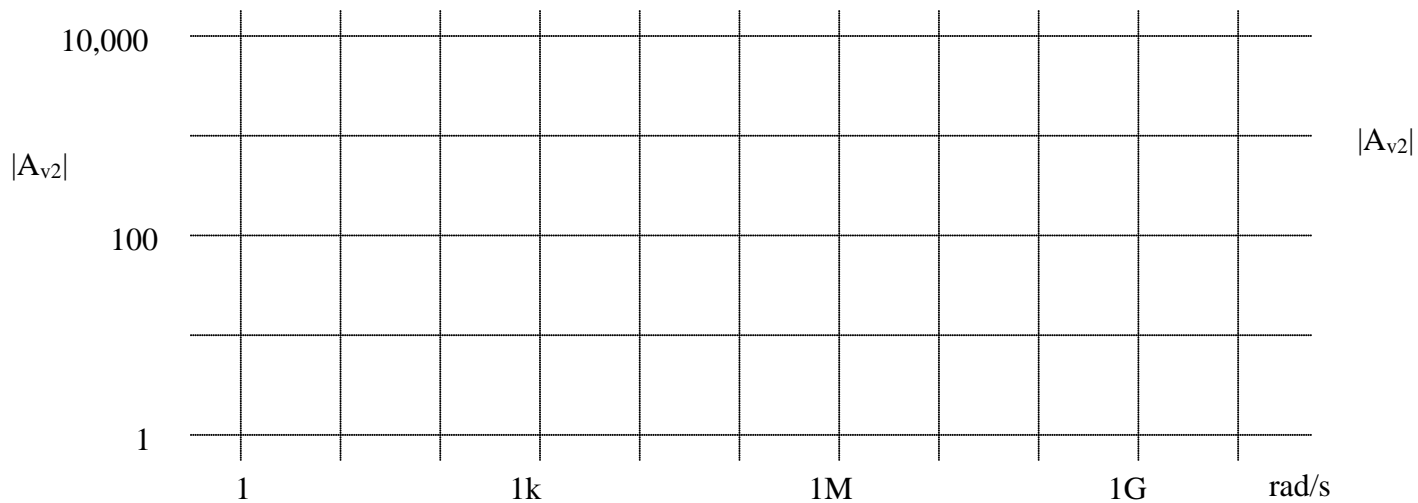


1i) Impedance at first stage output, $|Z_{o1}|$

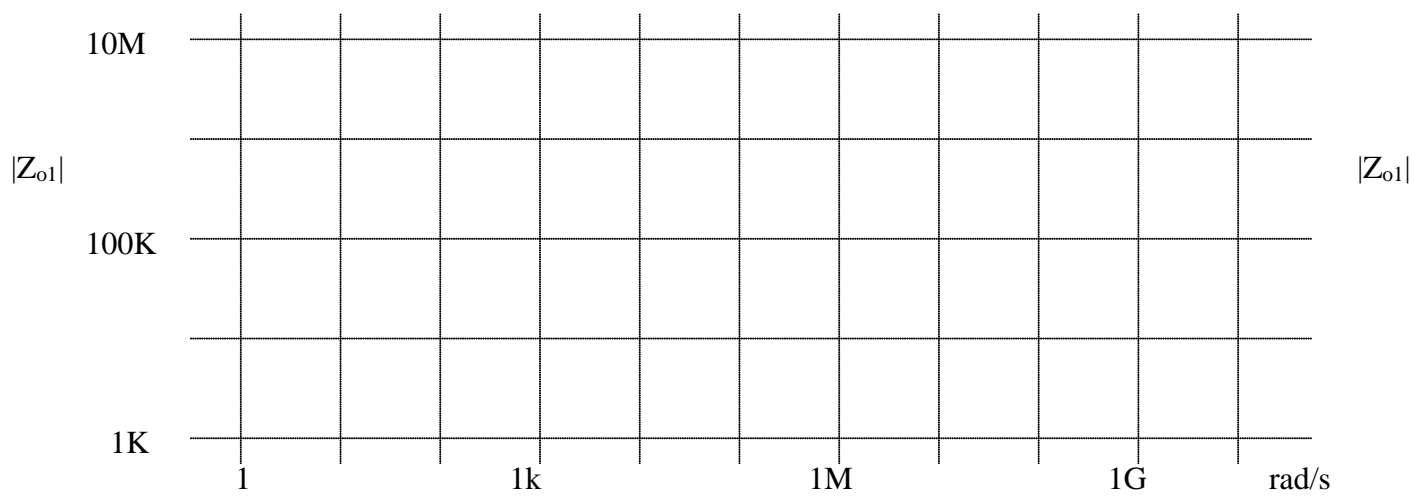


1j) First stage gain, $|A_{v1}|$

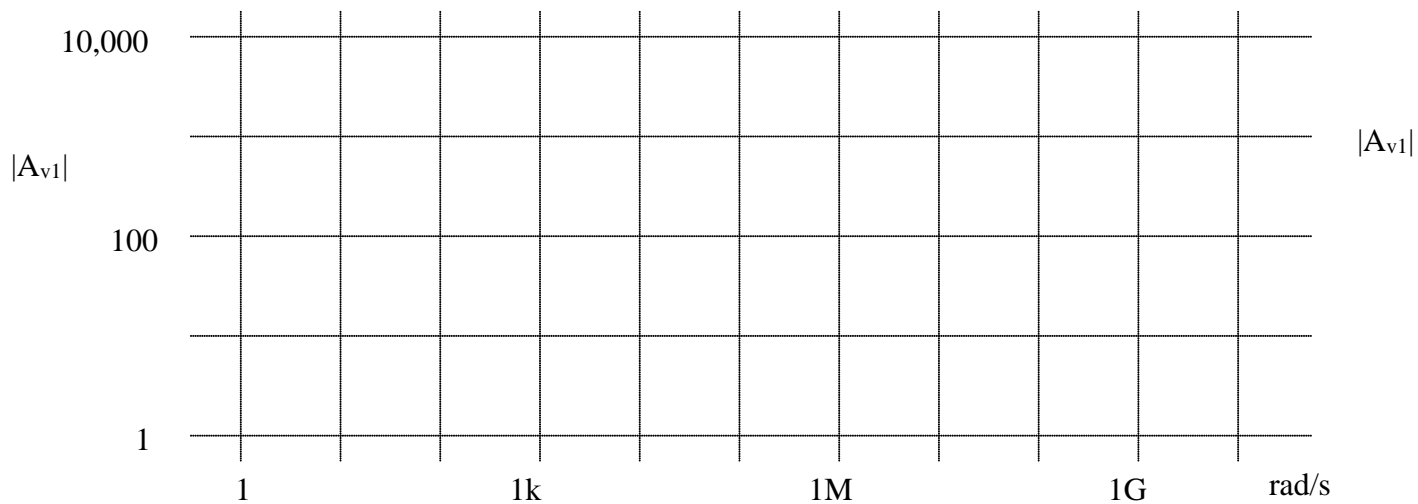

1kl) op amp Bode plot

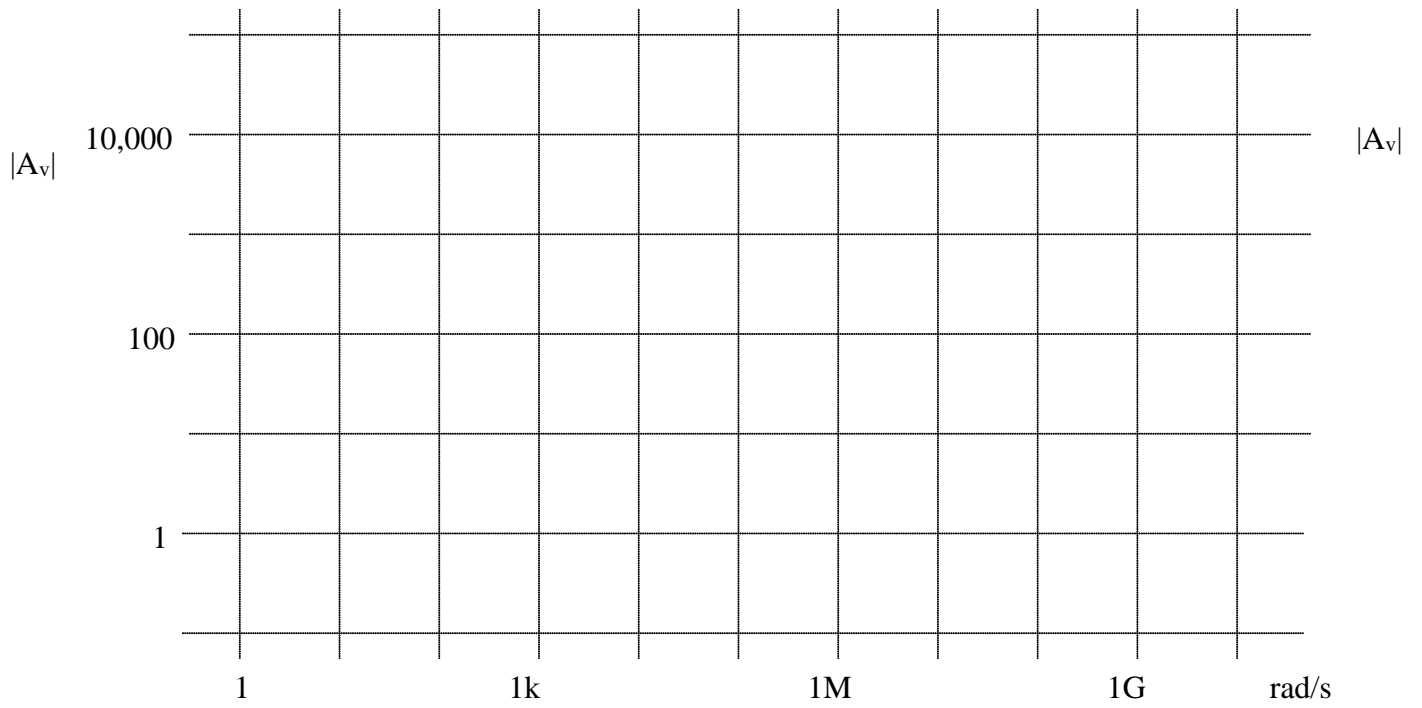

Label any poles and zeros clearly!

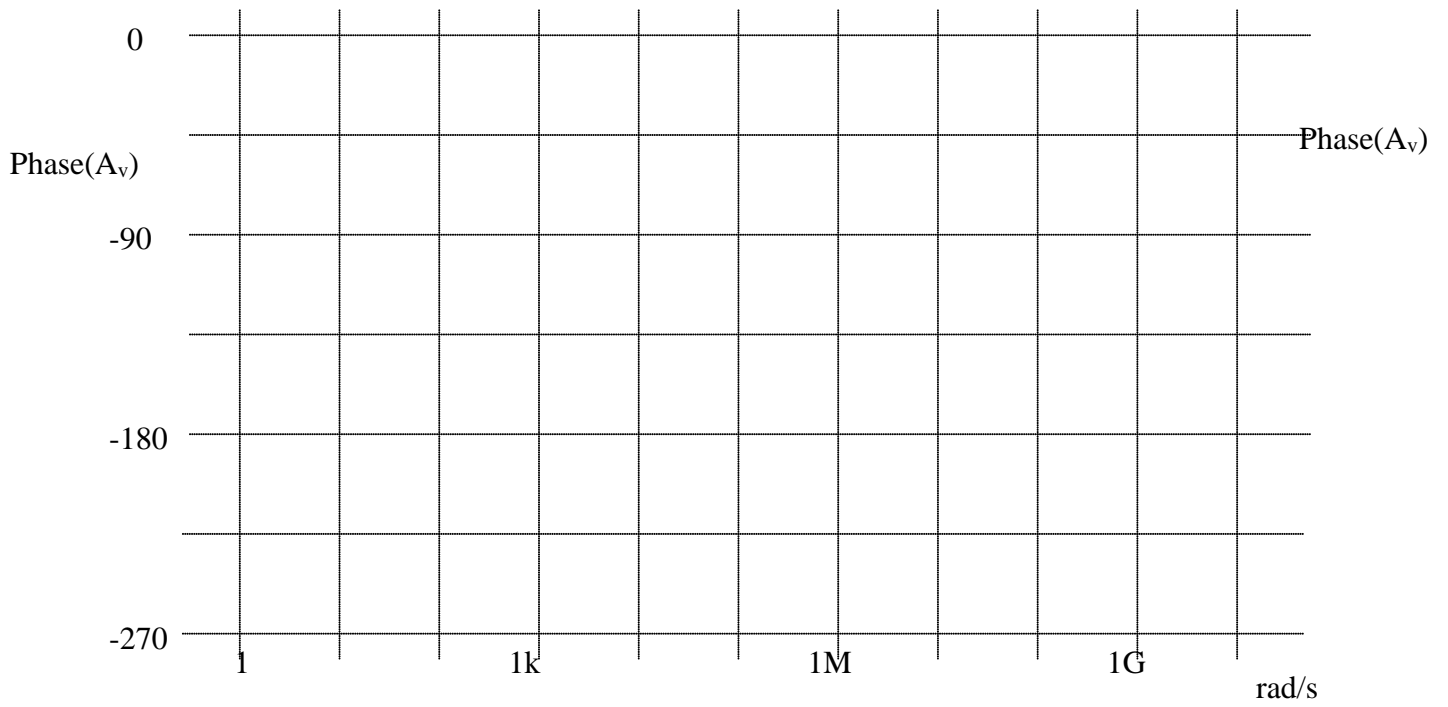



2) [8] A single-pole amplifier has a gain of 1,000 and a pole at 1MHz. It is used in feedback with a feedback factor $f=0.01$.

- What is the approximate closed-loop gain,
- percent gain error,
- closed-loop pole location,
- and time constant of the step response?

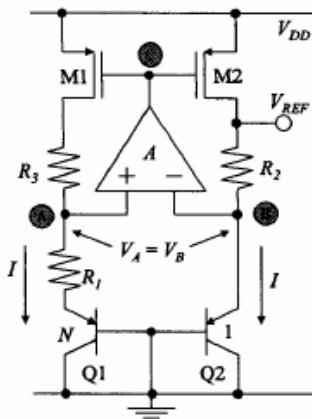3) [22] A particular diode D1 has a saturation current of 1pA, and at 1mA current at room temperature the diode voltage has a temperature coefficient of -2mV/K. You are using copies of this diode to make a bandgap reference as in Lab 4, with D2 composed of seven copies of D1. You can use the approximation that $\ln(7) \approx 2$. Assuming that the current in both diodes is maintained at 1mA at room temperature

- What is the voltage on D1 at room temperature?
- What is the voltage on D2 at room temperature?
- What is the different between the two diode voltages at 200K, 300K, and 400K?
- What is the temperature coefficient of the voltage on D2?
- Roughly what is the right value for R1?
- On the following page, carefully sketch by hand the voltage on D1, the voltage on D2, and the difference between them as a function of temperature from 200K to 400K.
- On the same plot, if $R_3=R_2=10 R_1$, sketch V_{ref} vs. temperature from 200K to 400K.



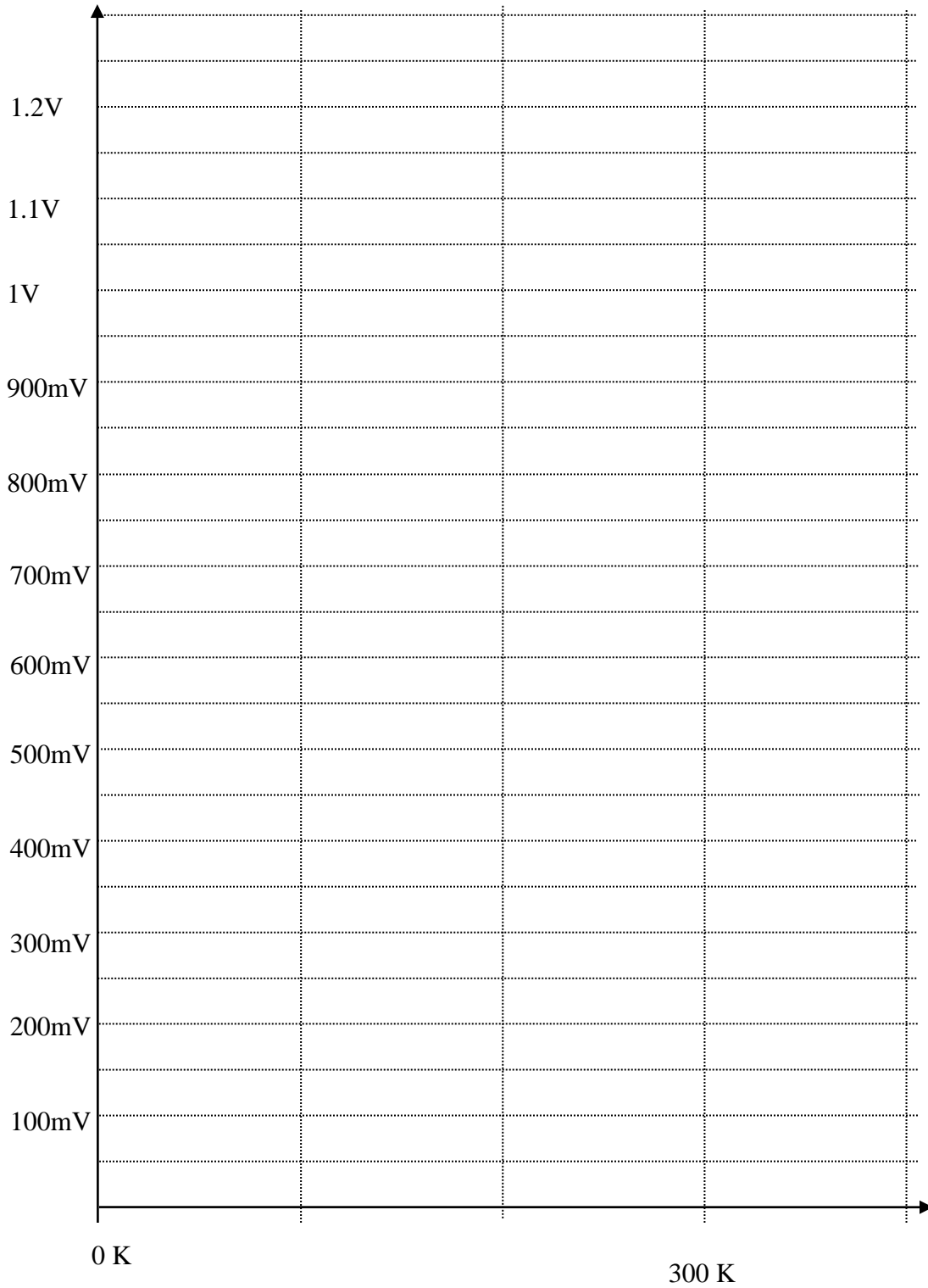

It will help your grade if you draw carefully and label the voltage values of any dots that you draw.

