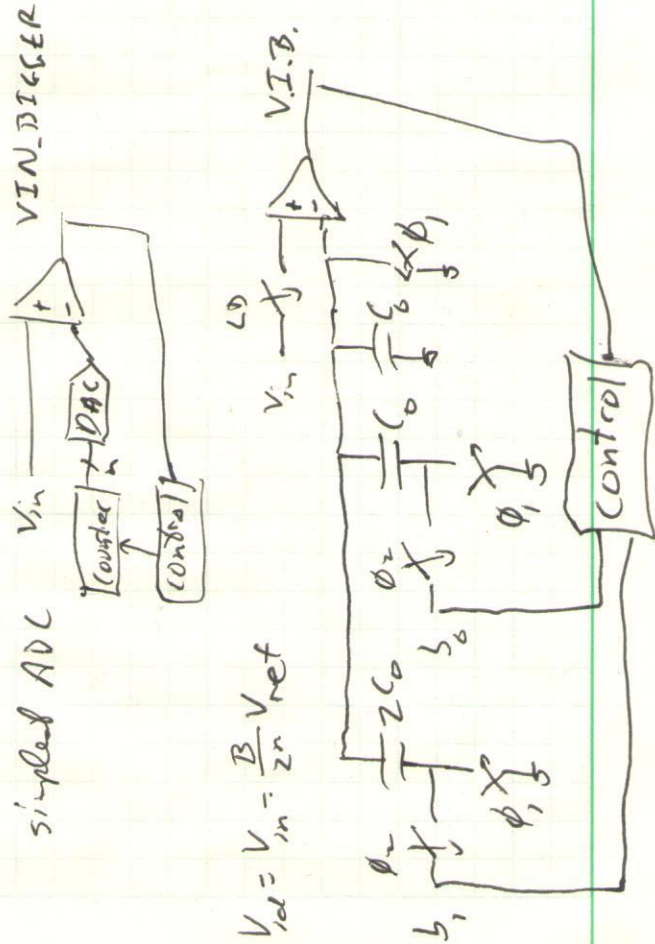


Project ~~100~~
 presn this week (12)
 division of labor, intro
 presn week 14
 design review
 in class RRR week

HW9
 SC ADC

now we have a DAC




switched cap DAC, ADC

last time



S_i

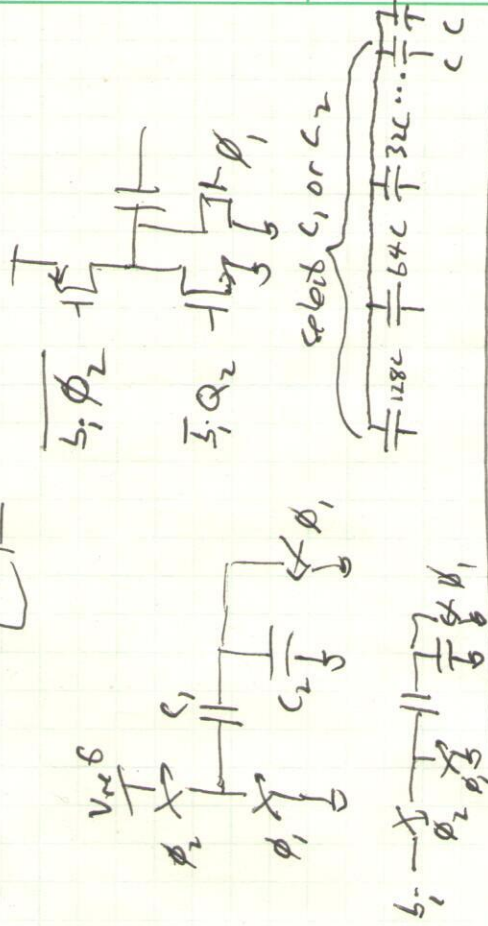


binary search is better than linear


3 bits S_2, S_1, S_0 4 caps: $4C_0, 2C_0, C_0, C_0$

$V_- = \frac{B}{8} V_{ref}$ during ϕ_2

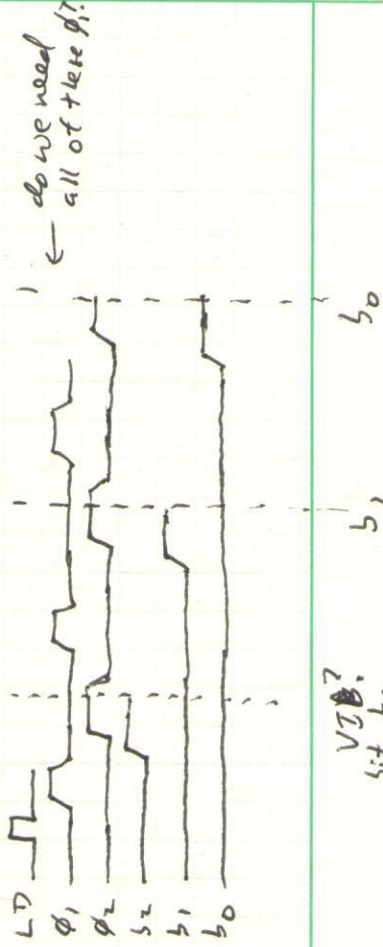
$V_{id} = V_{in} - \frac{B}{8} V_{ref}$ during ϕ_2




Vout?

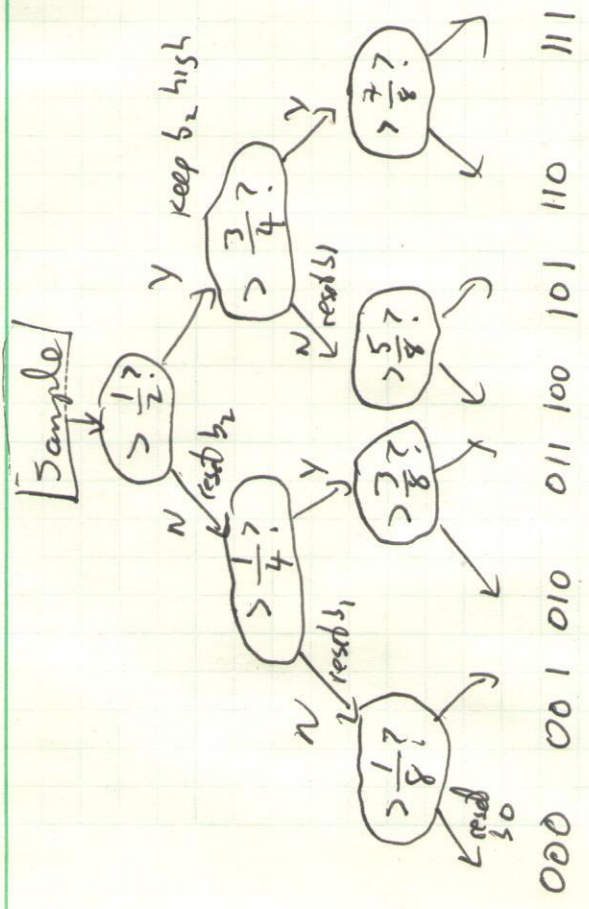

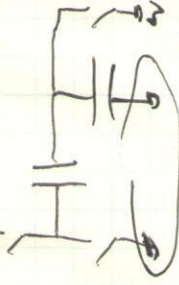need to find a way to convert at same voltage no matter V_{in} . How? SC cleverness



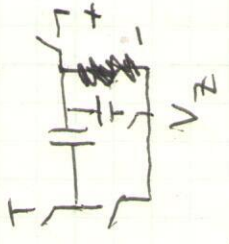Recall $V_x = \frac{B}{2^n} V_{ref}$ what if ~~this~~ this is V_z ? initial voltage on caps is V_z then charge redistrib.




make $V_z = V_{ref} - V_{in}$ then $V_x = \frac{B}{2^n} V_{ref} - \frac{B}{2^n} V_{in} + V_{ref}$

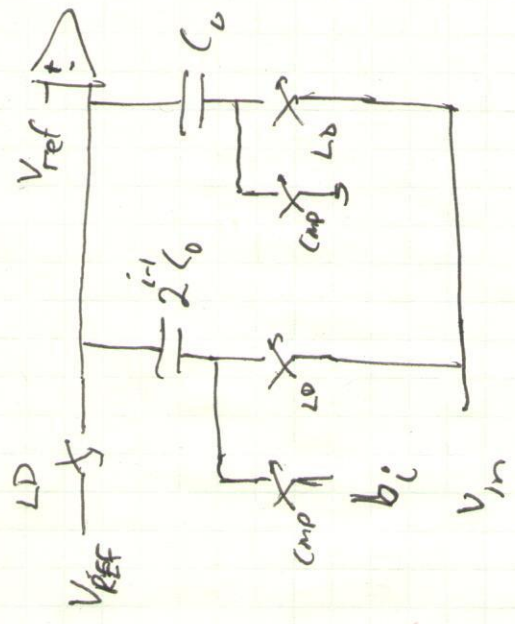
problem: tough to set comparator offset $\approx 1/LSB$ over $(0, V_{DD})$



V_{cm} varies $(0, V_{DD})$ - bad!
 $V_{in} = small$
 $V_{in} = large$
 $V_{cm} = V_{ref}$
 V_{cm} changes the decision point \Leftrightarrow imbalanced



During the LD phase

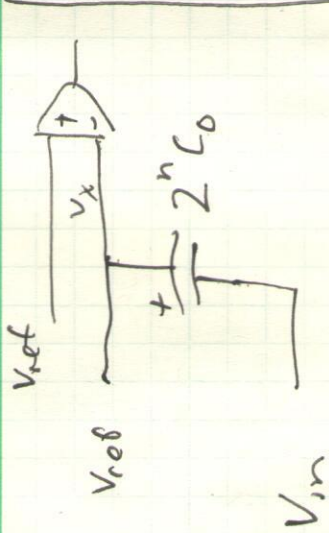

$$Q_{x,LD} = (V_{ref} - V_{in}) 2^n C_0$$

this charge is fixed when LD goes low
How long will it stay?

assume 1pF cap, 1pA leakage $\Rightarrow 1V/s$ 100kS/s
19uV in 1 signal

$$(V_{ref} - V_{in}) 2^n C_0 = V_x (2^n C_0) - V_{ref} \beta C_0$$

$$V_{ref} - V_{in} = V_x - V_{ref} \frac{\beta C_0}{2^n C_0}$$

$$V_x = V_{ref} + V_{ref} \frac{\beta}{2^n} \approx V_{in}$$


$$V_{id} = V_{ref} - V_x = V_{in} - V_{ref} \frac{\beta}{2^n}$$

one problem: if V_{in} small, during 1st compare

$$b_n = 1 \quad V_x \approx 1.5 V_{ref}$$

Comp be an issue

During CMP

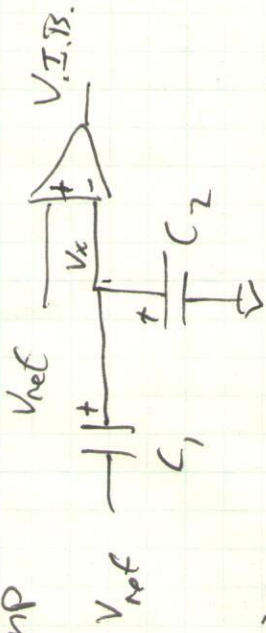

$$C_1 = \beta C_0$$

$$C_2 = (2^n - \beta) C_0$$

$$Q_{x,CMP} = (V_x - V_{ref}) C_1 + V_x C_2$$

$$= (\beta + C_2) V_x - V_{ref} C_1$$

which we know: $Q_{x,LD} = (V_{ref} - V_{in}) 2^n C_0$