
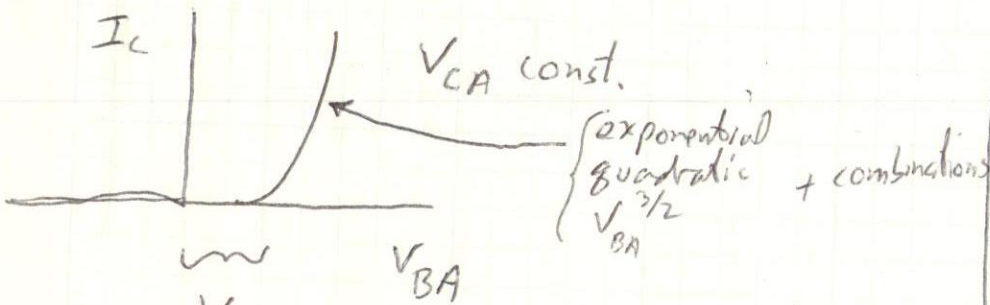


HW1 - grading
 Lab1 - issues?
 up next:

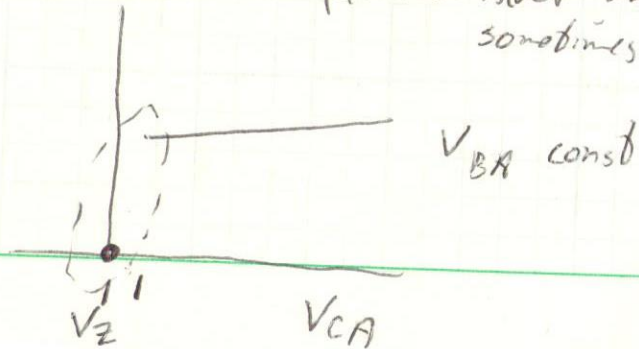linearization: large signal, operating point, device physics
 frequency response




V_X - some kind of turn-on voltage (almost never sharp) sometimes negative



many 3 terminal devices where

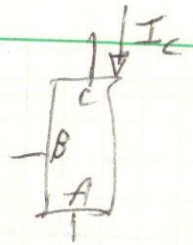I_C is a strong function of V_{BA}
 weak fn of V_{CA}



other currents are "small" (I_B)




BJT, JFET, vacuum tube, MOSFET, ...

BBS 1947

Nishizawa
 Watanohe
 1950

de Forest
 ~1911

Lilienthal
 1927

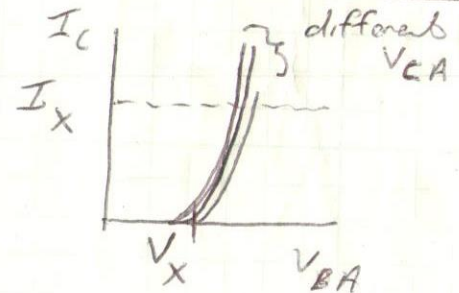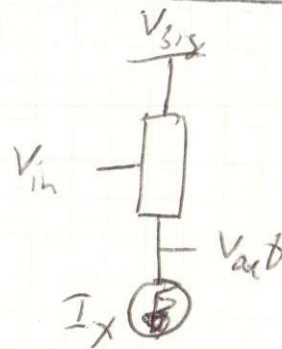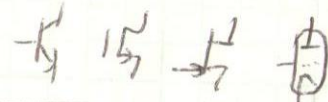

to pass I_X , $V_{BA} \approx \text{const}$

therefore


$$V_{out} = V_{in} - V_{BA}$$

$$\approx V_{in} - (V_X + \dots)$$

source follower, emitter follower, cathode follower

140/240A


18 SP W122

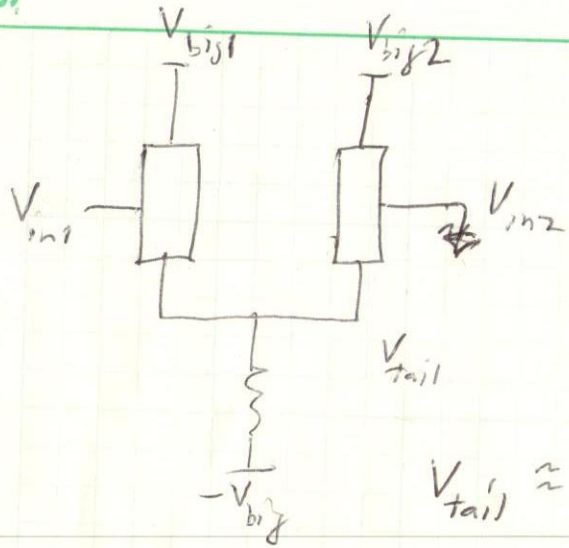

$$V_{tail} \approx \max(V_{in1}, V_{in2}) - V_X$$

Do V_{bis1} and V_{bis2} matter much?



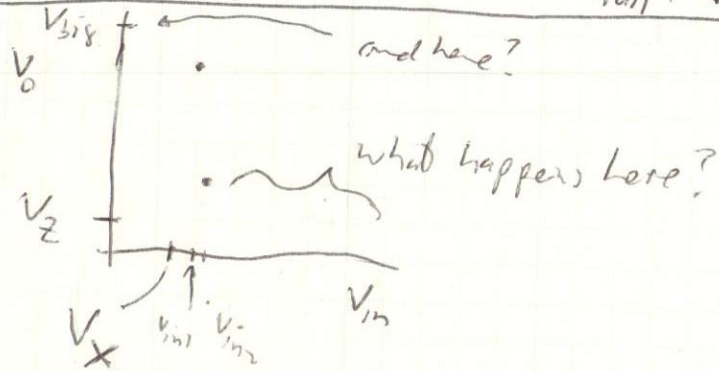
not as long as they are $> V_{tail} + V_Z$




what's the gain? $\delta i = g_m \delta v$

but I_X is constant, so $\delta i = 0$, so must have
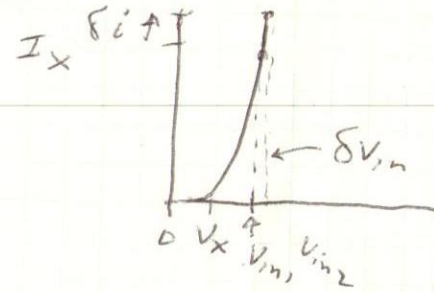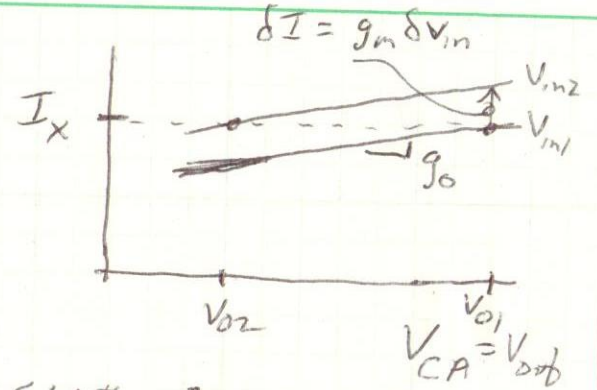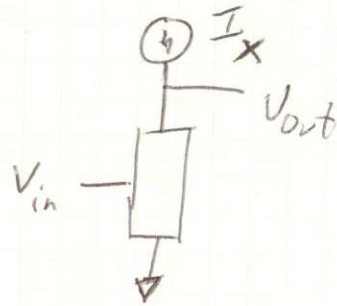
$$g_o \delta v_{out} = -\delta i = -g_m \delta v_i \quad \frac{\delta v_{out}}{\delta v_{in}} = -\frac{g_m}{g_o} = -g_m r_o$$



why not just calculate it directly?

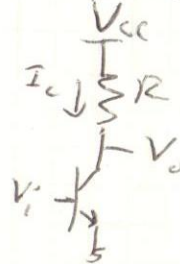

$$V_o = V_{CC} - I_C R$$


$$I_C = I_S \left(e^{\frac{V_{BE}}{V_{TH}}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

simple BJT model

$$V_o = V_{CC} - R I_S \left(e^{\frac{V_{in}}{V_{TH}}} - 1 \right) \left(1 + \frac{V_{ov}}{V_A} \right)$$

painful to solve by hand

easy for computers

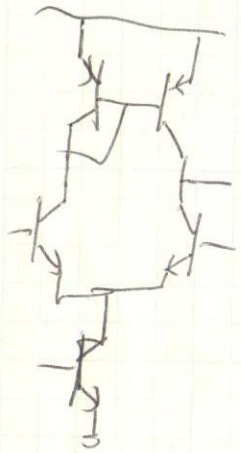

Lab 3

closed form equations
 \approx unsolvable by hand,
 (easy for computer = DC sweep)

linearization gives very
 accurate answer as long as
 you get the Region of Operation
 right.

$$I_D = \begin{cases} 0 \\ \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS}) \\ \dots \end{cases}$$

$$I_D(V_{GS}, V_{DS})$$

at some point V_{GS}, V_{DS} $I_D(V_{GS}, V_{DS}) = I_D$
 near that point

$$I_D(V_{GS} + v_{gs}, V_{DS} + v_{ds}) = I_D + \frac{\partial I_D}{\partial V_{GS}} \bigg|_{V_{GS}, V_{DS}} v_{gs} + \frac{\partial I_D}{\partial V_{DS}} \bigg|_{V_{GS}, V_{DS}} v_{ds}$$

$$= I_D + g_m v_{gs} + g_o v_{ds}$$

Linearization. (Taylor)

$f(x, y)$ continuous. $f(x_0, y_0) = F_0$
 best approx to f near x_0, y_0 is?

$$f(x_0 + \delta x, y_0 + \delta y) = f(x_0, y_0) + \frac{\partial f}{\partial x} \bigg|_{x_0, y_0} \delta x + \frac{\partial f}{\partial y} \bigg|_{x_0, y_0} \delta y + \dots$$

$$= F_0 + (x \text{ slope}) \delta x + (y \text{ slope}) \delta y + \dots$$

$$\left(\begin{matrix} \text{full non-linear} \\ \text{dynamics} \end{matrix} \right) = \left(\begin{matrix} \text{single} \\ \text{point} \\ \text{solution} \end{matrix} \right) + \left(\begin{matrix} \text{small} \\ \text{signal} \\ \text{model} \end{matrix} \right) + \text{h.o.t.}$$

\uparrow one nonlinear solution \uparrow local derivatives

