

HW3
Lab2

IC Design?

Simple pole model

What are the specs that we work from?

Often vague - "you're the analysis person - figure it out!"

try to translate into

- gain, bandwidth
- power, (noise)
- input/output swing
- source, load impedance
- gain stability (feedback, stability)

Project helps you tie it all together

Circuit design - library of building blocks
CS, CG, CD, diff pair, current mirror
(cascode, ...)

analysis

find operating point

solve nonlinear algebraic equations

find linear model there



redraw circuit in local
coords v_i, i_o, v_o

apply linear systems tools

Bode plots

transient analysis

estimate nonlinear effects

output swing, gain variation

design

what are we designing?

choose a collection of building blocks & assemble

each transistor has design choices


bipolar: emitter area, current

$$I_d = \frac{\mu_n C_{ox} W}{2 L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$


Process parameters
sometimes w/ a few
discrete choices, e.g.
thick oxide, high V_t ,
...

design

bias pt.


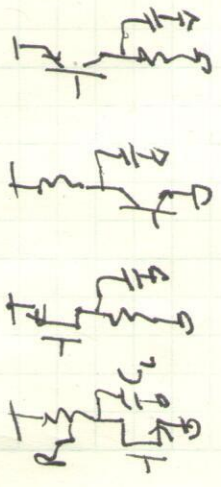


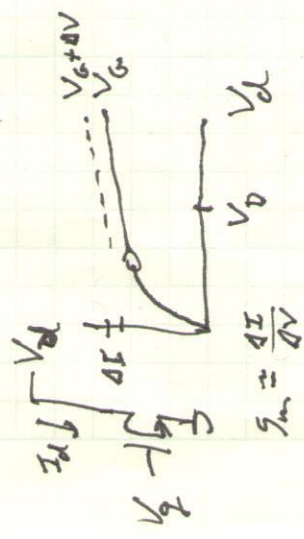all CS or CE
all have \approx same
small signal model





positive ΔV
 \Rightarrow positive $\Delta I = g_m \Delta V$


small signal model

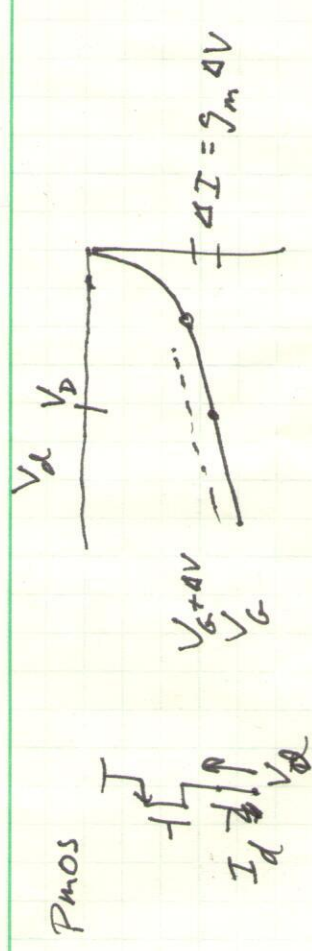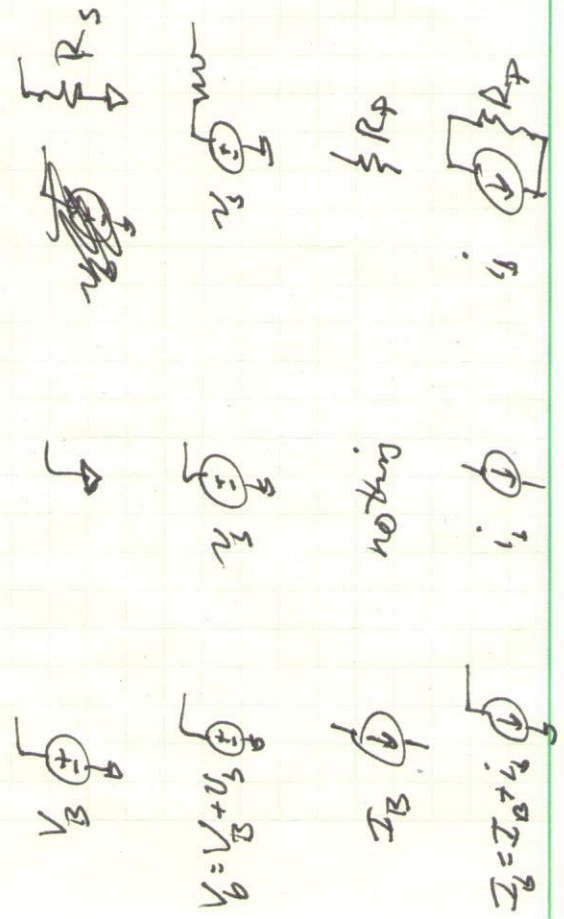


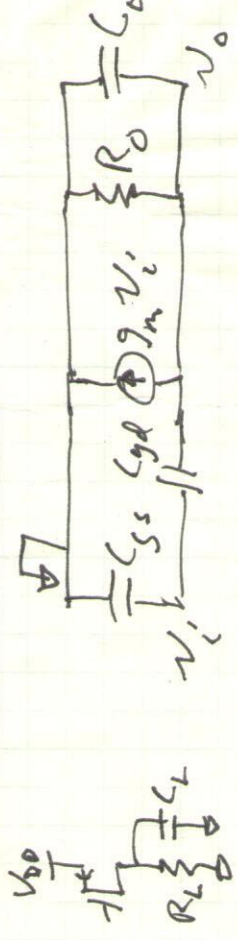
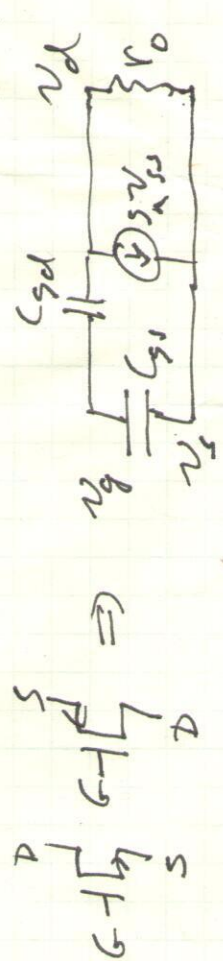
positive $\Delta V \Rightarrow$ positive ΔI (I_d less negative)



$$R_o = R_L || r_o \quad C_o = C_L || C_{out}$$

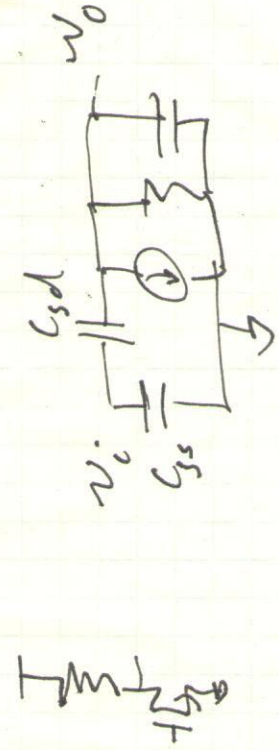

exactly same circuit

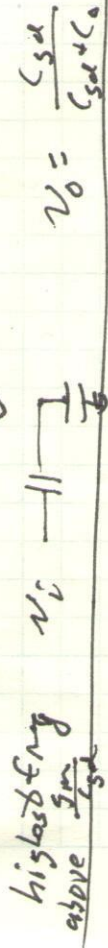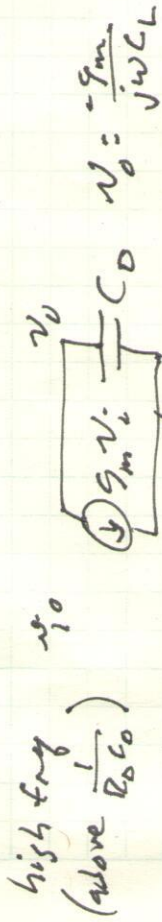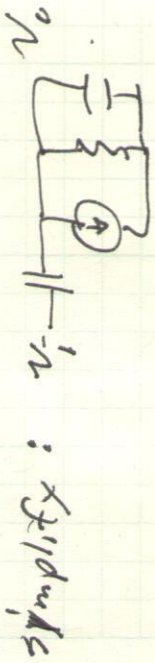

when $s = j\omega$ $\omega \ll \omega_p$ $\omega \ll \omega_z$

$$H(j\omega) \approx -g_m R_o$$

when $\omega_p < \omega < \omega_z$

$$H(j\omega) \approx \frac{-g_m R_o}{\frac{j\omega}{\omega_p}} = \frac{-g_m R_o}{j\omega R_o (C_o + C_{sd})} = \frac{-j\omega}{j\omega (C_o + C_{sd})}$$

when $\omega_p < \omega_z < \omega$

$$H(j\omega) \approx -g_m R_o \left(\frac{-j\omega_p}{j\omega} \right) = g_m R_o \frac{1}{R_o (C_o + C_{sd})} g_m = \frac{C_{sd}}{C_o + C_{sd}}$$

KCL @ v_o : $sC_o(v_o - v_i) + g_m v_i + \frac{1}{R_o} v_o + \frac{1}{sC_o} v_o = 0$

$$-(g_m - sC_{sd})v_i = v_o \left(sC_{sd} + \frac{1}{R_o} + sC_o \right)$$

$$H(s) = \frac{v_o}{v_i} = \frac{-g_m \left(1 - \frac{sC_{sd}}{g_m} \right)}{\frac{1}{R_o} + s(C_o + C_{sd})}$$

$$= -g_m R_o \frac{1 - s/\omega_z}{1 + s/\omega_p} \quad \omega_p = \frac{1}{R_o (C_o + C_{sd})}$$

Simplify even further: $C_{sd} = 0$

$$H(s) = \frac{v_o}{v_i} = \frac{-g_m R_o}{1 + s/\omega_p} = \frac{A_{vo}}{1 + s/\omega_p}$$

